



# ELEMENTS OF ELECTRICAL ENGINEERING

---

**Prof. Jyothi T N & Prof. Kruthika N**

Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

---


## Numerical Examples on Basic Laws

**Prof. Jyothi T N & Prof. Kruthika N**

Department of Electrical & Electronics Engineering

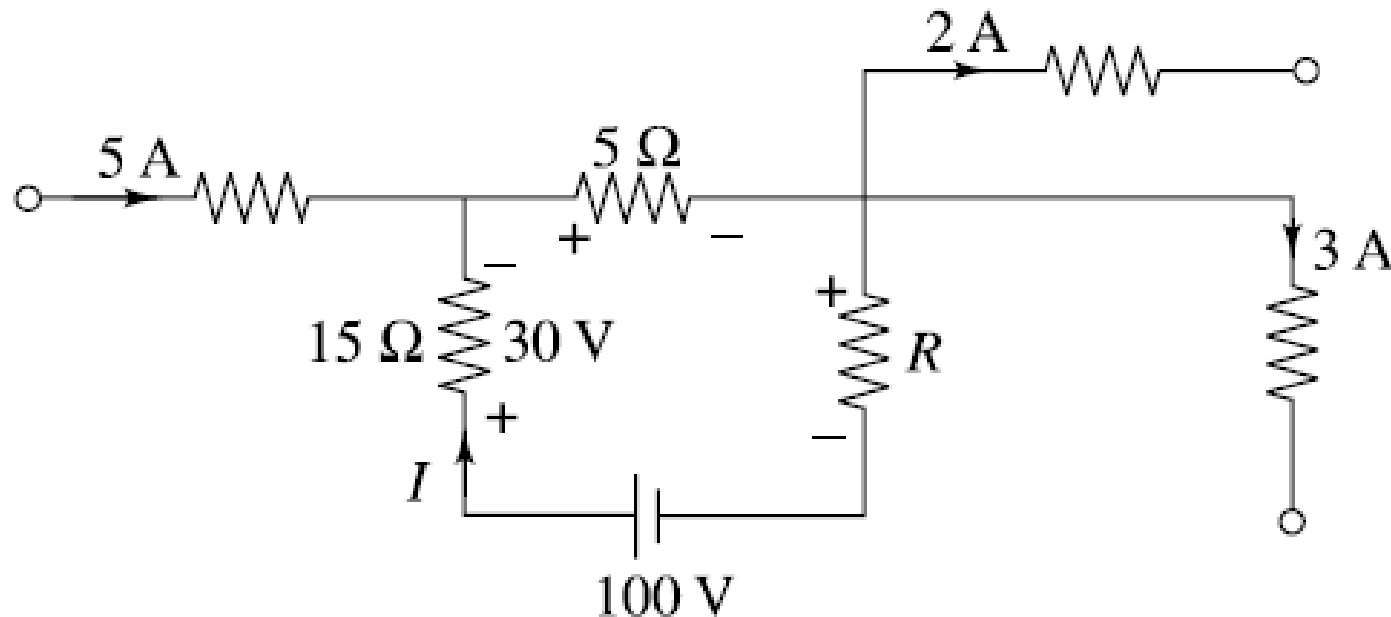
### Question:

Find the value of the unknown resistance  $R$  in the given network, if the voltage drop across  $15\Omega$  resistor is  $30\text{ V}$ , having the polarity as indicated.



**Solution:** Applying Ohm's Law, current through  $15\Omega$  resistor is,

$$I = \frac{30V}{15\Omega} = 2A$$

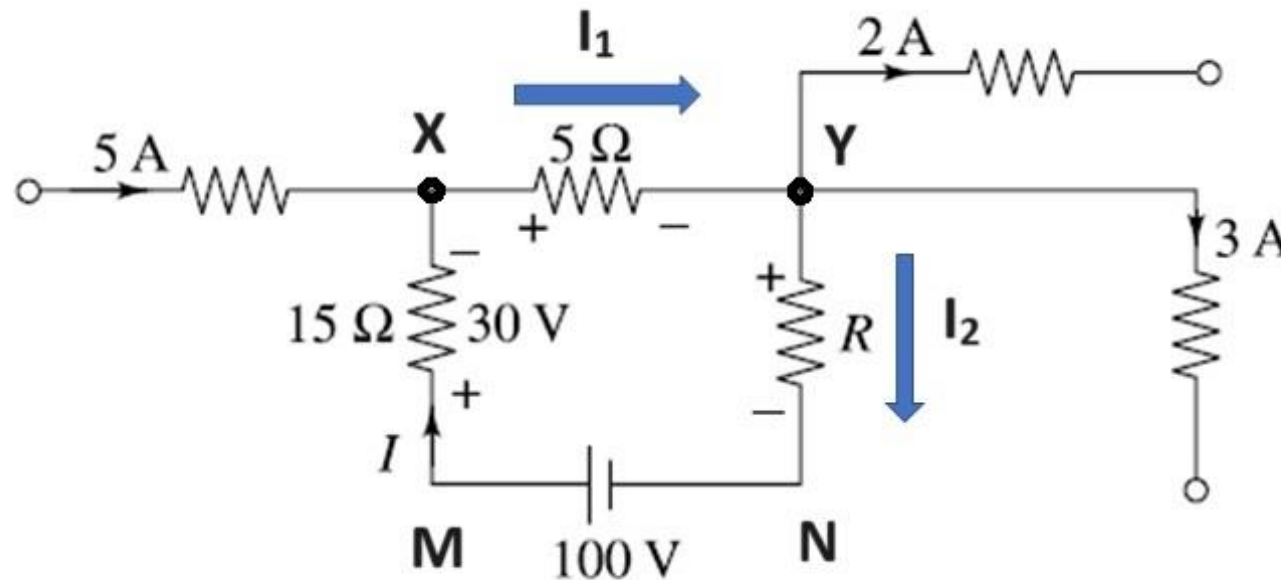


By KCL at node X,  $I_1 = 5 A + 2 A = 7 A$



# ELEMENTS OF ELECTRICAL ENGINEERING
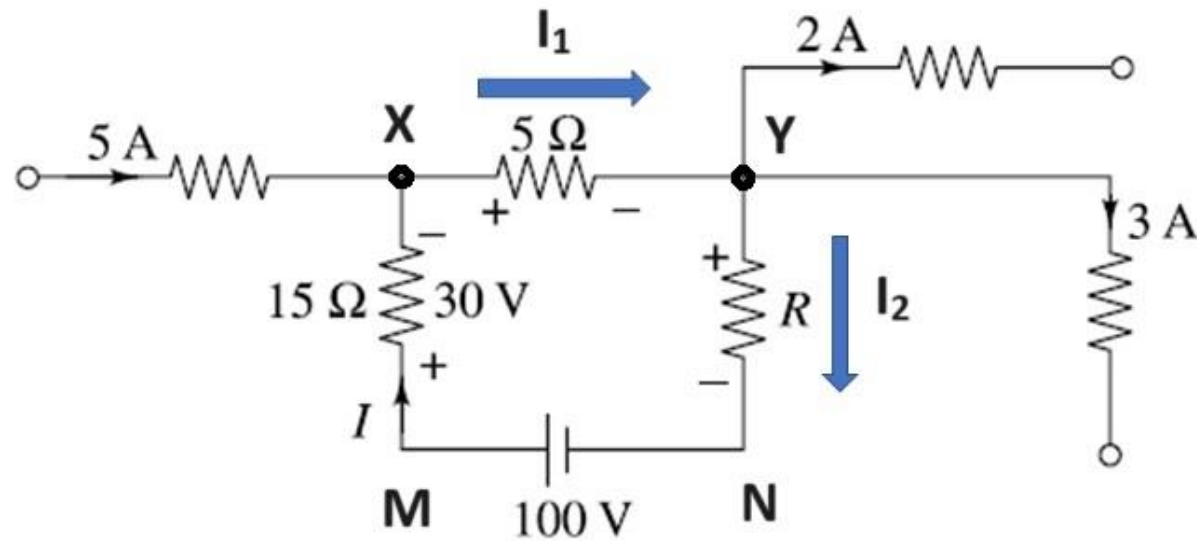
## Numerical Example on Ohm's Law, KCL & KVL




By KCL at node Y,  $I_2 = 7 \text{ A} - 2 \text{ A} - 3 \text{ A} = 2 \text{ A}$

By KVL in the path XYNMX,  $-5 * I_1 - R * I_2 + 100 - 30 = 0$


Solving,  **$R = 17.5 \Omega$**

**Question:**

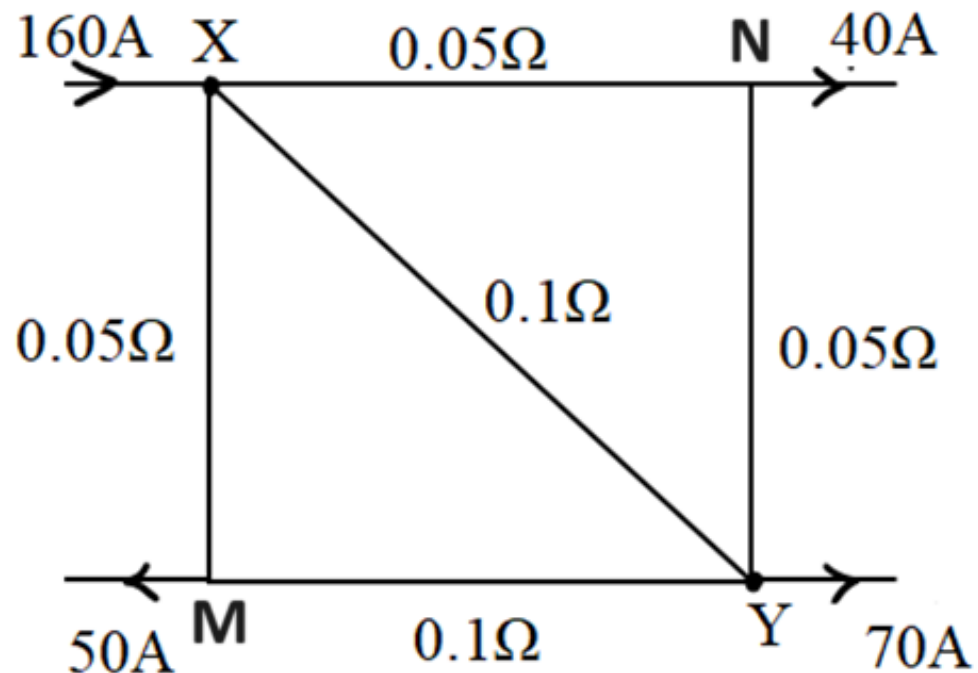**By using Kirchhoff's laws, Find the current in branch XY for the given circuit.**




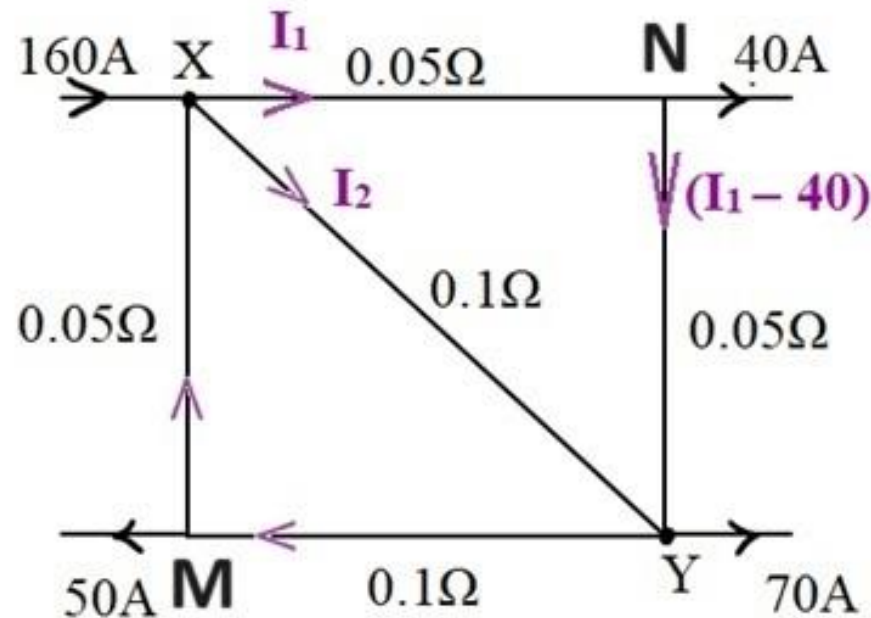**Solution:** Let us consider current in branch XN as  $I_1$  and branch XY as  $I_2$



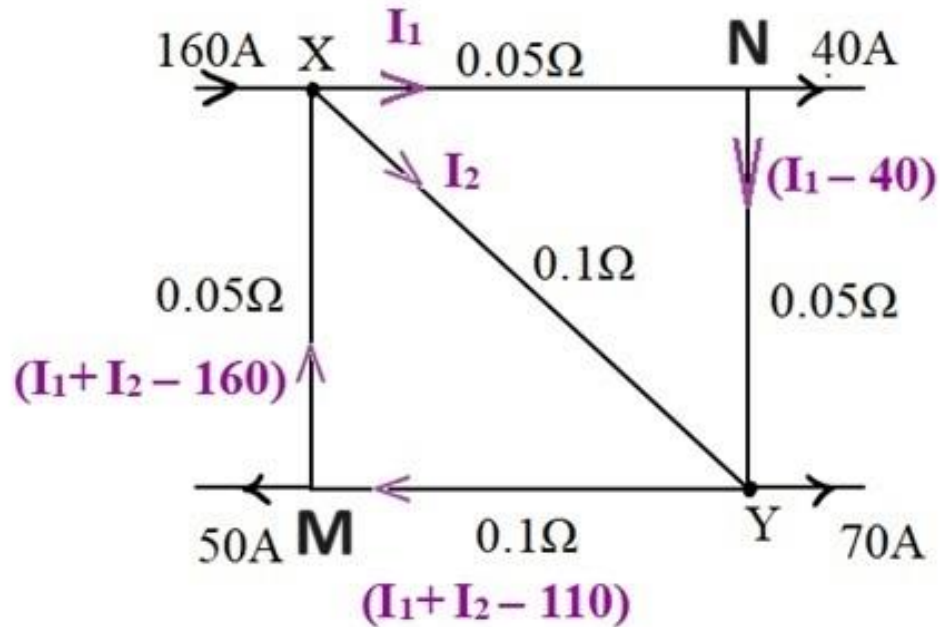By KCL at N, current in branch NY will be  $(I_1 - 40)$






By KCL at Y, current in branch YM will be  $(I_1 + I_2 - 110)$

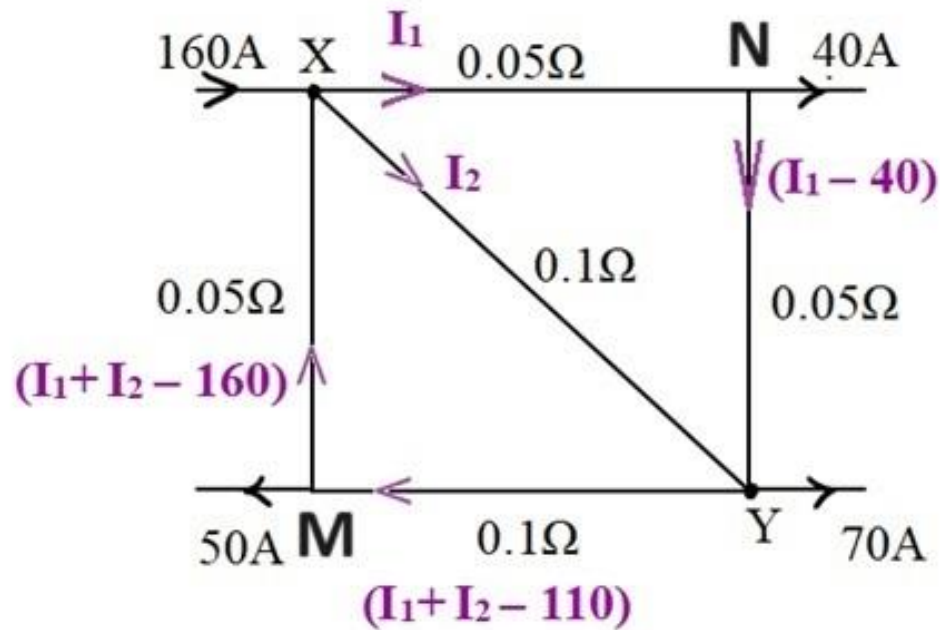By KCL at M, current in branch MX will be  $(I_1 + I_2 - 160)$





By KVL in the path XN<sub>Y</sub>X,  $-0.05 \cdot I_1 - 0.05 \cdot (I_1 - 40) + 0.1 \cdot I_2 = 0$

By KVL in the path XYMX,  
 $-0.1 \cdot I_2 - 0.1 \cdot (I_1 + I_2 - 110) + 0.05 \cdot (I_1 + I_2 - 160) = 0$

By Solving above KVL equations,  $I_{XY} = I_2 = 40 \text{ A}$

# ELEMENTS OF ELECTRICAL ENGINEERING

## Text Book & References

---



### Text Book:

1. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup> Edition, McGraw-Hill. 2019

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



# THANK YOU

---

**Prof. Jyothi T N & Prof. Kruthika N**

Department of Electrical & Electronics Engineering