

~~+ve~~

- ⑧ Two ~~w~~ TWO wattmeters are connected to measure input to a balanced three phase circuit indicate 2000 W and 500W. Find $\cos\phi$ when.

① Both readings are +ve

② Latter reading is obtained after reversing CC.

case ①

$$\tan\phi = \frac{\sqrt{3}(w_1 - w_2)}{w_1 + w_2} = \frac{\sqrt{3}\left(\frac{3}{5}\right)}{1} \Rightarrow \phi = 46.10^\circ$$

$$\cos\phi = 0.693$$

case ②

$$\begin{aligned} \tan\phi &= \frac{\sqrt{3}(w_1 - (-w_2))}{w_1 + w_2} = \frac{\sqrt{3}(2000 - (-500))}{2500} \\ &= \frac{\sqrt{3} \cdot 5}{3} \Rightarrow \phi = 70.888^\circ \end{aligned}$$

$$\cos\phi = 0.327$$

⑨

- One of the wattmeters read 10 kW when load $\text{PF} = 0.5$. When load PF changes to 0.8. Find new wattmeters readings if power remains unchanged.

$$B \cancel{R_f} = w_1 + w_2. \quad w_1 = 10 \text{ kW}$$

~~$\cos\phi = 0.5$~~

~~$P = VLI_L \cos(0.5)$~~

~~$0.5 = \cos\phi \Rightarrow \phi = 60^\circ$~~

$$W_2 + 10$$

$$W_1 + 10 = W_1 + 10$$

~~$$\frac{1}{2} \cos^{-1}(0.8) =$$~~

$$W_1 = 10 \text{ kW}$$

$$W_2 = 0$$

$$P = W_1 + W_2 = 10 \text{ kW} \quad \checkmark$$

when $\cos \phi = 0.5$

$$W_1' + W_2' = 10 \text{ kW} \quad \checkmark$$

$$\cos \phi = \cos \left(\tan^{-1} \left(\frac{W_2' - W_1'}{W_1 + W_2} \right) \right)$$

$$\begin{aligned} W_1' &= 2.835 \text{ kW} \\ W_2' &= 7.165 \text{ kW} \end{aligned}$$

$$0.8 = \cos \left(\tan^{-1} \left(\frac{3W_2' - W_1'}{W_1 + W_2} \right) \right)$$

$$0.74 = \sqrt{3} \left(\frac{W_2' - W_1'}{10} \right)$$

$$7.4 = W_2' - W_1'$$

$$10 = W_2' + W_1'$$

$$2W_2 = (17.4) / \sqrt{3}$$

$$W_1' = (1.3) / \sqrt{3}$$

$$W_2 = (8.7) \sqrt{3}$$

✓ Q) consider 3 impedances $(6+j8)$ are connected across $400V$ ~~delta~~^{delta}, supply. determine &

(a) $\# I_L$

(b) readings of watt meters.

(a) $\phi = \tan^{-1}\left(\frac{8}{6}\right) = 53.13^\circ$

$$|Z| = \sqrt{36+64} = 10 \Omega$$

$V_L = V_{ph}$ in delta

$$\# I_{ph} = \frac{V_{ph}}{|Z|} = \frac{400}{10} = 40 A$$

$$I_L = I_{ph} \sqrt{3} = 69.28 A$$

(b) $W_1 = V_L I_L \cos(30 + \phi)$ ~~83.13°~~

$$= 400 (69.28) \cos(83.13)$$

$$= 3.314 kW$$

$$W_2 = V_L I_L \cos(30 - 53.13^\circ) \\ = 25.48 \text{ kW} \quad \checkmark$$

1st value remains same.

$$V_L = 200 \text{ V} \quad \checkmark$$

$$I_{ph} = \frac{V_{ph}}{Z_1} = \frac{200}{\sqrt{3}(10)} = 11.547 \text{ A} \quad \checkmark$$

$$I_L = I_{ph} = 11.547 \text{ A} \quad \checkmark$$

$$W_1 = 200 (11.54) \cos(30 + 53.13^\circ) \\ = 276.07 \text{ W} \quad \checkmark$$

$$W_2 = 200 (11.54) \cos(30 - 53.13^\circ) \\ = 2.122 \text{ kW} \quad \checkmark$$

⑥ A 400V, 3Ø motor has full load output of 20 hp. efficiency being 88% and power factor lagging 0.8 lagging. Find readings of 2 wattmeters.

$$\phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$P = 20 \text{ HP} = 20 \times 0.746 = 14.92 \text{ kW} \quad \checkmark$$

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{in} = \frac{P_{out}}{\eta} = \frac{14.92}{0.88} = 16.95 \text{ kW} \quad \checkmark$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$16.95 \times 10^3 = \sqrt{3} (400) (I_L) 0.8$$

$$I_L = 30.58 \text{ A} \quad \checkmark$$

$$W_1 = V_L I_L \cos(30 + \phi) \quad [0^\circ \text{ lagging PF}]$$

$$W_1 = 400 (30.58) \cos(30 + 36.86^\circ) = 4.806 \text{ kW}$$

$$W^2 = VLI_L \cos(\theta - \phi)$$

$$= (400)(30 \cdot 58) \cos(30 - 36.86)$$

$$= 12.144 \text{ kW}$$

~~Two wattmeters are connected to measure power in 3d circuit. The reading of one wattmeter is zero when $\cos\phi$ is 1.~~

~~A balanced 3φ star connected load of 100kW takes a leading current of 80A connected to 3φ 1.1kV 50Hz supply. Find R, XL and capacitive. Also calculate $\cos\phi$~~

$$\text{star} \Rightarrow I_L = I_{ph} = 80A$$

$$V_{ph} = \frac{1.1}{\sqrt{3}} \times 1000 = 635.085V$$

$$P = \sqrt{3}V_L I_L \cos\phi$$

$$100 \times 10^3 = \sqrt{3} (1.1)(10)^3 \times 635.085 (80) (\cos\phi)$$

$$0.656 = \cos\phi$$

$$\phi = \arccos^{-1}(0.656) = 49^\circ$$

$$|Z| = \frac{V_{ph}}{I_{ph}} = \frac{635.085}{80} = 7.9 \angle 49^\circ$$

$$= 7.9 (\cos 49^\circ) - \sin 49^\circ j$$

$$= [5.182 - 5.96j] \Omega$$

$$R = 5.182 \Omega$$

$$X_C = 5.96 \Omega$$

$$\frac{1}{WC} = 5.96$$

$$C = \frac{1}{106 \pi (5.96)} = 534.07 \times 10^{-6} F$$

⑨ One of w

- ⑩ When three identical star connected coils are supplied with 440V 50Hz. 3d supply. Rana wattmeter is connected in R line and ~~R~~ Neutral pressure coil reads 6 kW. Ammeter connected in phase reads 30A. Assuming RYB Find.
- (i) R and X_L (ii) $\cos\phi$ of load and
(iii) Reactive power.


$$V_L = 440V \checkmark$$

$$V_{RN} = \frac{440}{\sqrt{3}}$$

$$W_L = V_{RN} I R \cos(\phi)$$

$$6 \text{ kW} = \frac{440 \cdot 30 \cos(\phi)}{\sqrt{3}}$$

$$6 \times 10^3 = 440 (30) \cos(\phi)$$

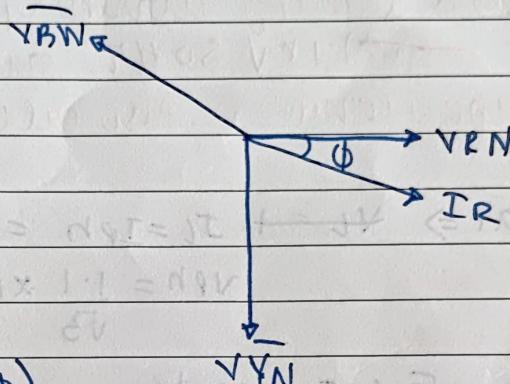

$$(b) \cos\phi = 0.777$$

$$\phi = 38.093^\circ$$

$$(a) |Z| = \frac{V_{ph}}{I_{ph}} = \frac{440}{\sqrt{3}(30)} = 8.467 \angle 38.093^\circ$$

$$z = 6.66 + j 5.223$$

$$R = 6.66 \Omega$$

$$X_L = 5.223 \Omega$$

$$t \cancel{t} =$$

$$(c) \text{Reactive power} = \sqrt{3} V_L I_L \sin \phi$$
$$= \sqrt{3} (440)(30) \sin(38.093^\circ)$$
$$= 14.105 \text{ kVAR}$$

⑩ Two wattmeters are connected to measure the power input of a 15HP, 30Hz, 3 phase induction motor at full load. The full load efficiency of the motor are 0.9 and 0.8 lag resp. Find the readings of 2 wattmeters.

$$15 \text{ HP} = 15 \times 0.746 = 11.19 \text{ kW}$$

$$\text{Power } P = \frac{P_{\text{out}}}{\eta_{\text{in}}} \quad \checkmark$$

$$0.9 = \frac{11.19}{\eta_{\text{in}}} \rightarrow \eta_{\text{in}} = 12.43 \text{ kW}$$

$$\cos \phi = 0.8 \text{ lag (Inductive load)}$$

$$\phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$W_1 = V_L I_L$$

$$P = \sqrt{3} V_L I_L \cos(\phi)$$

$$V_L I_L = \frac{12.43 \times 10^3}{\sqrt{3} (0.8)} = 8970.57$$

$$W_1 = V_L I_L \cos(30 + \phi)$$

$$= 8970.57 \cos(66.86)$$

$$= 3.525 \text{ kW}$$

$$W_2 = V_L I_L \cos(30 - \phi)$$

$$= 8970.57 \cos(30 - 36.86)$$

$$= 8.906 \text{ kW}$$

⑩ A balanced 3 phase star connected load is supplied from a symmetrical 30 400V, 50Hz. The current in each phase load 10A and lags by 60° behind phase voltage.

(a) Impedance per phase.

(b) Resistance and Inductance per phase.

(c) Active and reactive powers.

$$V_L = 400 \text{ V} \quad \checkmark$$

$$V_{ph} = \frac{400}{\sqrt{3}} \text{ V}$$

$$I_{ph} = 10 \text{ A} = I_L$$

$$|Z| = \frac{V_{ph}}{I_{ph}} = \frac{400}{\sqrt{3}(10)} = 23.094 \angle 60^\circ \Omega$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right) \quad Z = [11.54 + j 19.99] \Omega$$

~~$$60^\circ = \tan^{-1} X_L$$~~

$$(a) X_L = 19.99 \approx 20 \Omega$$

$$wL = 20 \Omega$$

$$L = \frac{20}{w} = \frac{20}{500\pi} = \frac{1}{5\pi} \text{ H}$$

Impedance per phase

$$= 23.094 \Omega$$

$$= 0.063 \text{ H}$$

$$= 63.66 \text{ mH} \quad \checkmark$$

(b) Resistance 11.54Ω .

Inductance $= 63.66 \text{ mH}$.

(c) P active $= \sqrt{3} V_L I_L \cos \phi$


$$= \sqrt{3}(400)(10) \cos(60^\circ)$$

$$P_{3\Phi} = 3.464 \text{ kW} \quad \checkmark$$

P reactive $= \sqrt{3} V_L I_L \sin \phi$

$$= \sqrt{3}(400)(10) \sin(60^\circ)$$

$$Q_{3\Phi} = 6 \text{ kW}$$

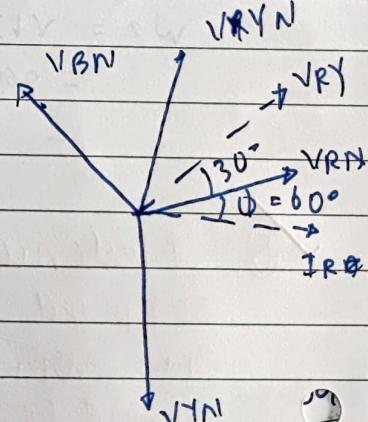

Q) Two wattmeters connected to measure 3ϕ power for a balanced star connected 3ϕ load. Measure 10 kW and 3 kW . If $\text{I}_L = 20\text{ A}$ at lagging power factor. determine

- (a) V_L
- (b) V_{ph}
- (c) resistance
- (d) Inductance

$d = +ve.$

$$P = W_1 + W_2 = 15\text{ kW}$$

$$\cos \phi = \cos(\tan^{-1}(\frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2}))$$

$$\cos \phi = \cos(\tan^{-1}(\frac{\sqrt{3} \times 8}{18.5}))$$

$$\cos \phi = \cos(\tan^{-1}(\frac{1}{\sqrt{3}}))$$

$$\cos \phi = 0.866 \quad \phi = 30^\circ$$

$$(a) P = \sqrt{3} V_L I_L \cos \phi$$

$$15\text{ kW} = \sqrt{3} V_L (20) (0.866)$$

$$\underline{15 \times 10^3} = V_L$$

$$\sqrt{3} (20) (0.866)$$

$$V_L = 500.01 \text{ V.}$$

$$(b) V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{500.01}{\sqrt{3}} = 288.68 \text{ V.}$$

$$(c) \text{Res } Z = \underline{V_{ph}} = \frac{288.68}{20} = 14.43 \angle 30^\circ \Omega$$

$$10^\circ I_L = 30 \text{ A}$$

$$Z = [12.5 + j 6.25] \Omega$$

$$\textcircled{c} \quad R = 12.5 \Omega$$

$$\textcircled{d} \quad WL = 6.25$$

$$L = \frac{6.25}{100\pi} = 0.0198 \text{ H}$$

$$= 19.89 \text{ mH} \quad \checkmark$$

* (b) A balanced star connected load consumes 3kW of power at lagging 0.8 power factor when connected to a 3 ϕ supply. If $I_L = 12.5 \text{ A}$ calculate R and X_L in each branch. What will be I_{ph} and P if same load is connected in delta?

$$P = 3 \text{ kW} \quad \cos\phi = 0.8$$

$$P = \sqrt{3} V_L I_L \cos\phi \quad I_L = I_{ph} = 12.5 \text{ A}$$

$$3(10)^3 = \sqrt{3} (V_L) (12.5) (0.8)$$

$$V_L = \frac{3000}{\sqrt{3}(12.5)} = 173.20 \text{ V}$$

$$\text{star } V_L =$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{173.20}{12.5} = 8$$

$$\phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$Z = 8(0.8) + j(0.569)(8) = 6.4 + j4.792$$

$$R = 6.4 \Omega$$

$$X_L = 4.792 \Omega$$

for delta

$$I_L = \sqrt{3} I_{ph} = \quad V_L = V_{ph} = 173.20 \text{ V}$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{173.20}{8} = 21.65 \text{ A}$$

$$I_L = \sqrt{3} I_{ph} = 37.5 \text{ A}$$

$$P = \sqrt{3} V_L I_L \cos\phi = 8.9 \text{ kW}$$