



# ELECTRONIC PRINCIPLES AND DEVICES


---

**Dr. Ananda M**

Department of Electronics and Communication.

# ELECTRONIC PRINCIPLES AND DEVICES

---

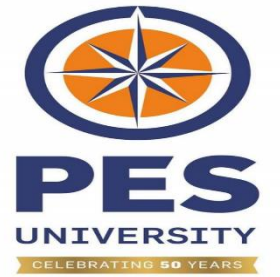

## Unit-3 Digital Electronics

### Realization of Boolean expression using Universal Gates

**Dr. Ananda M**


Department of Electronics and Communication.

❖ **Universal Gates :**    (i) NAND Gate  
                                     (ii) NOR Gate

❖ Any digital logic circuit can be implemented by using NAND or NOR logic gates.

❖ NAND and NOR gates are easier to fabricate with electronic components and are used in all Integrated Circuit (IC's) digital logic families.

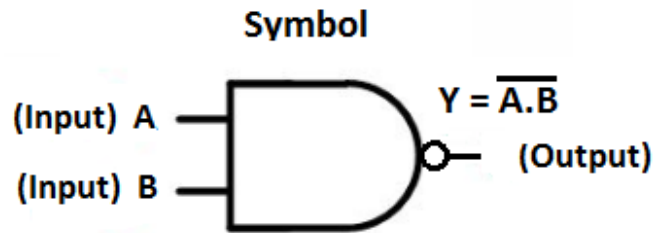
### ❖ Realization of logic gates using NAND Gates:




Truth Table

NAND		
Input		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

### ❖ NOT Gate:

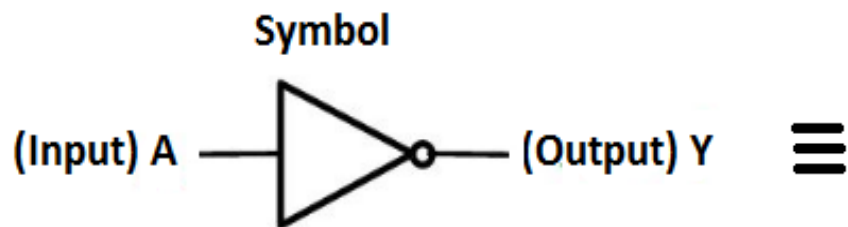


≡

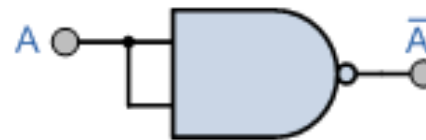


$$Y = (A.A)' = (A)' = A'$$

### ❖ AND Gate:

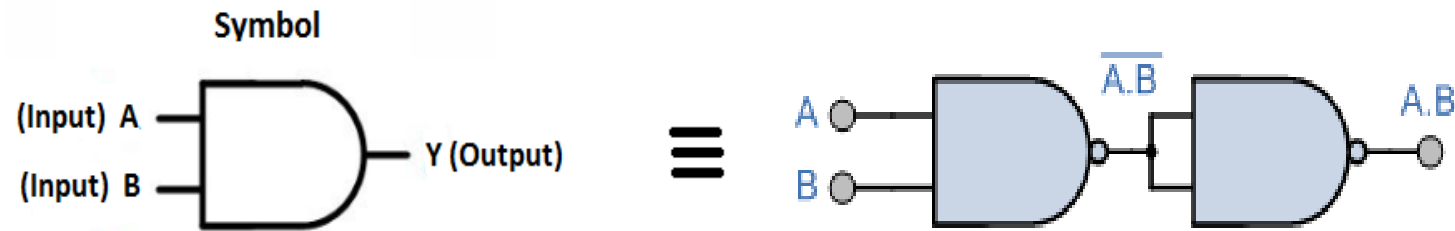


$$Y = ((A.B)')' = A.B$$

### ❖ OR Gate:

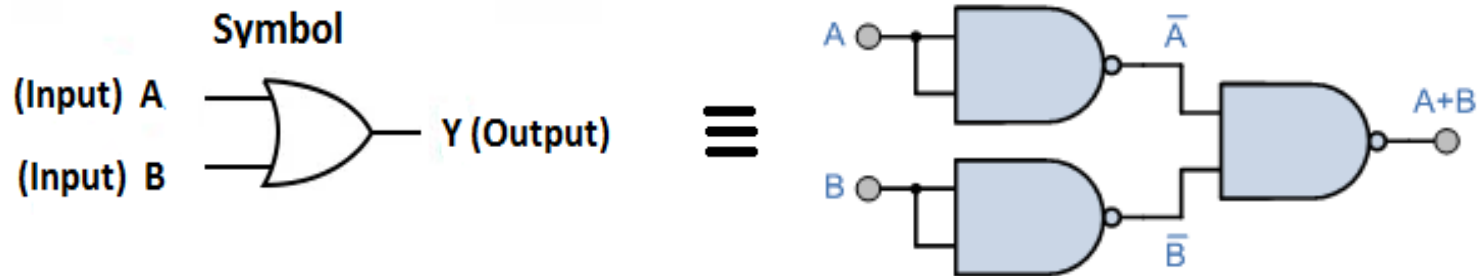


$$Y = ((A+B)')' = (A' . B')' = A+B$$


### ❖ NOR Gate:

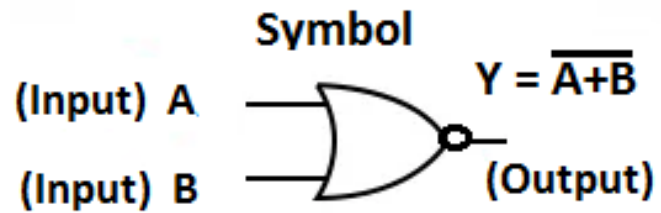


≡

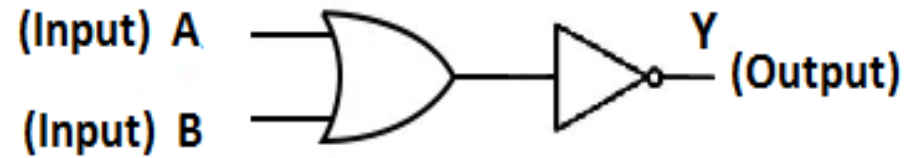

≡

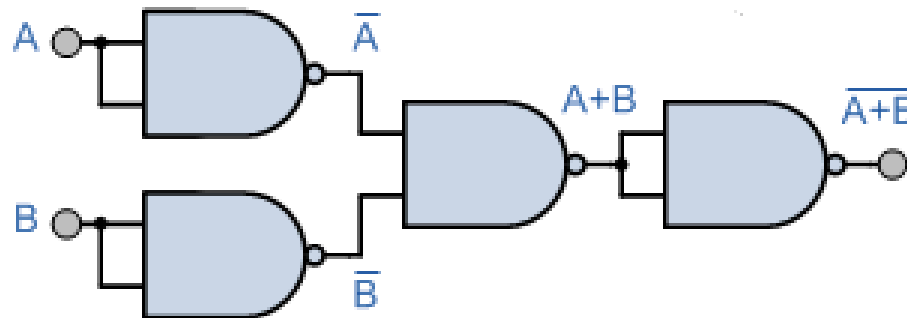

### ❖ XOR Gate:

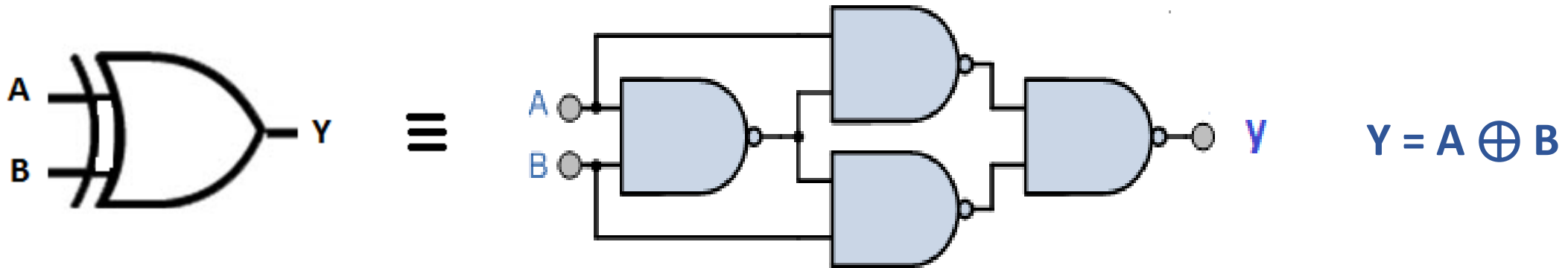

$$Y = A.B' + A'B = A (A.B)' + B. (A.B)'$$

$$Y = ((A (A.B)' + B. (A.B)'))'$$

$$Y = ( (A. (A.B)')' . (B.(A.B)')' )'$$


$$Y = A (A.B)' + B. (A.B)'$$

$$Y = A (A' + B') + B. (A' + B')$$


$$Y = A.A' + A.B' + A'.B + B.B'$$

$$Y = A.B' + A'.B$$

### ❖ XNOR Gate:

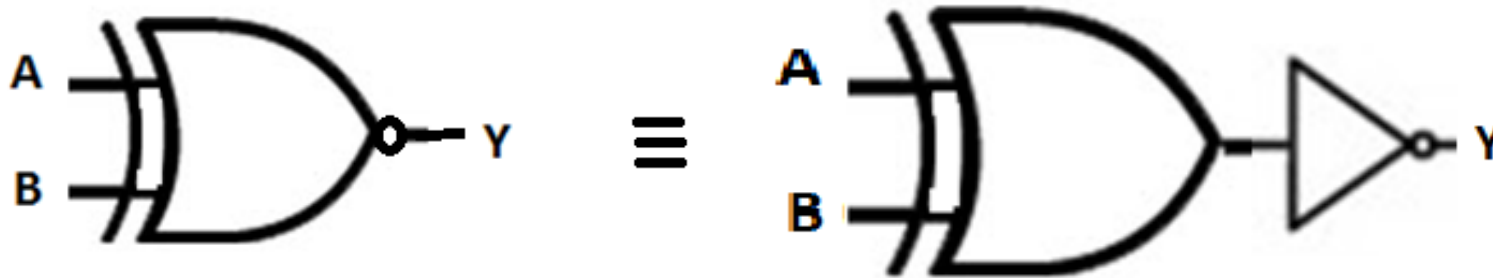


$$Y = (A \oplus B)' = A \odot B$$

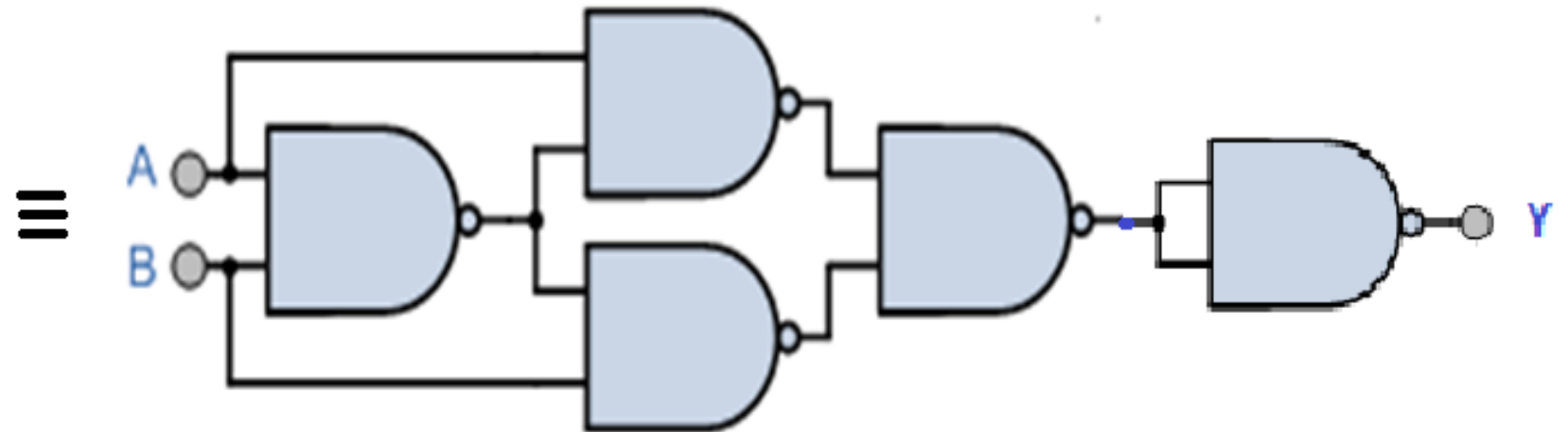



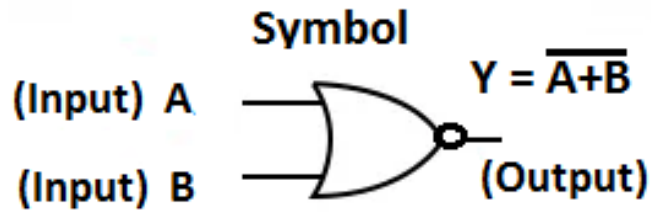
### ❖ Realization of logic gates using NOR Gates:





Truth Table

NOR		
Input		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

### ❖ NOT Gate:


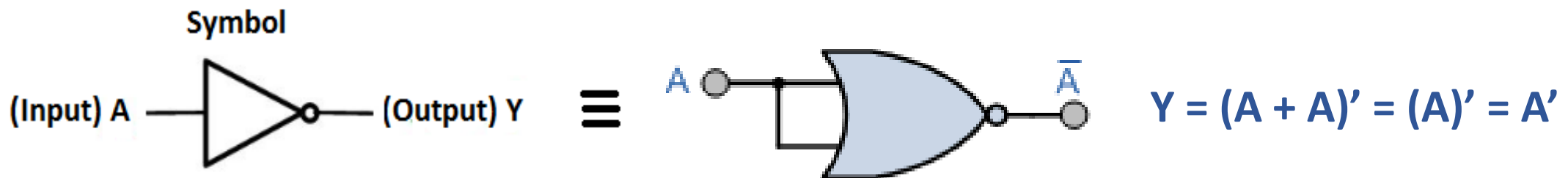


### ❖ AND Gate:

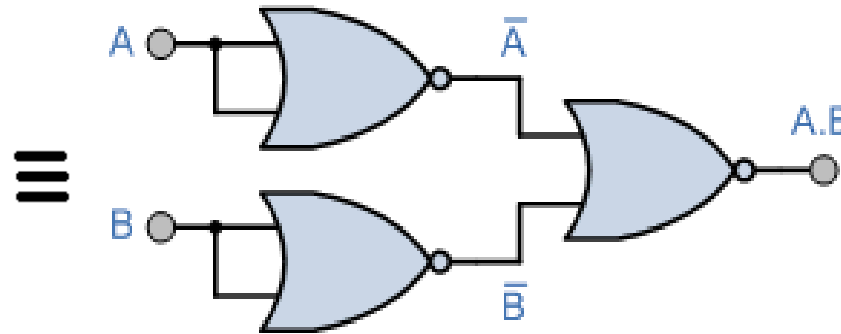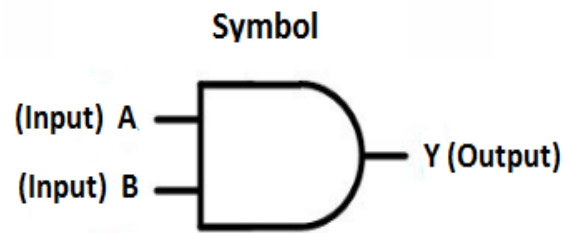


$$Y = ((A.B)')' = (A' + B')' = A.B$$

### ❖ OR Gate:

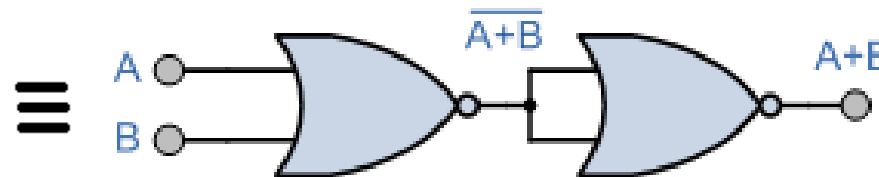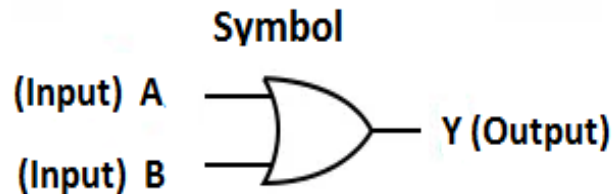


$$Y = ((A+B)')' = A + B$$


### ❖ NAND Gate:

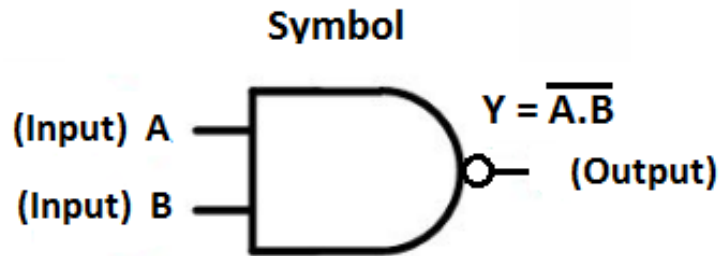


≡

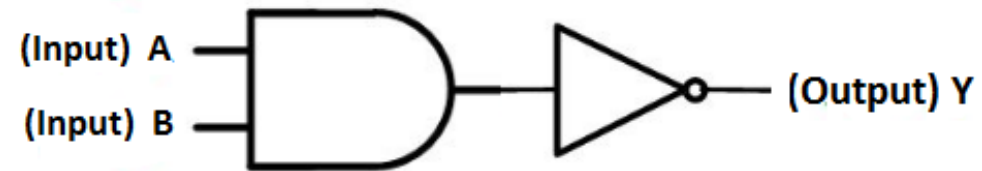

≡

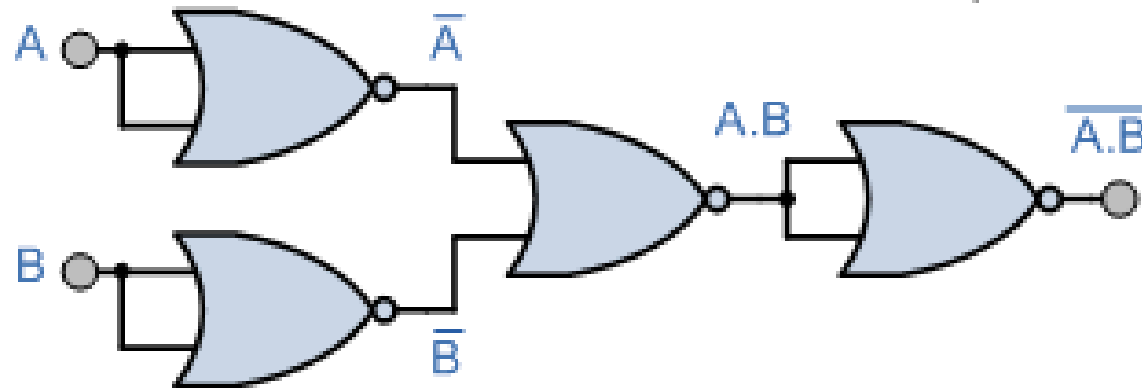

### ❖ XNOR Gate:

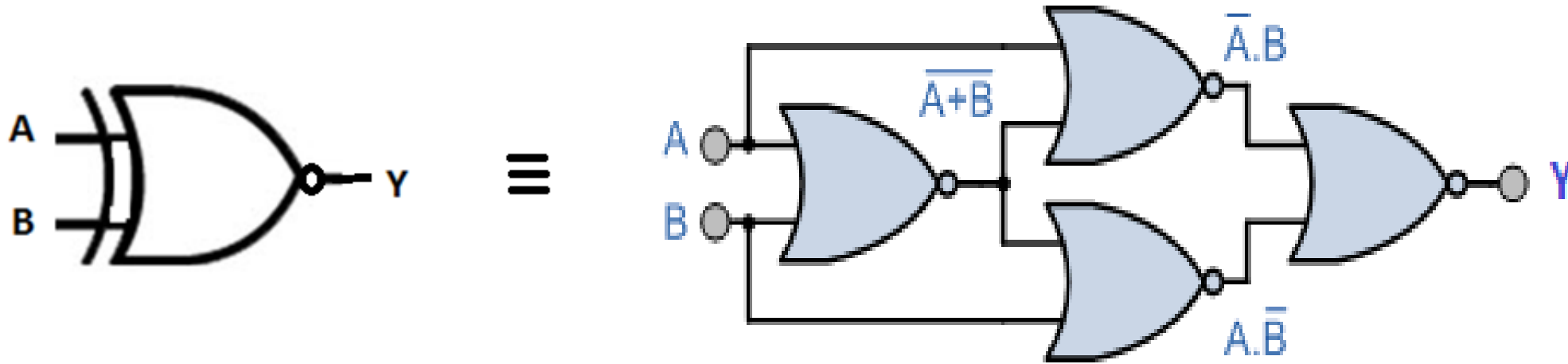

$$Y1 = ((A+B)' + A)' = (A+B). A' = A'.B$$


$$Y2 = ((A+B)' + B)' = (A+B). B' = A.B'$$

$$Y = (A'.B + A.B')' = (A'.B)' . (A.B')' = (A + B') . (A' + B)$$


$$Y = A.B + A'.B'$$

$$Y = A \odot B$$

### ❖ XOR Gate:

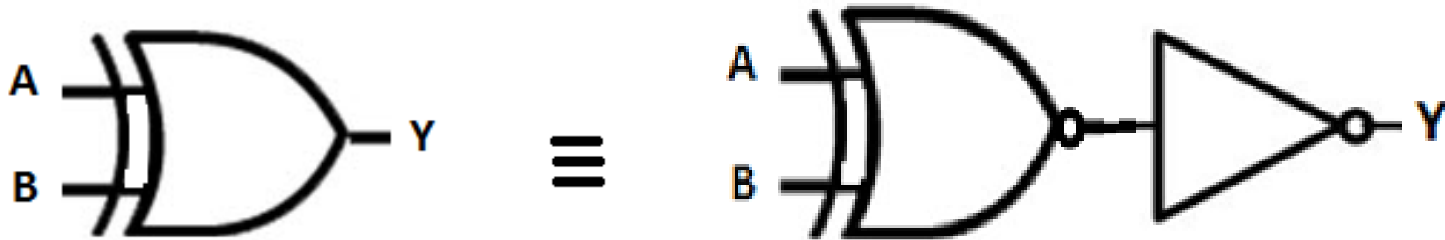

$$Y = (A \odot B)' = A \oplus B$$

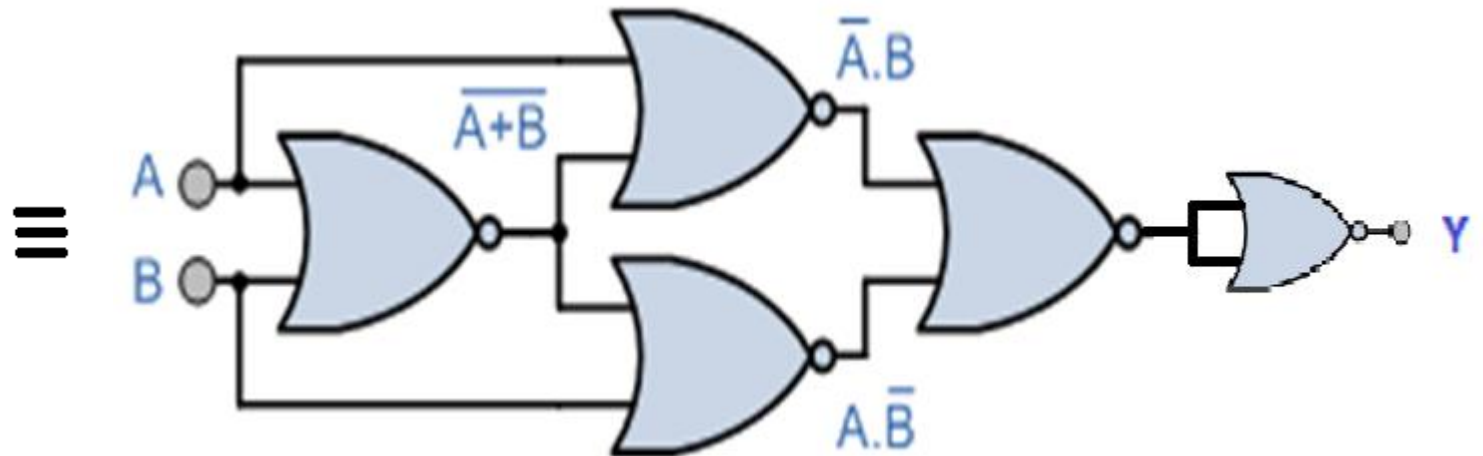


❖ Implement the given function using NAND Gates only.

$$F = X.Y + Z$$

$$F = ((X.Y + Z)')'$$

$$F = ((X.Y)' . Z')'$$

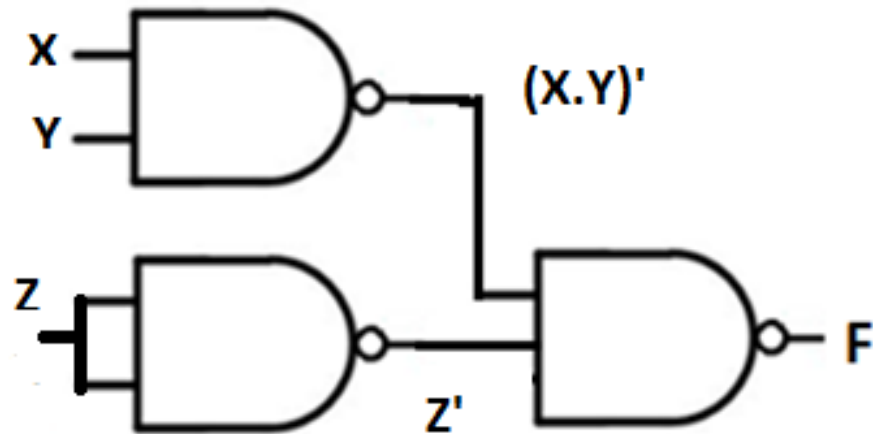



# THANK YOU

---

**Dr. Ananda M**

Department of Electronics and Communication

**[anandam@pes.edu](mailto:anandam@pes.edu)**