



# ELEMENTS OF ELECTRICAL ENGINEERING

---

**LOKESH L**

Department of Electronics & Communication Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

---


## Numerical Examples on Star Delta Transformations

**Lokesh L**

Department of Electronics and Communication Engineering

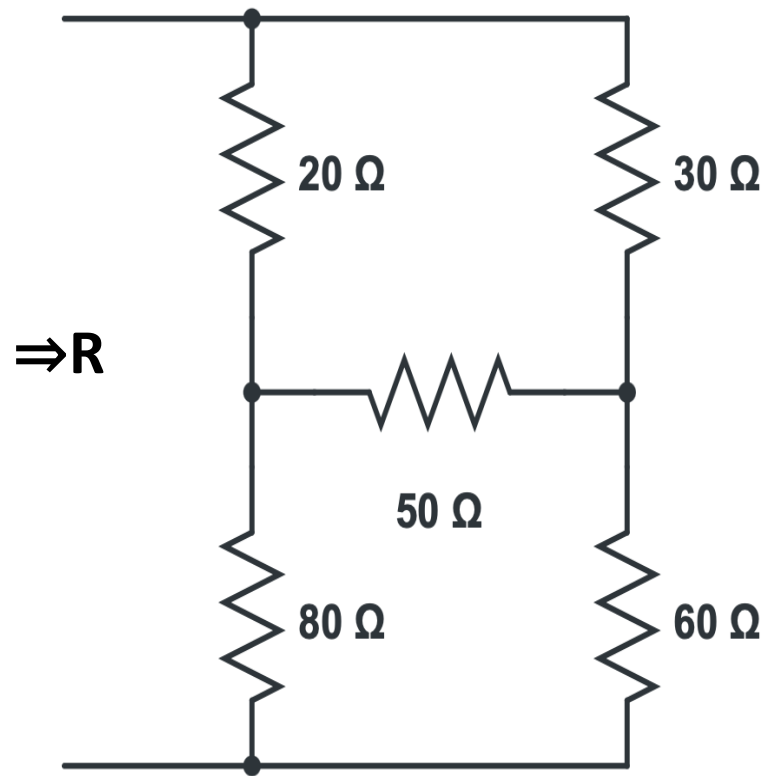
## Numerical Example 1

Find the input resistance  $R$  for network shown below :



## Numerical Example 1

**SOLUTION:**


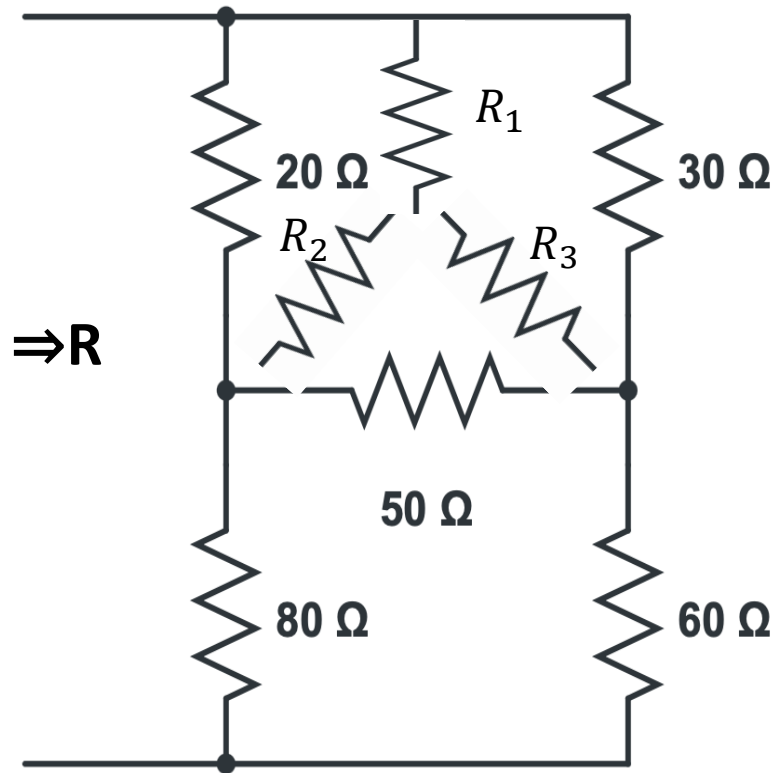


## Numerical Example 1

$$R_1 = \frac{20 \times 30}{20 + 30 + 50} = 6\Omega$$


$$R_2 = \frac{20 \times 50}{20 + 30 + 50} = 10\Omega$$
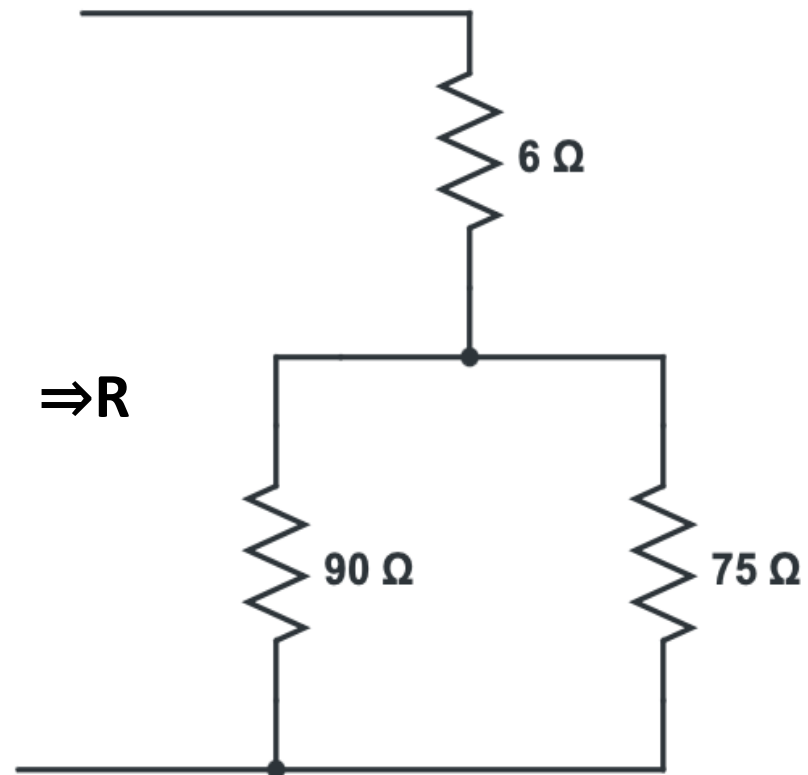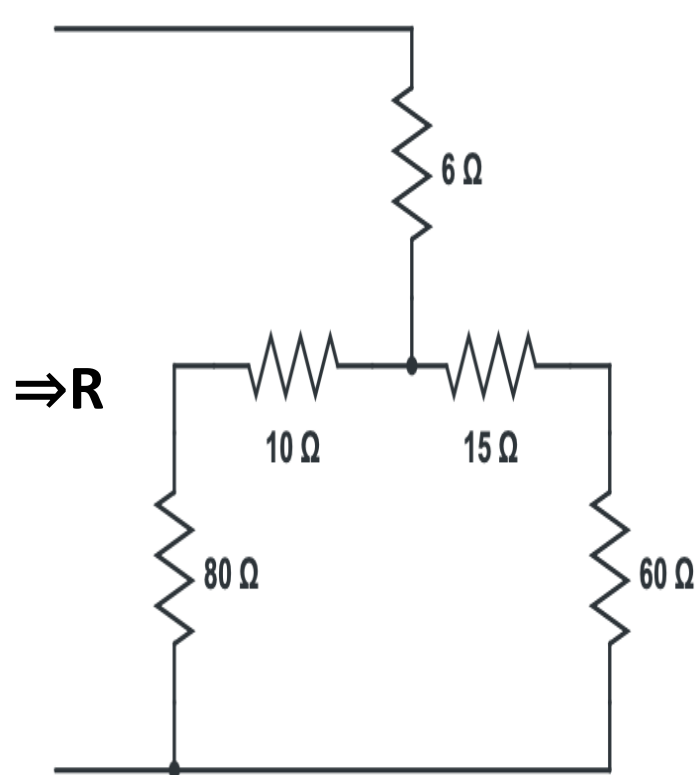
$$R_3 = \frac{30 \times 50}{20 + 30 + 50} = 15\Omega$$



# ELEMENTS OF ELECTRICAL ENGINEERING


## Numerical Example 1

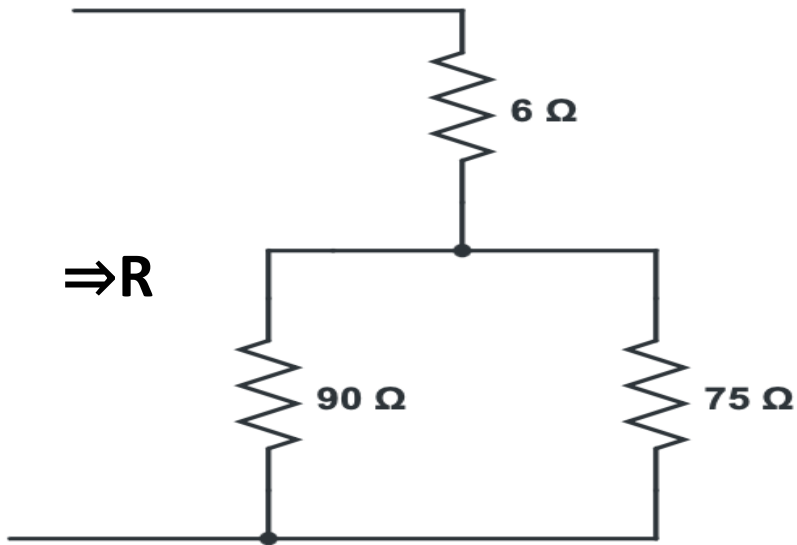



$$\begin{aligned} R &= 6 + \frac{90 \times 75}{90 + 75} \\ &= 46.9\Omega \end{aligned}$$
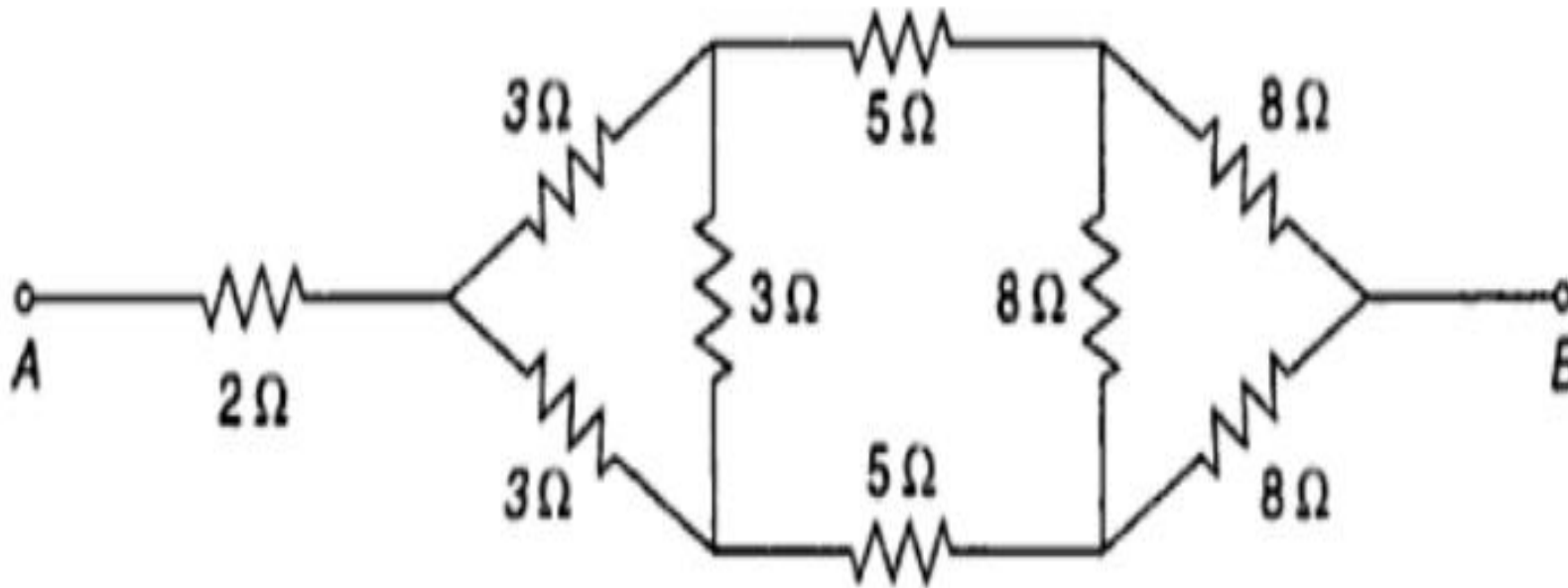
## Numerical Example 2

Find the resistance across terminals A and B in network shown below :



**SOLUTION:**

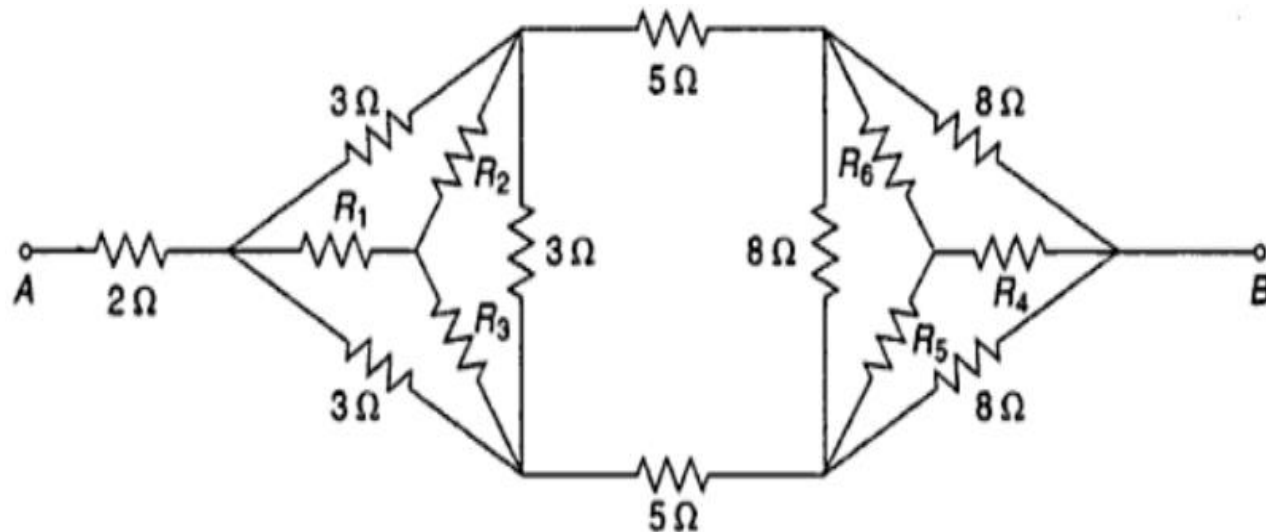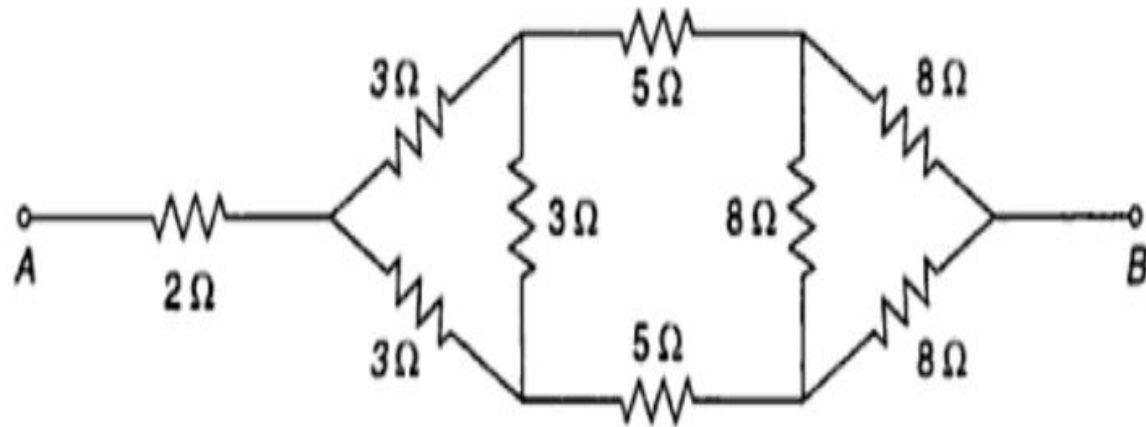




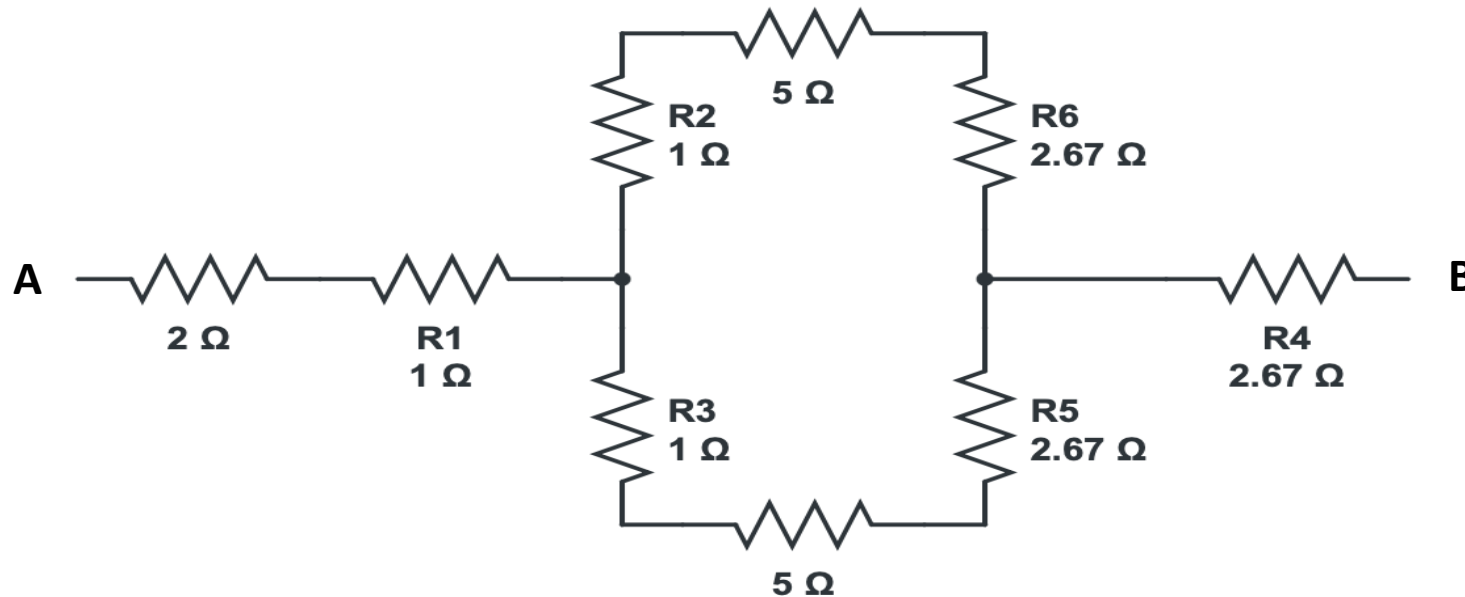
## Numerical Example 2

$$R_1 = R_2 = R_3 = \frac{3 \times 3}{3 + 3 + 3} = 1\Omega$$

$$R_4 = R_5 = R_6 = \frac{8 \times 8}{8 + 8 + 8} = 2.67\Omega$$



## Numerical Example 2

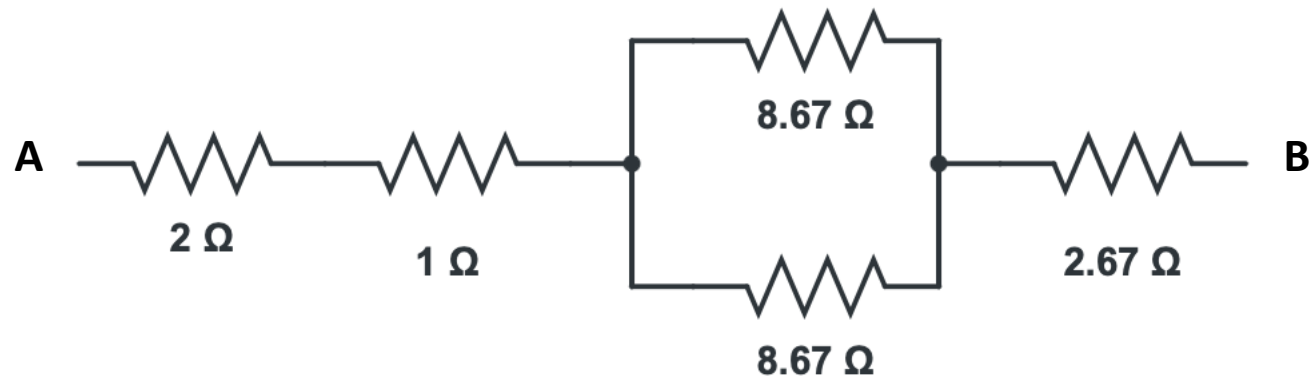


$$\frac{8.67 \times 8.67}{8.67 + 8.67} = 4.33\ \Omega$$



$$R_{AB} = 2 + 1 + 4.33 + 2.67 = 10\ \Omega$$


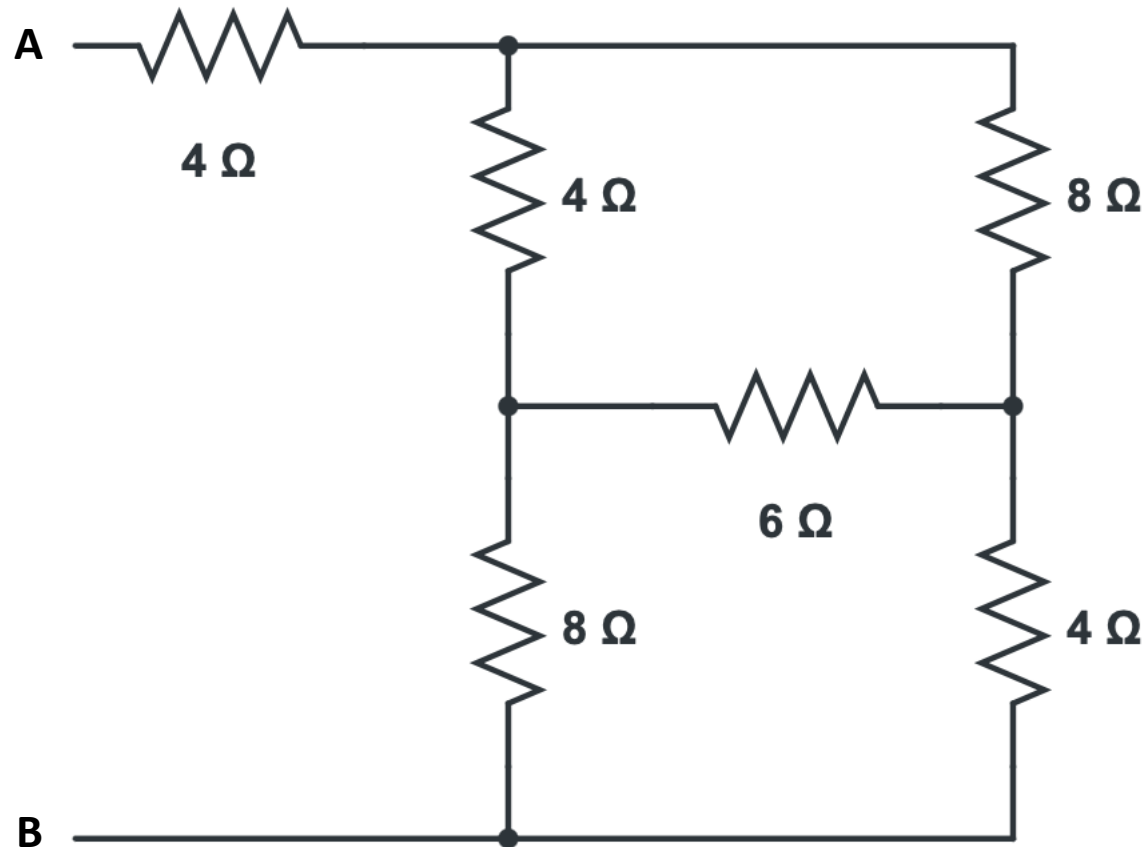
## Numerical Example 3

Find the equivalent resistance between A and B in the given network.



## Numerical Example 3

**SOLUTION:**

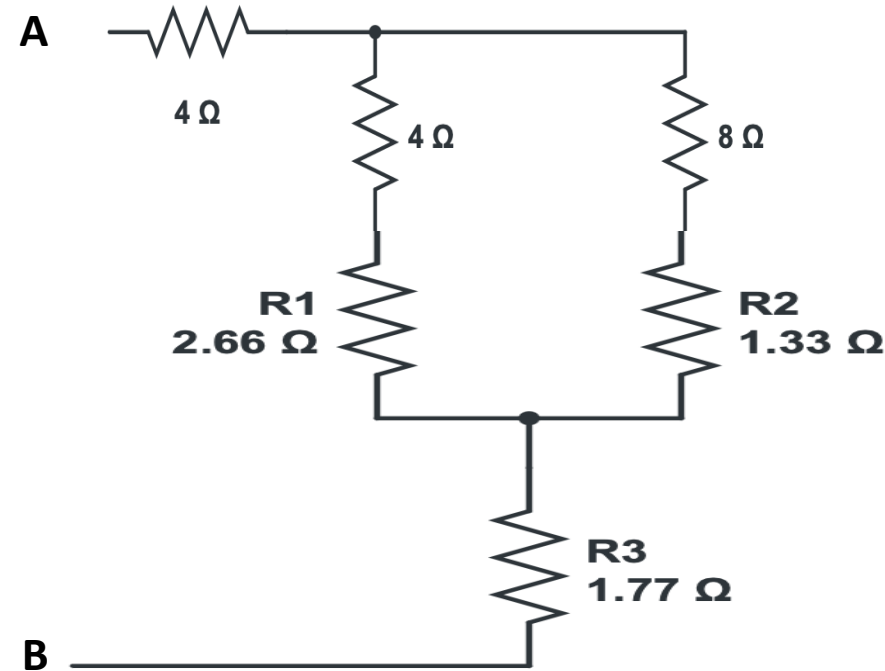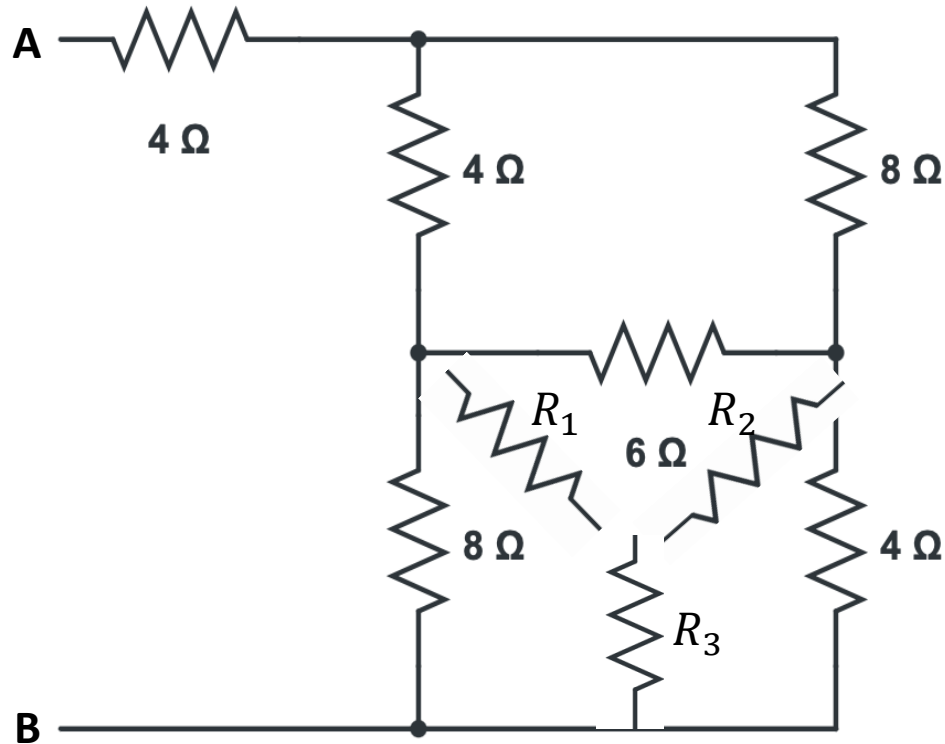


$$R_1 = \frac{8 \times 6}{8 + 6 + 4} = 2.66\Omega$$

$$R_2 = \frac{6 \times 4}{8 + 6 + 4} = 1.33\Omega$$


$$R_3 = \frac{8 \times 4}{8 + 6 + 4} = 1.77\Omega$$

## Numerical Example 3

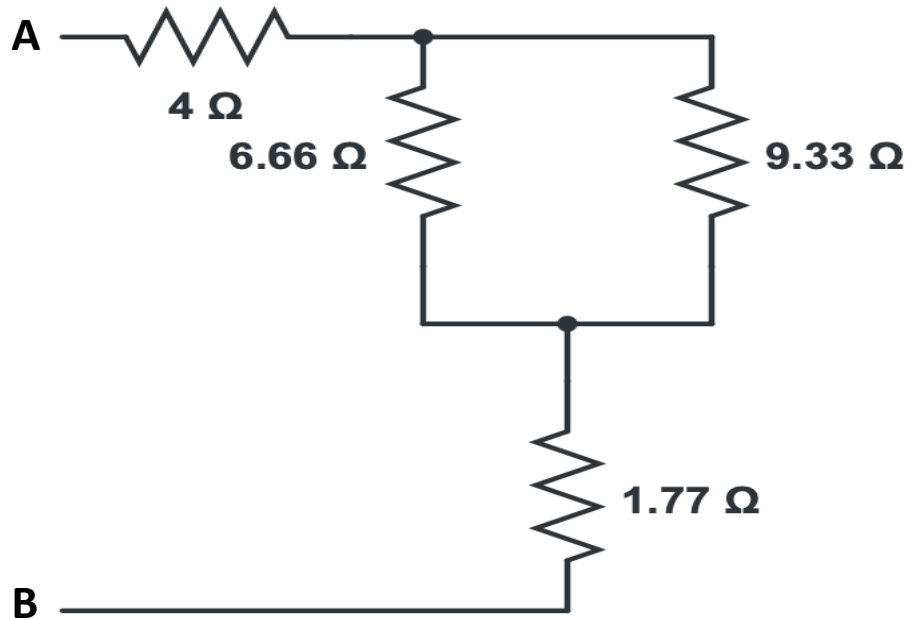

$$\frac{6.66 \times 9.33}{6.66 + 9.33} = 3.88 \Omega$$
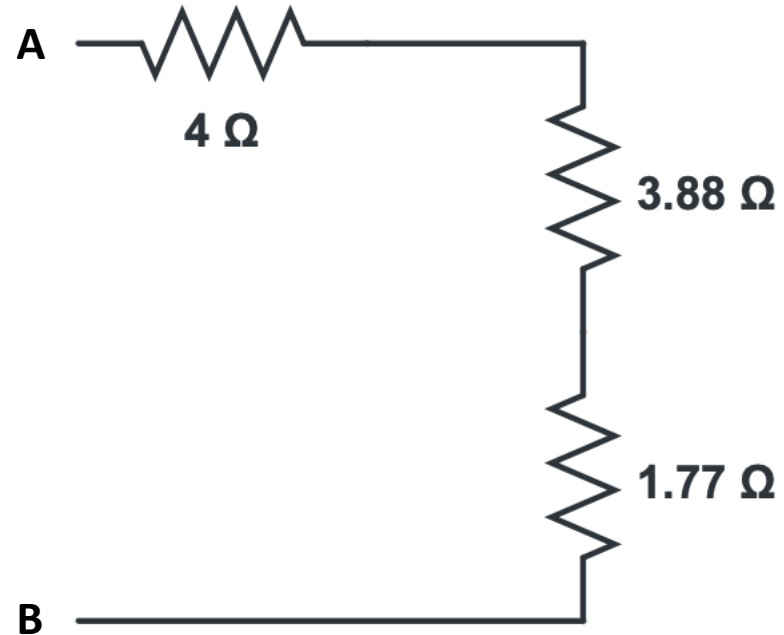
$$R_{AB} = 4 + 3.88 + 1.77 = 9.65 \Omega$$



# ELEMENTS OF ELECTRICAL ENGINEERING

## Text Book & References

---



### Text Book:

1. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup> Edition, McGraw-Hill. 2019

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



# THANK YOU

---

**LOKESH L**

Department of Electronics &  
Communication Engineering