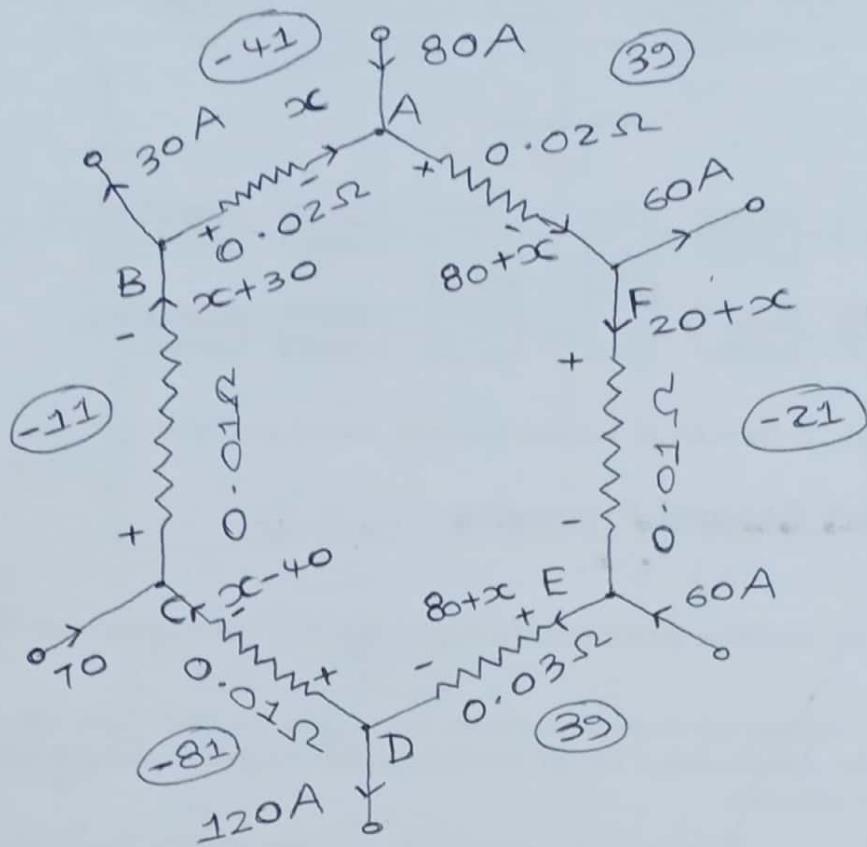


① Find the current in all the branches in the network shown :-



Solution :- Let us assume that current to be in conventional clockwise direction

$$-0.02x - 0.02(80+x) - 0.01(20+x) - 0.03(80+x)$$

$$-0.01(x-40) - 0.01(x+30) = 0$$

$$-0.02x - 0.02x - 1.6 - 0.01x - 0.2 - 0.03x - 2.4$$

$$-0.01x + 0.4 - 0.01x - 0.3 = 0$$


$$-0.1x = 4.1$$

$$\boxed{x = -41 \text{ A}}$$

current flow is in opposite direction

(2)

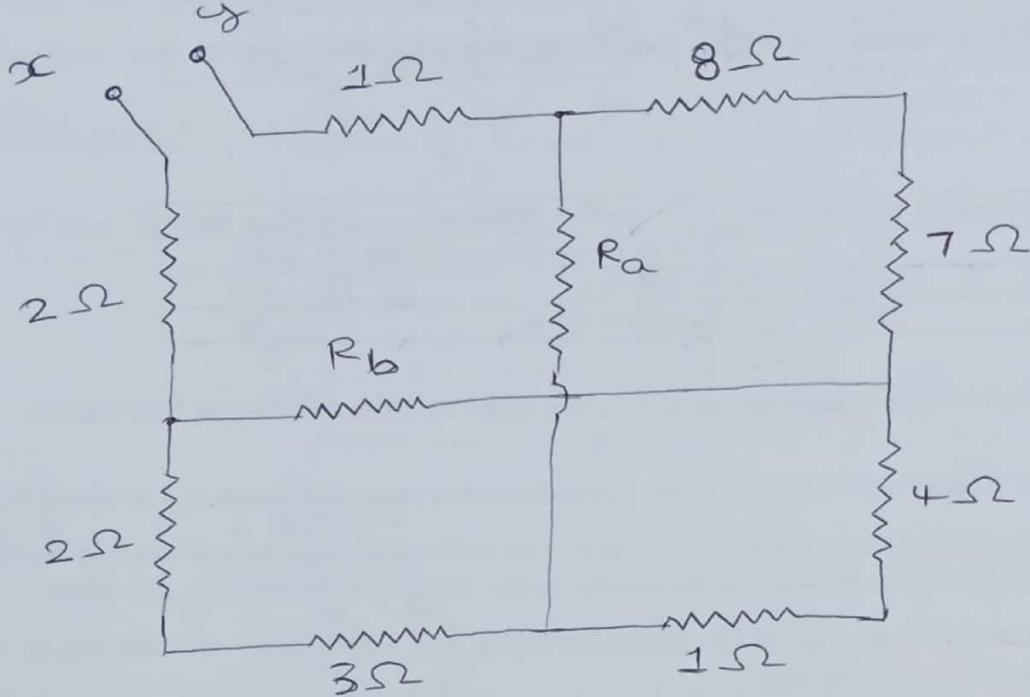2) Find the equivalent resistance between x & y




$$\text{i)} R_a = \infty, R_b = \infty$$

\rightarrow both are open circuit

$$R_{xy} = 28\Omega$$


$$\text{ii)} R_a = 0, R_b = \infty$$

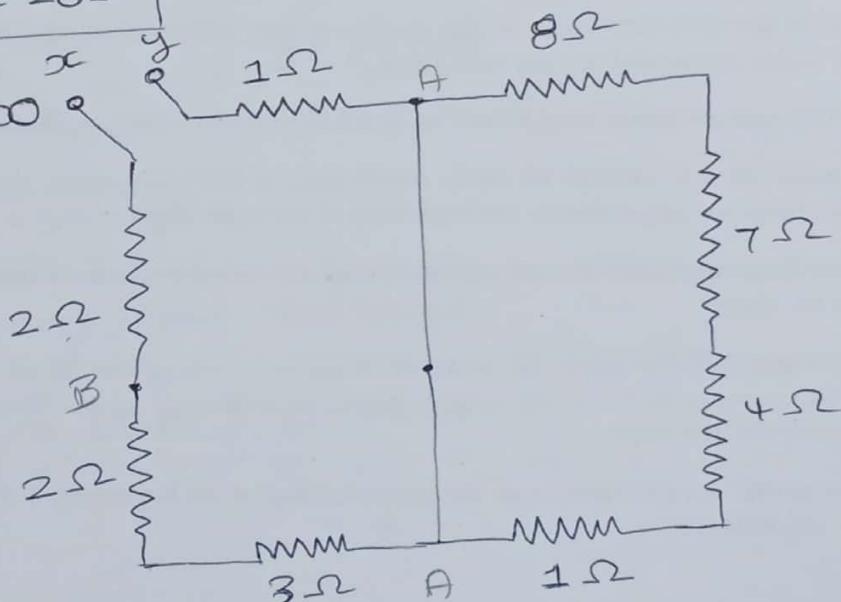

$$R_{xy} = 8\Omega$$

iii) $R_a = \infty$; $R_b = 0$

(3)


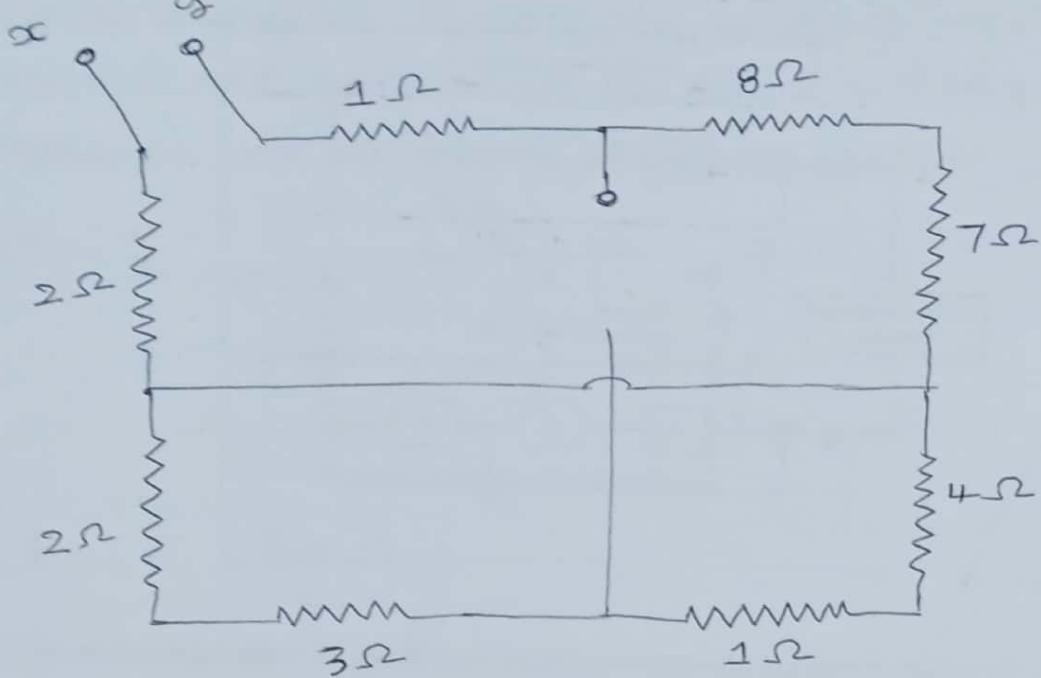


$$R_{xy} = 18\Omega$$

iv) $R_a = 0$; $R_b = 0$


$$\frac{5 \times 5}{10} = \frac{25}{10} = \frac{5}{2}$$

$$\frac{5 \times 15}{2} = \frac{75}{2}$$

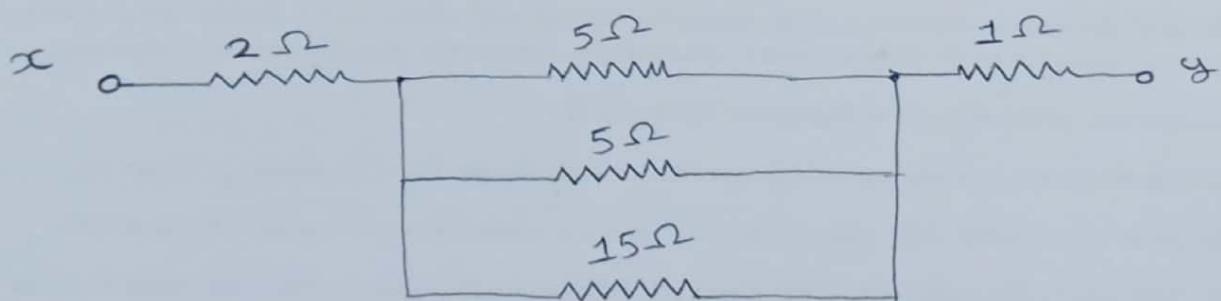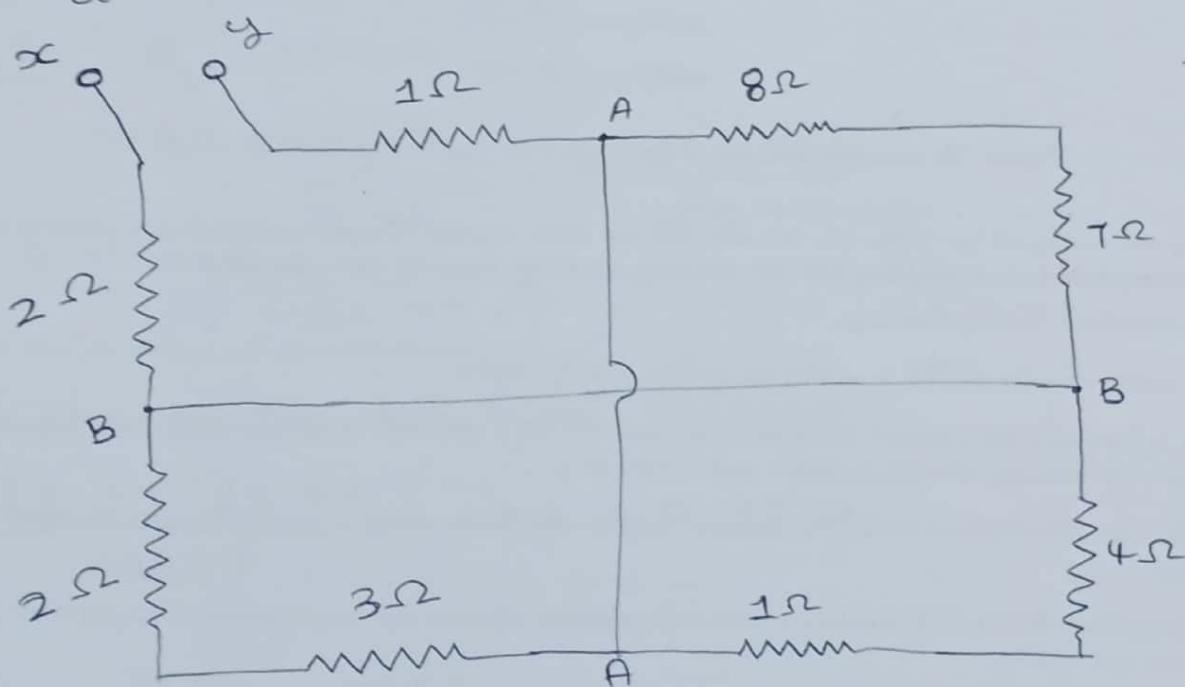

③ A battery of EMF 12V and internal resistance 0.05Ω supplies power to a load resistance R_L . Determine the % change in load voltage as load resistance varies from 10Ω to 100Ω . ④

Solution :-

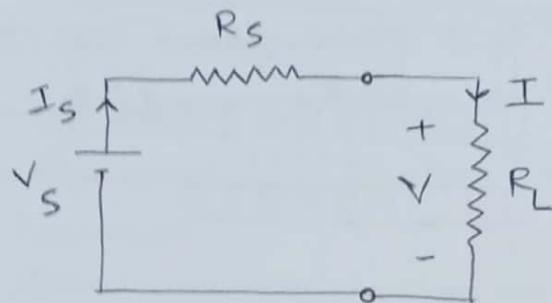

case 1 $R_L = 10\Omega$

$$V = \frac{V_s \cdot R_L}{R_s + R_L} = \frac{12 \times 10}{10 + 0.05}$$

$$\boxed{V = 11.94V}$$

case 2 $R_L = 100\Omega$

$$V = \frac{V_s \cdot R_L}{R_s + R_L} = \frac{12 \times 100}{100 + 0.05}$$


$$\boxed{V = 11.99V}$$

% change in the load voltage

$$\frac{11.99 - 11.94}{11.94} \times 100 = 0.42\%$$

4) Two batteries A and B are connected in parallel (5)
 and a load of 10Ω is connected across them. Battery A has an EMF of 9V and internal resistance of 0.5Ω and B has an EMF of 12V and internal resistance of 1Ω . Determine i) the magnitude & direction of current flowing through load resistance ii) current supplied by each battery and iii) potential difference across the load resistance

Solution

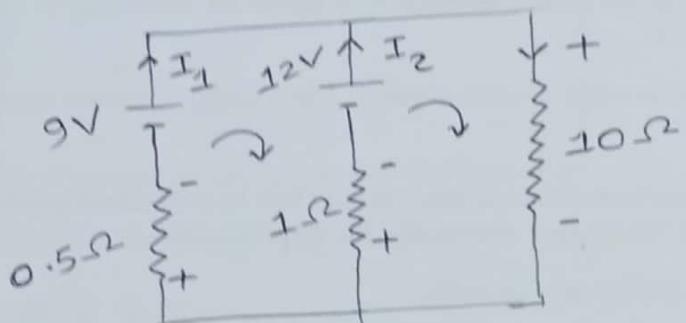

loop ①

$$9 - 12 + I_2 - 0.5I_1 = 0$$

$$I_2 - 0.5I_1 = 3V$$

loop ②

$$12 - 10(I_1 + I_2) - I_2 = 0$$

$$12 - 10I_1 - 10I_2 - I_2 = 0$$

$$11I_2 + 10I_1 = 12$$

Solving for I_1 & I_2


$$\left. \begin{array}{l} I_1 = -1.35A \\ I_2 = 2.322A \end{array} \right\} \begin{array}{l} \text{current supplied} \\ \text{by each battery} \end{array}$$

$$\text{Current through } 10\Omega = I_1 + I_2 = 0.972A$$

$$\begin{aligned} \text{Potential difference across } 10\Omega &= 0.972 \times 10 \\ &= 9.72V \end{aligned}$$

5) Find the current through 5Ω resistor in the network shown :-

(6)

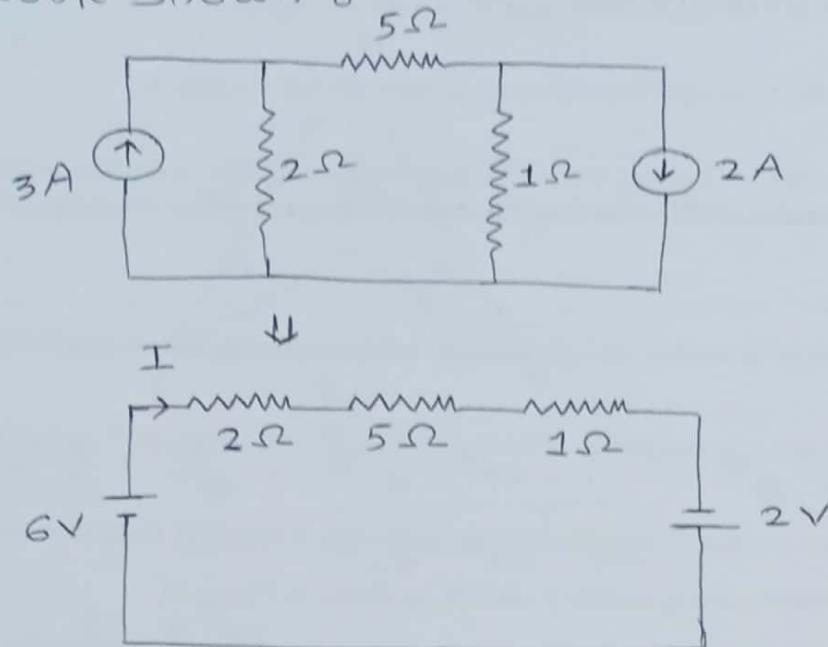


$$6 - 2I - 5I - I + 2 = 0$$

$$8 = 8I$$

$$\boxed{I = 1A}$$

Star-Delta transformation

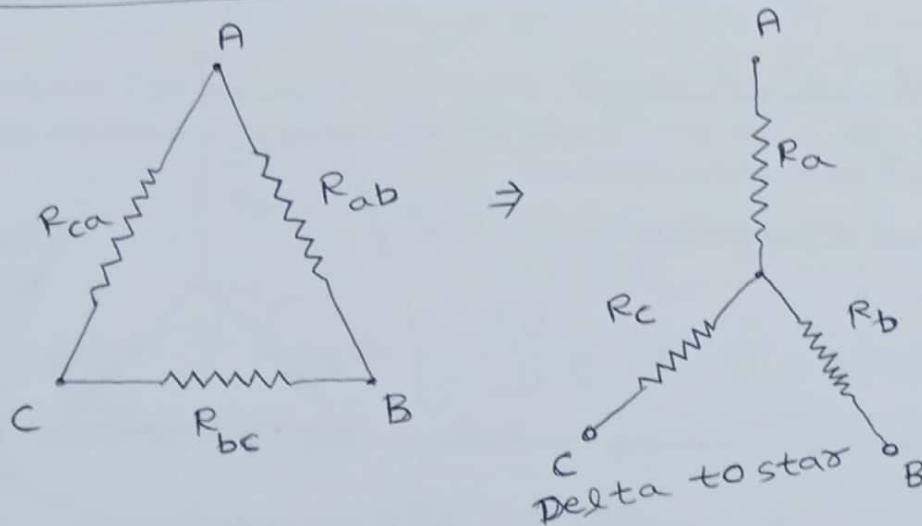


$$R_a = \frac{R_{ab} * R_{ca}}{R_{ab} + R_{bc} + R_{ca}} ; R_b = \frac{R_{bc} * R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{ca} * R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

$$\text{star to delta} \quad R_{ab} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_a}$$

$$R_{bc} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_b} ; R_{ca} = \frac{R_c}{R_a * R_b + R_b * R_c + R_c * R_a}$$

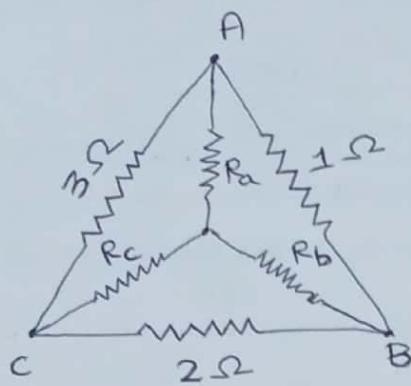1) Transform the given delta to equivalent star?




Solution :-

$$R_{ba} = \frac{R_{ab} \cdot R_{bc}}{R_{ab} + R_{bc} + R_{ca}} ; R_{a} = \frac{R_{ab} * R_{ca}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{ac} * R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_b = \frac{1 * 2}{6} = \frac{1}{3} \Omega ; R_a = \frac{3}{6} = \frac{1}{2} \Omega ; R_c = \frac{2 * 3}{6} = 1 \Omega$$

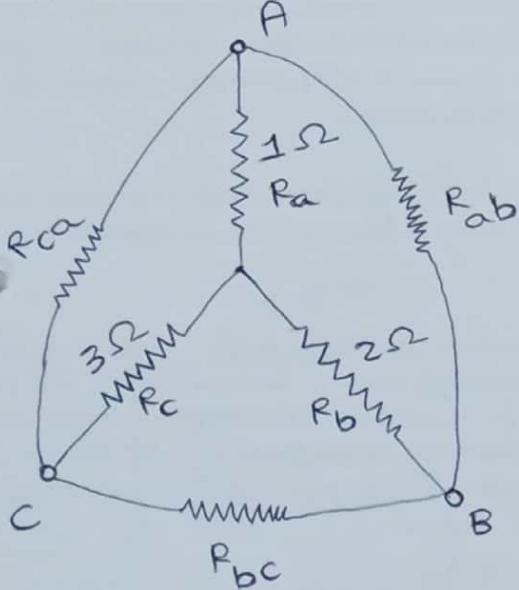2) Transform the given star to equivalent delta?



$$R_{bc} = \frac{R_a \cdot R_b + R_b \cdot R_c + R_c \cdot R_a}{R_b}$$

$$R_{bc} = \frac{1 \times 2 + 2 \times 3 + 3 \times 1}{1} = 11 \Omega$$


$$R_{ca} = \frac{R_a \times R_b + R_b \times R_c + R_c \times R_a}{R_b}$$

$$\boxed{R_{ca} = 11 \frac{1}{2} \Omega}$$


$$R_{ab} = \frac{R_a \cdot R_b + R_b \cdot R_c + R_c \cdot R_a}{R_c}$$

$$\boxed{R_{ab} = 11 \frac{1}{3} \Omega}$$


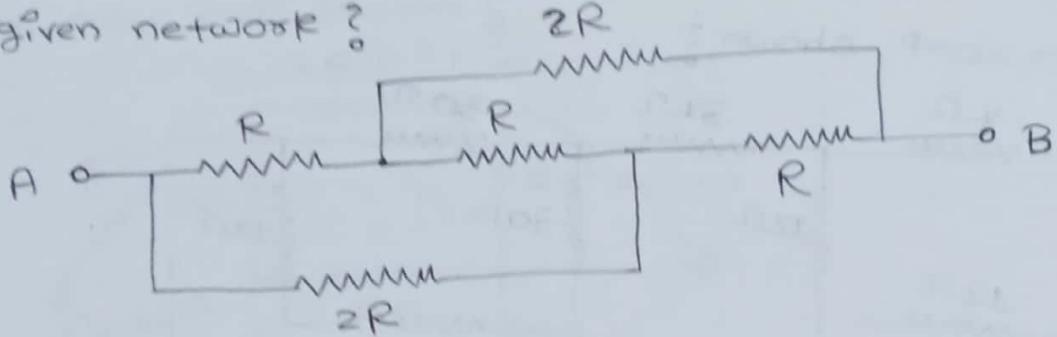
3) Find the equivalent resistance between the terminals A & B in the given network? (8)



Solution :-

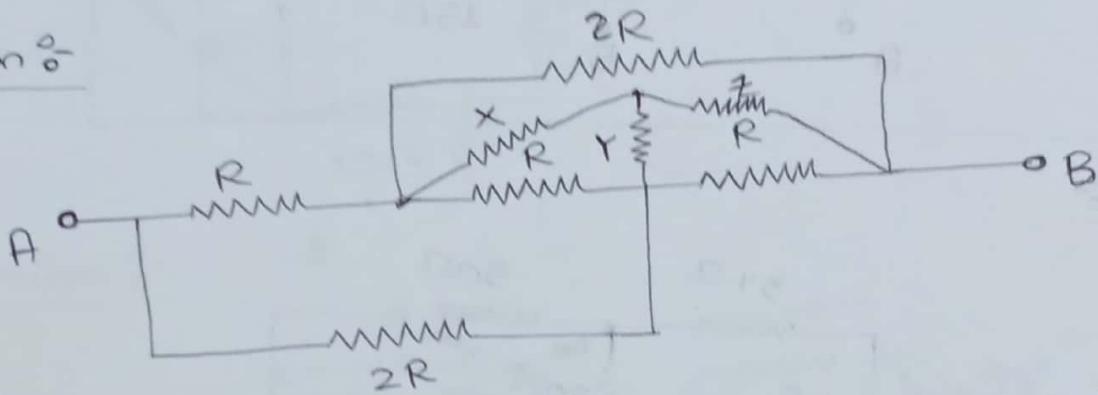

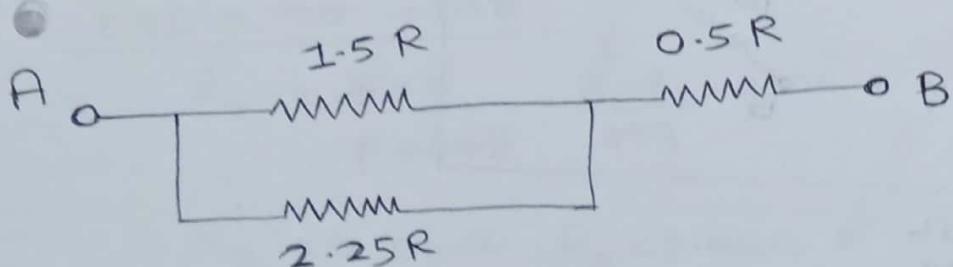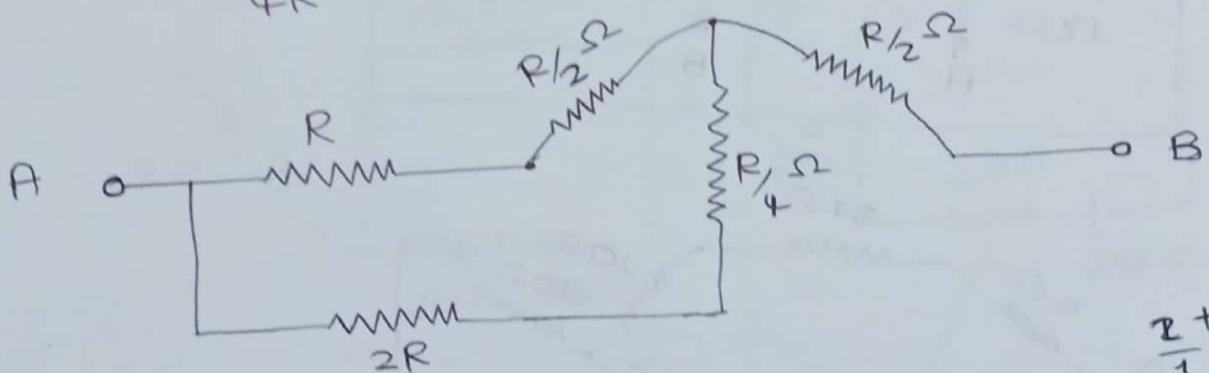
$$X = \frac{R \times 2R}{4R} = R/2 \Omega; Y = \frac{R \times R}{4R} = R/4 \Omega; Z = \frac{2R \times R}{4R} = R/2 \Omega$$



$$\frac{\frac{1}{2} + \frac{1}{4}}{1} = \frac{8+1}{4} = \frac{9}{4}$$


$$\begin{array}{r} 2.25 \\ 4) 9 \\ \underline{-8} \\ \frac{10}{20} \\ \frac{8}{20} \end{array}$$
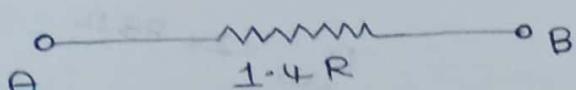
$$\frac{1.5R \times 2.25R}{3.75R} = 0.9R$$






⑨

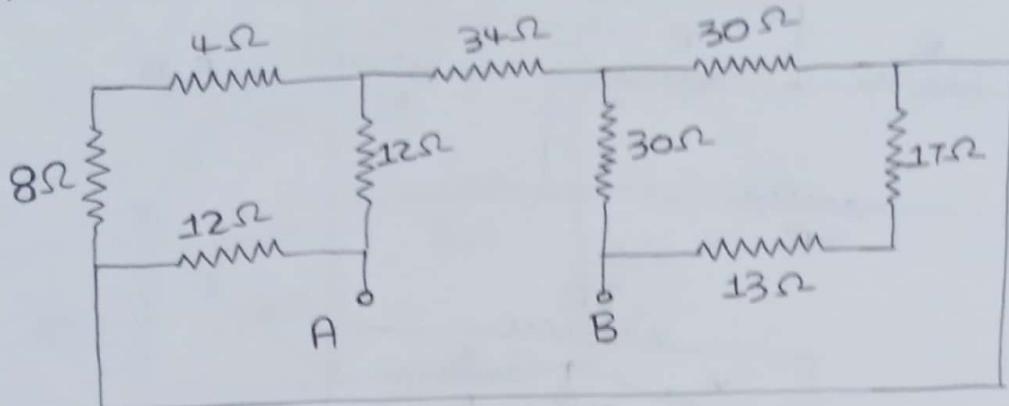4) Find the equivalent resistance between the terminals A & B in the network shown?




Solution :-

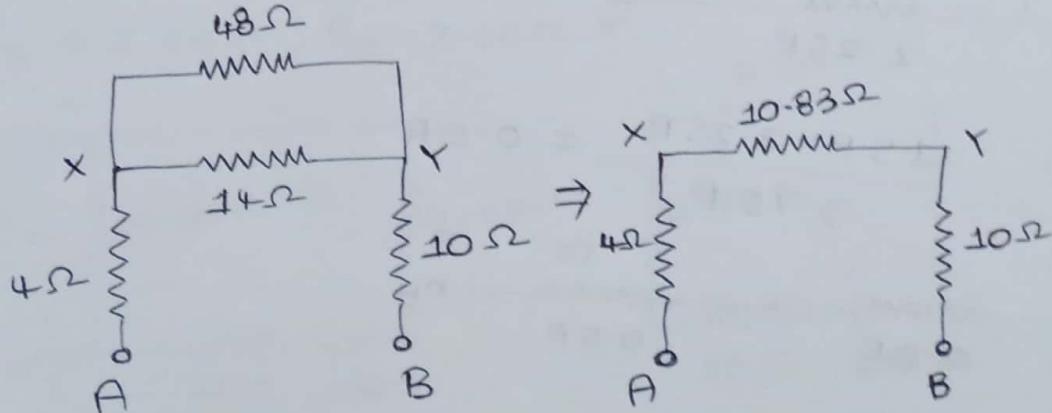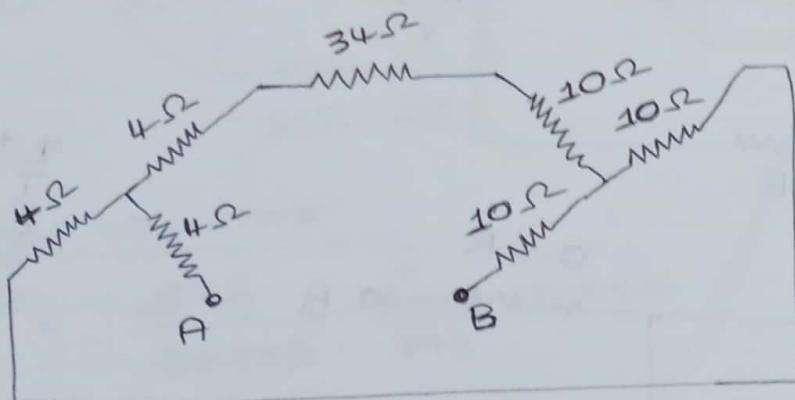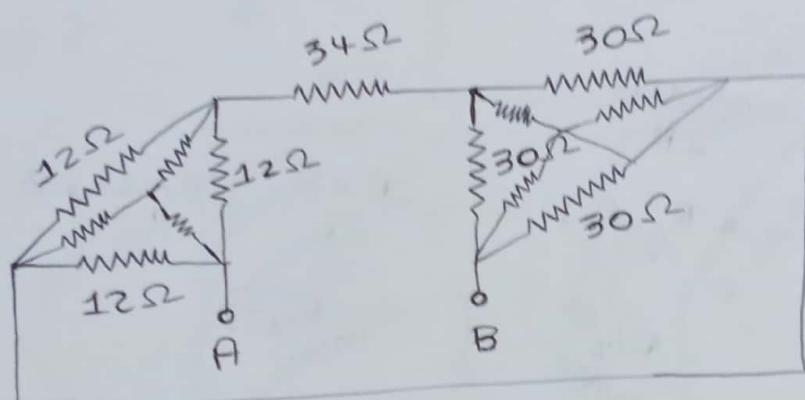


$$R_{AB} = 24.83\Omega$$

5) Find the voltage drop across 10Ω resistor in the network shown ?

(10)

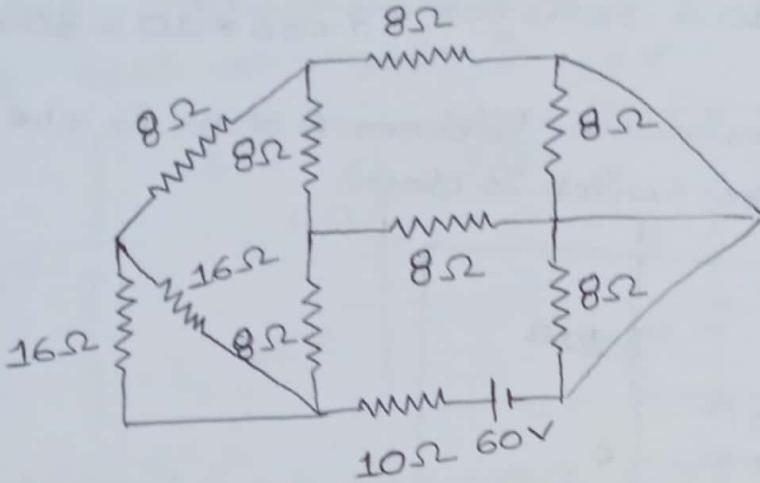


solution :-

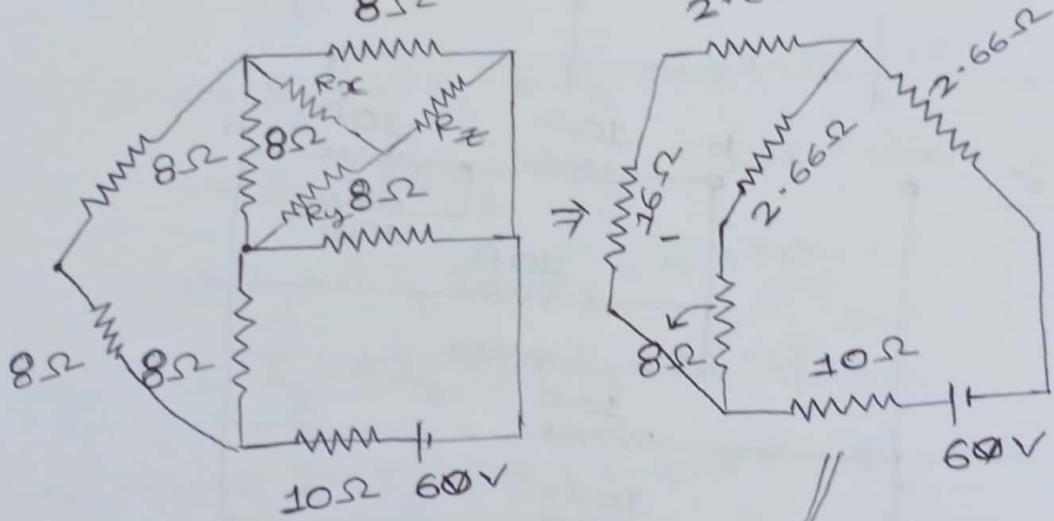

Delta to star

$$R_x = \frac{8 \times 8}{8 \times 8 \times 8} = \frac{1}{243} = 2.66\Omega$$

$$R_y = 2.66\Omega ; R_z = 2.66\Omega$$

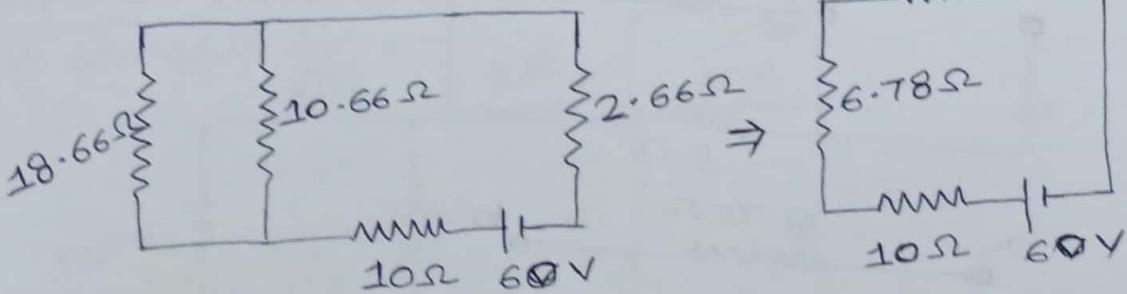


(11)





current delivered by 60V source, $I_s = \frac{60}{R_{\text{eq}}} = \frac{60}{19.44} = 3.086 \text{ A}$

voltage drop across 10Ω resistor = $3.086 * 10 = 30.86 \text{ V}$

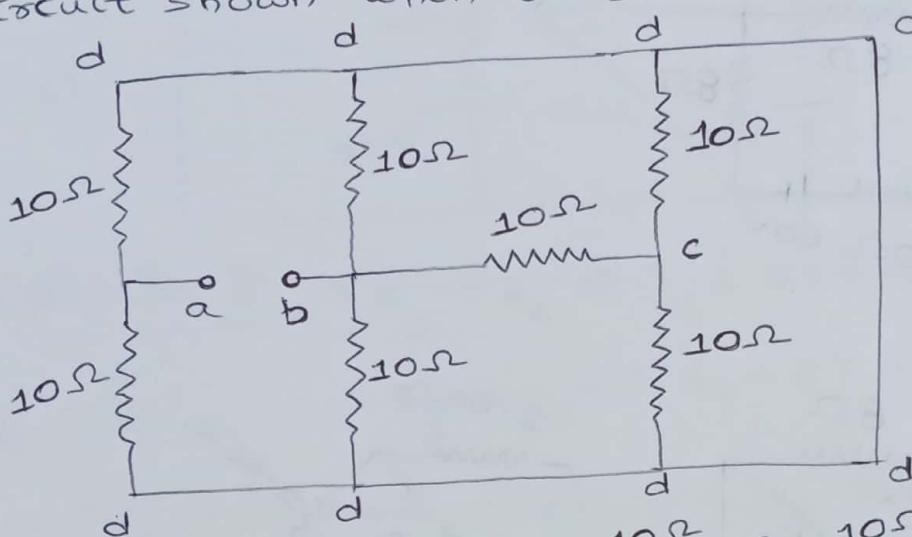Find the equivalent resistance between A & B in the circuit shown when the switch is closed




Solution :-

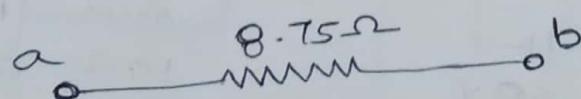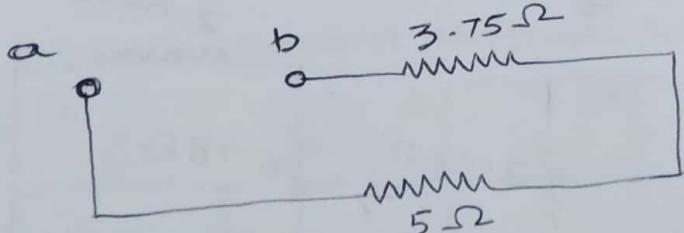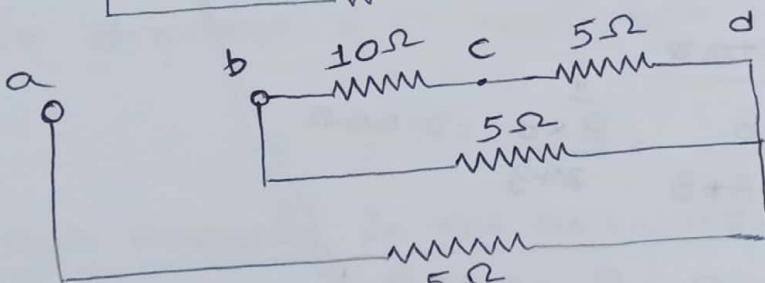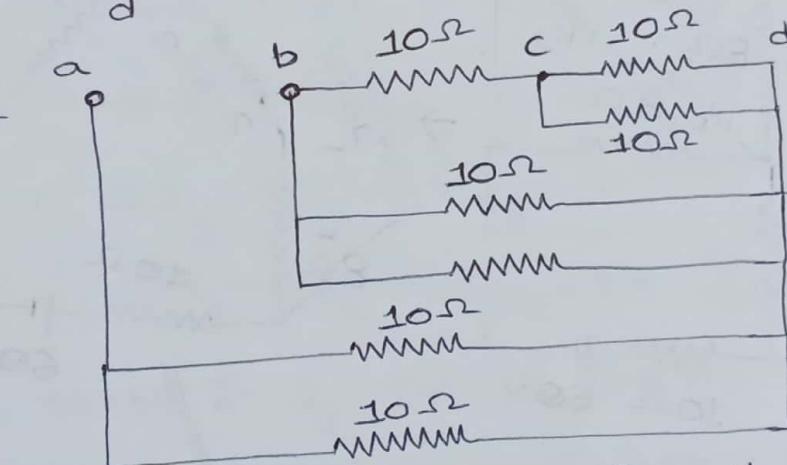

Lecture 7 - Mesh Analysis

(12)

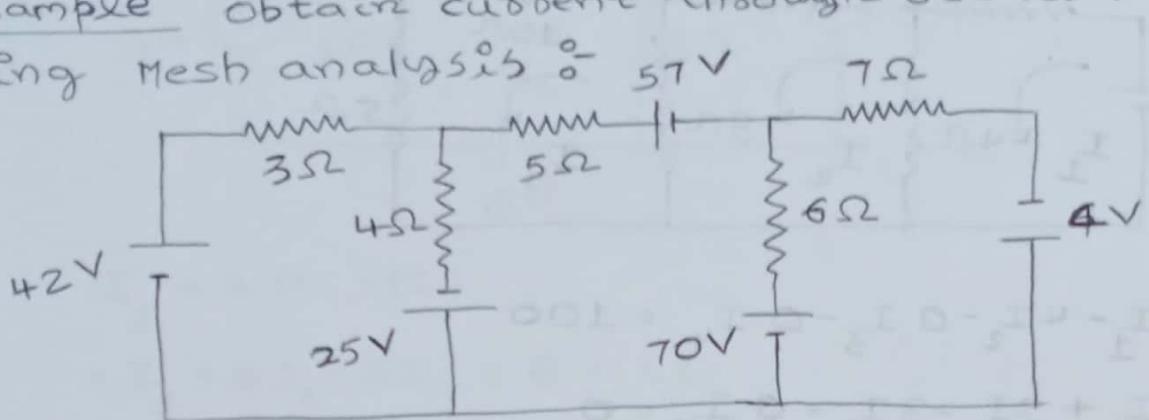Example obtain current through 6Ω resistor using mesh analysis



Solution \therefore $7I_1 - 4I_2 - 0 \cdot I_3 = 25 + 42$

$$7I_1 - 4I_2 - 0 \cdot I_3 = 67 \quad \textcircled{1}$$

$$-4I_1 + 15I_2 - 6I_3 = -57 - 70 + 25$$

$$-4I_1 + 15I_2 - 6I_3 = -102 \quad \textcircled{2}$$

$$0 \cdot I_1 - 6I_2 + 13I_3 = 4 + 70$$

$$0 \cdot I_1 - 6I_2 + 13I_3 = 74 \quad \textcircled{3}$$

Solving these $\therefore I_1 = 5A; I_2 = -8A; I_3 = 2A$


current through 6Ω resistor $= I_2 \sim I_3$

$$= 10A$$


Lecture 8 - Mesh Analysis in the Networks with current sources

Example 1 Obtain current through 4Ω resistor using mesh analysis

Mesh analysis?

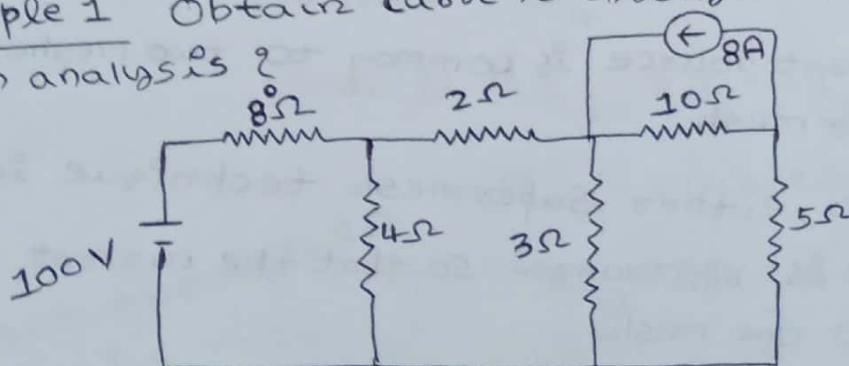

(13)

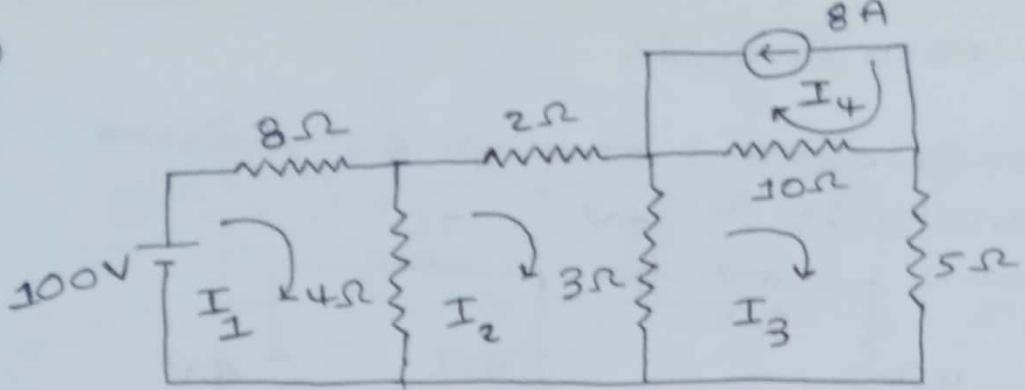

$$12I_1 - 4I_2 - 0 \cdot I_3 - 0 \cdot I_4 = 100$$

$$-4I_1 + 9I_2 - 3I_3 - 0 \cdot I_4 = 0$$

$$0 \cdot I_1 - 3I_2 + 18I_3 - 10I_4 = 0$$


$$I_4 = -8$$

Solving (1) (2) (3) & (4)

$$I_1 = 9.26 \text{ A}; I_2 = 2.79 \text{ A}; I_3 = -3.57 \text{ A}$$


$$\text{current through } 4\Omega \text{ resistance} = I_1 - I_2 = 6.47 \text{ A}$$

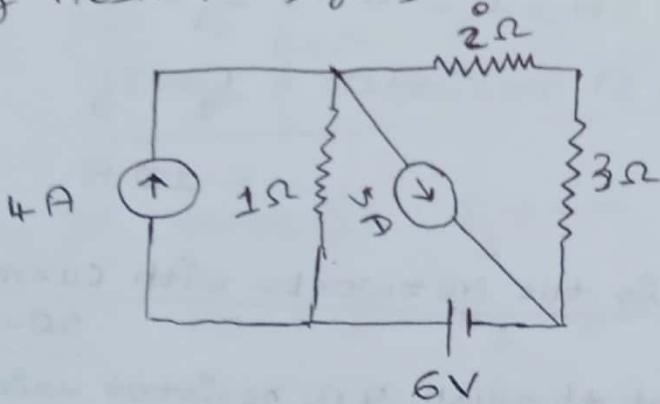Example 2 obtain Voltage across 3Ω resistor
using Mesh Analysis ?



→ whenever a current source is common to two meshes, it creates a supermesh.

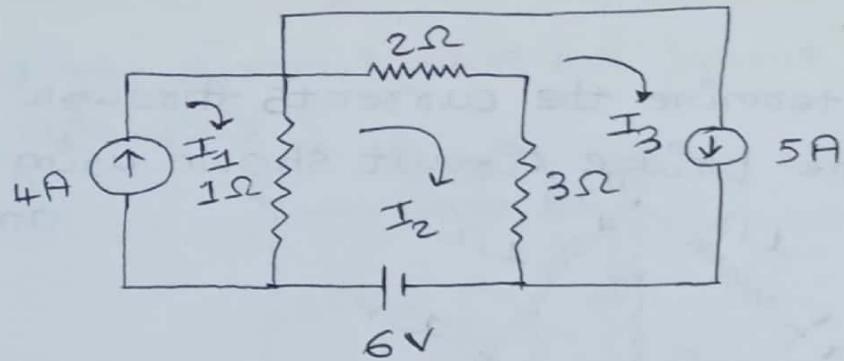→ In such networks, either Supermesh technique is applied or network is rearranged so that the current source is confined to one mesh.



$$I_1 = 4 \text{ A} \quad \text{--- (1)}$$

$$-I_1 + 6I_2 - 5I_3 = 6 \quad \text{--- (2)}$$


$$I_3 = 5 \text{ A} \quad \text{--- (3)}$$

$$\text{Solving for (1), (2) \& (3)} \quad I_2 = 5.83 \text{ A}$$

Current through 3Ω = $I_2 \sim I_3 = 0.83 \text{ A}$

Voltage across 3Ω resistor = 2.49 V

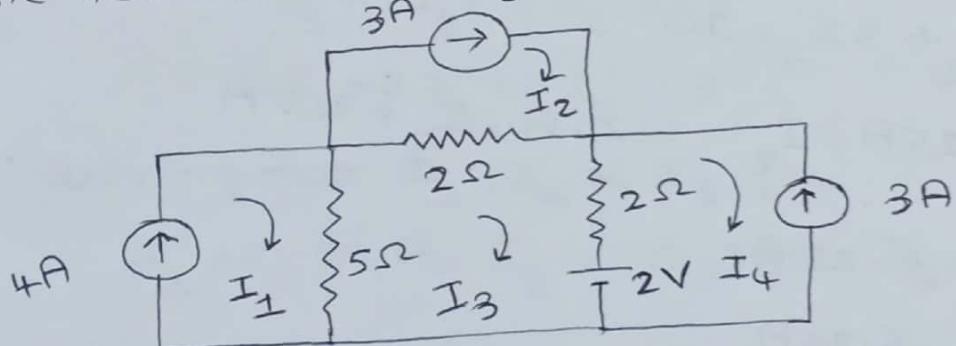Example 3 Determine the current through 5Ω resistor in the network shown?



Solution :- Mesh ① $I_1 = 4 \text{ A}$

Mesh ② $I_2 = 3 \text{ A}$

Mesh ④ $I_4 = -3 \text{ A}$

$$\text{Mesh ③ } 9I_3 - 5I_1 - 2I_2 - 2I_4 = -2$$

$$9I_3 - 5(4) - 2(3) - 2(-3) = -2$$

$$9I_3 - 20 - 6 + 6 = -2$$


$$9I_3 = 18$$

$$\boxed{I_3 = 2 \text{ A}}$$

current through 5Ω
 $= I_1 - I_3$
 $= 2 \text{ A}$

(15)

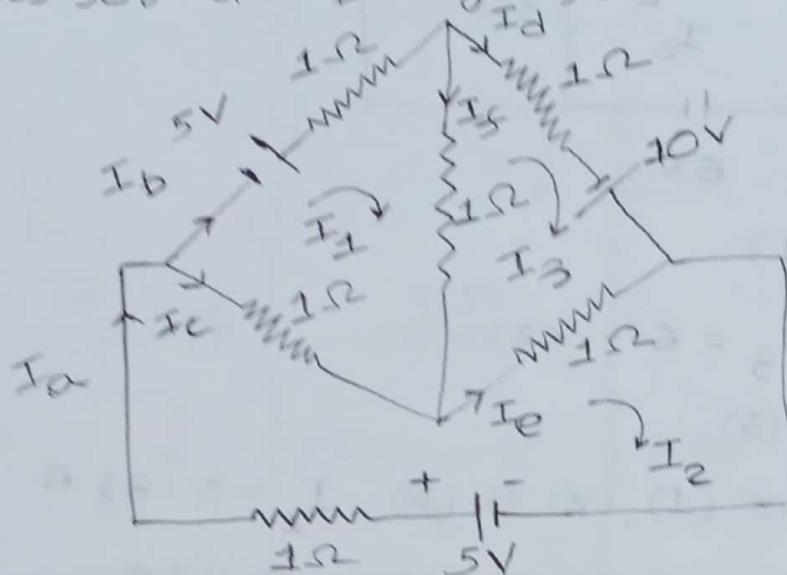Example 4 Determine the currents through various branches for the bridge circuit shown using mesh analysis?



$$3I_1 - I_2 - I_3 = 5$$

$$-I_1 + 3I_2 - I_3 = 5$$

$$-I_1 - I_2 + 3I_3 = 10$$

$$I_1 = 6.25 \text{ A}; I_2 = 6.25 \text{ A}; I_3 = 7.5 \text{ A}$$

$$I_a = I_2 = 6.25 \text{ A}$$

$$I_b = I_1 = 6.25 \text{ A}$$


$$I_c = I_2 - I_1 = 0 \text{ A}$$

$$I_d = I_3 = 7.5 \text{ A}$$

$$I_e = I_2 - I_3 = -1.25 \text{ A}$$

$$I_f = I_1 - I_3 = -1.25 \text{ A}$$

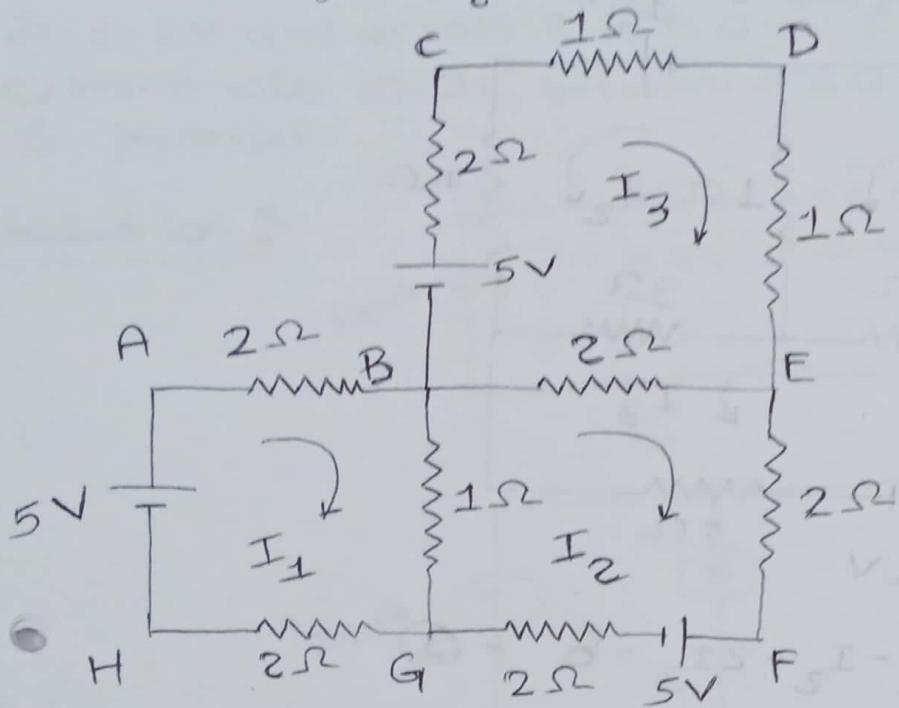5) Find the current through branch BC using mesh analysis ?



$$\text{solution :- } 5I_1 - I_2 - 0 \cdot I_3 = 5$$

$$-I_1 + 7I_2 - 2I_3 = -5$$


$$0 \cdot I_1 - 2I_2 + 6I_3 = 5$$

Solving for I_1 , I_2 & I_3 :-

$$I_1 = 0.92 \text{ A}; I_2 = -0.38 \text{ A}; I_3 = 0.70 \text{ A}$$

(17)

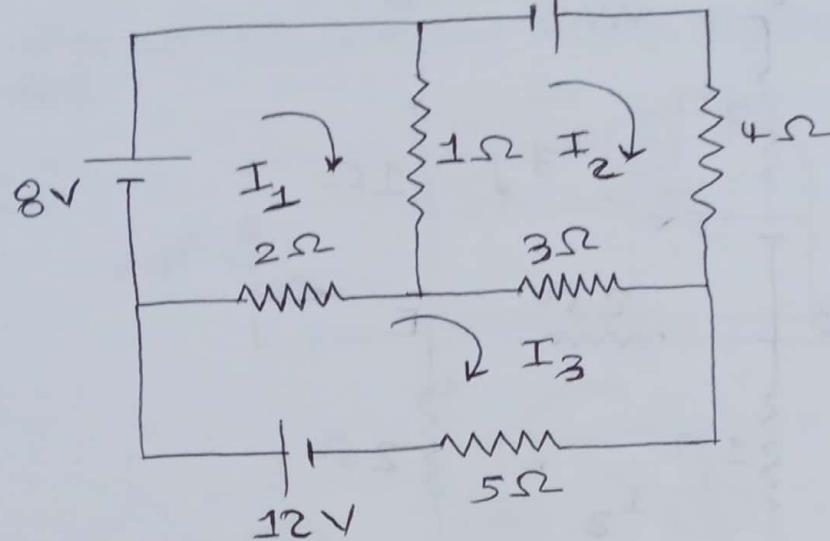6) Determine the current through 5Ω resistor using Mesh analysis :-



Solution :-

$$3I_1 - I_2 - 2I_3 = 8 \quad \text{--- (1)}$$

$$-I_1 + 8I_2 - 3I_3 = 10 \quad \text{--- (2)}$$

$$-2I_1 - 3I_2 + 10I_3 = 12 \quad \text{--- (3)}$$

$$\begin{array}{r} 12+2/3 \\ \hline 36+16 \\ \hline 3 \end{array}$$

Solve for equations (1) (2) & (3)

$$\left[\begin{array}{cccc} 3 & -1 & -2 & 8 \\ -1 & 8 & -3 & 10 \\ -2 & -3 & 10 & 12 \end{array} \right] \xrightarrow{\quad} \left[\begin{array}{cccc} 3 & -1 & -2 & 8 \\ 0 & 23 & -8 & 38 \\ 0 & -\frac{11}{3} & \frac{26}{3} & \frac{52}{3} \end{array} \right] \quad \begin{array}{l} -3 + \frac{2}{3}(-1) \\ \hline \end{array}$$

$$-\frac{3}{1} - \frac{2}{3}$$

$$\left[\begin{array}{cccc} 3 & -1 & -2 & 8 \\ 0 & 23 & -8 & 38 \\ 0 & -\frac{11}{3} & \frac{26}{3} & \frac{52}{3} \end{array} \right] \xrightarrow{R_3 + \frac{11}{69}R_2} \left[\begin{array}{cccc} 3 & -1 & -2 & 8 \\ 0 & 23 & -8 & 38 \\ 0 & 0 & 0 & 0 \end{array} \right] \quad \begin{array}{l} -\frac{9-2}{3} \\ \hline 10 + \frac{2}{3}(-2) \\ \hline \end{array}$$

$$\begin{array}{r} 10 - \frac{4}{3} \\ \hline 30 - 4 \\ \hline 3 \end{array}$$

$$\frac{26}{3} - \frac{88}{69}$$



$$\frac{-11}{3} + 23x = 0$$

$$\frac{-11}{3} = -23x$$

$$x = \frac{11}{69}$$


A current of 20A flows through two Ammeters A & B joined in series. Across A, the potential difference is 0.2V and across B it is 0.3V. Find how the same current will divide between A and B when they are joined in parallel.

Solution :-

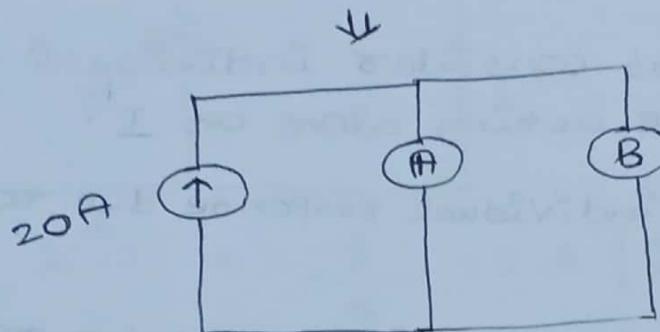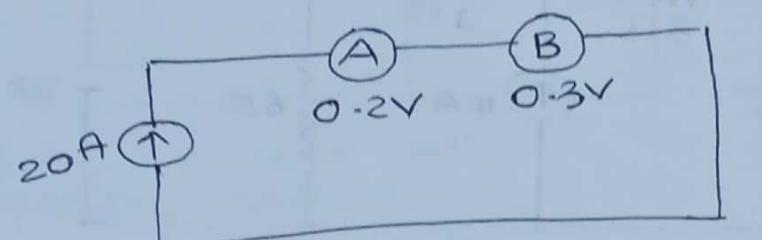

Internal resistances of Ammeter A & B are $\frac{0.2}{20}$ & $\frac{0.3}{20}$ respectively i.e 0.01Ω & 0.015Ω

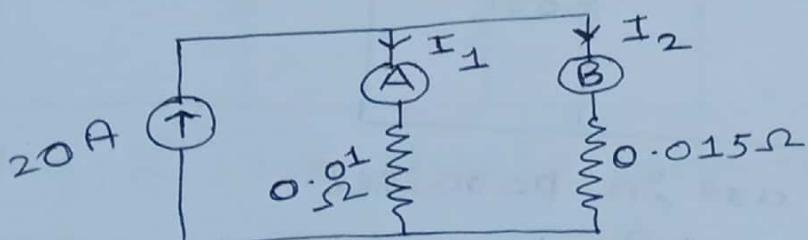20A current will get divided according to resistance in the paths.




$$I_1 = \frac{20 \times 0.015}{0.01 + 0.015} = 12A$$

$$I_2 = I - I_1 = 8A$$

(19)

Problems on Superposition Theorem :-

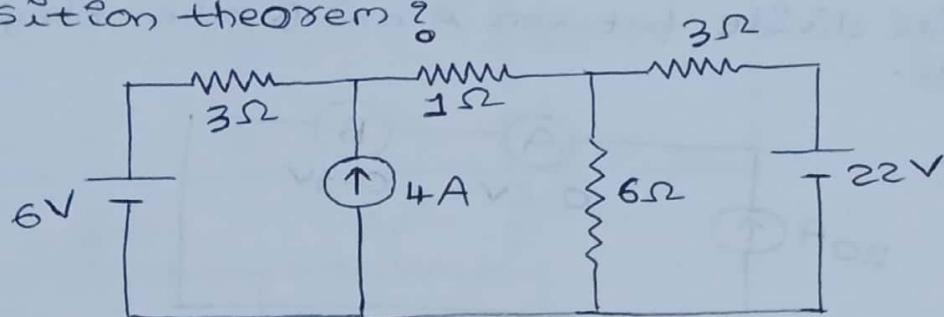- 1) Obtain current through 1Ω resistor using superposition theorem ?




Solution :- Let us consider individual response due to 6V source acting alone as I' .


Let us consider individual response due to 4A source acting alone as I'' .

Let us consider individual response due to 22V source acting alone as I''' .

Considering 6V source alone


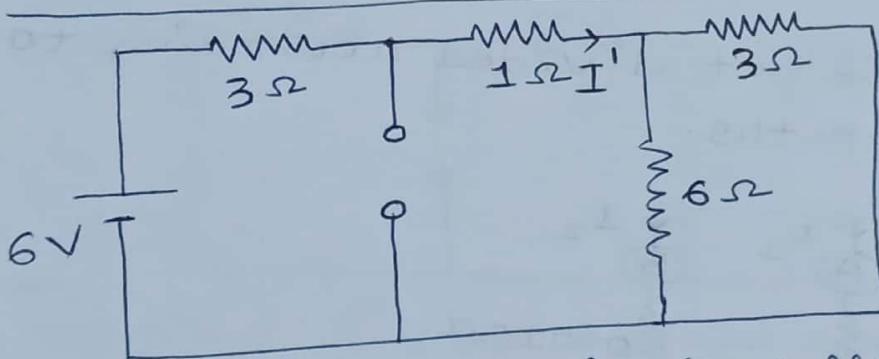


6Ω & 3Ω are in parallel

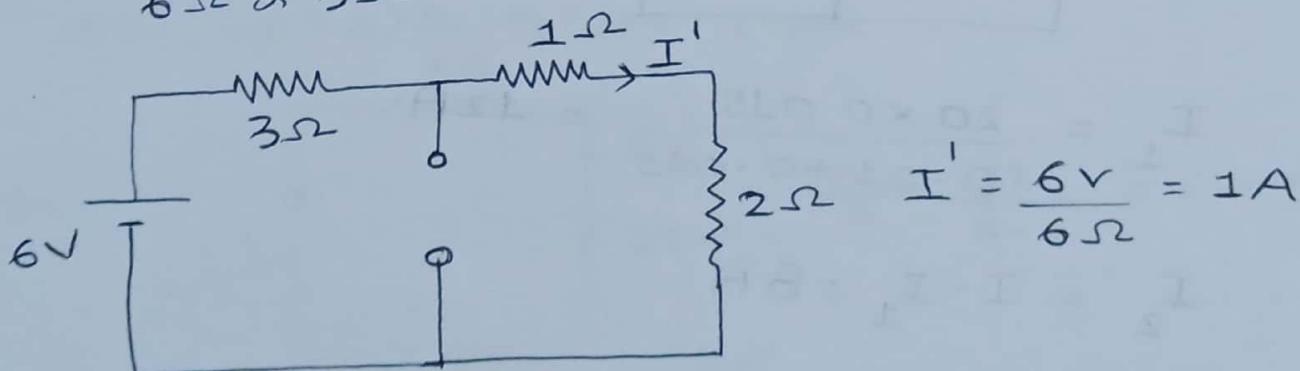

$$I' = \frac{6V}{6\Omega} = 1A$$


Considering 4V source alone :-

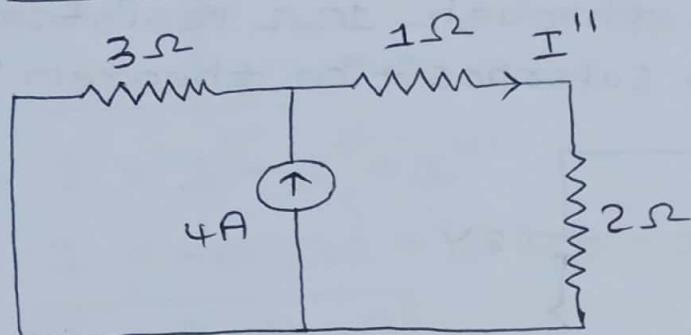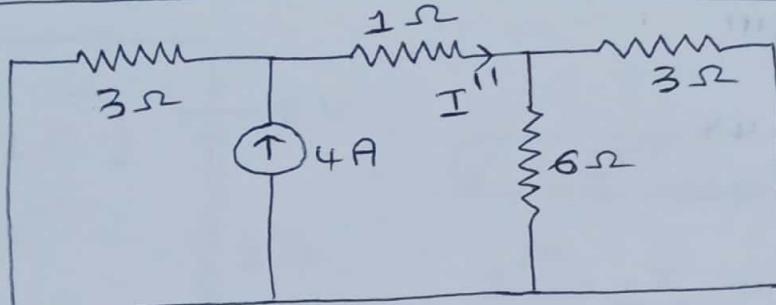

$$I'' = 4 \times \frac{3}{6} = 2 \text{ A} \quad [\text{By current division rule}]$$


$$I'' = 2 \text{ A}$$

Considering 22V source alone :-

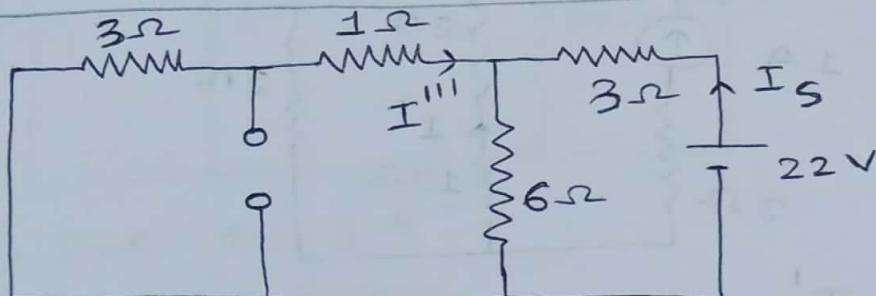


To find I''' , we should compute I_S

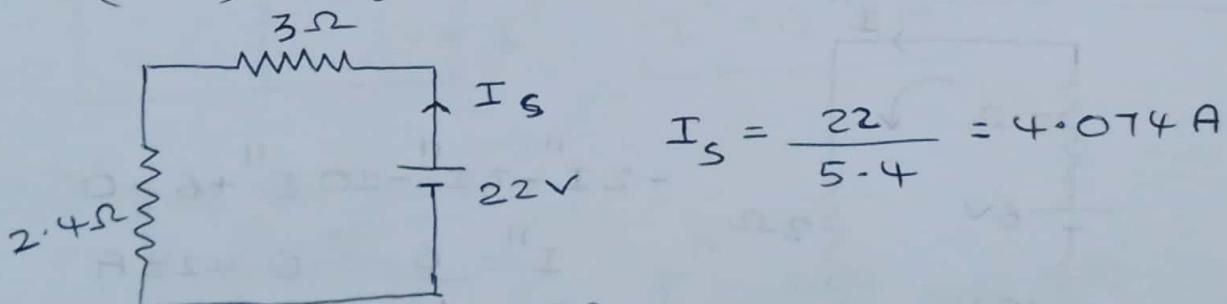$6\Omega \parallel (3+1)\Omega$ gives 2.4Ω


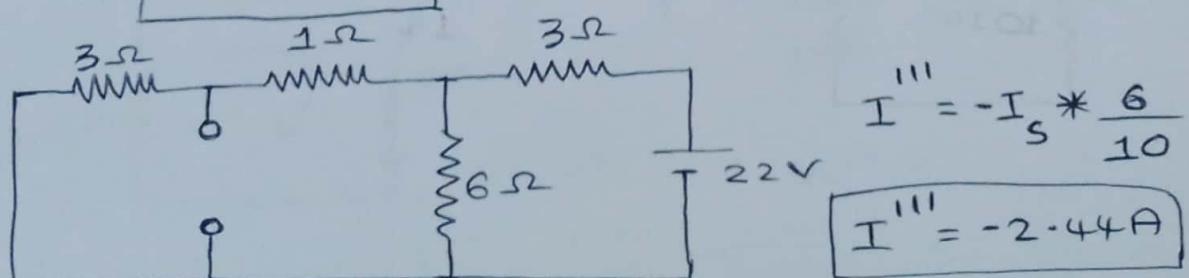
$$I_S = \frac{22}{5.4} = 4.074 \text{ A}$$



$$I''' = -I_S \times \frac{6}{10}$$

$$I''' = -2.44 \text{ A}$$

(21)



By superposition theorem :-

$$I = I' + I'' + I'''$$


$$I = 1 + 2 - 2 \cdot 44$$

$$\boxed{I = 0.56 \text{ A}}$$

2) Find the current through 10Ω resistor in the network shown using superposition theorem :-

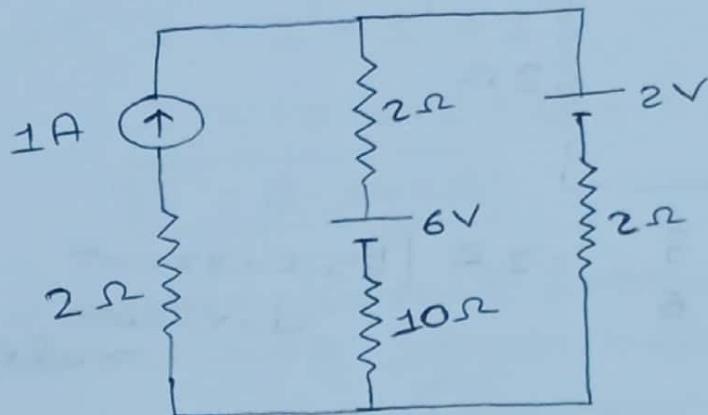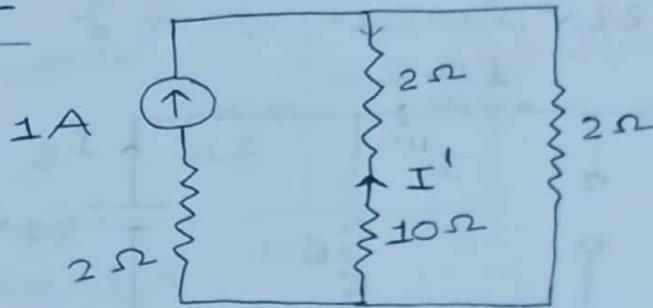Due to 1A :-


$$I' = \frac{-1(2)}{14} = -0.142 \text{ A}$$

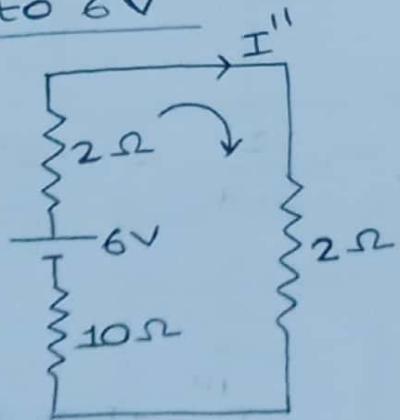Due to 6V

$$-2I'' - 2I'' - 10I'' + 6 = 0$$

$$I'' = \frac{6}{14} = 0.428 \text{ A}$$

Due to 2V

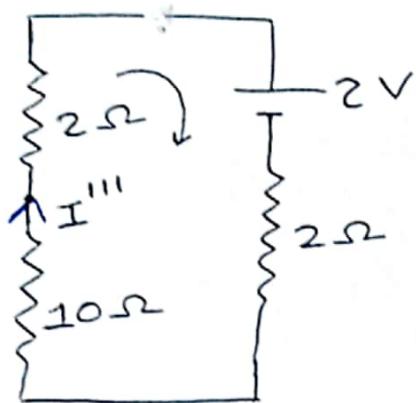

$$2 + 2I''' - 10I''' + 2I''' = 0$$


$$I''' = \frac{-2}{14} = -0.142 \text{ A}$$

$$\textcircled{a} \quad I = I' + I'' + I'''$$


$$I = -0.142 + 0.428 - 0.142$$

$$\boxed{I = 0.144 \text{ A}}$$

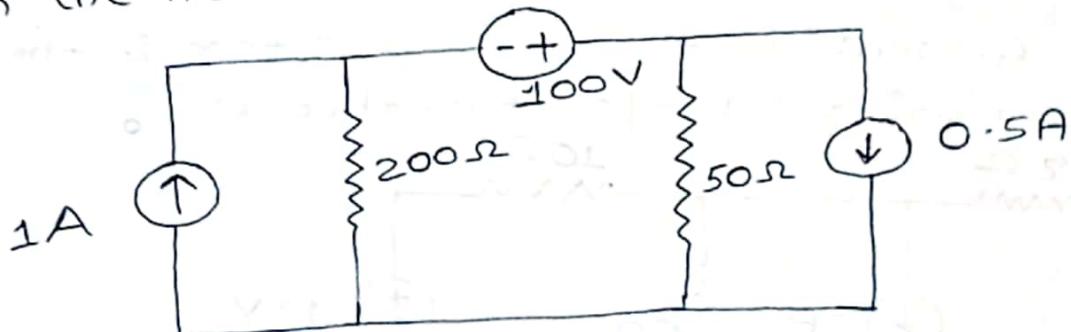- 3) Find the current through 50Ω resistor in the network shown below?




case i) Due to 1A

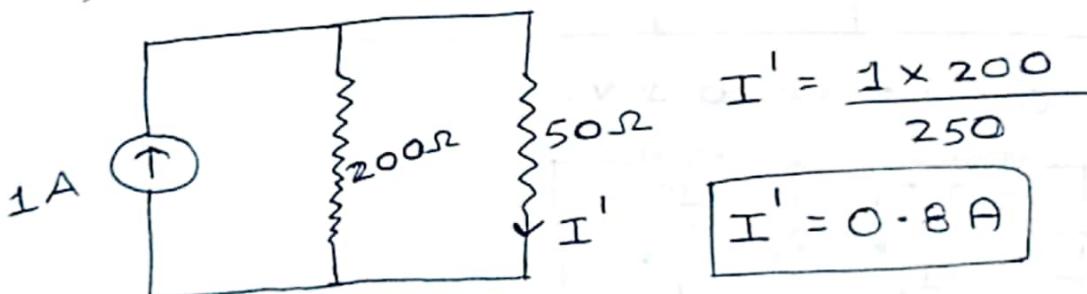

$$I' = \frac{1 \times 200}{250}$$


$$\boxed{I' = 0.8 \text{ A}}$$

case ii) Due to 100V

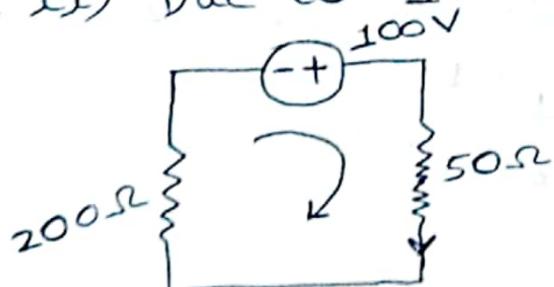

$$I'' = \frac{100}{250} = 0.4 \text{ A}$$

(23) case (ii) due to 0.5 A

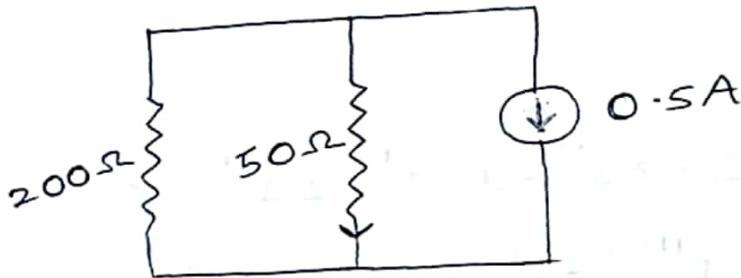

$$I''' = \frac{-0.5 \times 200}{250}$$


$$I''' = -0.4 \text{ A}$$

$$I = I' + I'' + I'''$$

$$I = 0.8 + 0.4 - 0.4$$

$$I = 0.8 \text{ A}$$

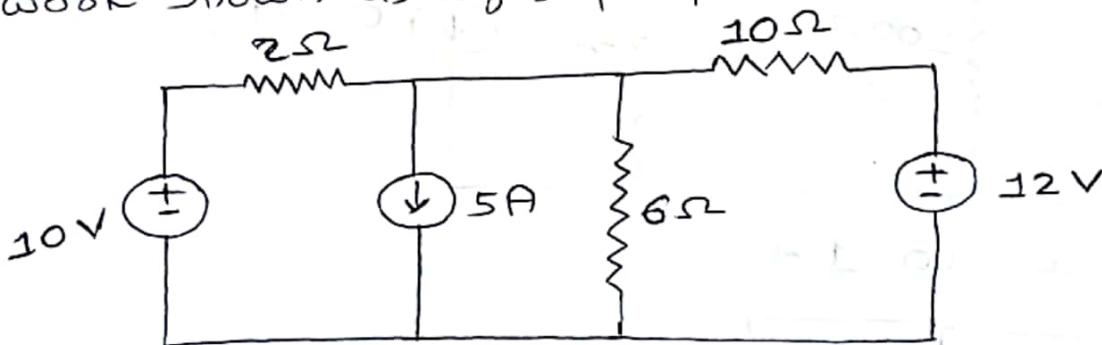4) Find the current in the 6 Ω resistor in the network shown using superposition theorem?



Solution :- current due to 10V




$$\begin{cases} 8I_1 - 6I_2 = 10 \\ -6I_1 + 16I_2 = 0 \end{cases} \quad \text{Solving for } I_1 \text{ & } I_2$$


$$\begin{aligned} I_1 &= 1.74 \text{ A} \\ I_2 &= 0.65 \text{ A} \end{aligned}$$

$$I' = I_1 - I_2 = 1.09 \text{ A}$$

Current due to 5A

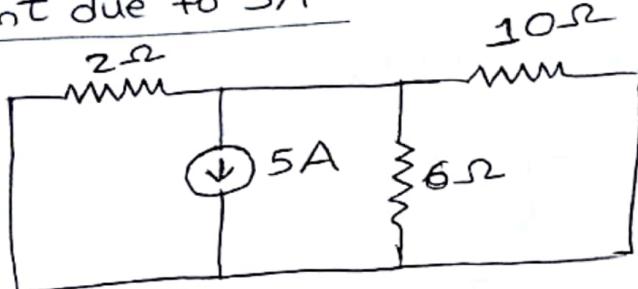


$6\Omega \parallel 10\Omega$

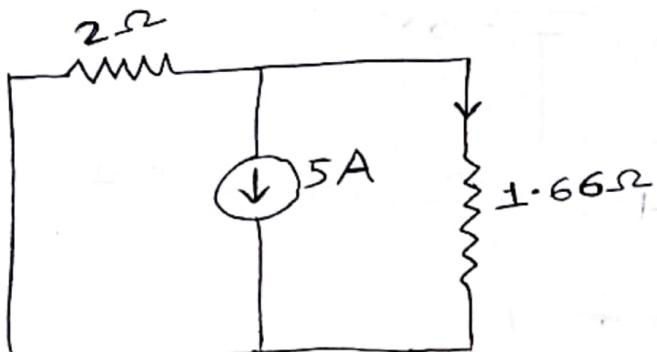

$$I' = \frac{-5 \times 1.66}{6 + 1.66} = -1.08 \text{ A}$$

Current ~~EXPOSED~~ due to 12V

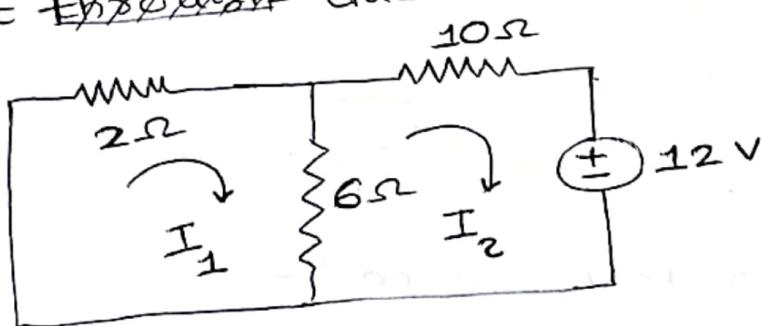

$$8I_1 - 6I_2 = 0$$

$$-6I_1 + 16I_2 = -12$$


$$I_1 = -0.78 \text{ A}; I_2 = -1.04 \text{ A}$$

$$I''' = I_1 - I_2 = 0.26 \text{ A}$$


$$\therefore I = 1.09 - 1.08 + 0.26$$

$$\boxed{I = 0.27 \text{ A}}$$

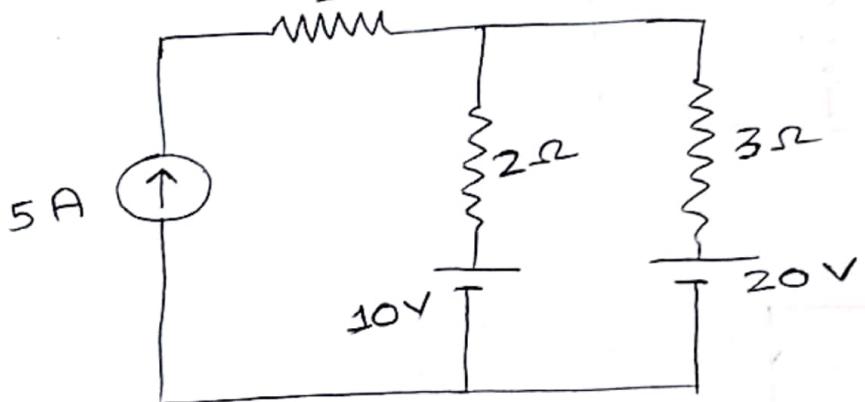(25) 5) Find the current through 2Ω resistor given using superposition theorem?




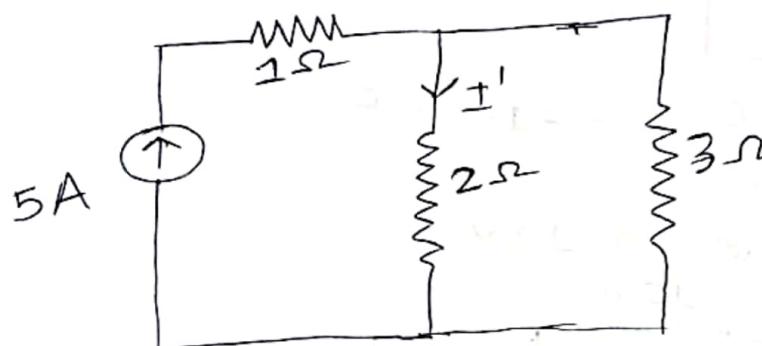Solution :- current ~~through~~ due to $5A$



$$I' = \frac{5 \times 3}{5} \Rightarrow I' = 3A$$


current due to $10V$ source :-

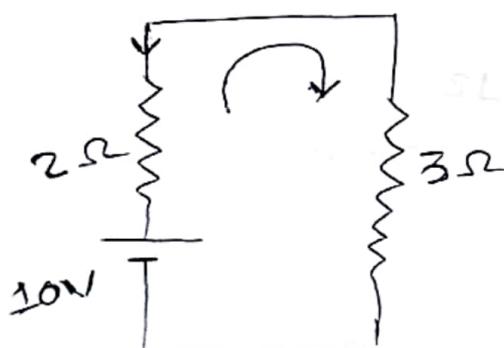

$$I'' = -\frac{10}{5} = -2A$$

current due to 12 V o-

(26)

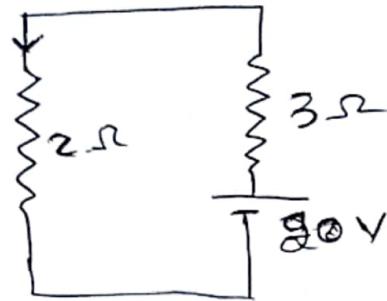


$$I''' = \frac{20}{5} = 4 \text{ A}$$


o° Total current = $I' + I'' + I'''$

$$\begin{aligned} &= 3 - 2 + 4 \\ &= 5 \text{ A} \end{aligned}$$

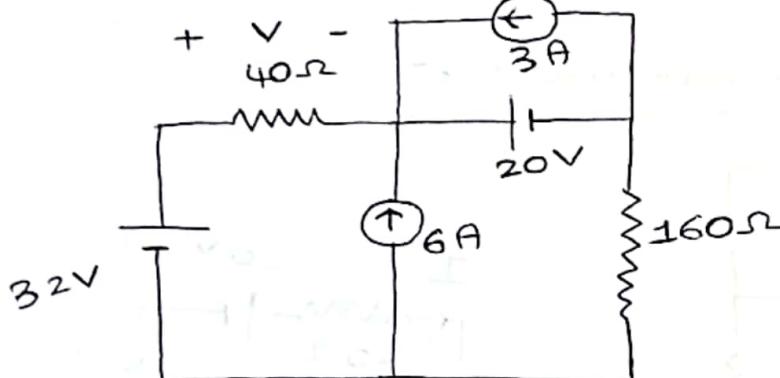6) Obtain voltage 'V' using superposition theorem?





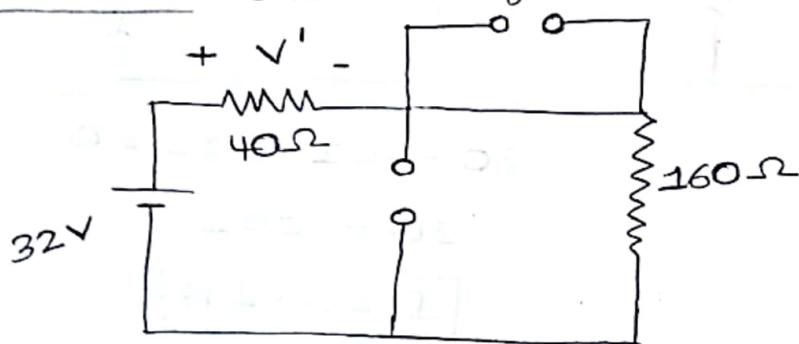Solution o- considering 32V source alone,





$$V' = 32 \times \frac{40}{200} = 6.4 \text{ V} \quad [\text{Voltage division rule}]$$

(27)

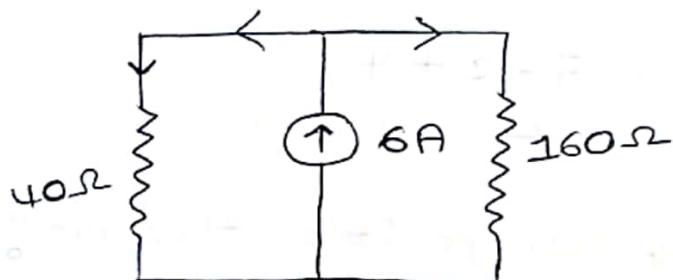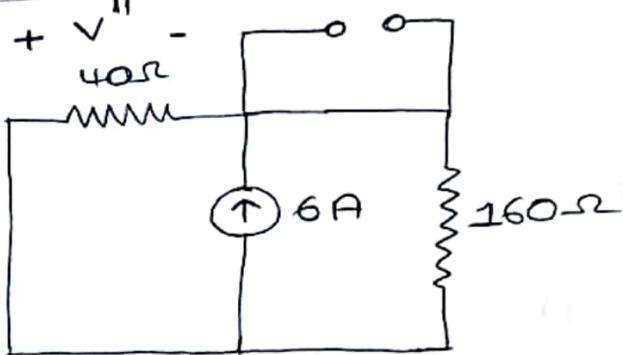considering 6 A source alone \therefore 

$$I = \frac{6 \times 160}{200} = 4.8 \text{ A}$$

$$V''' = -4.8 \times 40 = -192 \text{ V}$$

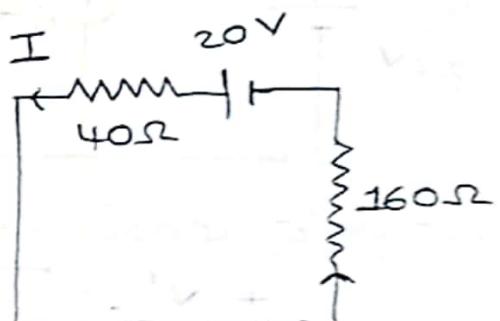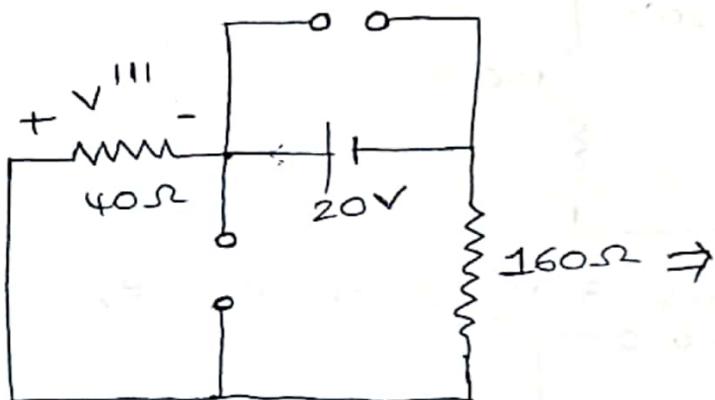
considering 20V source alone \therefore 

$$20 - 40I - 160I = 0$$

$$20 = 200I$$

$$\boxed{I = 0.1 \text{ A}}$$

$$V''' = -0.1 \times 40 = -4 \text{ V}$$

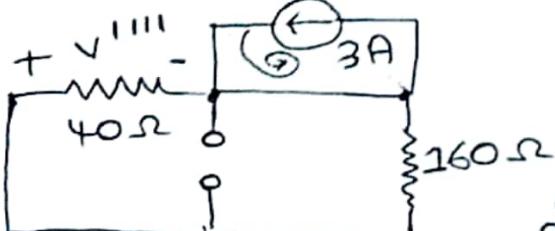
considering 3 A source alone \therefore 

current flows through least resistance path
Open circuit \therefore

$$V'''' = 0$$

$$\begin{aligned} V &= V' + V'' + V''' + V'''' \\ &= 6.4 - 192 - 4 = -189.6 \text{ V} \end{aligned}$$

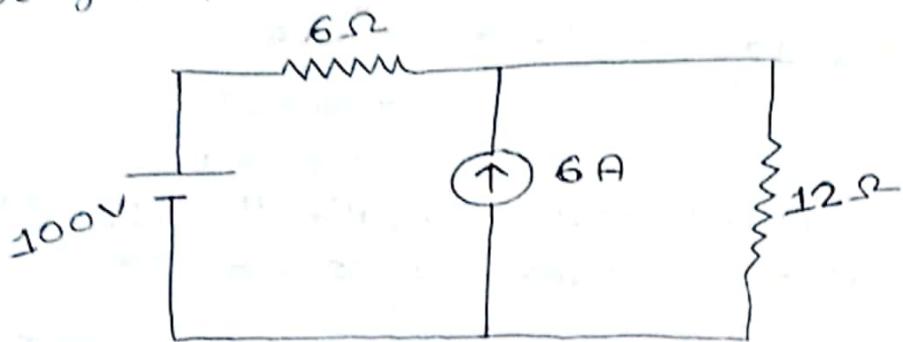
7) Find the power absorbed by 12Ω resistor using superposition theorem?



Solution :- Let us consider individual current & power responses due to $100V$ source acting alone as I' & P' .


Let us consider individual current & power responses due to $6A$ source acting alone as I'' & P'' .

Considering $100V$ source alone :-

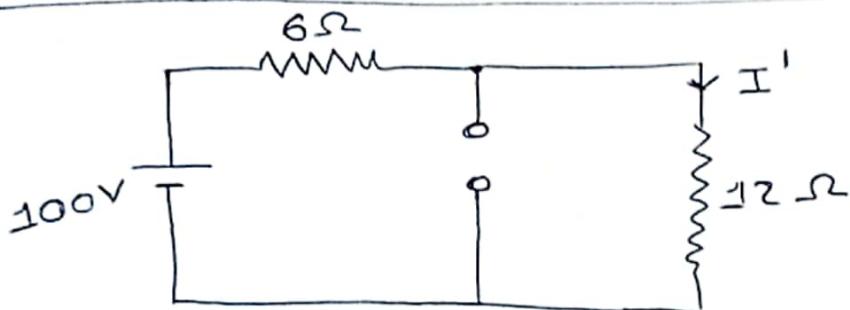

$$I' = \frac{100}{18} = 5.56 \text{ A}; P' = (I')^2 \times 12 \\ P' = 370.96 \text{ W}$$

Considering $6A$ source alone :-

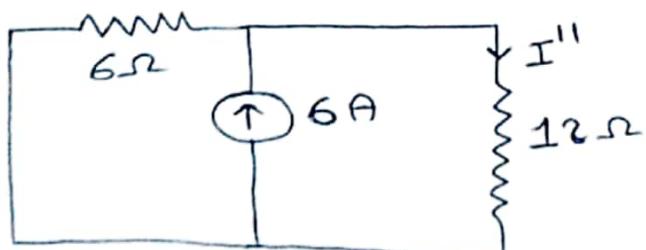

$$I'' = \frac{6 \times 6\Omega}{6 + 12}$$

$$\boxed{I'' = 2 \text{ A}}$$

$$P'' = (I'')^2 \times 12 = 48 \text{ W}$$

(29)

By superposition, current in 12Ω resistor = $I = I' + I'' = 7.56 \text{ A}$

$$\begin{aligned}\text{Power absorbed by } 12\Omega \text{ resistor} &= I^2 \times 12 \\ &= 7.56^2 \times 12 \\ &= 685.84 \text{ W}\end{aligned}$$


Adding the individual power responses, $P' + P'' = 418.96 \text{ W}$
which is not equal to the actual power absorbed.

→ Here, individual power responses cannot be superimposed to get total power because power is a quadratic term.


→ Thus, to get total power response, apply superposition principle to get total current or total voltage & using that find the power.

Problems on Thevenin's Theorem :-

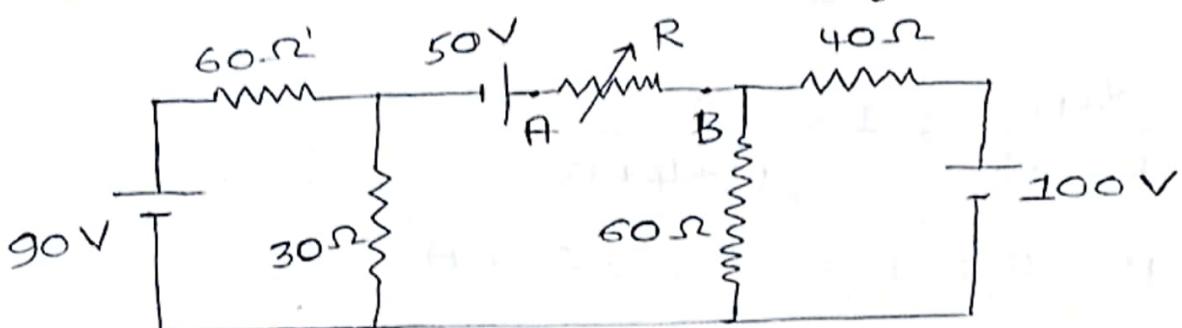1) Using Thevenin's theorem, calculate the range of current flowing through the resistance R , as it varies from 6Ω ~~and~~ 36Ω ?



Solution :- Finding V_{th}

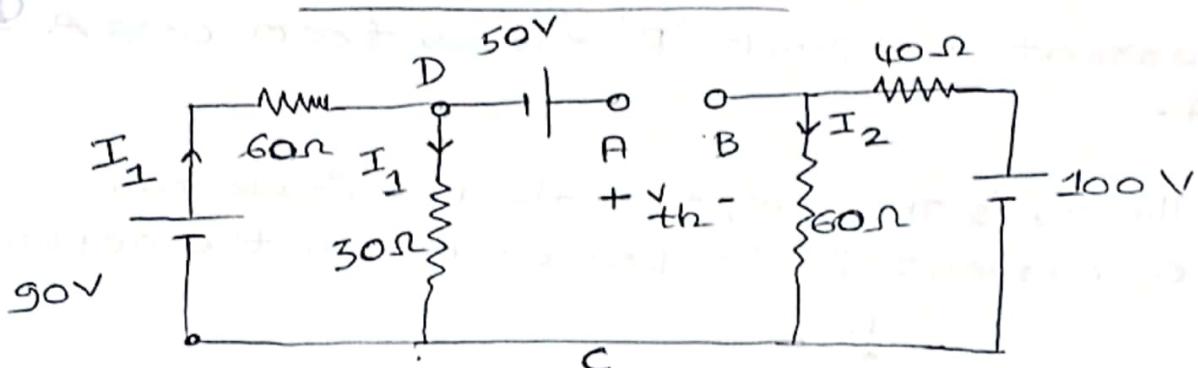


$$I_1 = \frac{90}{30} = 1 \text{ A} \quad I_2 = \frac{100}{100} = 1 \text{ A}$$

$$\text{By KVL } 50 - V_{th} - 60 I_2 + 30 I_1 = 0$$

$$50 - V_{th} - 60 + 30 = 0$$

$$V_{th} = 20 \text{ V}$$

Finding R_{th}

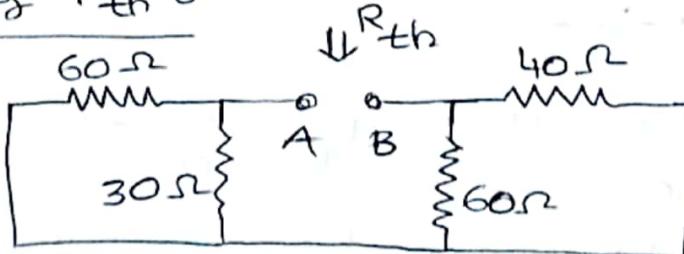


$$R_{th} = (60\Omega || 30\Omega) + (60\Omega || 40\Omega)$$

$$= 20\Omega + 24$$

$$R_{th} = 44\Omega$$

(31)

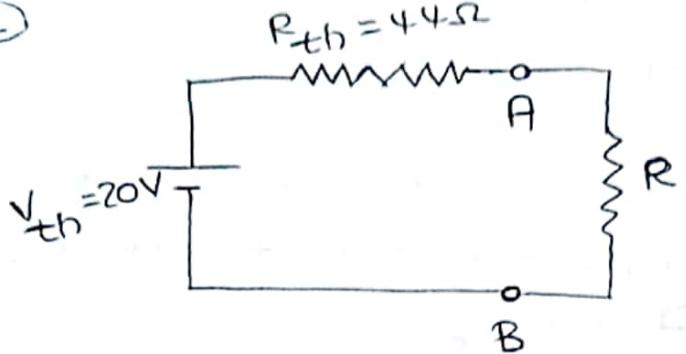


$$I_L = \frac{V_{th}}{R_{th} + R}; I = \frac{20}{R + 44\Omega}$$

when $R = 6\Omega$; $I = \frac{20}{30} = 0.4A$


when $R = 36\Omega$; $I = \frac{20}{80} = 0.25A$

Hence, current through 'R' ranges from 0.25A to 0.4A.

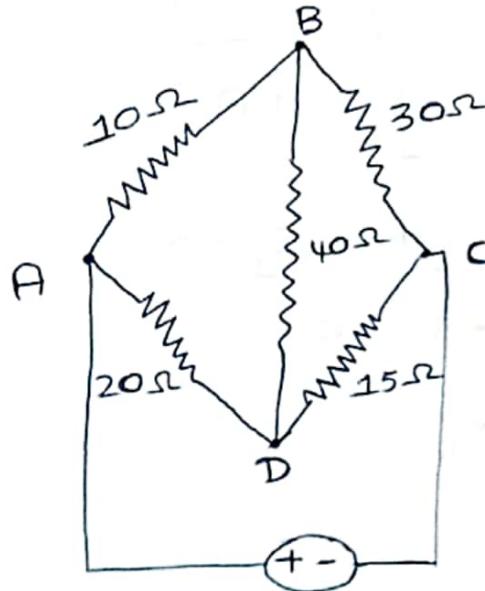2) Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown?



Solution :- Finding V_{th} :-

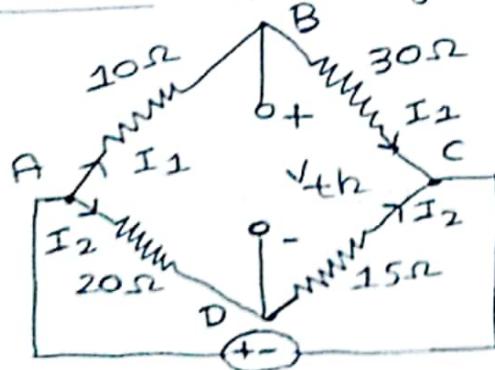

$$I_1 = \frac{2}{40} = 0.05A$$

$$I_2 = \frac{2}{35} = 0.057A$$

By KVL :- ABDA



$$-10I_1 - V_{th} + 20I_2 = 0$$

$$V_{th} = -10I_1 + 20I_2$$

$$V_{th} = -10(0.05) + 20(0.057)$$

$$V_{th} = 0.64 \text{ V}$$


Finding R_{th}

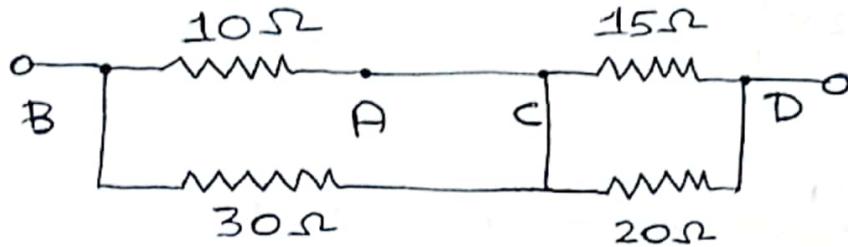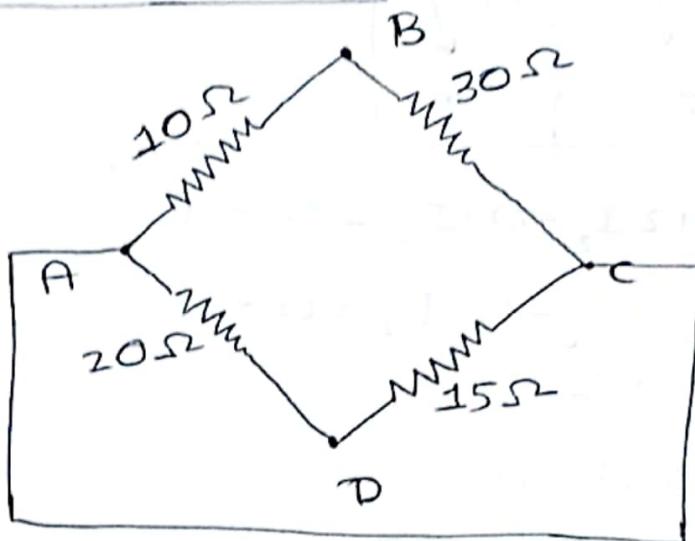

$$\frac{10 \times 30}{40}$$

$$\frac{15 \times 20}{35}$$

$$R_{th} = 16.07 \Omega$$

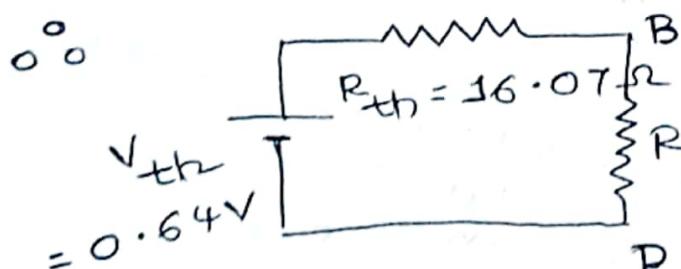


$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$= \frac{0.64}{16.07 + 40} = 11.41 \text{ mA}$$

Hence, current through the branch BD is 11.41 mA and flows from B to D.

33

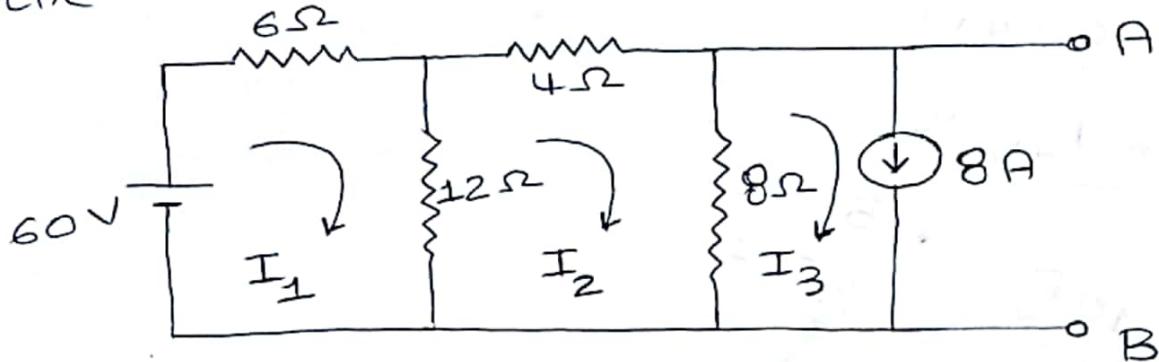3) Obtain the Thevenin's Equivalent across the terminals A & B for the network given



Solution :-

$$18I_1 - 12I_2 - 0 \cdot I_3 = 0 \quad \text{--- (1)}$$

$$-12I_1 + 24I_2 - 8 \cdot I_3 = 0 \quad \text{--- (2)}$$

$$I_3 = 8 \text{ A} \quad \text{--- (3)}$$


Solving for (1) (2) & (3)

$$I_1 = 7.66 \text{ A}; I_2 = 6.5 \text{ A}; I_3 = 8 \text{ A}$$

$$V_{th} = (I_2 - I_3)8$$

$$\boxed{V_{th} = -12 \text{ V}}$$

To find R_{th} :-

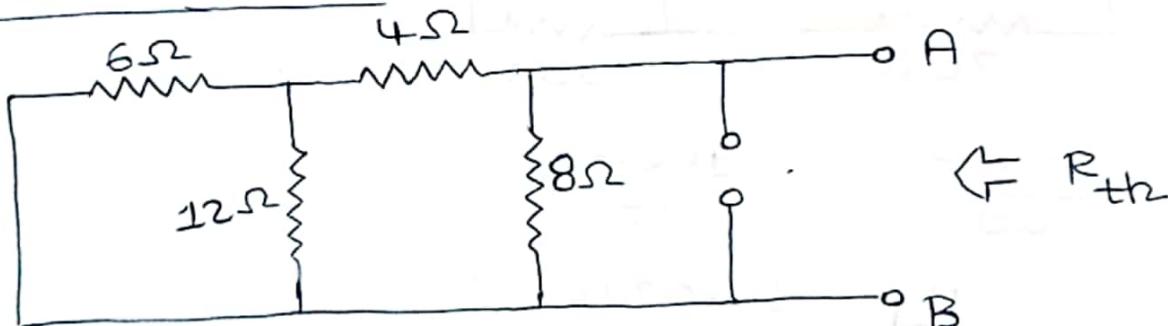

$$R_{th} = [(6\Omega || 12\Omega) + 4\Omega] || 8\Omega$$


$$R_{th} = [4\Omega + 4\Omega] || 8\Omega$$

Thevenin's Equivalent Circuit :-
 $R_{th} = 4\Omega$

$$\boxed{R_{th} = 4\Omega}$$



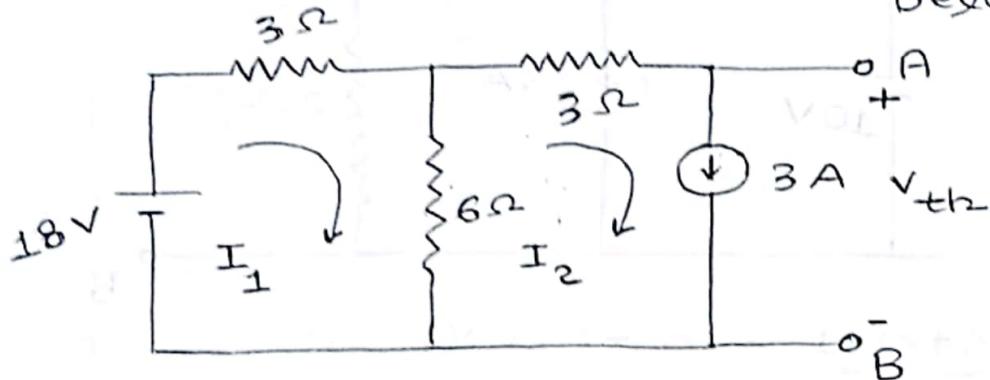④ Find Thevenin's equivalent voltage & Thevenin's equivalent resistance between the terminals A & B for the network shown below ?



Solution :-

$$I_2 = 3 \text{ A} \quad \text{--- (1)}$$

$$9I_1 - 6I_2 = -v_{th} \quad [\text{Mesh 2}]$$

$$v_{th} = 6I_1 - 9I_2$$

$$9I_1 - 6I_2 = 18 \quad [\text{Mesh 1}]$$

$$9I_1 - 18 = 18$$


$$I_1 = \frac{36}{9}$$

$$\boxed{I_1 = 4 \text{ A}}$$

$$v_{th} = 6(4) - 9(3)$$

$$\boxed{v_{th} = -3 \text{ V}}$$

To find R_{th} :-

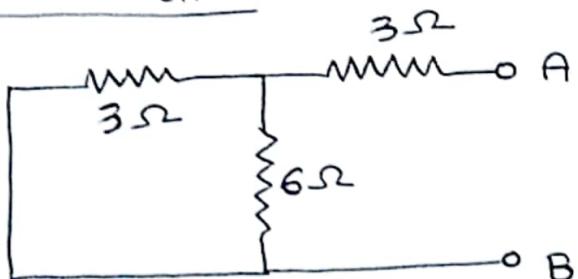


$$R_{th} = [3\Omega \parallel 6\Omega] + 3\Omega$$


$$= 2\Omega + 3\Omega$$

$$\boxed{R_{th} = 5\Omega}$$


Thevenin's Equivalent :-

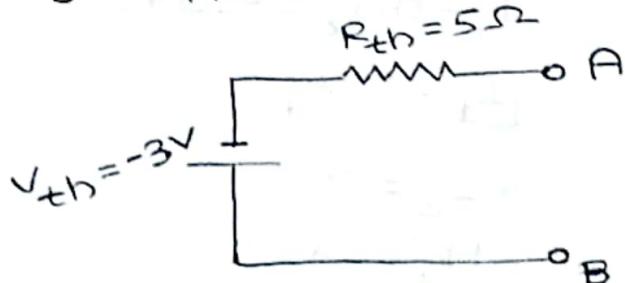

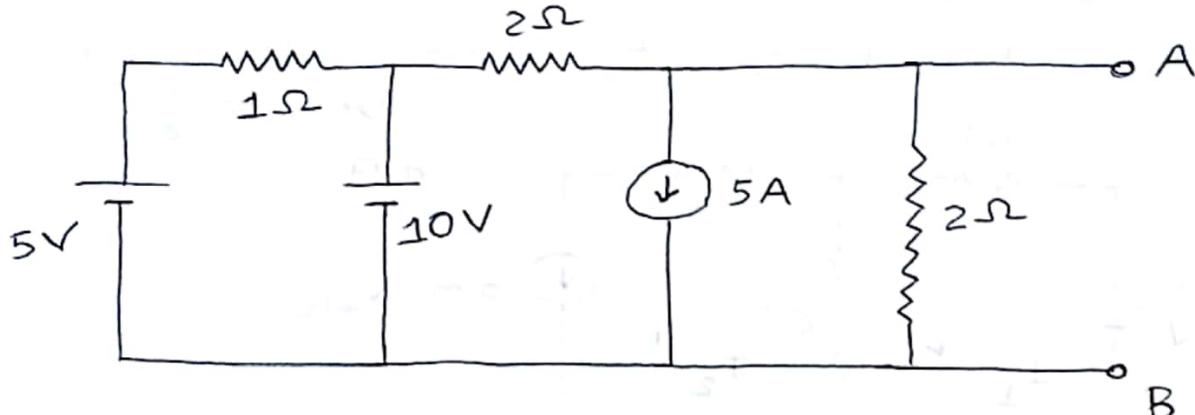
(35) 5) Obtain the Thevenin's Equivalent across the terminals A & B in the network shown below?



Solution :- Step 1 - To find V_{th} :-

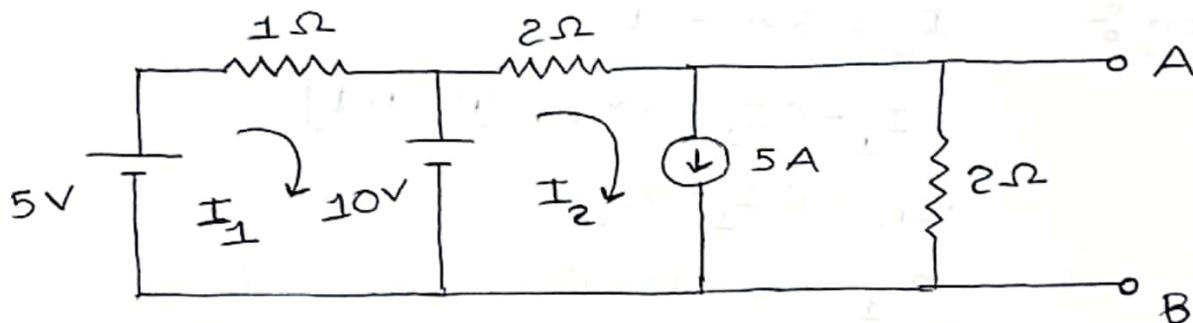

Applying Source transformation :-

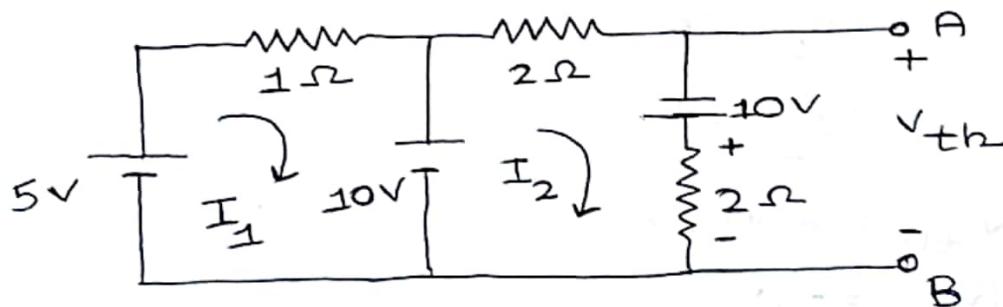

Applying KVL across V_{th} :-

$$2I_2 - 10 - V_{th} = 0$$

$$V_{th} = 2I_2 - 10$$

Mesh analysis :-

$$I_1 - 0 \cdot I_2 = -10 + 5$$

$$I_1 = -5 \text{ A}$$


$$4I_2 = 20$$

$$I_2 = 5 \text{ A}$$

$$0^\circ V_{th} = 2(5) - 10$$

$$V_{th} = 0 \text{ V}$$


Step 2 To find R_{th}

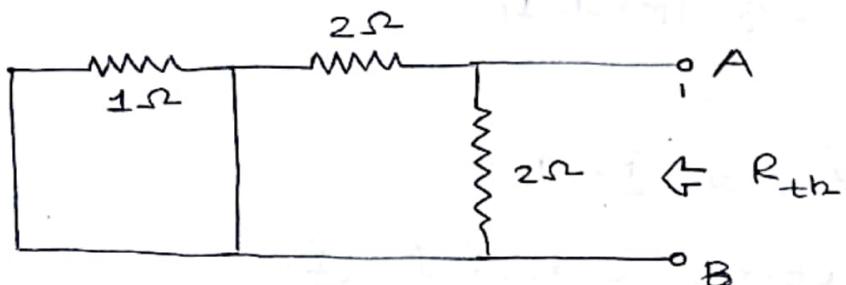


1 ohm resistance will go because of short circuit

$$R_{th} = 2\Omega \parallel 2\Omega = 1\Omega$$


Thevenin's Equivalent Circuit

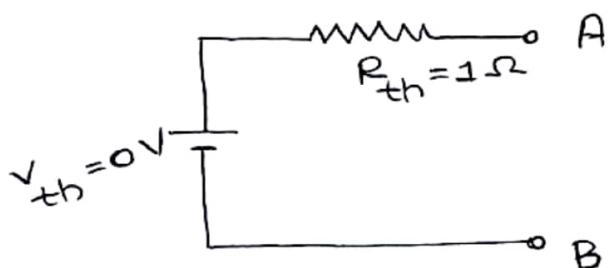

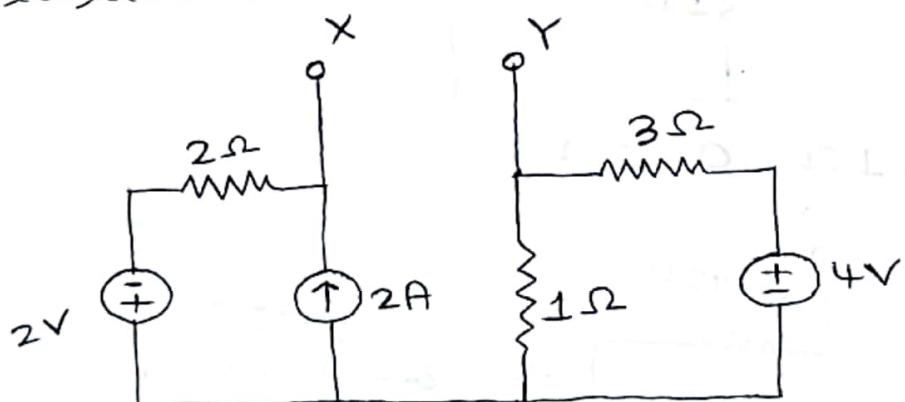Q) calculate the thevenin's equivalent in the circuit shown?



Solution

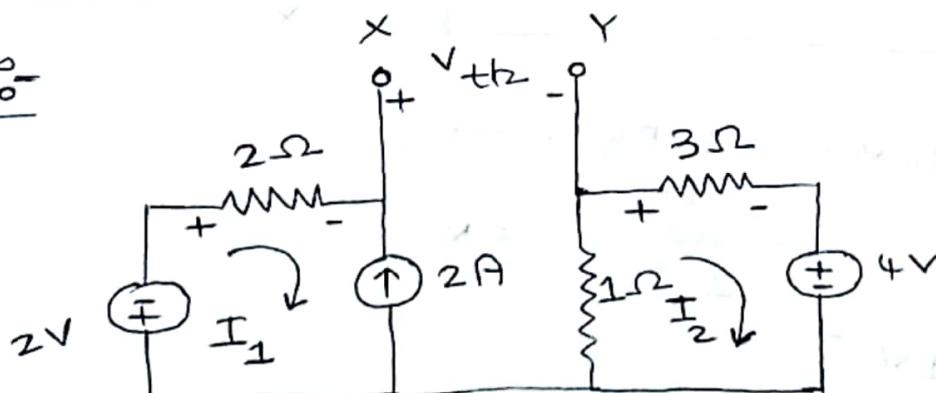

(37) TO find v_{th}

Applying KVL to the outer loop :-

$$-v_{th} - 3I_2 - 4 - 2 - 2I_1 = 0 \quad \text{--- (1)}$$

Mesh analysis :-

$$I_1 = -2A \quad \text{--- (2) [Mesh 1]}$$

$$4I_2 = -4$$

$$I_2 = -1A \quad \text{--- (3) [Mesh 2]}$$


so substituting (2) & (3) in (1)

$$v_{th} = -3(-1) - 4 - 2 - 2(-2)$$


$$v_{th} = 3 - 4 - 2 + 4$$

$$\boxed{v_{th} = 1V}$$


TO find R_{th}

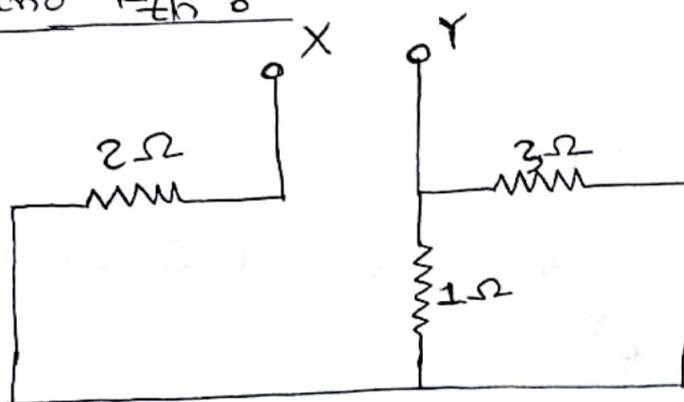

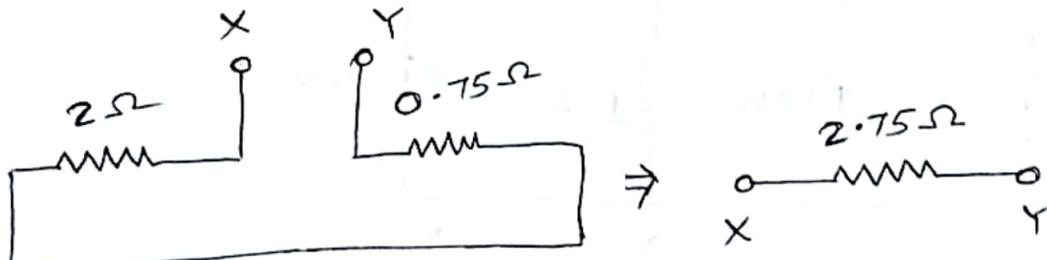
$$3\Omega \parallel 1\Omega = 0.75\Omega$$




so Thevenin's Equivalent :-

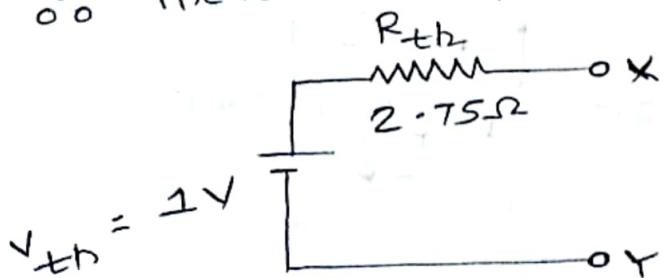

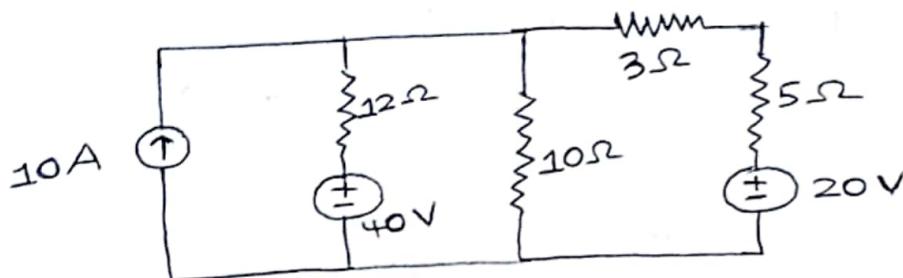Determine the current through 5Ω resistor in the given circuit using superposition theorem?



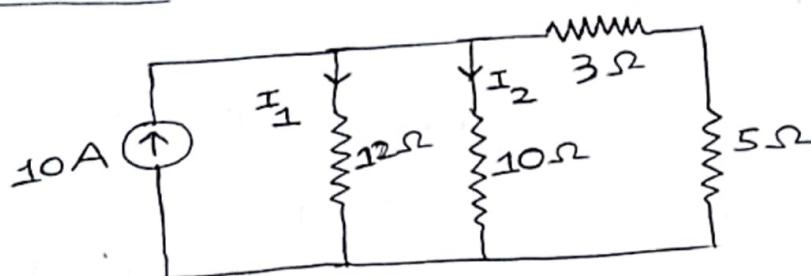Solution :- i) with only 10A source active




$$(3+5) \parallel 10 = \frac{8 \times 10}{18} = 4.44\Omega$$

$$I_2 = \frac{10 \times 12}{12 + 4.44} = 7.29 A$$

$$I_3 = \frac{7.29 \times 10}{10 + 8} = 4.05 A$$

$$\boxed{I_{5\Omega}^1 = 4.05 A \downarrow}$$

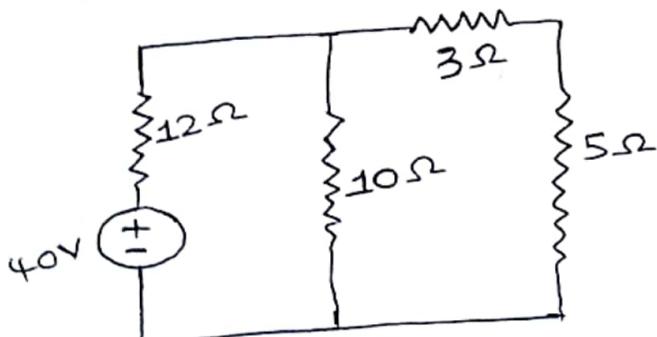
ii) using 40V as active source iii) using 20V source
as active



$$R_{\text{rear}} = 16.44\Omega$$

$$I = \frac{40}{16.44} = 2.43 A$$
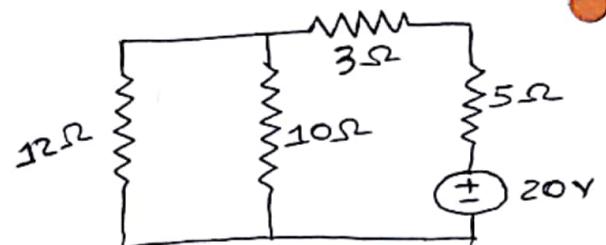
$$I_{5\Omega}^{II} = \frac{2.43 \times 10}{10 + 8} = 1.35 A \downarrow$$




$$R_{\text{rear}} = 13.45\Omega$$

$$I_{5\Omega}^{III} = \frac{20}{13.45} = 1.486 A \uparrow$$


$$I_{5\Omega} = 4.05 + 1.35 - 1.486$$

$$\boxed{I_{5\Omega} = 3.914 A \downarrow}$$

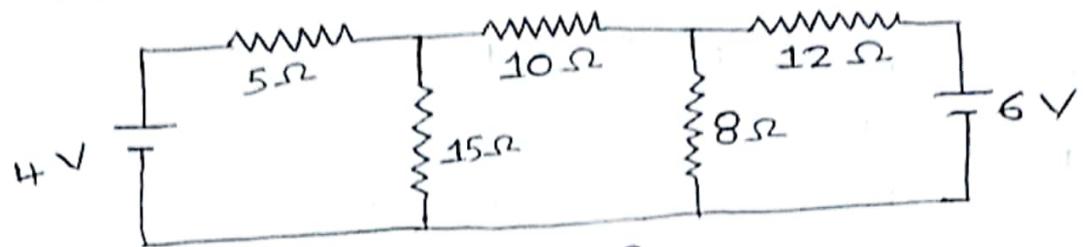39) Solve the circuit shown below for the current in $8\ \Omega$ resistor using Thevenin's theorem?



Solution :-

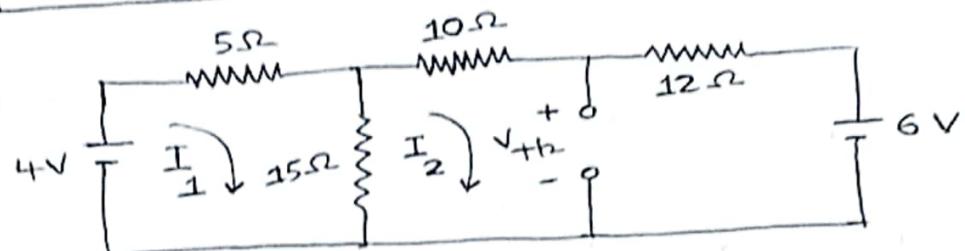

KVL for Mesh 1

$$4 - 5I_1 - 15(I_1 - I_2) = 0$$

$$4 - 5I_1 - 15I_1 + 15I_2 = 0$$

$$-20I_1 + 15I_2 = -4 \quad \text{--- (1)}$$

KVL for Mesh 2

$$-15(I_2 - I_1) - 22I_2 - 6 = 0$$

$$-15I_2 + 15I_1 - 22I_2 = 6$$

$$15I_1 - 37I_2 = 6 \quad \text{--- (2)}$$


Solving (1) & (2) $I_1 = 0.112\ A$; $I_2 = -0.1165\ A$

$$\sqrt{th} - 12I_2 - 6 = 0$$

$$\sqrt{th} - 12\{-0.1165\} - 6 = 0$$

$$\boxed{\sqrt{th} = 4.602\ V}$$

To find R_{th} :-

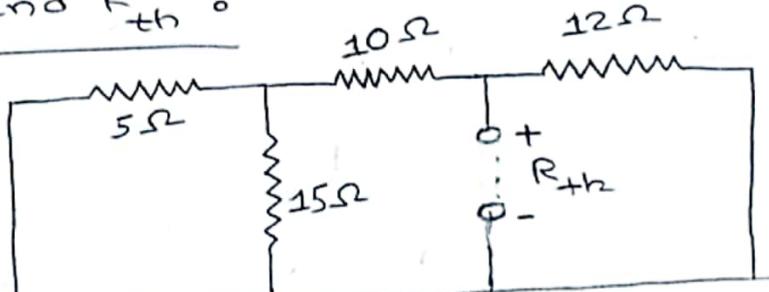


$$R_{th} = [5 || 15 + 10] || 12$$

$$\boxed{R_{th} = 6.407\ \Omega}$$

Thevenin's Equivalent :-


$$R_{th} = 6.407\ \Omega$$

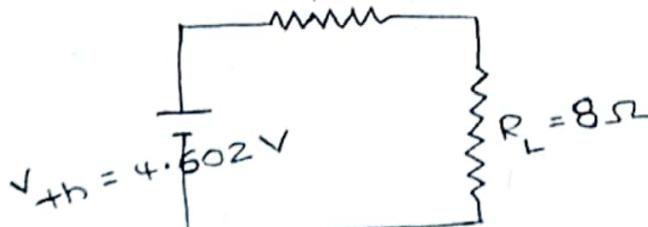


$$I_{8\Omega} = \frac{4.602}{6.407 + 8}$$

$$\boxed{I_{8\Omega} = 0.32\ A}$$

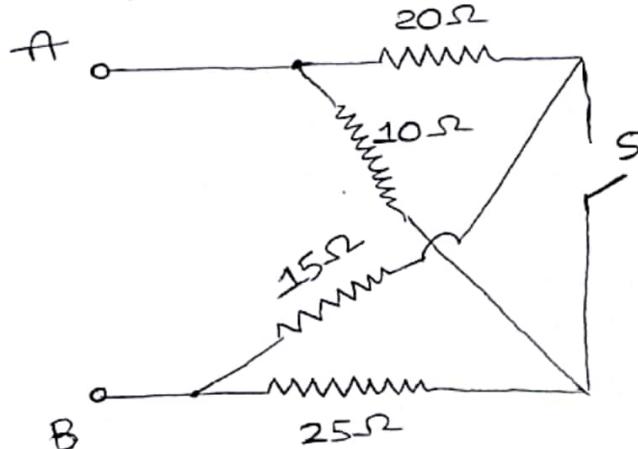Find V_{AB} , if current through 15Ω resistor is $3A$
when switch is i) closed ii) open



solution :- i) when switch is closed :-

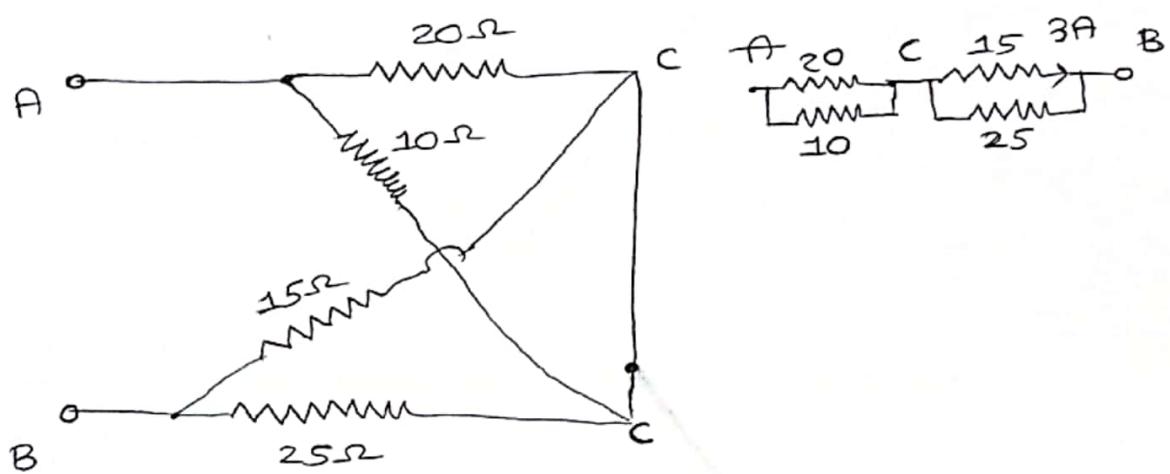



$$V_{CB} = 45V; \text{ current through } 25\Omega = \frac{45}{25} = 1.8A$$

∴ Total current entering node C is $3 + 1.8 = 4.8A$.

$$\text{If } 20||10 \Rightarrow R_{AC} = 6.66\Omega; \text{ so } V_{AC} = \frac{\text{Total current}}{\text{current}} \times R_{AC}$$

$$\Rightarrow V_{AC} = 31.968V; V_{CB} = 45V; \boxed{V_{AB} = 76.968V}$$

ii) when the switch is open :-

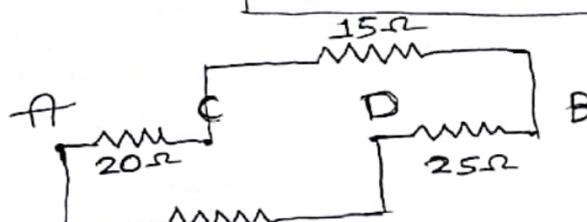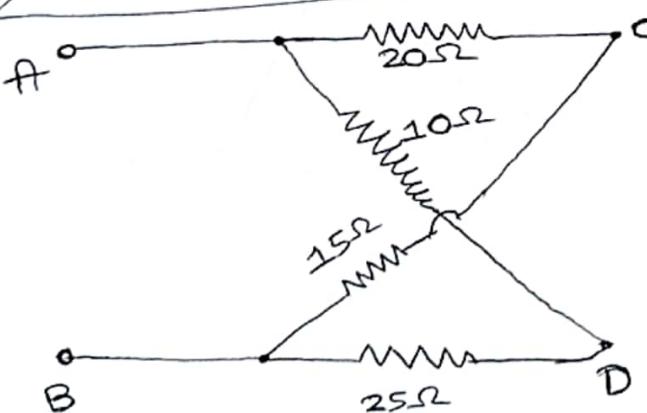

Total resistance across AB = 35Ω

Total current through $15\Omega = 3A$

$$\text{so } V_{AB} = 35 \times 3 = 105V$$