



# ELEMENTS OF ELECTRICAL ENGINEERING

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

---

## Numerical Examples on Thevenin's Theorem

**Vadhiraj K P P**


Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

## Numerical Example 1
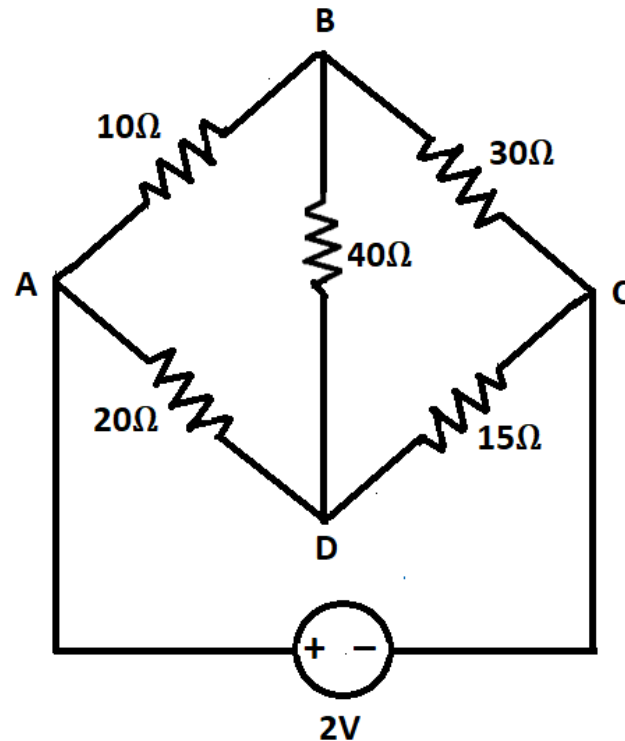
### Question:


Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.



## Numerical Example 1

**Solution :**

Finding  $V_{TH}$  :

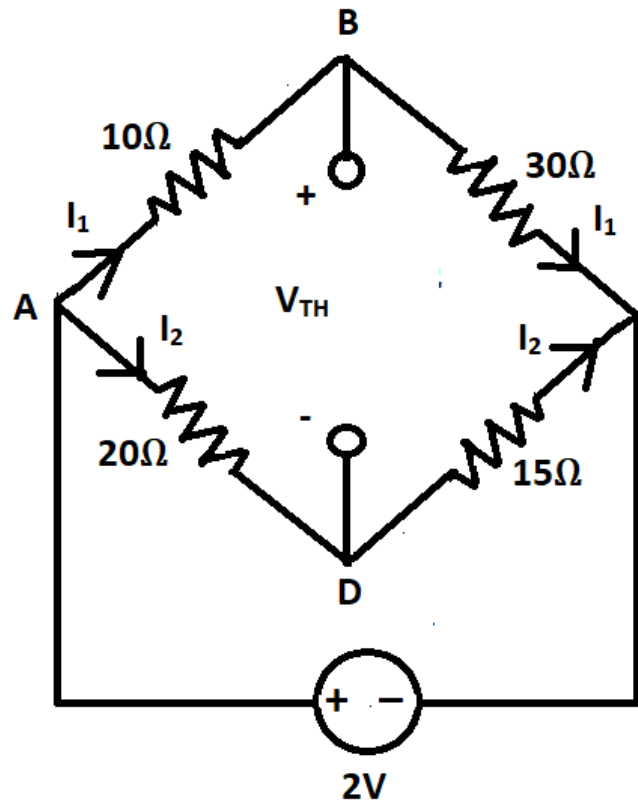

$$I_1 = \frac{2V}{40\Omega} = 0.05A ; I_2 = \frac{2V}{35\Omega} = 0.057A$$

By KVL (ABDA),  $-10 \cdot I_1 - V_{TH} + 20 \cdot I_2 = 0$


$$V_{TH} = 0.64V$$

# ELEMENTS OF ELECTRICAL ENGINEERING


## Numerical Example 1

**Solution (Continued..) :**

Finding  $R_{TH}$  :

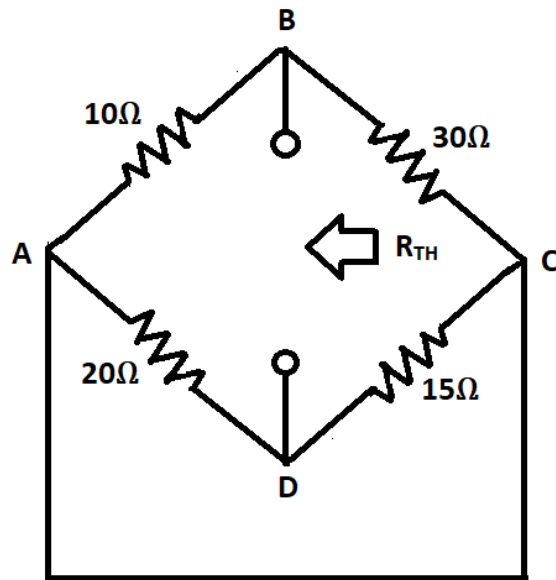

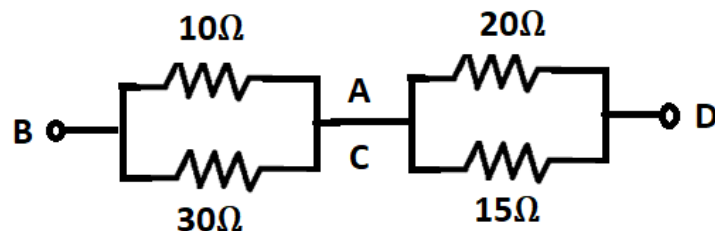
$$R_{TH} = (10\Omega \parallel 30\Omega) + (20\Omega \parallel 15\Omega) = 16.07\Omega$$



**Solution (Continued..) :**

**Thevenin's Equivalent Circuit:**

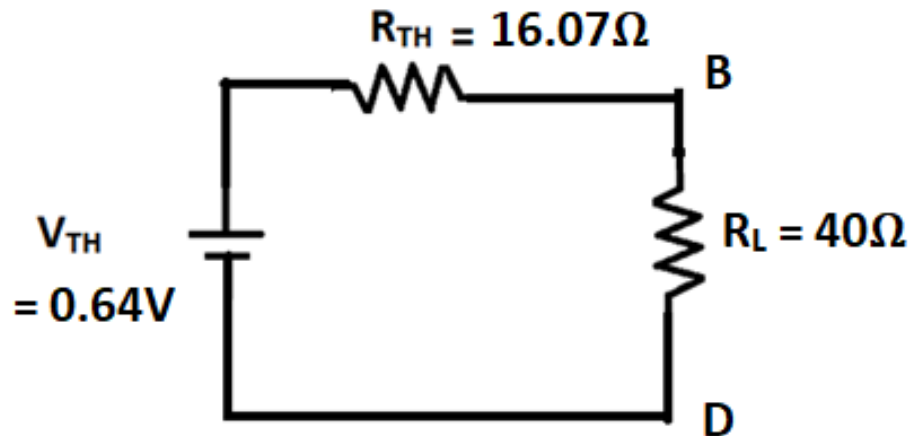


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Hence, current through the branch BD is 11.41mA and flows from terminal B to terminal D

## Numerical Example 2
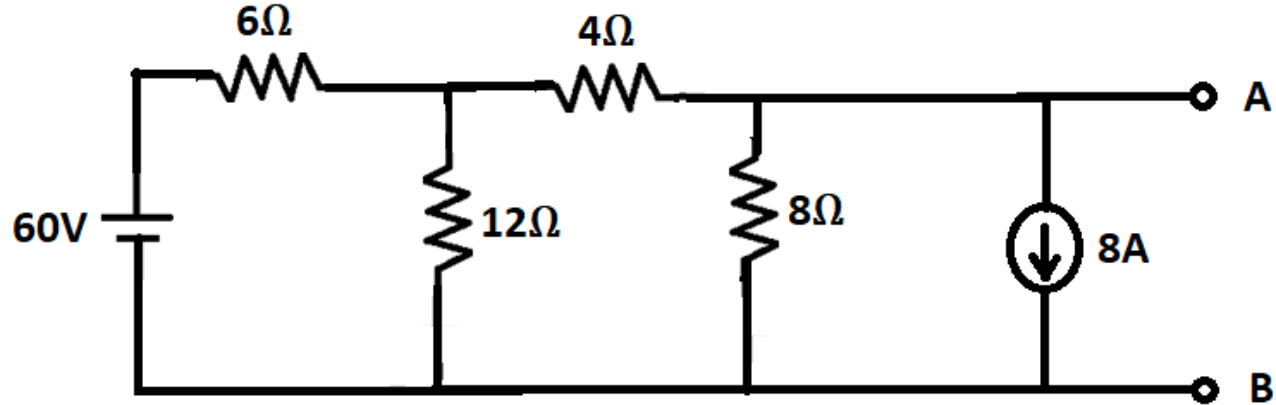
### Question:

Obtain the Thevenin's Equivalent across the terminals A & B for the network given.




# ELEMENTS OF ELECTRICAL ENGINEERING

## Numerical Example 2

**Solution :**

Finding  $V_{TH}$  :

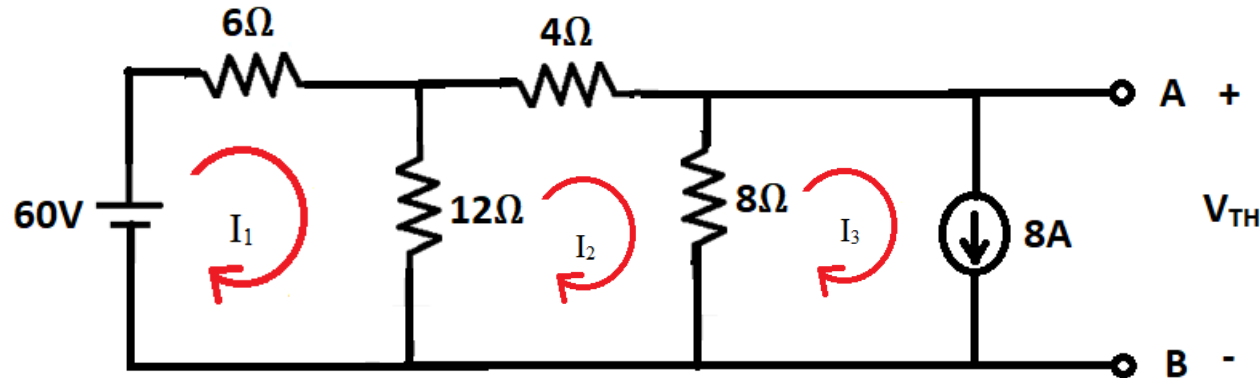

$$\text{KVL (Mesh 1)} : 18I_1 - 12I_2 - 0I_3 = 60 \quad \text{---- (1)}$$

$$\text{KVL (Mesh 2)} : -12I_1 + 24I_2 - 8I_3 = 0 \quad \text{---- (2)}$$

$$\text{Current Equation (Mesh 3)} : I_3 = 8 \quad \text{---- (3)}$$

Solving (1), (2) & (3),  $I_1 = 7.66\text{A}$  ;  $I_2 = 6.5\text{A}$

$$V_{TH} = (I_2 - I_3) * 8\Omega = -12\text{V}$$




# ELEMENTS OF ELECTRICAL ENGINEERING

## Numerical Example 2

**Solution (Continued..) :**


Finding  $R_{TH}$  :

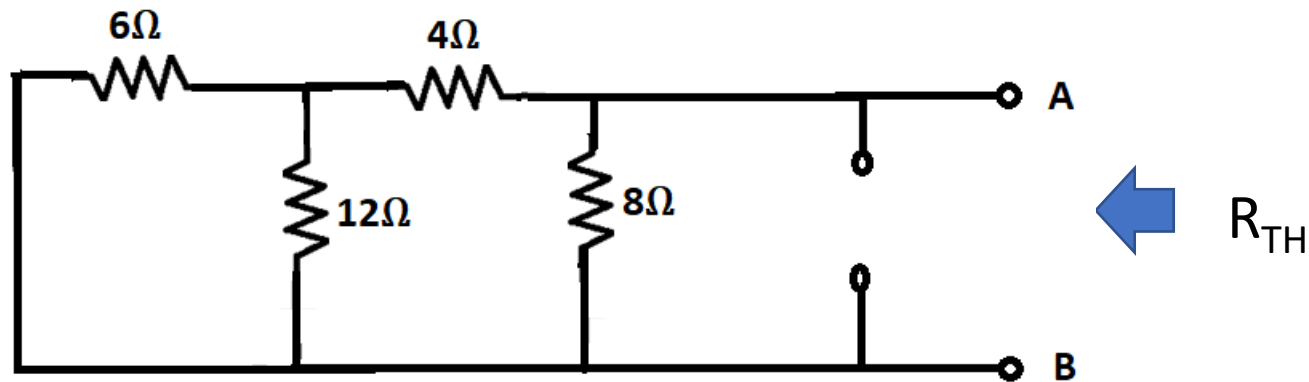

$$R_{TH} = \{(6\Omega \parallel 12\Omega) + 4\Omega\} \parallel 8\Omega = 4\Omega$$

Solution (Continued..) :

Thevenin's Equivalent Circuit:

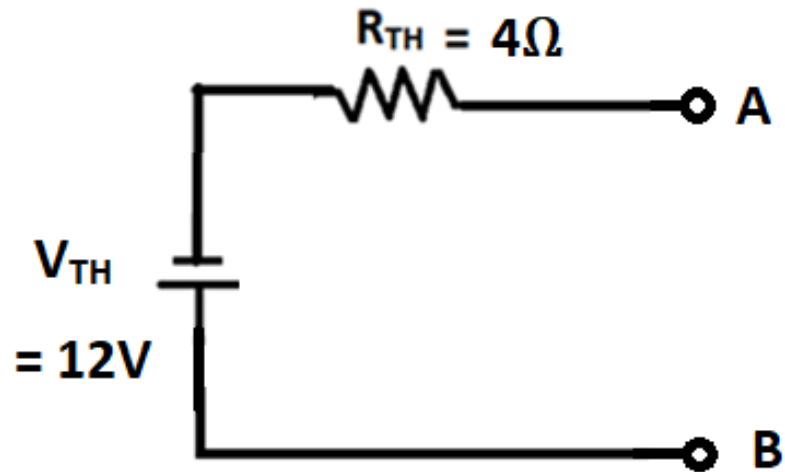


# ELEMENTS OF ELECTRICAL ENGINEERING

## Assignment Question
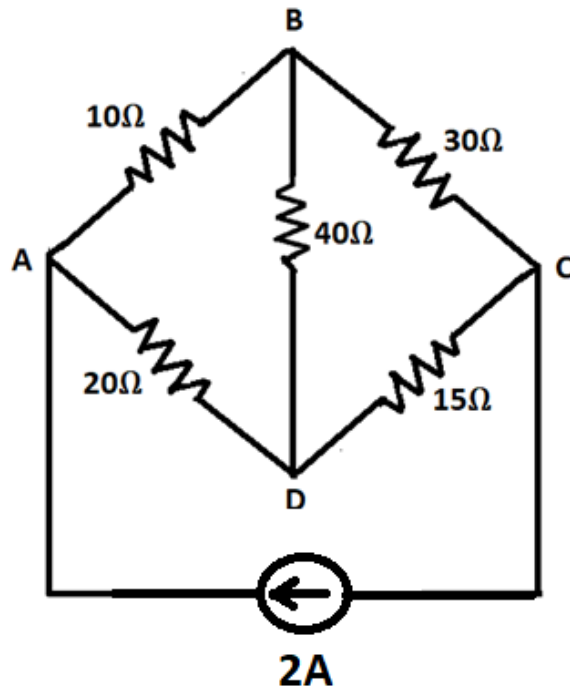
### Question:

Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.



# ELEMENTS OF ELECTRICAL ENGINEERING

## Text Book & References

---



### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



# THANK YOU

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**