



# ELEMENTS OF ELECTRICAL ENGINEERING

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

# ELEMENTS OF ELECTRICAL ENGINEERING

---


## Star Delta Transformations

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering
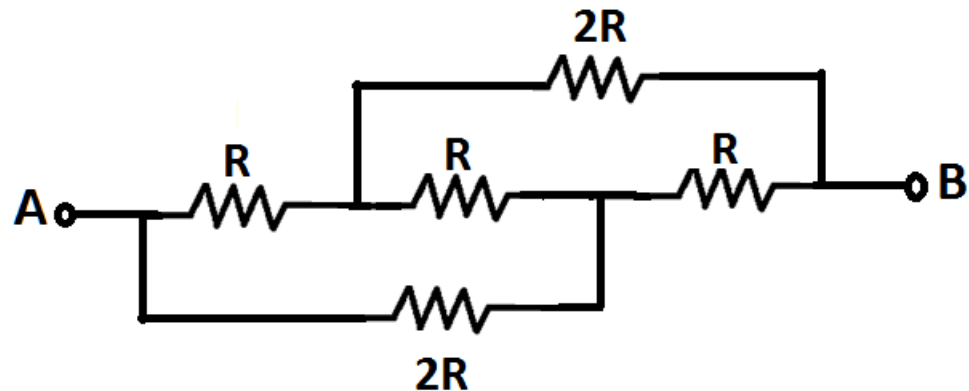
### Question:



Find the equivalent resistance between the terminals A & B in the given network.



# ELEMENTS OF ELECTRICAL ENGINEERING

## Star Delta Transformations – Numerical Example 3

**Solution:**


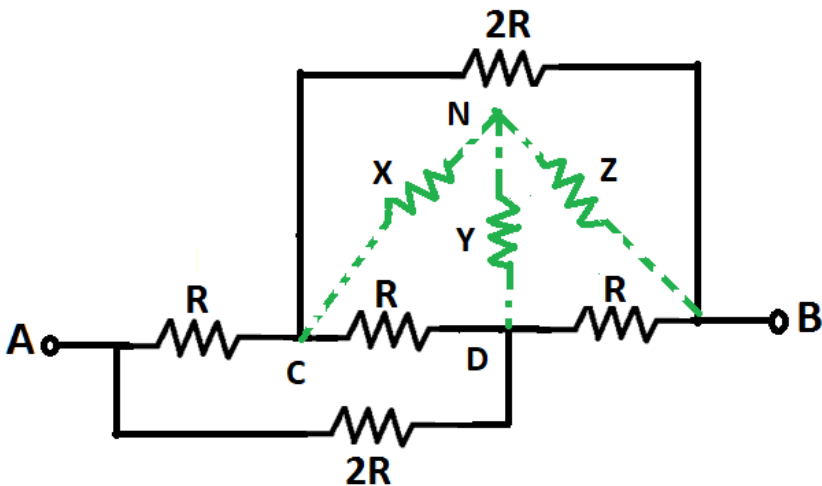
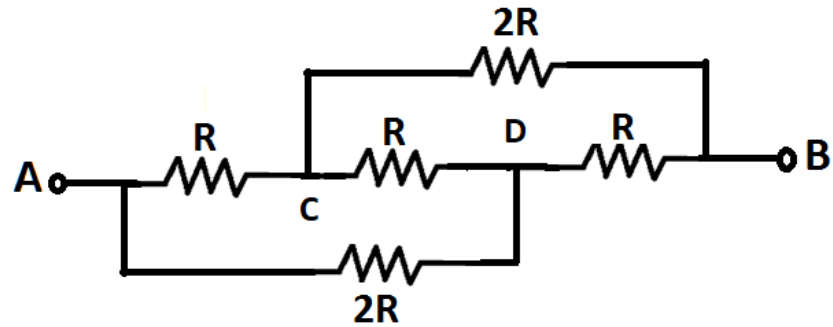


$$X = \frac{R * 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$

$$Y = \frac{R * R}{(R + 2R + R)} = \frac{R}{4} \Omega$$


$$Z = \frac{R * 2R}{(R + 2R + R)} = \frac{R}{2} \Omega$$

Solution (Continued..) :

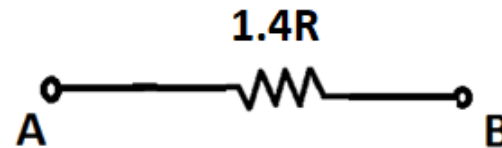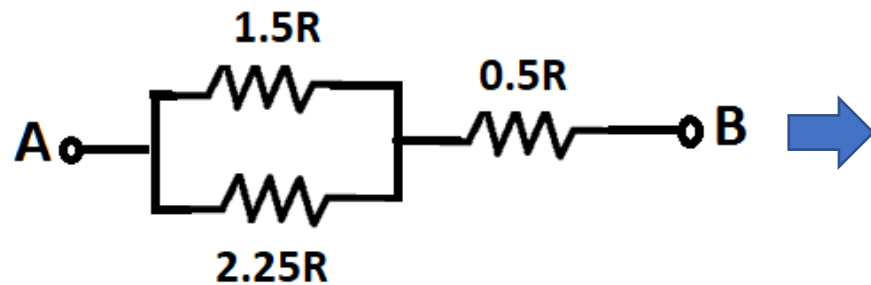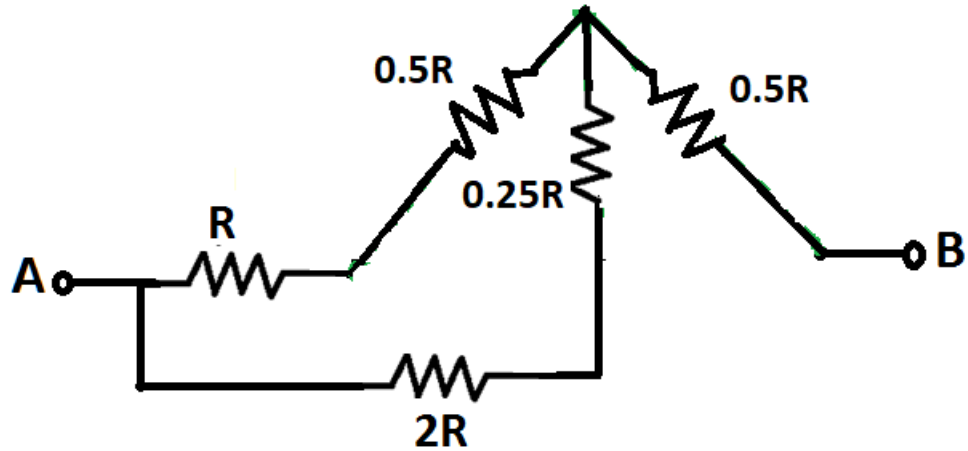
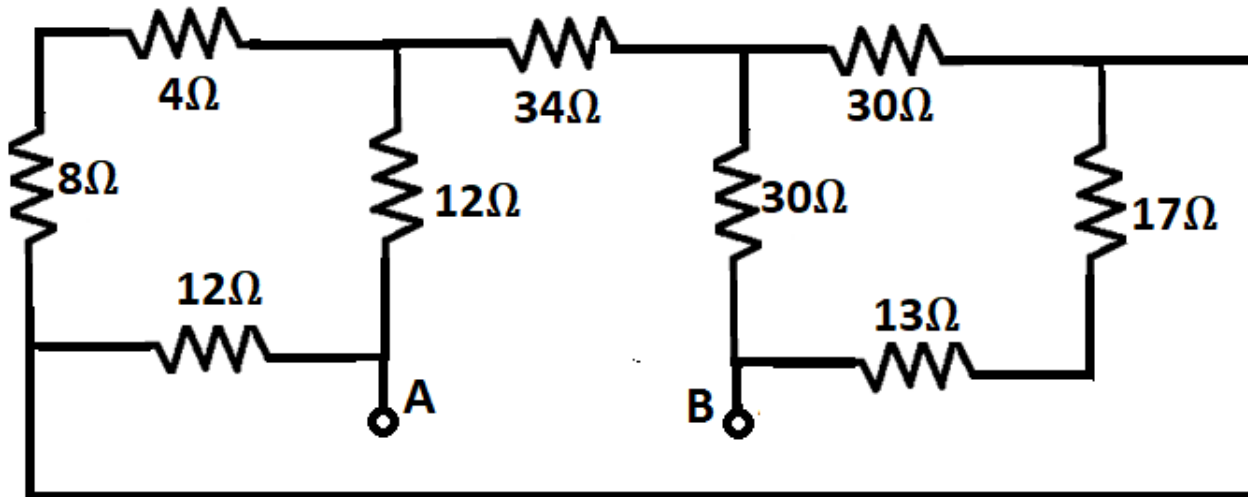
### Question:



Find the equivalent resistance between the terminals A & B in the network shown.







# ELEMENTS OF ELECTRICAL ENGINEERING

## Star Delta Transformations – Numerical Example 4

**Solution:**

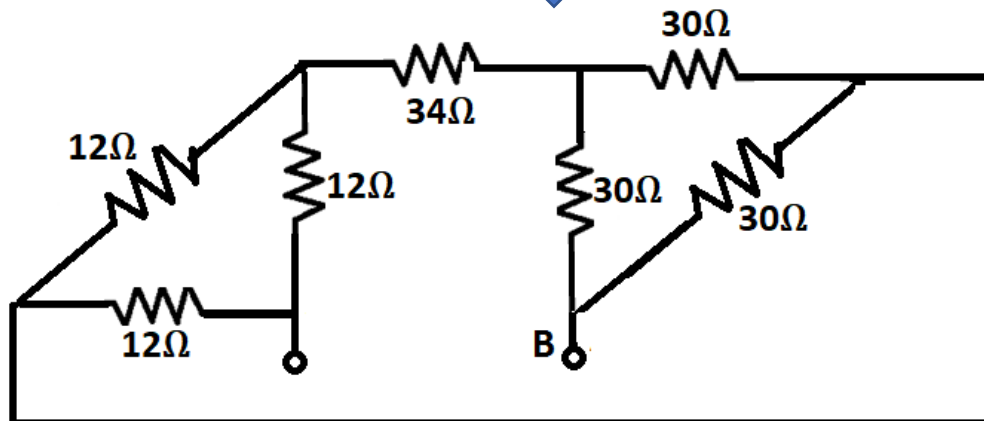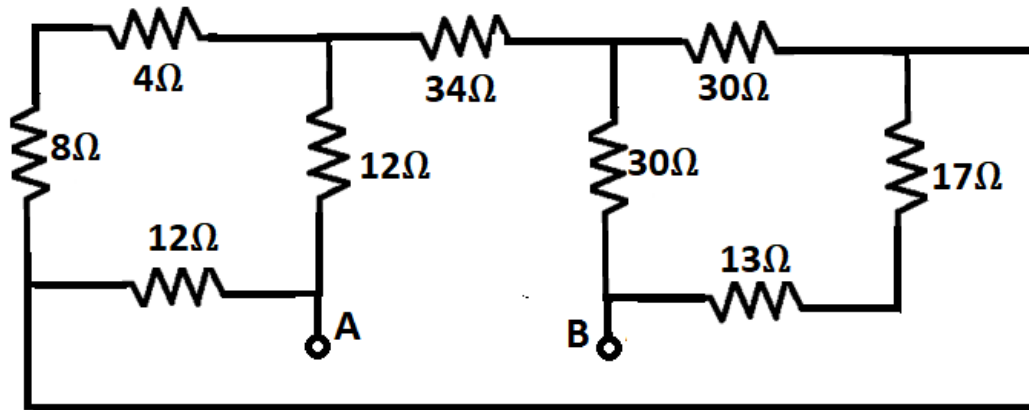

Solution (Continued..) :

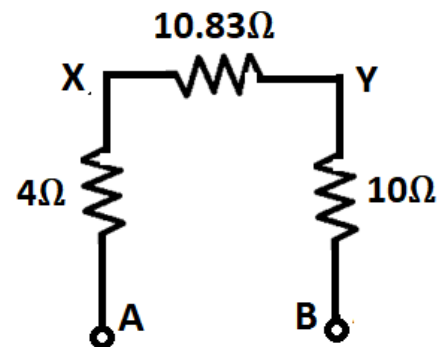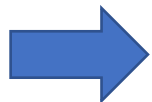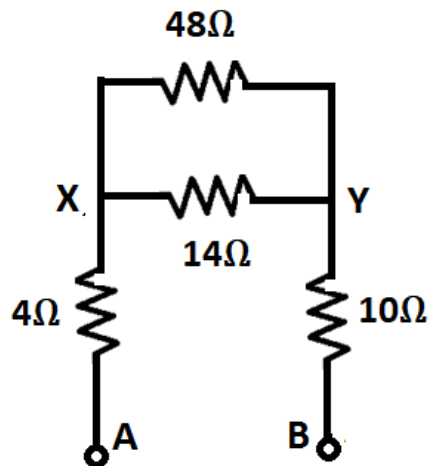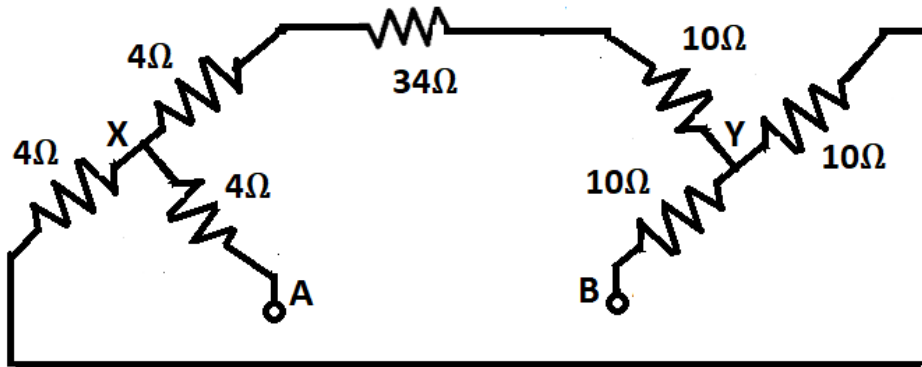

$$R_{AB} = 24.83\Omega$$




# ELEMENTS OF ELECTRICAL ENGINEERING

## Star Delta Transformations – Numerical Example 5
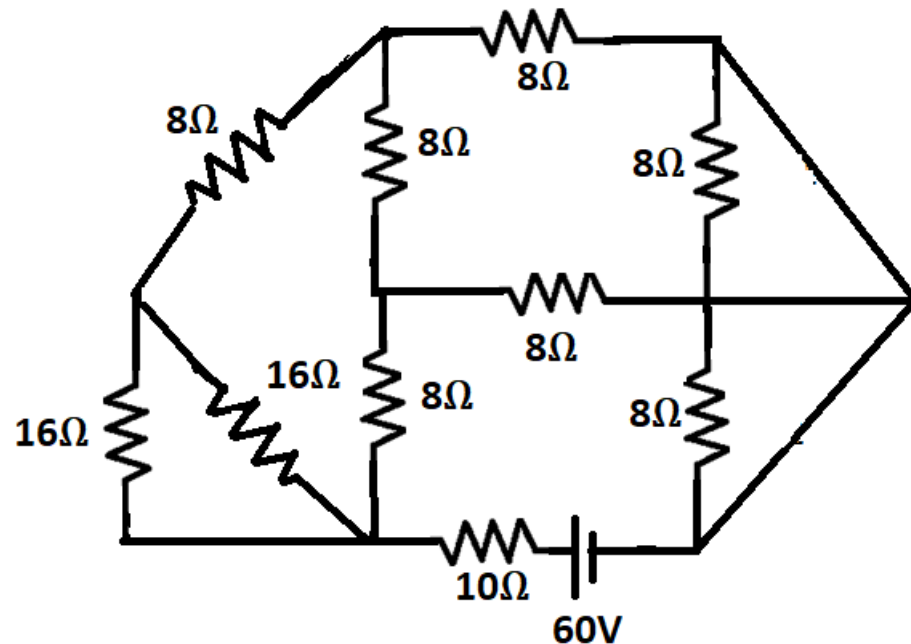
### Question:


Find the voltage drop across  $10\Omega$  resistor in the network shown.






# ELEMENTS OF ELECTRICAL ENGINEERING

## Star Delta Transformations – Numerical Example 5


**Solution:**

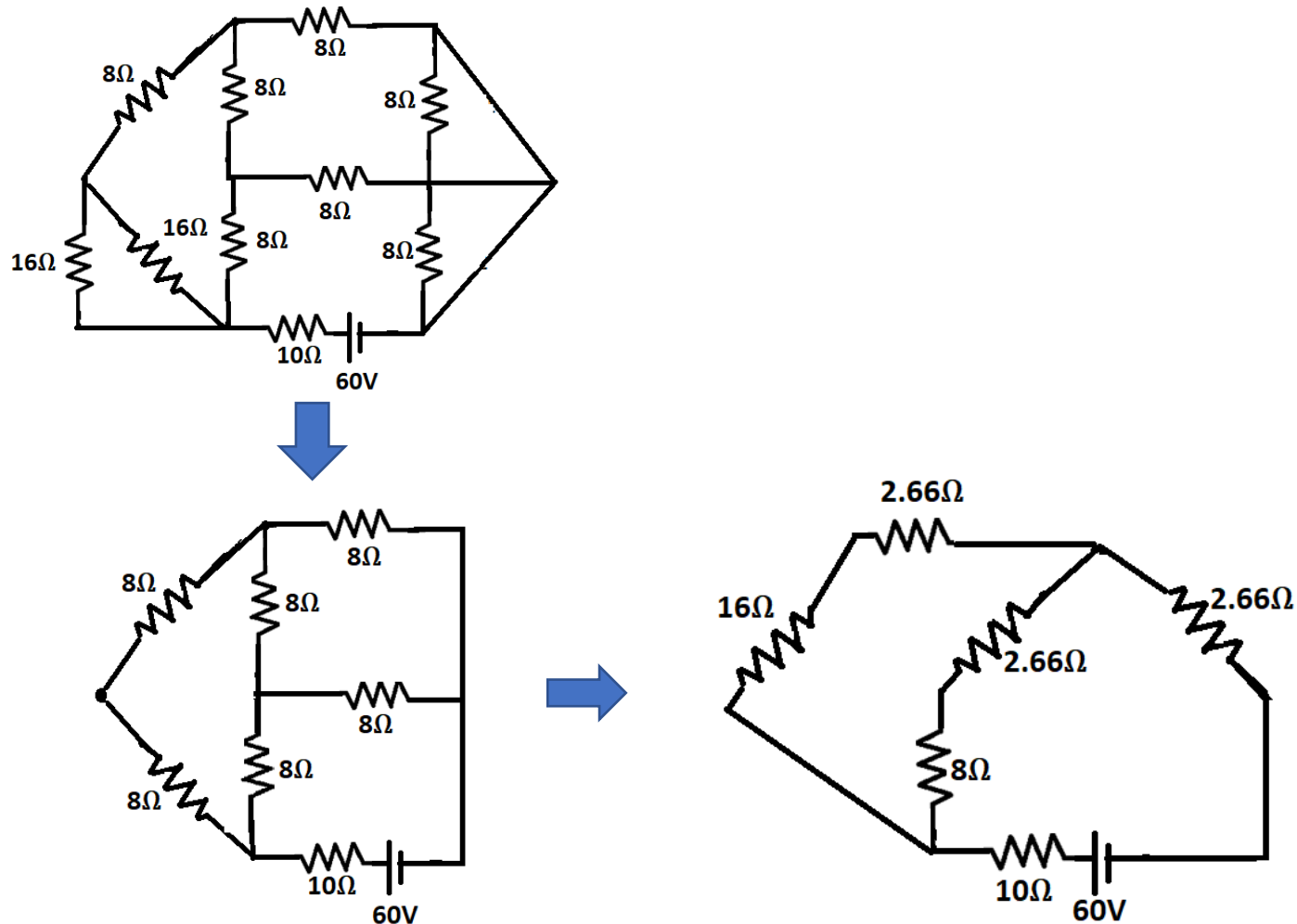

**Solution (Continued..) :**

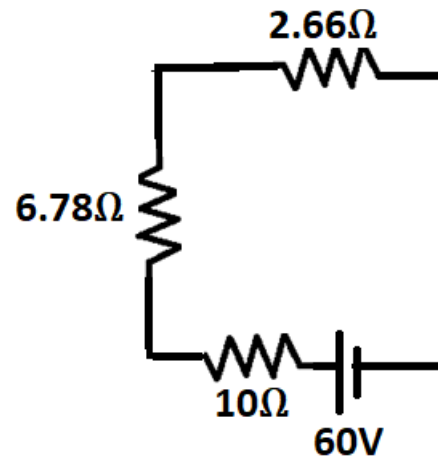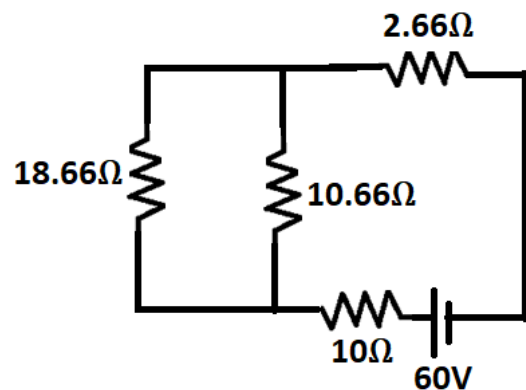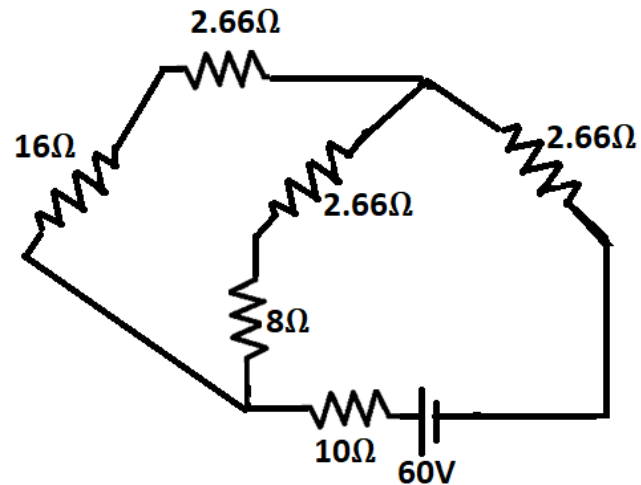

**Solution (Continued..) :**

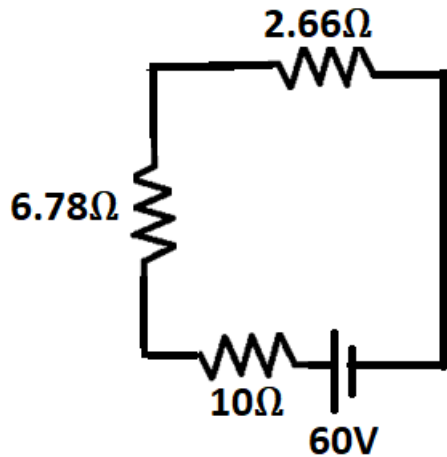

Current delivered by 60V source,  $I_S = \frac{60}{R_{eq}} = \frac{60}{19.44} = 3.086\text{A}$

Voltage drop across 10Ω resistor =  $I_S * 10 = 30.86\text{V}$

# ELEMENTS OF ELECTRICAL ENGINEERING

## Text Book & References

---



### Text Book:

“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 11<sup>th</sup> Edition, Pearson Education, 2012.

### Reference Books:

1. “Basic Electrical Engineering”, K Uma Rao, Pearson Education, 2011.
2. “Basic Electrical Engineering - Revised Edition”, D. C. Kulshreshta, Tata- McGraw-Hill, 2012.
3. “Engineering Circuit Analysis”, William Hayt Jr., Jack E. Kemmerly & Steven M. Durbin, 8<sup>th</sup> Edition, McGraw-Hill, 2012.



**THANK YOU**

---

**Vadhiraj K P P**

Department of Electrical & Electronics Engineering

**[vadhirajkpp@pes.edu](mailto:vadhirajkpp@pes.edu)**