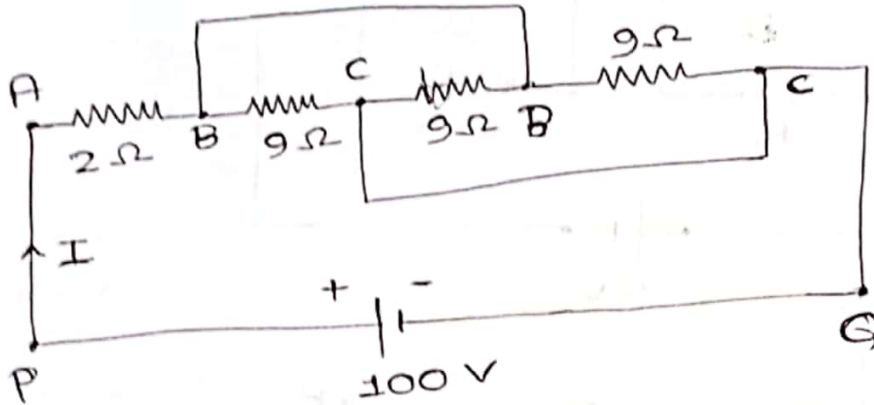



EEE- Assignment 1 - solutions

①


1) Find the power consumed by the combination of resistances when connected to a voltage source of 100 V at terminals P-Q.




Solution :-

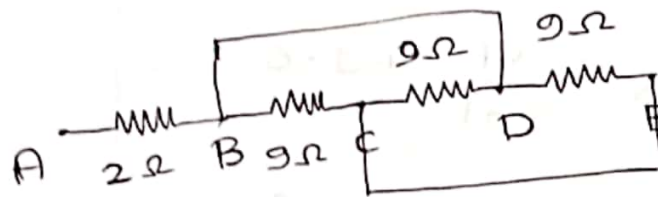

$$\frac{9+9}{10} = 4.5$$

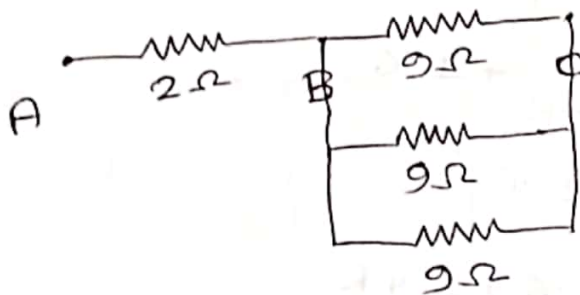
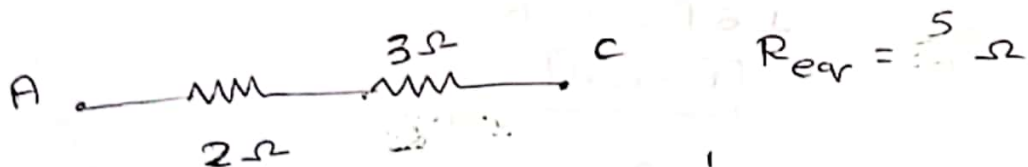
$$\frac{1}{\frac{1}{9} + \frac{1}{9} + \frac{1}{9}} = 3$$




$$R_{eq} = 5 \Omega$$

$$P = \frac{V^2}{R} = \frac{100 \times 100}{5} = 2 \text{ kW}$$

②

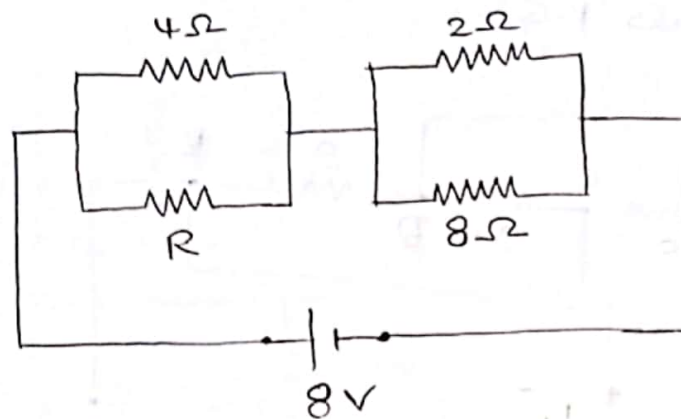- 2) The total power consumed by the circuit is 16 W. Find the value of R if applied voltage is 8 V. Also calculate total current.



Solution :-

$$R_{eq} = \frac{R \times 4}{R + 4} + \frac{2 \times 8}{10}$$

$$R_{eq} = \frac{4R}{4+R} + 1.6$$

$$P = \frac{V^2}{R_{eq}} \Rightarrow R_{eq} = \frac{V^2}{P} = \frac{8 \times 8}{16} = 4\Omega$$

$$\boxed{R_{eq} = 4\Omega}$$

$$4\Omega = \frac{4R}{4+R} + 1.6$$

$$\frac{4R}{4+R} = 2.4$$

$$4R = 9.6 + 2.4R$$

$$1.6R = 9.6$$


$$\boxed{R = 6\Omega}$$

$$P = I^2 \cdot R_{eq}$$




$$I^2 = \frac{16}{4}$$

$$\boxed{I = 2A}$$



3)

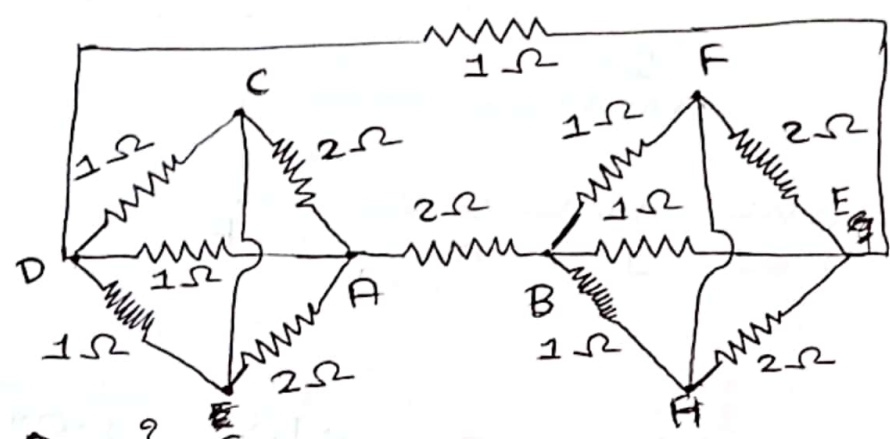


Find R_{AB} ?

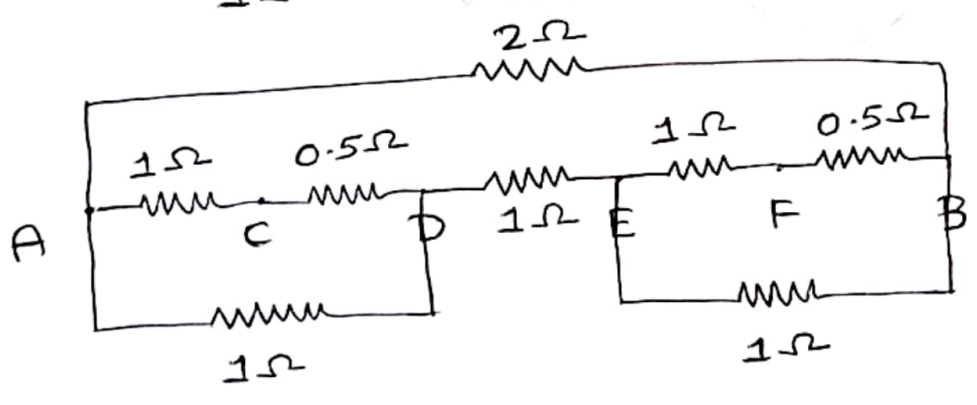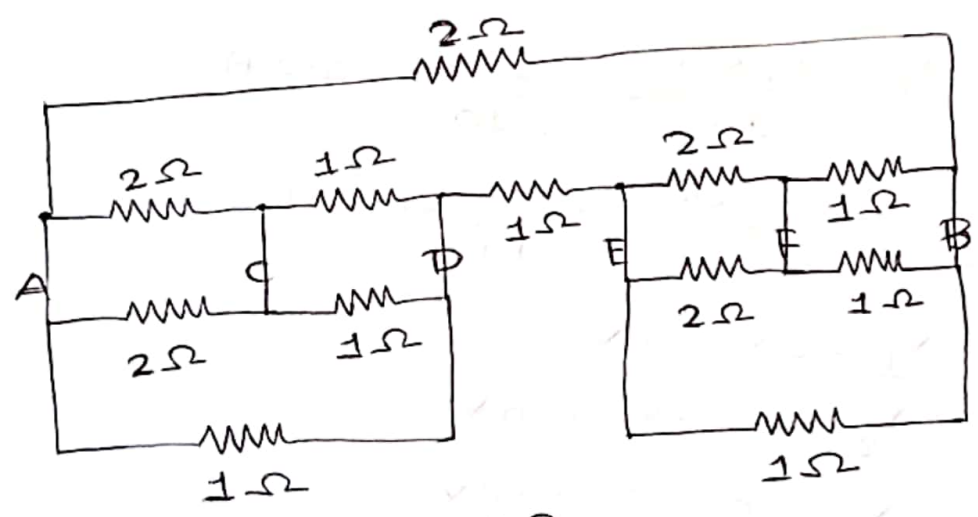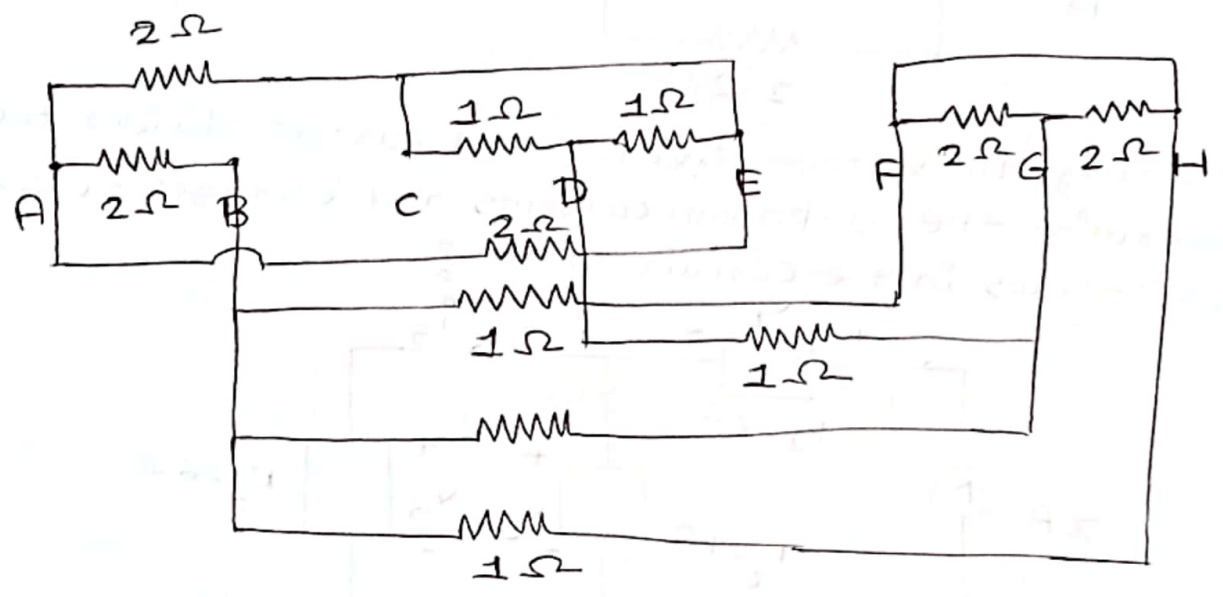

(4)

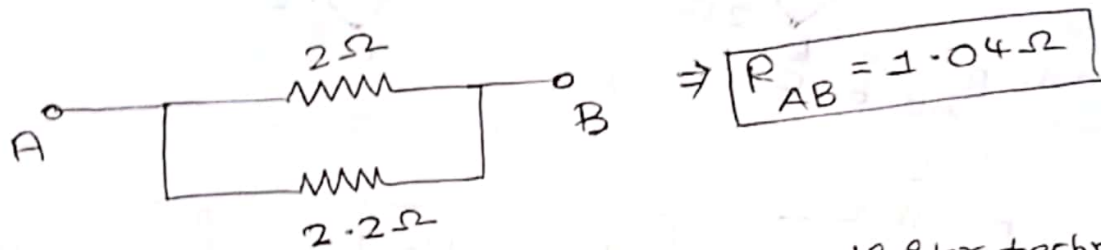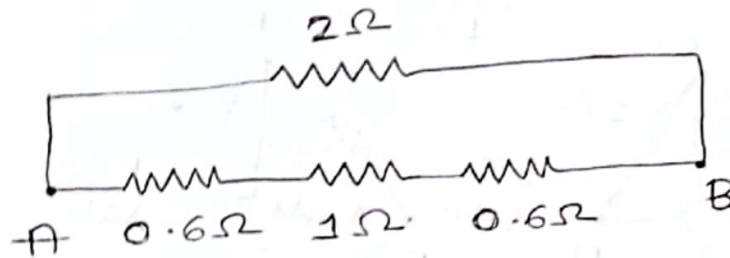

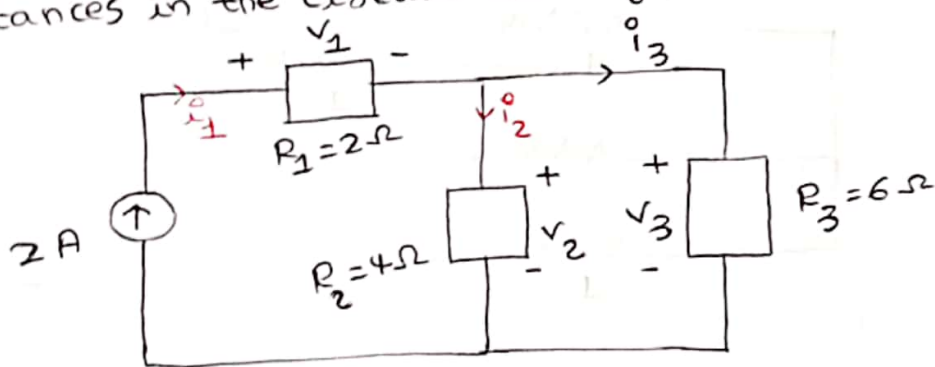4) using the voltage divider and current divider techniques, determine the unknown currents and voltages across the resistances in the circuit shown?



Solution

$$i_2 = \frac{i_1 \times 6}{10} = \frac{2 \times 6}{10} = 1.2 \text{ A}$$


$$i_3 = \frac{i_1 \times 4}{6+4} = \frac{8}{10} = 0.8 \text{ A}$$

$$V_1 = 2 \times 2 = 4 \text{ V}$$

$$V_2 = 1.2 \times 4 = 4.8 \text{ V}$$

$$V_3 = 0.8 \times 6 = 4.8 \text{ V}$$

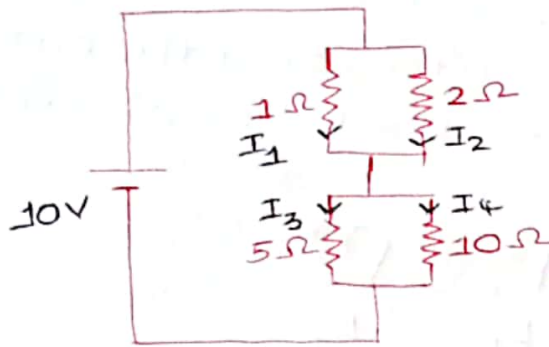5) Find all the currents & voltages across resistors as shown in the network below:




Solution

$$1\Omega \parallel 2\Omega = \frac{1 \times 2}{1+2} = \frac{2}{3} \Omega$$

$$5\Omega \parallel 10\Omega = \frac{5 \times 10}{5+10} = \frac{50}{15} = \frac{10}{3} \Omega$$
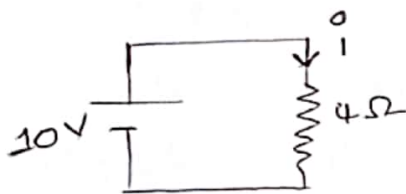
$$R_{eq} = \frac{2}{3} + \frac{10}{3} = \frac{12}{3} = 4\Omega$$



$$I_0 = 2.5 \text{ A}$$

$$I_1 = \frac{2.5 \times 2}{3} = 1.67 \text{ A}$$


$$I_2 = \frac{2.5 \times 1}{3} = 0.83 \text{ A}$$

$$I_3 = \frac{2.5 \times 10}{15} = 1.67 \text{ A}$$

$$I_4 = \frac{2.5 \times 5}{15} = 0.83 \text{ A}$$

$$V_1 = 1.67 \text{ V}; V_2 = 8.34 \text{ V}$$

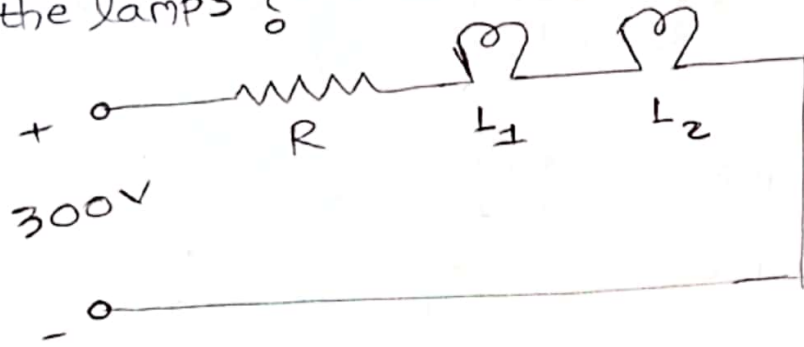⑥ In the circuit shown, find the value of the resistor R so that the lamps L_1 and L_2 operate at rated conditions. The rating of each of the lamps is $12V, 9W$.
If L_2 becomes short circuited, find the current through the circuit and the power dissipated in each of the lamps?



$$P = 9W$$

$$V = 12V$$

$$P = \frac{V^2}{R}$$

$$\checkmark I = \frac{P}{V}$$

$$R_{eq} = R + R_1 + R_2$$

$$R_{eq} = \frac{300}{I}$$

$$R_1 = R_2 = \frac{V^2}{P}$$

$$\text{Current through } L_1, R, L_2 = \frac{9}{12} = \frac{P}{V} = 0.75A$$

$$R_1 = R_2 = \frac{V^2}{P} = \frac{12^2}{9} = 16\Omega$$

$$R_{eq} = R + R_1 + R_2$$

$$R_{eq} = \frac{300}{I} = 400\Omega$$

$$R = R_{eq} - R_1 - R_2$$

$$R = 400 - 32$$

$$\boxed{R = 368\Omega}$$

If L_2 is short,

$$I = \frac{300}{R + 16}$$

$$\boxed{I = 0.78A}$$

Power dissipated in each of the lamps

$$= 0.75^2 \times 16$$

$$= 9W$$