

### Generation of Balanced Three Phase EMFs:

A balanced three phase system of EMFs is a set of three EMFs which are equal in amplitude (or) magnitude and displaced in phase from one another by  $120^\circ$ .

For instance,

$$e_1(t) = E_m \sin(\omega t)$$


$$e_2(t) = E_m \sin(\omega t - 120^\circ)$$

$$e_3(t) = E_m \sin(\omega t - 240^\circ)$$

represent balanced three phase system of EMFs.

A balanced three phase system of EMFs is generated in a machine called 'Three Phase Generator', also called 'Alternator'.

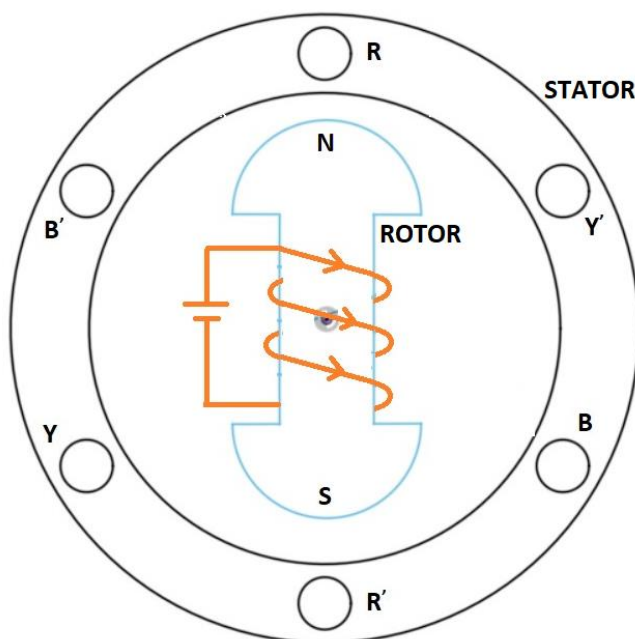
### Three Phase Generator (or) Alternator – Construction:



The '**Stator**' which is the stationary member consists of three coils R, Y & B which are physically displaced from one another by  $120^\circ$ . The '**Rotor**' which is the rotating member consists of set of electromagnets excited by a field winding connected to a DC supply. The shaft of the rotor is coupled to a prime mover such as steam turbine (or) hydro turbine (or) Diesel engine.

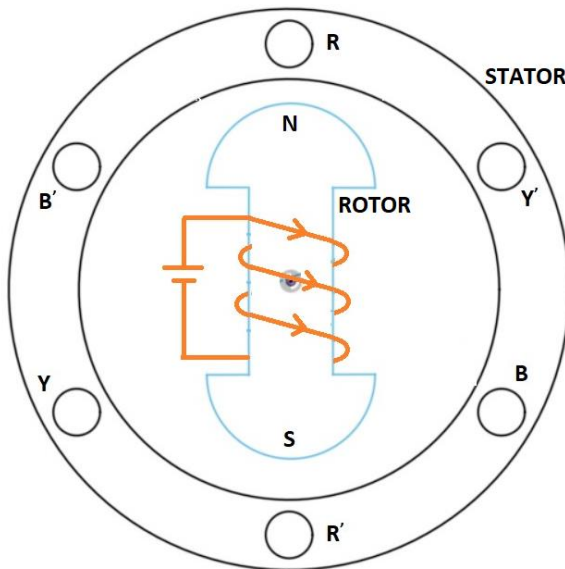
## Principle of Operation:

Let us consider Position 1: Coil R facing centre of North Pole




In this position, R-coil will have maximum rate of change of flux linkages hence, maximum positive EMF is induced in it in this position.

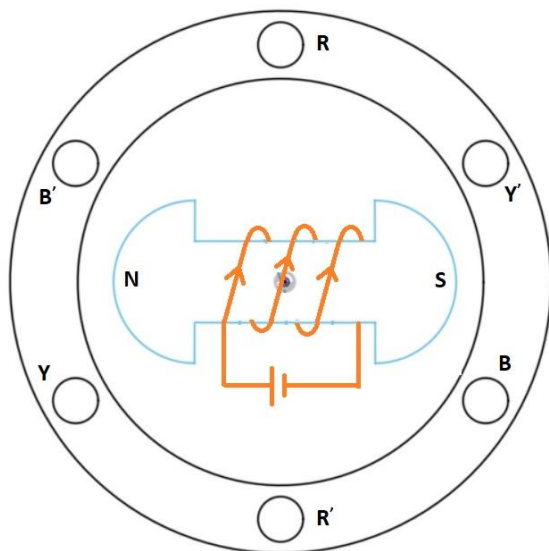Let us consider Position 2: Coil R facing interpolar axis



In this position, R-coil will have minimum rate of change of flux linkages hence, Zero EMF is induced in it in this position.

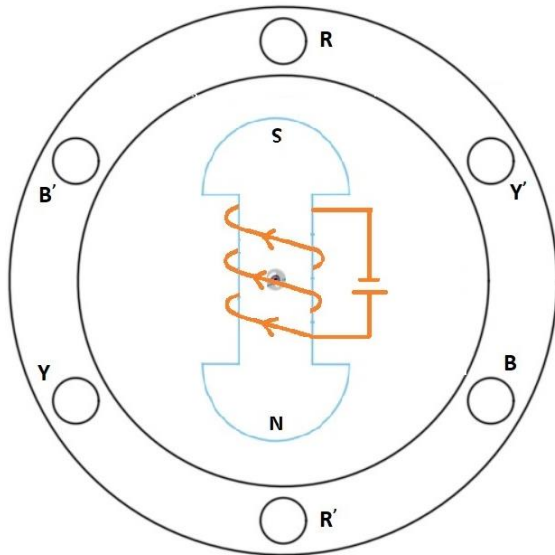Let us consider Position 3: Coil R facing centre of South Pole




In this position, R-coil will have maximum rate of change of flux linkages and since facing south pole, will have maximum negative EMF induced in it.

As rotor completes one revolution, one cycle of sinusoidal EMF is induced in R – coil. In Y – coil, another sinusoidal EMF is induced which has same amplitude and frequency as that in R – coil but it lags R – coil EMF by  $120^\circ$ . Similarly in B – coil, another sinusoidal EMF is induced which has same amplitude and frequency as that in R – coil but it lags R – coil EMF by  $240^\circ$ .

Thus, As rotor completes one revolution, balanced three phase system of EMFs are generated in the three coils placed in the stator.

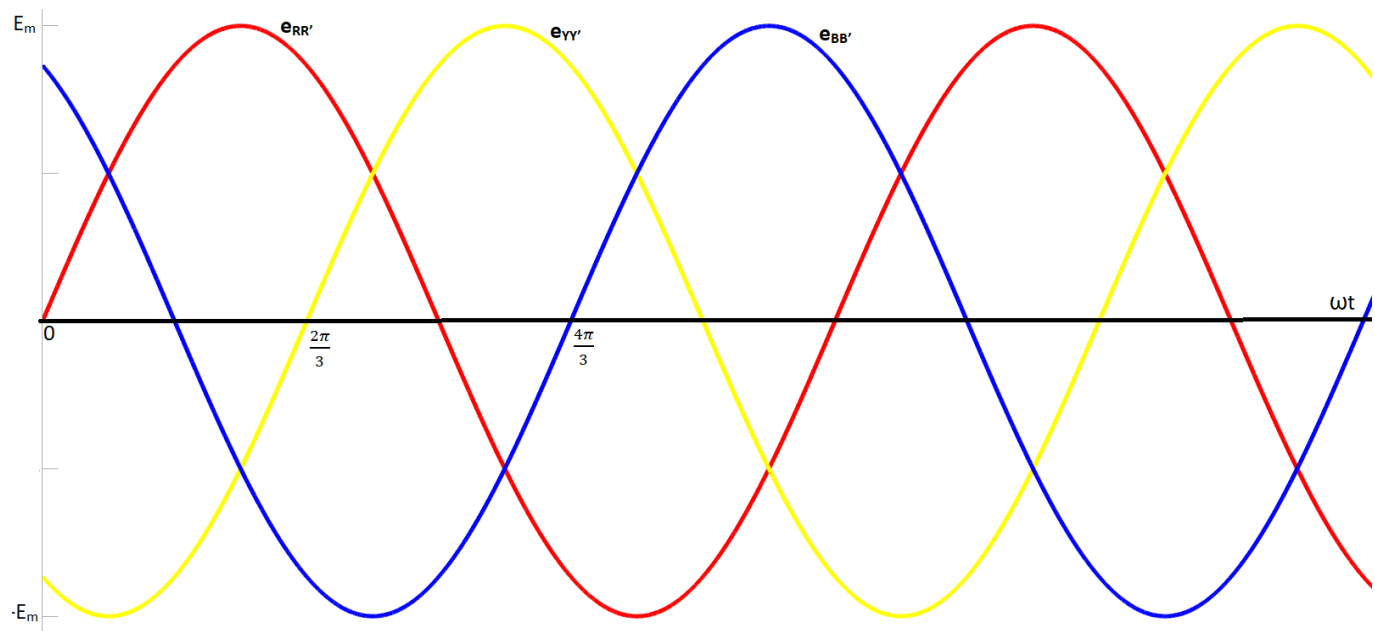
### Phase Sequence:

Phase Sequence of a Three Phase System is defined as the sequence in which the three phase EMFs attain peak value. Usual phase sequence is RYB.


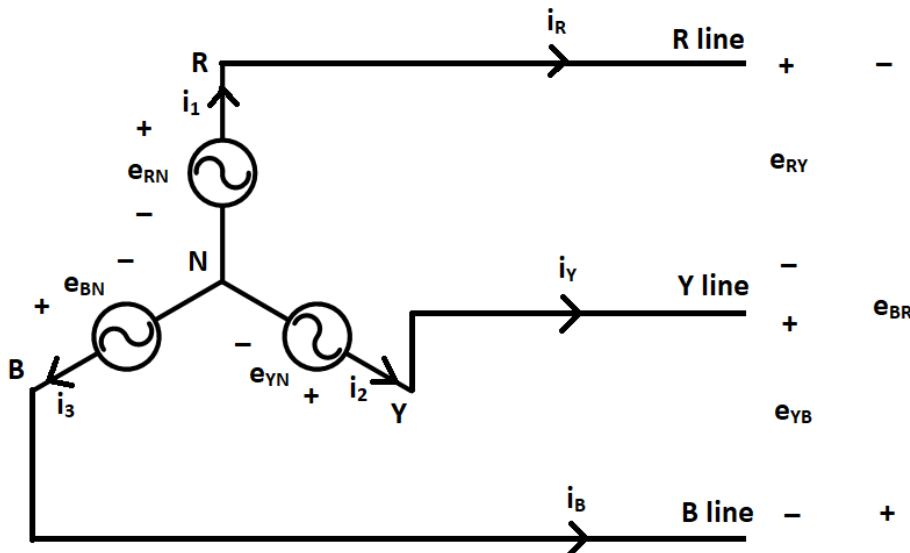
## Balanced Star (or) WYE Connected Three Phase System

To make a star connected three phase system, similar terminals such as R' , Y' and B' are connected together to make 'Neutral' point (N) of the three phase system. And lines are run from the other three terminals i.e., R, Y and B.



### Phase Voltage:

The voltage across the terminals of a phase is called the Phase Voltage.

Here,  $e_{RN}$  ,  $e_{YN}$  &  $e_{BN}$  represent phase voltages.

### Line Voltage:

The voltage across any two lines is called the Line Voltage.

Here,  $e_{RY}$  ,  $e_{YB}$  &  $e_{BR}$  represent Line (or) Line to line voltages.

### Phase Current:

The current flowing through a phase is called the Phase Current.

Here,  $i_1$  ,  $i_2$  &  $i_3$  represent phase currents.

### Line Current:

The current flowing through a line is called the Line Current.

Here,  $i_R$  ,  $i_Y$  &  $i_B$  represent line currents.

### Relation between Line & Phase currents – Balanced Star System:

In a balanced star connected three phase system, it can be observed that


Line current = Phase current

$$\text{i.e., } i_1 = i_R$$

$$i_2 = i_Y$$

$$i_3 = i_B$$
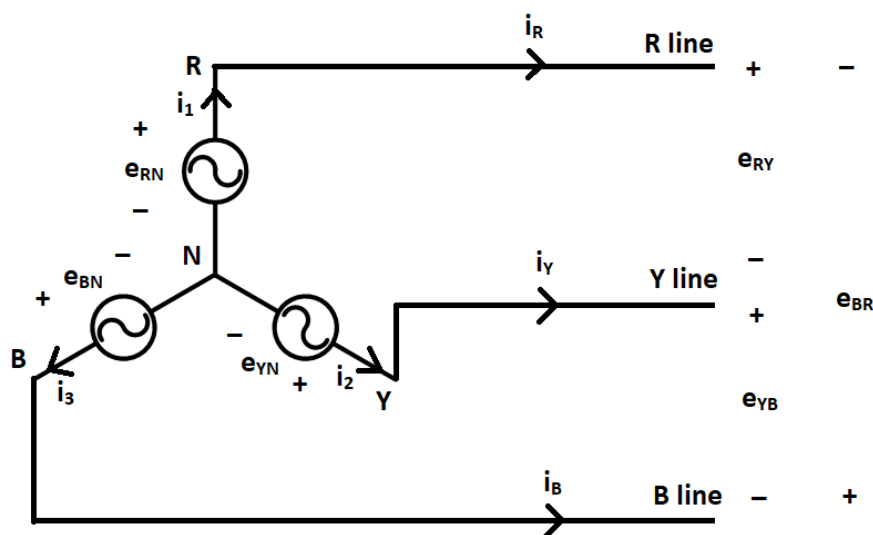
### Relation between Line & Phase voltages – Balanced Star System:



By KVL in the path RYNR,  $-e_{RY} - e_{YN} + e_{RN} = 0$

Hence,  $e_{RY} = e_{RN} - e_{YN}$

$$\overline{E_{RY}} = \overline{E_{RN}} - \overline{E_{YN}}$$

$$\overline{E_{RN}} = \frac{E_m}{\sqrt{2}} \angle 0^\circ = E_{ph} \angle 0^\circ$$

where,  $E_{ph}$  is the RMS value of phase voltage.

$$\overline{E_{YN}} = \frac{E_m}{\sqrt{2}} \angle -120^\circ = E_{ph} \angle -120^\circ$$

$$\overline{E_{BN}} = \frac{E_m}{\sqrt{2}} \angle -240^\circ = E_{ph} \angle -240^\circ$$

$$\overline{E_{RY}} = E_{ph} \angle 0^\circ - E_{ph} \angle -120^\circ$$

$$= E_{ph} (1 - (\cos 120^\circ - j \sin 120^\circ))$$

$$= E_{ph} \left( \frac{3}{2} + j \frac{\sqrt{3}}{2} \right)$$

$$= \sqrt{3} E_{ph} (\cos 30^\circ + j \sin 30^\circ)$$

$$= \sqrt{3} E_{ph} \angle 30^\circ$$


$$\overline{E_{YB}} = \overline{E_{YN}} - \overline{E_{BN}} = \sqrt{3} E_{ph} \angle -90^\circ$$

$$\overline{E_{BR}} = \overline{E_{BN}} - \overline{E_{RN}} = \sqrt{3} E_{ph} \angle -210^\circ$$

Thus, in a balanced star connected three phase system,


- (i) Magnitude (RMS value) of Line Voltage =  $\sqrt{3}$  \* (Magnitude of Phase Voltage)
- (ii) Each line voltage leads the corresponding phase voltage by  $30^\circ$
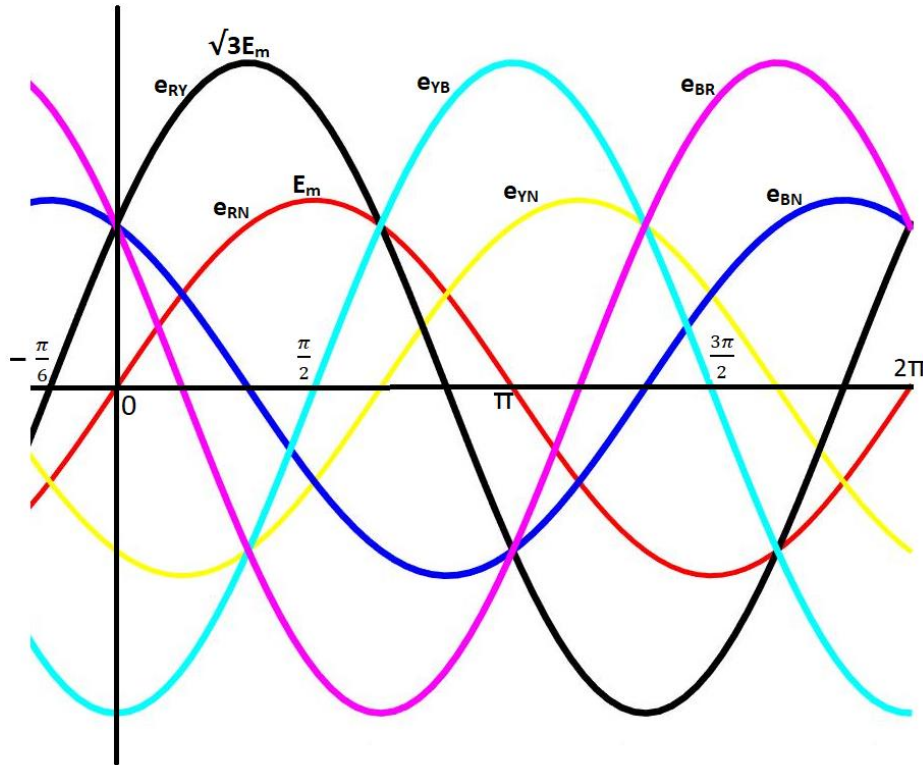
### Balanced Star System – Line and Phase Voltage Waveforms:


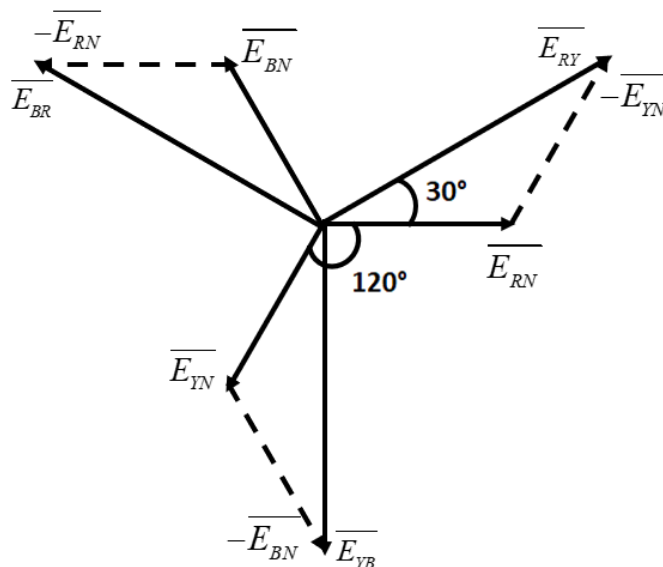
### Balanced Star System – Phasor diagram:


$$\overline{E_{RY}} = \overline{E_{RN}} - \overline{E_{YN}}$$




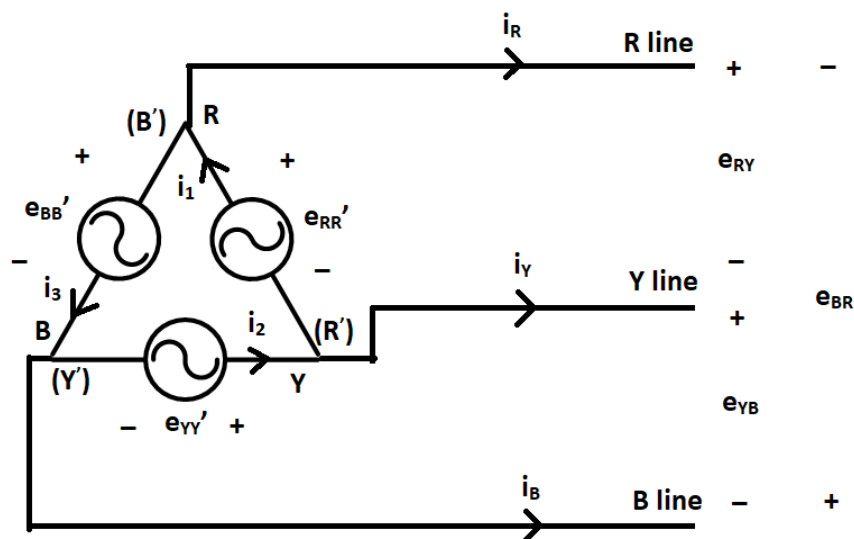
## Balanced Delta (or) Mesh Connected Three Phase System

To make a delta connected three phase system, the three coils R, Y & B are connected back to back (or) end to end. And lines are run from the junction points R, Y and B.



### Phase Voltage:

The voltage across the terminals of a phase is called the Phase Voltage.

Here,  $e_{RR'}$ ,  $e_{YY'}$  &  $e_{BB'}$  represent phase voltages.

### Line Voltage:

The voltage across any two lines is called the Line Voltage.

Here,  $e_{RY}$ ,  $e_{YB}$  &  $e_{BR}$  represent Line (or) Line to line voltages.

### Phase Current:

The current flowing through a phase is called the Phase Current.

Here,  $i_1$ ,  $i_2$  &  $i_3$  represent phase currents.

### Line Current:

The current flowing through a line is called the Line Current.

Here,  $i_R$ ,  $i_Y$  &  $i_B$  represent line currents.

### Relation between Line & Phase Voltages – Balanced Delta System:

In a balanced delta connected three phase system, it can be observed that


Line Voltage = Phase Voltage

i.e.,  $e_{RY} = e_{RR'}$

$e_{YB} = e_{YY'}$

$e_{BR} = e_{BB'}$
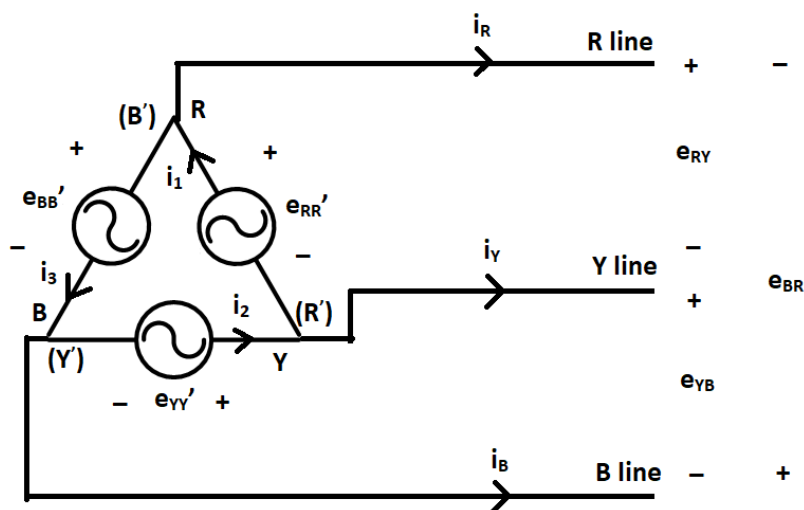
### Relation between Line & Phase Currents – Balanced Delta System:



By KCL at R,  $i_1 = i_R + i_3$

Hence,  $i_R = i_1 - i_3$

$$\bar{I}_R = \bar{I}_1 - \bar{I}_3$$

$$\bar{I}_1 = \frac{I_m}{\sqrt{2}} \angle 0^\circ = I_{ph} \angle 0^\circ$$

where,  $I_{ph}$  is the RMS value of phase current.

$$\bar{I}_2 = \frac{I_m}{\sqrt{2}} \angle -120^\circ = I_{ph} \angle -120^\circ$$

$$\overline{I}_3 = \frac{I_m}{\sqrt{2}} \angle -240^\circ = I_{ph} \angle -240^\circ$$

$$\begin{aligned}\overline{I}_R &= I_{ph} \angle 0^\circ - I_{ph} \angle -240^\circ \\ &= I_{ph} (1 - (\cos 240^\circ - j \sin 240^\circ))\end{aligned}$$

$$\begin{aligned}&= I_{ph} \left( \frac{3}{2} - j \frac{\sqrt{3}}{2} \right) \\ &= \sqrt{3} I_{ph} (\cos 30^\circ - j \sin 30^\circ) \\ &= \sqrt{3} I_{ph} \angle -30^\circ\end{aligned}$$


$$\overline{I}_Y = \overline{I}_2 - \overline{I}_1 = \sqrt{3} I_{ph} \angle -150^\circ$$

$$\overline{I}_B = \overline{I}_3 - \overline{I}_2 = \sqrt{3} I_{ph} \angle -270^\circ$$


Thus, in a balanced delta connected three phase system,

- (i) Magnitude (RMS value) of Line current =  $\sqrt{3}$  \* (Magnitude of Phase current)
- (ii) Each line current lags the corresponding phase current by  $30^\circ$
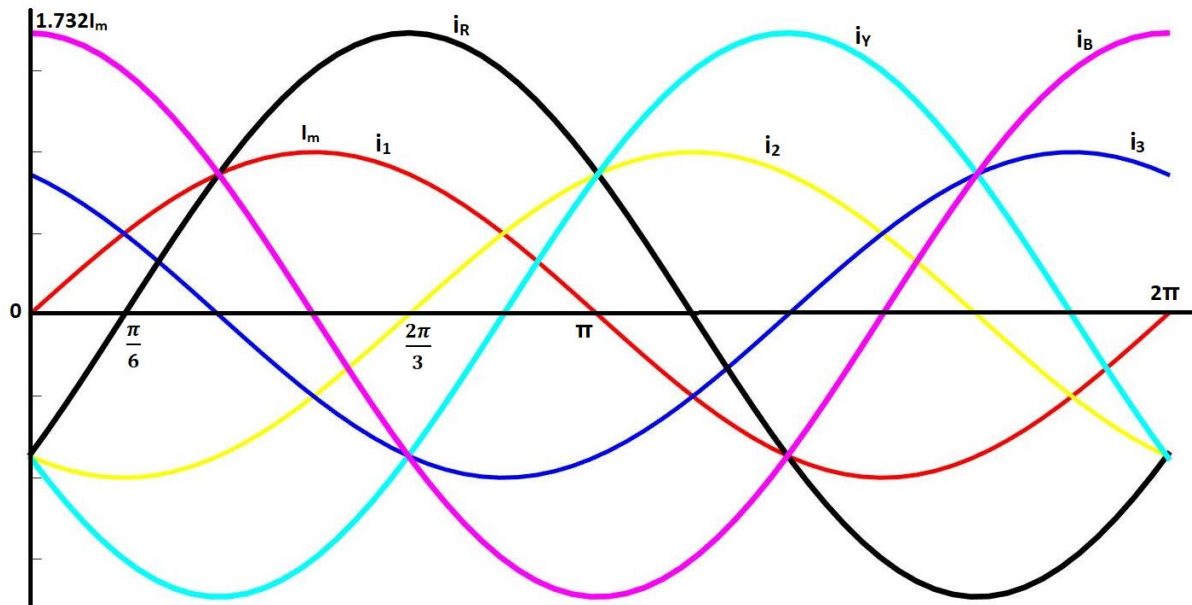
### Balanced Delta System – Line and Phase current Waveforms:


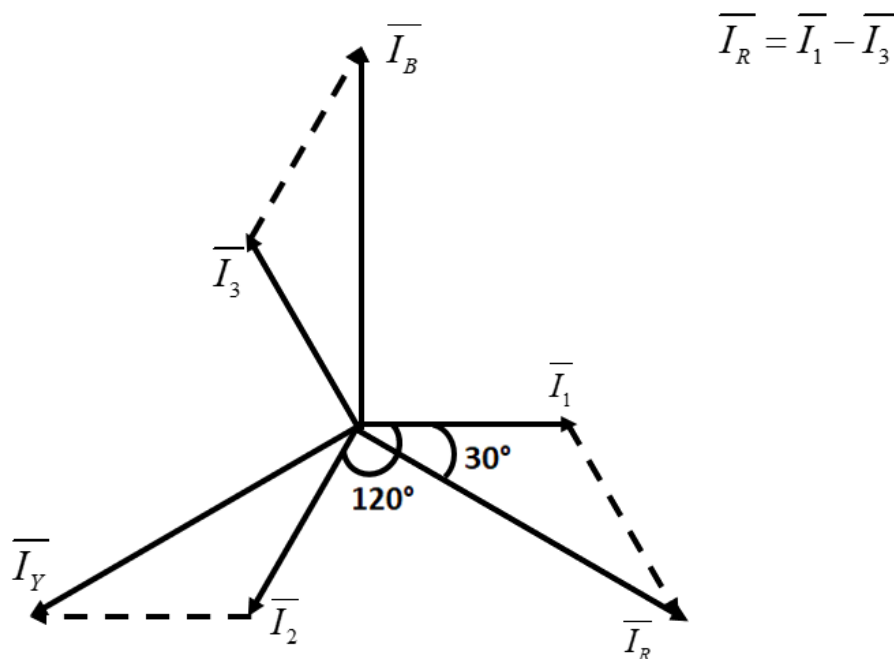
### Balanced Delta System – Phasor diagram:



### Balanced Three Phase Supply:

A Three phase supply is said to be balanced if

- i) The three EMFs are equal in magnitude
- ii) Phase displaced from one another by  $120^\circ$

For example,  $e_1 = 100\sin(\omega t)$

$$e_2 = 100\sin(\omega t - 120^\circ)$$

$$e_3 = 100\sin(\omega t + 120^\circ)$$

represents balanced three phase supply.

Examples of unbalanced three phase supply systems are:

- i)  $e_1 = 100\sin(\omega t)$  ,  $e_2 = 110\sin(\omega t - 120^\circ)$  ,  $e_3 = 100\sin(\omega t + 120^\circ)$
- ii)  $e_1 = 100\sin(\omega t)$  ,  $e_2 = 100\sin(\omega t - 125^\circ)$  ,  $e_3 = 100\sin(\omega t + 120^\circ)$

### Balanced Three Phase Load:

A Three phase Load can be either star connected type or delta connected type.

A Three phase Load is said to be balanced if in each phase of the load both resistance and reactance are exactly same.

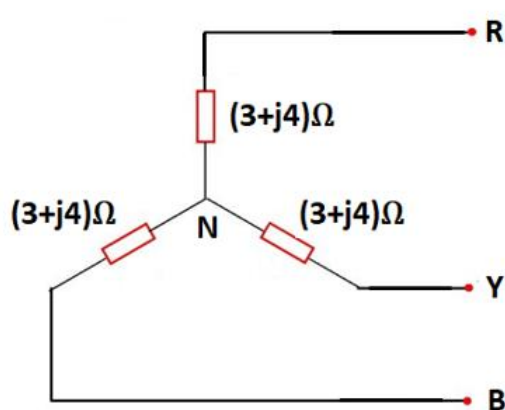


Fig 1: Balanced Star connected Load

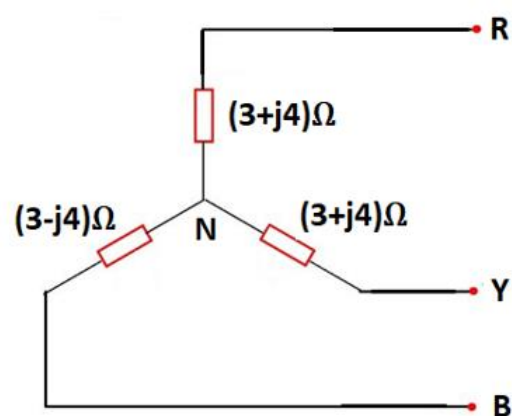


Fig 2: Unbalanced Star connected Load

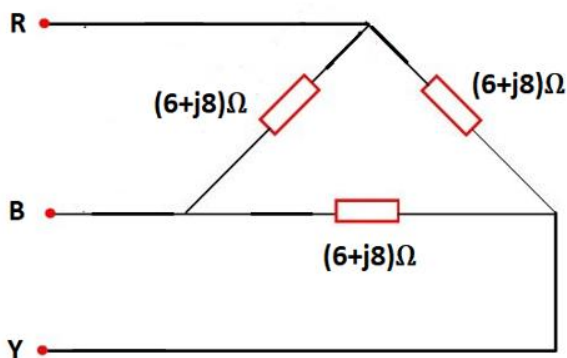


Fig 1: Balanced Delta connected Load

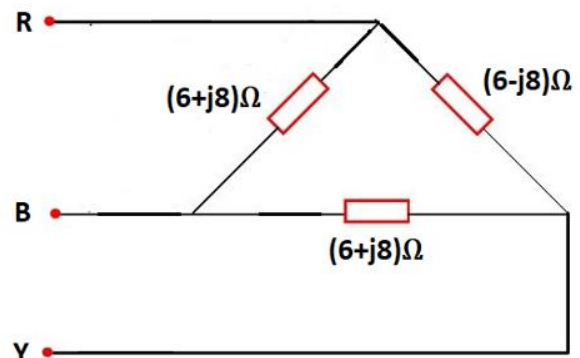


Fig 2: Unbalanced Delta connected Load

When a balanced three phase load is connected across a balanced three phase supply, the three phase currents drawn will also be balanced in nature.

### Power Relations in Balanced Three Phase Systems:

When a balanced three phase load is connected across a balanced three phase supply, the three phase currents drawn will also be balanced in nature.

This leads to an advantage that balanced three phase systems can be analysed per phase basis and the results can be extended to all three phases.

Thus, in balanced three phase systems, power can be calculated for any one phase and the total three phase power will be thrice that of any one phase.

### Active Power in Balanced Three Phase Systems:

Three phase Active Power,  $P_{3\text{-phase}} = 3 * P_{1\text{-phase}} = 3 * (V_{ph} * I_{ph} * \cos\phi)$

For a balanced star connected three phase system,

$$P_{3\text{-phase}} = 3 * V_{ph} * I_{ph} * \cos\phi = \sqrt{3} * (\sqrt{3} * V_{ph}) * I_{ph} * \cos\phi = \sqrt{3} * (V_L) * I_L * \cos\phi$$

For a balanced delta connected three phase system,

$$P_{3\text{-phase}} = 3 * V_{ph} * I_{ph} * \cos\phi = \sqrt{3} * V_{ph} * (\sqrt{3} * I_{ph}) * \cos\phi = \sqrt{3} * V_L * (I_L) * \cos\phi$$

Thus, alternatively either for star (or) delta system,  $P_{3\text{-phase}} = \sqrt{3} * V_L * I_L * \cos\phi$

Also, Alternatively,  $P_{3\text{-phase}} = 3 * (I_{ph}^2 * R)$

**Reactive Power in Balanced Three Phase Systems:**

Three phase Reactive Power,  $Q_{3-phase} = 3 * Q_{1-phase} = 3 * (V_{ph} * I_{ph} * \sin\phi)$

Alternatively,  $Q_{3-phase} = \sqrt{3} * V_L * I_L * \sin\phi$

Also, Alternatively,

$Q_{3-phase} = 3 * (I_{ph}^2 * X_L)$  for inductive loads

(or)

$Q_{3-phase} = -3 * (I_{ph}^2 * X_C)$  for capacitive loads

(or)

$Q_{3-phase} = 3 * (I_{ph}^2 * (X_L - X_C))$  for series RLC type of loads

**Apparent Power in Balanced Three Phase Systems:**

Three phase Apparent Power,  $S_{3-phase} = 3 * S_{1-phase} = 3 * (V_{ph} * I_{ph})$

Alternatively,  $S_{3-phase} = \sqrt{3} * V_L * I_L$

Also, Alternatively,

$S_{3-phase} = 3 * (I_{ph}^2 * |Z|)$

Apparent power can also be found as

$$S_{3-phase} = \sqrt{P_{3-phase}^2 + Q_{3-phase}^2}$$

Power factor of a balanced three phase system is

$$\cos\phi = \frac{P_{3-phase}}{S_{3-phase}}$$





## Numerical Examples on Balanced Star connected Three Phase System:

### Numerical Example 1:

#### Question:


A balanced 3 phase load consists of three coils, each of  $4\Omega$  resistance and  $0.02H$  inductance. Determine the total active and reactive power when the coils are connected in star, if the supply voltage is  $400V$ ,  $50\text{ Hz}$ .

#### Solution :
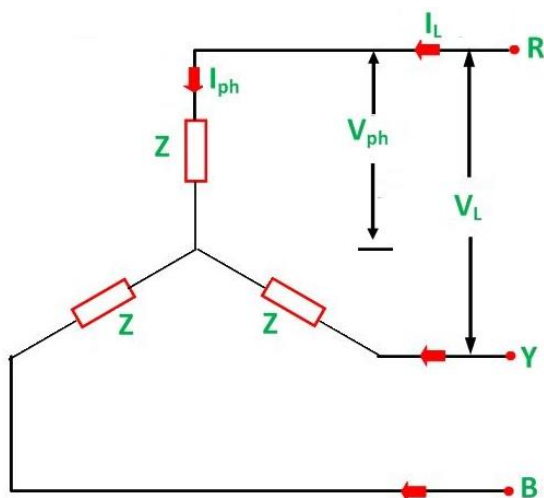
#### Note:

In three phase systems, by default, the voltages and currents given are line voltage and line current respectively.

Similarly, power given is three phase power by default.



#### Given Data:

Line voltage,  $V_L = 400V$  ;  $f = 50\text{Hz}$

Resistance per phase,  $R = 4\Omega$

Inductance per phase,  $L = 0.02H$

### Calculations:

Inductive reactance per phase,  $X_L = 2\pi fL = 6.28\Omega$

Impedance per phase,  $Z = R + jX_L = (4 + j6.28)\Omega$

Hence,  $|Z| = 7.45\Omega$  ; Phase Angle,  $\phi = 57.5^\circ$

Since star connected system, Phase voltage,  $V_{ph} = \frac{V_L}{\sqrt{3}} = 230.94V$

Hence, Phase current,  $I_{ph} = \frac{V_{ph}}{|Z|} = 31A$

Therefore, Line current,  $I_L = I_{ph} = 31A$

Three phase Active Power,  $P_{3-phase} = 3 \cdot P_{1-phase} = 3 \cdot V_{ph} \cdot I_{ph} \cdot \cos(\phi) = 11.54KW$

Alternatively,  $P_{3-phase} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi) = 11.54KW$

Alternatively,  $P_{3-phase} = 3 \cdot I_{ph}^2 \cdot R = 11.54KW$

Similarly, Three phase Reactive Power,

$Q_{3-phase} = 3 \cdot Q_{1-phase} = 3 \cdot V_{ph} \cdot I_{ph} \cdot \sin(\phi) = 18.11KVAR$

Alternatively,  $Q_{3-phase} = \sqrt{3} \cdot V_L \cdot I_L \cdot \sin(\phi) = 18.11KVAR$

Alternatively,  $Q_{3-phase} = 3 \cdot I_{ph}^2 \cdot X_L = 18.11KVAR$

### Numerical Example 2

#### Question:

**A balanced 3 $\Phi$ , star connected load of 100KW takes a leading current of 80A when connected to a 3 $\Phi$ , 1.1KV, 50Hz supply. Find the resistance, impedance, and the capacitance of the load per phase. Also calculate the power factor of the load.**

#### Solution :

#### Given Data:

Line voltage,  $V_L = 1.1KV$  ;  $f = 50Hz$

Line current,  $I_L = 80A$

Three phase Active Power,  $P_{3\text{-phase}} = 100\text{KW}$

**Calculations:**

Since star connected system, Phase current,  $I_{ph} = I_L = 80\text{A}$

And Phase voltage,  $V_{ph} = \frac{V_L}{\sqrt{3}} = 635.08\text{V}$

Impedance per phase,  $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$P_{3\text{-phase}} = 100\text{KW} = 3 \cdot I_{ph}^2 \cdot R$ ; Hence,  $R = 5.21\Omega$

Capacitive reactance per phase,  $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase,  $C = \frac{1}{\omega X_C} = 531.25\mu\text{F}$

Powerfactor of the load,  $\cos\phi = \frac{R}{Z} = 0.656$  Lead

**Alternative solution:**

Since star connected system, Phase current,  $I_{ph} = I_L = 80\text{A}$

And Phase voltage,  $V_{ph} = \frac{V_L}{\sqrt{3}} = 635.08\text{V}$

Impedance per phase,  $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$P_{3\text{-phase}} = 100\text{KW} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi)$

Hence, Powerfactor of the load,  $\cos\phi = 0.656$  Lead

Resistance per phase,  $R = Z \cdot \cos\phi = 5.21\Omega$

Capacitive reactance per phase,  $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase,  $C = \frac{1}{\omega X_C} = 531.25\mu\text{F}$

## Numerical Examples on Balanced Delta connected Three Phase System:

### Numerical Example 1:

#### Question:

A balanced delta connected load consumes 2 KW of power when connected to a three phase, 400 V, 50Hz supply. The same load when connected to a three phase 230V , 50 Hz supply, draws a current of 2 A at lagging power factor. Determine the load power factor and resistance and inductance per phase.

#### Solution :

##### Case1: Delta connected Load

##### Given Data:

Line voltage,  $V_L = 400V$  ;  $f = 50Hz$

Three phase Active Power,  $P_{3-phase} = 2KW$

Therefore,  $3 * V_{ph} * I_{ph} * \cos\phi = 2000W$

$$\text{i.e., } 3 * V_{ph} * \frac{V_{ph}}{Z} * \frac{R}{Z} = 2000W$$

Since, delta connected system,  $V_{ph} = V_L = 400V$

$$\text{Therefore, } 3 * 400^2 * \frac{R}{Z^2} = 2000W ; \text{ Hence, } \frac{R}{Z^2} = 0.004167 \text{ ----- (1)}$$

##### Case2: Same Delta connected Load

##### Given Data:

Line voltage,  $V_L = 230V$  ;  $f = 50Hz$

Line current,  $I_L = 2A$

Since same load,  $Z$  is same in both the cases.

Since, delta connected system,  $V_{ph} = V_L = 230V$

$$\text{And, } I_{ph} = \frac{I_L}{\sqrt{3}} = 1.155A$$

$$\text{Therefore, } Z = \frac{V_{ph}}{I_{ph}} = 199.13\Omega$$

Substituting 'Z' value in equation (1) above,

$$\text{Resistance per phase, } R = 165.24\Omega$$

$$\text{Inductive reactance per phase, } X_L = \sqrt{Z^2 - R^2} = 111.12\Omega$$

$$\text{Inductance per phase, } L = \frac{X_L}{\omega} = 0.354\text{H}$$

$$\text{Power factor of the Load, } \cos\phi = \frac{R}{Z} = 0.83 \text{ Lag}$$

### Numerical Example 2

#### Question:

The load connected to a three phase supply comprises three similar coils connected in star. The line current is 25 A, the real and apparent powers are 11KW, 20 KVA. Find the line voltage, resistance, and reactance of each coil. If the coils are connected in delta, find the line current and power taken.

#### Solution :

##### Case1: Balanced Star connected Load

Given Data:

$$\text{Line current, } I_L = 25\text{A}$$

$$\text{Three phase Active Power, } P_{3\text{-phase}} = 11\text{KW}$$

$$\text{Three phase Apparent Power, } S_{3\text{-phase}} = 20\text{KVA}$$

#### Calculations:

$$S_{3\text{-phase}} = \sqrt{3} * V_L * I_L = 20\text{KVA}$$

$$\text{Hence, } V_L = 461.88\text{V}$$

Since balanced star connected load,

$$I_{ph} = I_L = 25\text{A} ; V_{ph} = \frac{V_L}{\sqrt{3}} = 266.66\text{V}$$

Impedance per phase,  $Z = \frac{V_{ph}}{I_{ph}} = 10.66\Omega$

$P_{3-phase} = 11KW = 3 \cdot I_{ph}^2 \cdot R$ ; Hence,  $R = 5.86\Omega$

Inductive reactance per phase,  $X_L = \sqrt{(Z^2 - R^2)} = 8.905\Omega$

**Case2: Same Load reconnected as Delta Load across same supply**

Since same supply,  $V_L$  remains same and since same load,  $Z$ ,  $R$  &  $L$  in each phase remain same.

Since balanced delta connected load,  $V_{ph} = V_L = 461.88V$

Phase current,  $I_{ph} = \frac{V_{ph}}{Z} = 43.33A$

Line current,  $I_L = \sqrt{3} \cdot I_{ph} = 75.04A$


Power drawn,  $P_{3-phase} = 3 \cdot I_{ph}^2 \cdot R = 33KW$

Apparent Power,  $S_{3-phase} = \sqrt{3} \cdot V_L \cdot I_L = 60KVA$

## Measurement of Power and Power factor using Two Wattmeter Method:

### Wattmeter:


Wattmeter is a power measuring instrument. It consists of a fixed coil called 'Current Coil (CC)' and a moving coil called 'Pressure Coil' (PC). Pressure coil is also called 'Voltage coil' (VC).

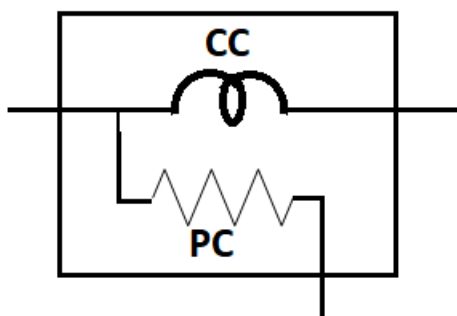

**Fig: Wattmeter symbol**

PC carries the pointer of the instrument and indicates the average power.

### Two Wattmeter Method:

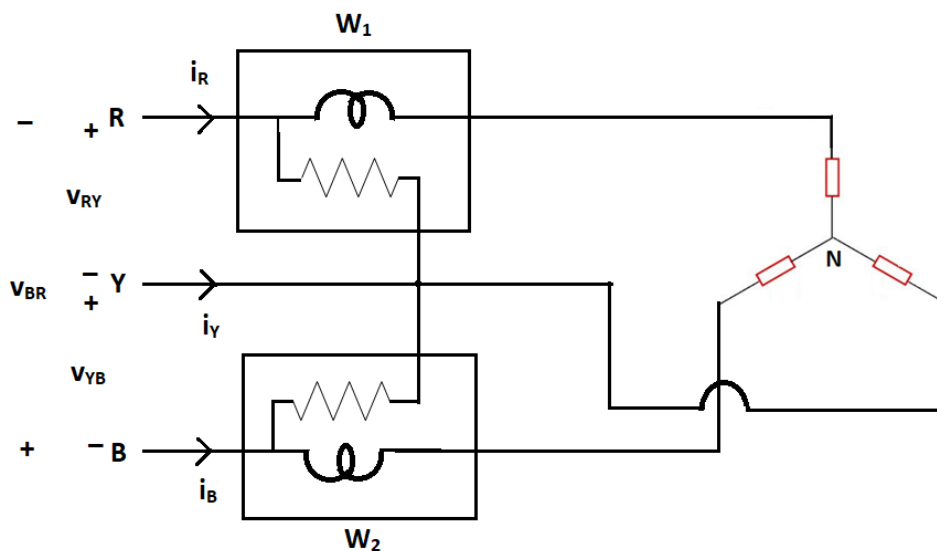

**Fig: Two Wattmeter Method circuit diagram**

Two wattmeters are sufficient to measure three phase active power irrespective of whether the load is star connected or delta connected and irrespective of whether the load is balanced or unbalanced.

First Wattmeter reading,  $W_1 = V_{RY} \cdot I_R \cdot \cos(\angle(V_{RY}, I_R))$


Second Wattmeter reading,  $W_2 = V_{BY} \cdot I_B \cdot \cos(\angle(V_{BY}, I_B))$

To obtain the angles, let us draw the phasor diagram.

Consider inductive load. Then, phase current lags phase voltage.

$$\overline{V_{RY}} = \overline{V_{RN}} - \overline{V_{YN}}$$
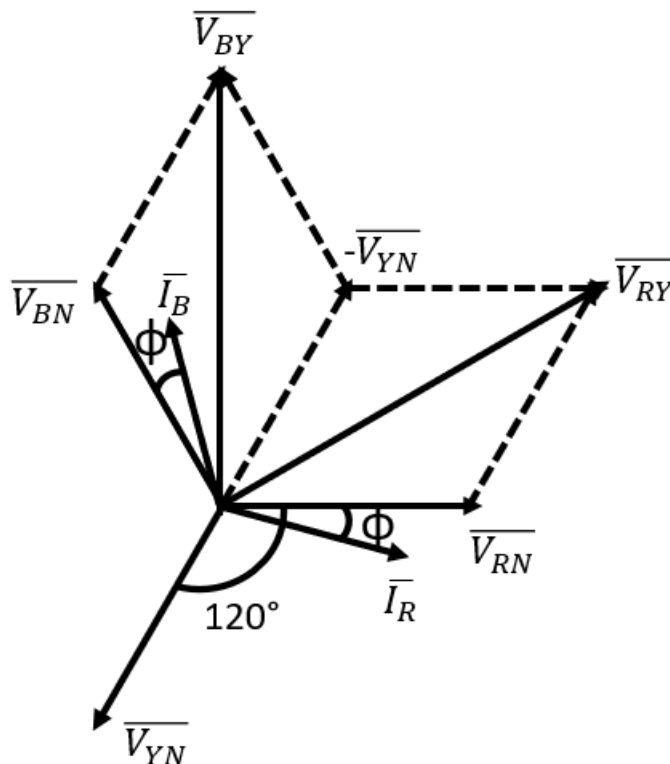
$$\overline{V_{BY}} = \overline{V_{BN}} - \overline{V_{YN}}$$



Therefore,  $W_1 = V_{RY} \cdot I_R \cdot \cos(30 + \phi)$

$W_2 = V_{BY} \cdot I_B \cdot \cos(30 - \phi)$



Hence,  $W_1 = V_L * I_L * \cos(30+\phi)$  &  $W_2 = V_L * I_L * \cos(30-\phi)$

Therefore,  $W_1 + W_2 = \sqrt{3} * V_L * I_L * \cos\phi = P_{3\text{-phase}}$  --- (1)

Similarly,  $\sqrt{3} * (W_2 - W_1) = \sqrt{3} * V_L * I_L * \sin\phi = Q_{3\text{-phase}}$  --- (2)

Therefore,  $\frac{(2)}{(1)}$  gives,

$$\frac{Q_{3\text{-phase}}}{P_{3\text{-phase}}} = \frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2} = \tan\phi$$

Hence, power factor of the system is,

$$\cos\phi = \cos\left(\tan^{-1}\left(\frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2}\right)\right)$$

## Variation in Wattmeter readings with power factor of the load

### Variation in wattmeter readings – Inductive load

For inductive loads,  $W_1 = V_L \cdot I_L \cdot \cos(30+\phi)$  &  $W_2 = V_L \cdot I_L \cdot \cos(30-\phi)$

As phase angle  $\phi$  increases, load power factor decreases.

With an increase in the phase angle  $\phi$ ,  $W_1 = V_L \cdot I_L \cdot \cos(30+\phi)$  decreases &

$W_2 = V_L \cdot I_L \cdot \cos(30-\phi)$  increases.

Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30+\phi)$	$W_2 = V_L I_L \cos(30-\phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3}V_L I_L}{2}$	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lag	$\frac{V_L I_L}{2}$	$V_L I_L$	$W_1 = \frac{W_2}{2}$
$60^\circ$	0.5 Lag	0	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = 0;$ $W_2 = P_{3\text{-phase}}$
$>60^\circ$	$< 0.5$ Lag	Negative	Positive	$W_1 = \text{-ve};$ $W_2 = \text{+ve}$


### Important observations:

- When phase angle is  $<60^\circ$  (or) power factor of the load is  $> 0.5$  Lag, both the wattmeters read positive readings.
- When phase angle =  $60^\circ$  (or) power factor of the load is = 0.5 Lag, one of the wattmeters reads zero and the other reads the total three phase active power.
- When phase angle is  $>60^\circ$  (or) power factor of the load is  $< 0.5$  Lag, one of the wattmeters reads negative i.e., its pointer moves behind zero. To

record its reading, either reverse its CC connections or PC connections (not both) & record this value with a negative sign.

### Variation in wattmeter readings – Capacitive load

Now, consider capacitive Loads

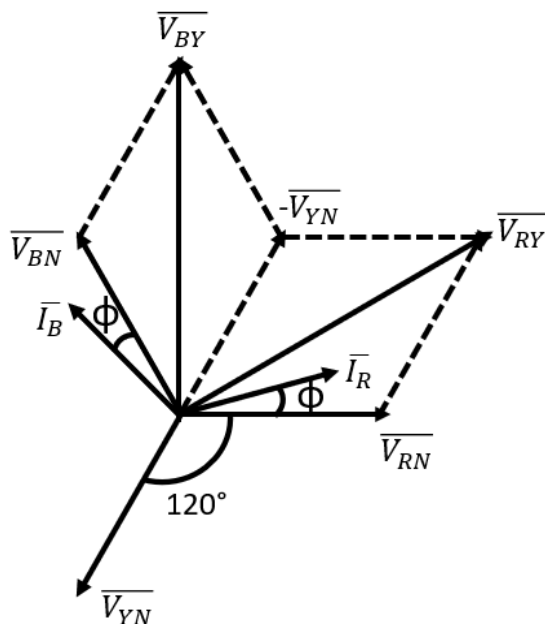

For this case,  $W_1 = V_{RY} \cdot I_R \cdot \cos(30 - \phi)$  &  $W_2 = V_{BY} \cdot I_B \cdot \cos(30 + \phi)$

Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30 - \phi)$	$W_2 = V_L I_L \cos(30 + \phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3} V_L I_L}{2}$	$\frac{\sqrt{3} V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lead	$V_L I_L$	$\frac{V_L I_L}{2}$	$W_2 = \frac{W_1}{2}$
$60^\circ$	0.5 Lead	$\frac{\sqrt{3} V_L I_L}{2}$	0	$W_1 = P_{3\text{-phase}};$ $W_2 = 0$
$>60^\circ$	$< 0.5$ Lead	Positive	Negative	$W_1 = +ve;$ $W_2 = -ve$

Thus, the readings become just the opposite to that of inductive load case.

### Numerical Example 1

#### Question:

In a two wattmeter method of measuring three phase power, it is observed that the wattmeter readings are in the ratio of 3:1. Determine the power factor of the Load.

#### Solution:

##### Given Data:

$$W_1 : W_2 = 3:1$$

$$\text{Power factor} = \cos\phi = \cos\left(\tan^{-1}\left(\sqrt{3} \cdot \frac{(W_1 - W_2)}{(W_1 + W_2)}\right)\right)$$

$$\text{Therefore, Power factor} = 0.756$$

### Numerical Example 2

#### Question:

Two wattmeters are connected to measure input to a balanced three phase circuit indicate 2000W and 500W respectively. Find the power factor when

- i) Both readings are positive
- ii) Latter reading is obtained after reversing its CC

#### Solution:

$$\text{Case 1: } W_1 = 2000\text{W}; W_2 = 500\text{W}$$

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\sqrt{3} \cdot \frac{(W_1 - W_2)}{(W_1 + W_2)}\right)\right) = 0.693$$

$$\text{Case 2: } W_1 = 2000\text{W}; W_2 = -500\text{W}$$

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\sqrt{3} \cdot \frac{(W_1 - W_2)}{(W_1 + W_2)}\right)\right) = 0.327$$

## Numerical Examples on Two Wattmeter Method

### Numerical Example 1

#### Question:

Three coils each having a resistance of  $20\Omega$  and a reactance of  $15\Omega$  are connected in star across a three phase 400V, 50Hz supply. Calculate the readings of the two wattmeters connected to measure the power input.

If the coils are now connected in delta across the same supply, calculate the new wattmeter readings.

#### Solution:

##### Case 1: Balanced Star connected Load

##### Given Data:

Line voltage,  $V_L = 400V$ ,  $f = 50Hz$

Resistance per phase,  $R = 20\Omega$

Reactance per phase,  $X_L = 15\Omega$

##### Calculations:

Impedance per phase,  $Z = (20+j15)\Omega$

Therefore,  $|Z| = 25\Omega$  & Phase Angle,  $\phi = 36.87^\circ$

Phase voltage,  $V_{ph} = \frac{V_L}{\sqrt{3}} = 230.94V$

Phase current,  $I_{ph} = \frac{V_{ph}}{|Z|} = 9.24A = I_L$  (since star system)

Therefore,  $W_1 = V_L I_L \cos(30+\phi) = 1.451KW$

Similarly,  $W_2 = V_L I_L \cos(30-\phi) = 3.67KW$

##### Case 2: Same Load reconnected as Delta Load

Since same supply,  $V_L$  remains same and since same load,  $Z$  remains same

Phase voltage,  $V_{ph} = V_L = 400V$

$$\text{Phase current, } I_{ph} = \frac{V_{ph}}{|Z|} = 16A$$

$$\text{Line current, } I_L = \sqrt{3} * I_{ph} = 27.71A$$

$$\text{Therefore, } W_1 = V_L I_L \cos(30+\phi) = 4.354KW$$

$$\text{Similarly, } W_2 = V_L I_L \cos(30-\phi) = 11KW$$

### Numerical Example 2

#### Question:

Two wattmeters are connected to measure power in a three phase circuit. The reading of one of the wattmeters is 5KW when the load power factor is unity. If the power factor of the load is changed to 0.707 lag without changing the total input power, calculate the new readings of the wattmeters.

#### Solution:

##### Case 1: Load Power factor is unity

##### Given Data:

$$W_1 = 5KW$$

##### Calculations:

Since, power factor is unity,  $W_1 = W_2$

$$\text{Therefore, } P_{3\text{-phase}} = W_1 + W_2 = 10KW$$

##### Case 2: Load Power factor is changed to 0.707 Lag with total input power unchanged.

$$\text{Since total input power is same, } P_{3\text{-phase}} = W_1 + W_2 = 10KW \text{ ---- (1)}$$

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\sqrt{3} * \frac{(W_2 - W_1)}{(W_1 + W_2)}\right)\right) = 0.707 \text{ ---- (2)}$$

$$\text{Solving (1) \& (2), } W_1 = 2.12KW \text{ ; } W_2 = 7.88KW$$

**Numerical Example 3****Question:**

Two wattmeters connected to measure three phase power for star connected load read 3KW and 1KW respectively. The line current is 10A. Calculate

- a) Line and Phase Voltage
- b) Resistance and reactance per phase

**Solution:****Given Data: Star connected Load**

$$W_1 = 3\text{KW} \text{ \& } W_2 = 1\text{KW}$$

$$\text{Line current, } I_L = 10\text{A}$$

**Calculations:**

$$\text{Power factor} = \cos\left(\tan^{-1}\left(\sqrt{3} \cdot \frac{(W_1 - W_2)}{(W_1 + W_2)}\right)\right) = 0.756$$

$$P_{3\text{-phase}} = W_1 + W_2 = 4\text{KW} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos\phi$$

$$\text{Therefore, Line voltage, } V_L = 305.48\text{V}$$

$$\text{Phase voltage, } V_{ph} = \frac{V_L}{\sqrt{3}} = 176.37\text{V}$$

$$\text{Impedance per phase, } Z = \frac{V_{ph}}{I_{ph}} = 17.64\Omega$$

$$\text{Resistance per phase, } R = Z \cdot \cos\phi = 13.33\Omega$$

$$\text{Reactance per phase, } X = \sqrt{Z^2 - R^2} = 11.55\Omega$$

## Advantages of Three Phase Systems over Single Phase Systems

1. For certain amount of power to be transmitted over certain distance, a three phase system requires less conductor material compared to single phase system.

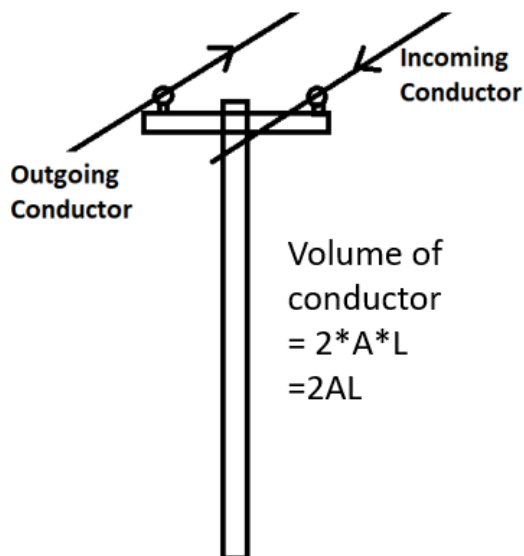


Fig: Single Phase Transmission Line

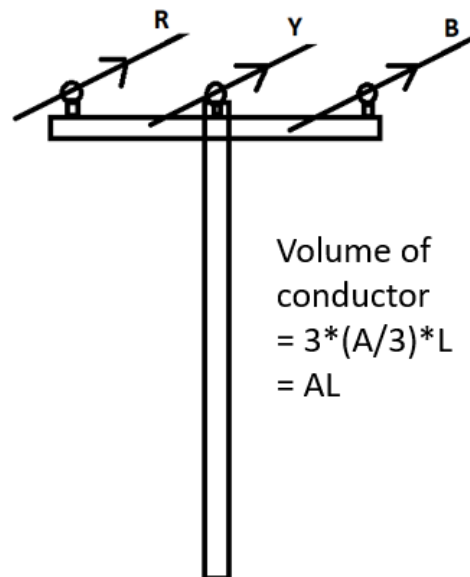


Fig: Three Phase Transmission Line

2. For the same frame size, a three phase machine can handle higher amount of power compared to its single phase counterpart.
3. Single Phase Power is pulsating in nature, whereas three phase power flowing into a three phase motor is almost constant at every instant. Hence, three phase motors run smoother and less noisy & hence, have better lifespan than a single phase motor.
4. Three Phase Induction Motors are self-starting whereas single phase induction motors are not self-starting in nature which makes three phase induction motors widely popular in industrial drives.

## Numerical Example on Wattmeter Method

### Question:

A 3-phase Y-connected, balanced load with a lagging power factor is supplied at 400 V (between the lines). A wattmeter when connected with its current coil in the R-line and voltage coil between R and Y lines gives a reading of



6kW. When the same terminals of the voltage coil are switched over to Y- and B-lines, the current coil connections remaining the same, the reading of the wattmeter remains unchanged. Calculate the line current and power factor of the load. Phase sequence is RYB.


**Solution:**

**Case 1: CC in R-line and PC between R & Y lines**

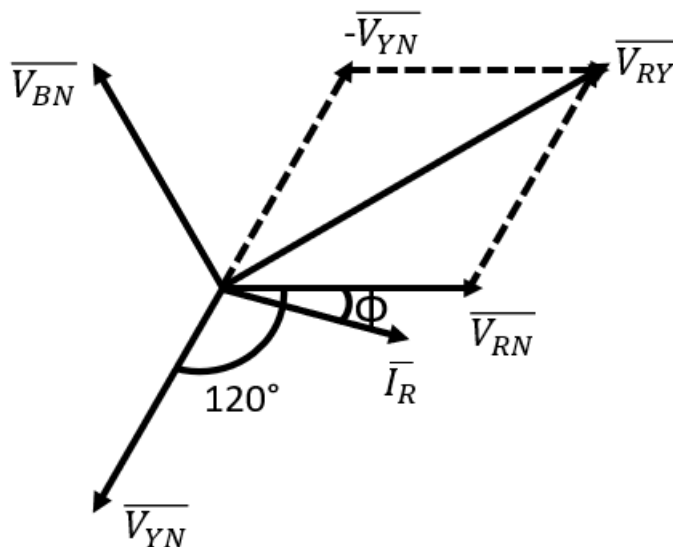**Wattmeter reading,**

$$W_1 = V_{RY} \cdot I_R \cdot \cos(\angle(V_{RY}, I_R))$$

$$\overline{V_{RY}} = \overline{V_{RN}} - \overline{V_{YN}}$$




Therefore,  $W_1 = V_L \cdot I_L \cdot \cos(30^\circ + \phi) = 6000\text{W}$  (given)

**Case 2: CC in R-line and PC between Y & B lines**

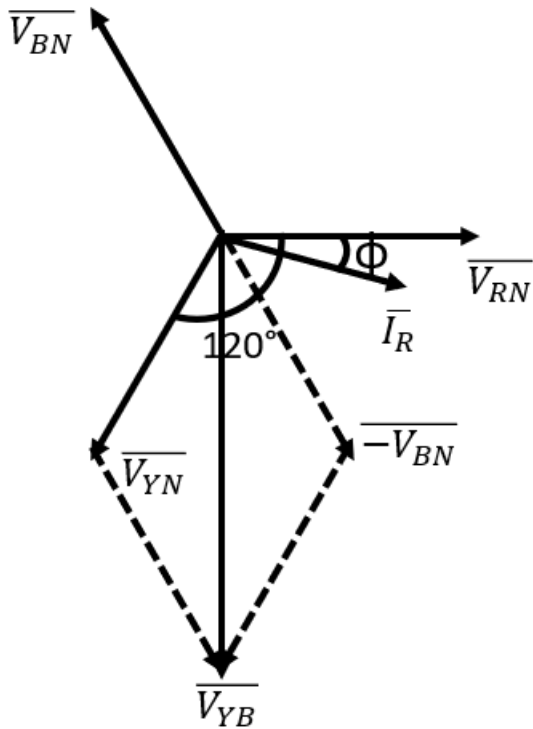**Wattmeter reading,**

$$W_2 = V_{YB} \cdot I_R \cdot \cos(\angle(V_{YB}, I_R))$$

$$\overline{V_{YB}} = \overline{V_{YN}} - \overline{V_{BN}}$$



Therefore,  $W_2 = V_L \cdot I_L \cdot \cos(90 - \phi) = 6000W$  (given)

**Since it is given that wattmeter reading is same in both the cases,**

$$W_1 = W_2$$

$$\text{i.e., } V_L \cdot I_L \cdot \cos(30 + \phi) = V_L \cdot I_L \cdot \cos(90 - \phi)$$

$$\text{Therefore, } \cos(30 + \phi) = \sin \phi$$

$$\text{Hence, } \phi = 30^\circ$$

$$\text{Therefore, Power factor} = \cos \phi = 0.866 \text{ Lag}$$

To find Line current  $I_L$ , substitute  $V_L$  &  $\phi$  values either in  $W_1$  equation or  $W_2$  equation above.

$$\text{Therefore, } W_1 = V_L \cdot I_L \cdot \cos(30 + \phi) = 6000W$$

$$\text{Hence, Line current, } I_L = 30A$$

## Calculation of Energy Consumption

### Step 1

- Calculate Watts per day consumption.

### Step 2

- Convert to KilloWatts per day consumption.

### Step 3

- Calculate energy uses over a month period.

### Step 4

- Figure out the cost considering the rate.

### Example:

Sl. No.	Item	Wattage	No. of Hours Working per Day	KWh per day
1	Lights	280	5	1.4
2	Fans	60 x 2	10	1.2
3	Geyser	2000	1/2	1
4	Mixer- grinder	750	1/3	0.25
5	Refrigerator	100	15	1.5
6	Freezer	300	4	1.2
7	Washing Machine	325	1	0.325
8	Iron	1000	1/2	0.5
9	Motor – 1 hp	746	1	0.746
10	Television	100	10	1
11	Laptop Charging	120	2	0.24
12	Mobile Charger	15	2	0.03
13	Internet Modem	8	24	0.192
14	Microwave	900	1	0.9
15	Vacuum Cleaner	350	1	0.35

Total Energy Consumption per day = 10.833 KWh

Total Energy Consumption in a month = 10.833 x 30 = 325 KWh

## Calculation of Energy Consumption

### Step 1

- Calculate Watts per day consumption.

### Step 2

- Convert to KilloWatts per day consumption.

### Step 3

- Calculate energy uses over a month period.

### Step 4

- Figure out the cost considering the rate.

## Example:

Sl. No.	Item	Wattage	No. of Hours Working per Day	KWh per day
1	Lights	280	5	1.4
2	Fans	60 x 2	10	1.2
3	Geyser	2000	1/2	1
4	Mixer- grinder	750	1/3	0.25
5	Refrigerator	100	15	1.5
6	Freezer	300	4	1.2
7	Washing Machine	325	1	0.325
8	Iron	1000	1/2	0.5
9	Motor – 1 hp	746	1	0.746
10	Television	100	10	1
11	Laptop Charging	120	2	0.24
12	Mobile Charger	15	2	0.03
13	Internet Modem	8	24	0.192
14	Microwave	900	1	0.9
15	Vacuum Cleaner	350	1	0.35

Total Energy Consumption per day = 10.833 KWh

Total Energy Consumption in a month = 10.833 x 30 = 325 KWh

### Tariff Calculation:

Effective from 1 <sup>st</sup> April'2018	Sanctioned Load Fixed Charge (FC)	Tariff
Domestic - Applicable to Areas under Bruhat Bangalore Mahangara Palike (BBMP), Municipal Corporations and all Urban Local Bodies	FC For 1st KW	Rs.50
	FC For addl. KW	Rs.60
	<b>Consumption Energy</b>	<b>Charges (EC)</b>
	0 to 30 KWH	350 Ps
	31 to 100 KWH	495 Ps
	101 to 200 KWH	650 Ps
	201 to 300 KWH	755 Ps
	301 to 400 KWH	760 Ps
	Above 400 KWH	765 Ps
	<b>Fuel Adjustment Charges (FAC)</b>	
	Unit consumed KWH	14 Ps

Fixed Charge			
Unit	Rate (Rs)	Amount (Rs)	Total Amount (Rs)
1	50	50 x 1	50
2	60	60 x 2	120
Energy Charges			
Unit	Rate (Rs)	Amount (Rs)	Total Amount (Rs)
30	3.5	30 x 3.5	105
100	4.95	70 x 4.95	346.5
200	6.5	100 x 6.5	650
300	7.55	100 x 7.55	755
325	7.6	25 x 7.6	190
Fuel Adjustment Charge			
Unit	Rate (Rs)	Amount (Rs)	Total Amount (Rs)

325	0.14	$325 \times 0.14$	45.5
-----	------	-------------------	------

**Total amount: Rs.2262**

**Tax amount (7.3%) =  $2262 \times 0.073 = \text{Rs.}165.126$**

**Total billing amount = Rs. 2427.126**