


OPERATIONAL AMPLIFIER

Introduction:

UDOSHI BASAVARAJ

- *) It is a high gain, directly coupled, differential amplifier.
- *) It can amplify signal frequency ranging between 0 & 1 MHz i.e. OP-AMP can amplify both AC & DC signals.
- *) Response of OP-AMP is controlled by passive component like resistor.
- *) OP-AMP is available in IC package.
- *) OP-AMP has no effect of temperature variations.
- *) It can perform mathematical operations such as, Addition, Subtraction, Multiplication, Differentiation, Integration & Comparison of Signals hence it is called as Operational Amplifier [OP-AMP].


Symbol of OP-AMP:

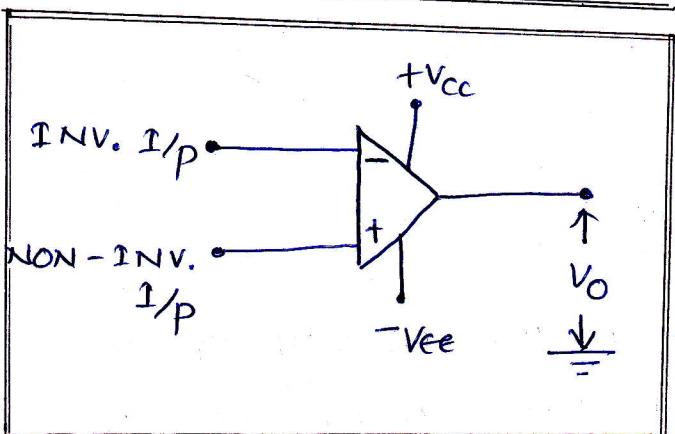

✓ Inverting I/p : If the signal is applied to inverting I/p terminal, output signal will be inverted part of applied i/p signal. i.e. I/p & O/p signals are out of phase by 180° .

✓ Non-Inverting I/p : If the signal is applied to non-inv. I/p, output & i/p signal are inphase. i.e. phase difference is zero.

* PIN-OUT DIAGRAM OF IC 741

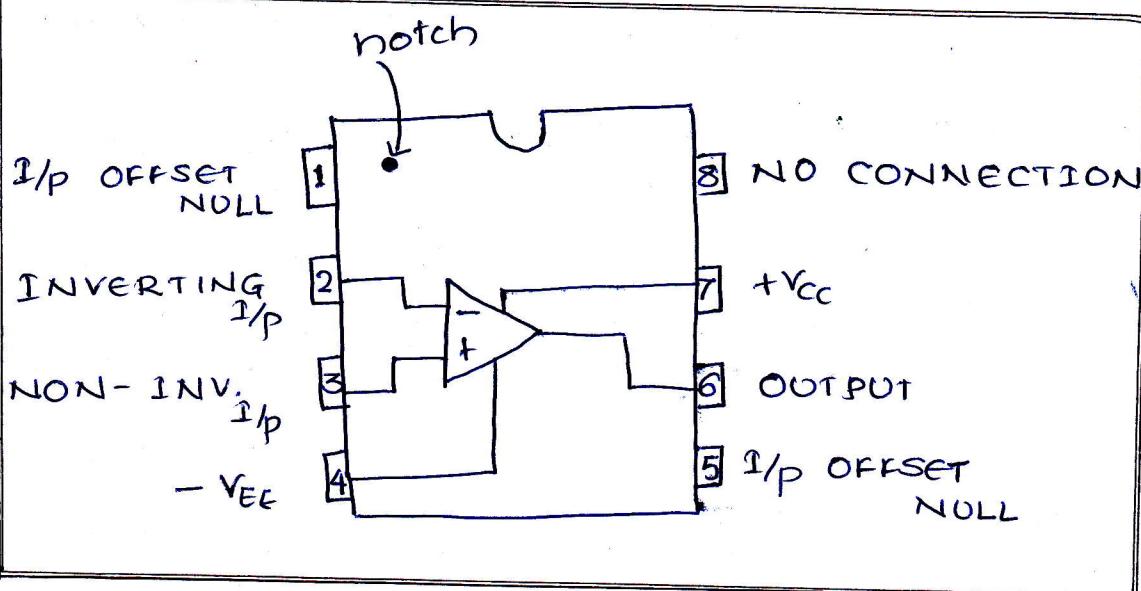


* > CHARACTERISTICS OP-AMP

i) Input OFFSET Voltage: It is the amount of voltage must be applied across input terminals of an OP-AMP to nullify whose output.

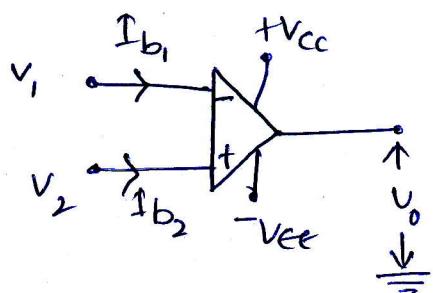ii) Input offset Current ; It is the algebraic difference between currents entering the input terminals of an OP-AMP.

i.e Input Offset Current = $[I_{b_1} - I_{b_2}]$



iii) Output Offset Voltage; It is the ability of an OP-AMP to produce o/p signal even though i/p's are maintained with zero potential.

* Slew Rate (S): Rate of change of Maximum Output voltage with time is called slew rate.

i.e $s = \frac{d(V_{max})}{dt}$ Unit of Slew rate is $V/\mu s$

* Common Mode Rejection Ratio [CMRR]: It is ratio of differential gain $[A_d]$ to the Common mode gain $[A_c]$

$$\text{i.e } CMRR = \frac{A_d}{A_c}$$

* Power Supply Rejection Ratio [PSRR]

Supply Voltage Rejection Ratio [SVRR] or

It is the ratio of change in input offset voltage to the change in supply voltage.

Ideally PSRR or SVRR is zero

** Unit of it is $\mu V/V$


Ideal characteristics of an OP-AMP

- i) Input Impedance is infinity i.e $Z_{in} = \infty$
- ii) Open loop Voltage gain is infinity i.e $A_v = \infty$
- iii) Bandwidth is infinity i.e $BW = \infty$
- iv) Slew rate is infinity i.e $S = \infty$
- v) CMRR is infinity i.e $CMRR = \infty$
- vi) Output Impedance is zero i.e $Z_{out} = 0$
- vii) Difference input Voltage to an op-Amp is zero, i.e $V_1 - V_2 = 0$
- viii) No effect of temperature

*> Concept of Virtual Ground:

Defn: A node which has zero potential w.r.t. ground but not connected to ground is called as Virtual Ground.

Concept:

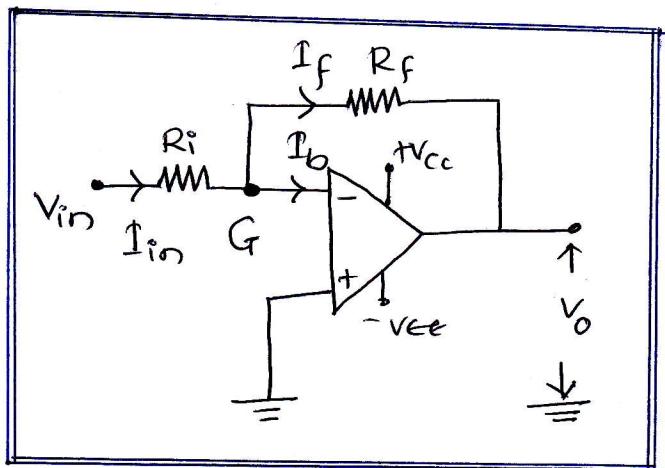

Let • V_1 is Voltage drop across inverting terminal.

$$\text{i.e. } V_1 = V_G$$

• V_2 is Voltage drop across non-inverting terminal

✓ but non-inverting terminal

is grounded hence $V_2 = 0$

(*) According to ideal characteristics of OP-AMP is

$$V_1 \approx V_2 = 0 \quad \text{or} \quad V_1 - V_2 = 0 \Rightarrow V_1 = V_2 \quad \text{since } V_2 = 0$$

$\therefore V_1 = 0$ i.e. $V_G = 0$ potential across node G is zero $\rightarrow (i)$

(*) ^{11th} According to ideal characteristics of OP-AMP.

$$Z_{in} = \infty \text{ hence } I_b = 0$$

\Rightarrow Current accepting or sinking capability of node G zero $\rightarrow (ii)$

. . . from case (i) & (ii) Node G is called virtual ground.

(*) Real Ground or Ground i.e. earth: whose current-sinking capability is infinity but potential is zero.

#) OP-AMP's mode of OPERATION as an AMPLIFIER

1) INVERTING Amplifier

2) NON-INVERTING Amplifier

#) APPLICATIONS OF OP-AMP

i) OP-AMP Adder [3 i/p signals]

ii) OP-AMP as Differentiator

iii) OP-AMP as Integrator


iv) OP-AMP as Buffer Amplifier

v) OP-AMP as Subtractor

1) OP-AMP as INVERTING AMPLIFIER:

Defn: An amplifier in which output signal is inverted part of the input signal is called as inverting amplifier i.e. input signal & output signal are out of phase by 180° .

Circuit Diagrams:

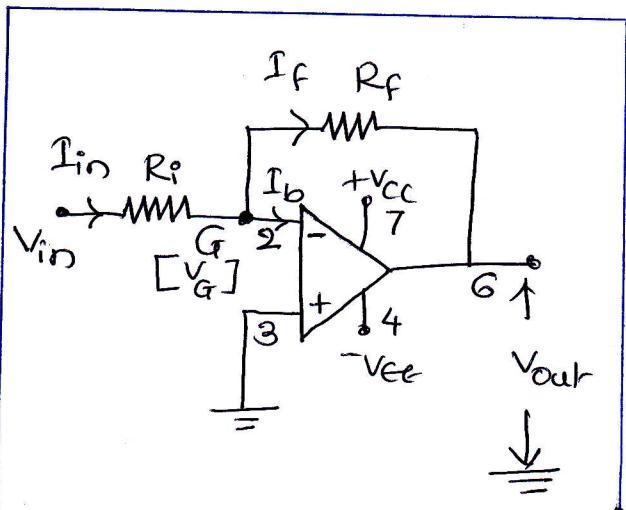

Construction:

→ OP-AMP is operated in inverting mode i.e. non-inverting terminal is grounded.

→ Where R_i & R_f are input & feedback resistors respectively

→ OP-AMP is energized by applying DC Sources $-V_{ee}$ & $+V_{cc}$

→ O/p is measured across Pin # 6 with respect to ground.

Derivation:

✓ Apply KCL to node G

$$I_{in} = I_b + I_f \rightarrow (1)$$

$$\text{but } I_b = 0 \therefore I_{in} = 0$$

$$\therefore I_{in} = I_f \rightarrow (2)$$

✓ Express Currents as ratio of voltage drop to opposition.

$$(2) \Rightarrow \frac{V_{in} - V_G}{R_{in}} = \frac{V_G - V_o}{R_f}$$

where $V_G = 0$ due to the concept of virtual ground

$$\Rightarrow \frac{V_{in}}{R_{in}} = -\frac{V_o}{R_f} \quad \text{or} \quad V_o = \left[-\frac{R_f}{R_{in}} \right] V_{in} \rightarrow (3)$$

[where '-' sign indicates inverting mode of operation]

eqn (3) is called o/p voltage expression for inverting amplifier.

IIIrd

Gain of the inverting mode of operation is,

$$(3) \Rightarrow \frac{V_o}{V_{in}} = A_v = \left[-\frac{R_f}{R_{in}} \right]$$

=====


2) OP-AMP as Summing Amplifier or Adder:

Defn: An amplifier in which output is sum of all the applied input signals.

$$\text{i.e } V_o = -[V_1 + V_2 + V_3]$$

Circuit Diagrams:

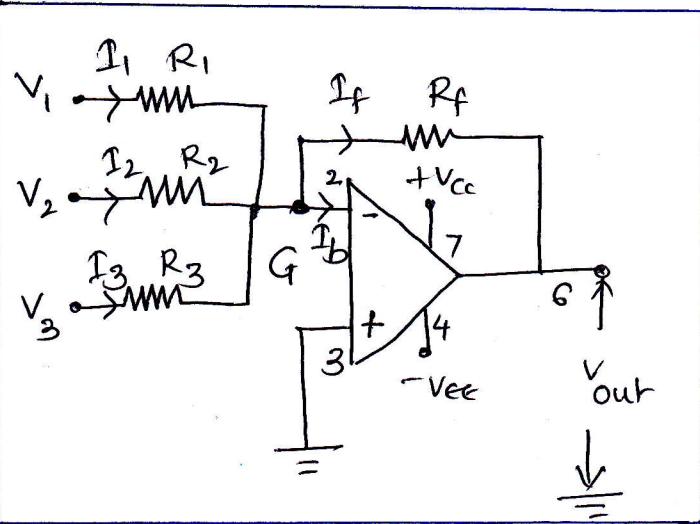where V_1, V_2 & V_3 are i/p signals,
 '-ve' indicates OP-AMP is operated in inverting mode.



Derivation:

✓ Apply KCL to node "G"

$$\Rightarrow I_1 + I_2 + I_3 = I_b + I_f \rightarrow (1)$$

Since $I_b = 0 \therefore Z_{in} = \infty$

$$\therefore I_1 + I_2 + I_3 = I_f$$

✓ Express currents as ratio of voltage drops to opposition.

$$\text{i.e } \frac{V_1 - V_G}{R_1} + \frac{V_2 - V_G}{R_2} + \frac{V_3 - V_G}{R_3} = \frac{V_G - V_o}{R_f} \rightarrow (2)$$

where $V_G = 0$ due to the concept of virtual ground.

$$(2) \Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f}$$

or
$$V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \rightarrow (3)$$

where eq 2 (3) \Rightarrow O/p Voltage expression for 3 i/p OP-AMP Adder,


$$\text{if } R_f = R_1 = R_2 = R_3 = R$$

$$(3) \Rightarrow V_o = -[V_1 + V_2 + V_3]$$

3) OP-AMP as Differentiator:

Defn: An amplifier in which output is derivative of applied input signal. i.e $V_o \propto \frac{d[V_{in}]}{dt}$

Circuit Diagram:

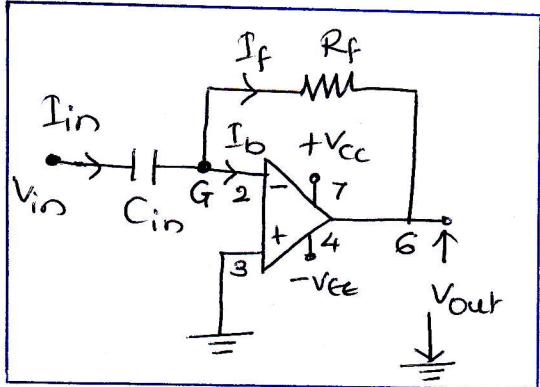

Derivation:

✓ Apply KCL to node "G"

$$I_{in} = I_b + I_f \rightarrow (1)$$

but $I_b = 0 \therefore Z_{in} = \infty$

$$(1) \Rightarrow I_{in} = I_f \rightarrow (2)$$

✓ Express Current as ratio of Voltage drops to opposition.

where $I_{in} \rightarrow$ Current flowing Capacitor, hence it is given

by $I_{in} = I_c = C \frac{d(V_c)}{dt}$

where $C \rightarrow$ capacitance of capacitor

$V_c \rightarrow$ Voltage drop across the capacitor.

hence eq(2) $\Rightarrow C_{in} \frac{d[V_{in} - V_G]}{dt} = \frac{V_G - V_o}{R_f} \rightarrow (3)$

where $V_G = 0$ due to the concept of Virtual Ground

eq(3) $\Rightarrow C_{in} \frac{dV_{in}}{dt} = -\frac{V_o}{R_f} \quad \text{or} \quad V_o = [-C_{in} \cdot R_f] \frac{d(V_{in})}{dt} \quad (4)$

Eq(4) is called as output voltage expression for OP-AMP Differentiator.

✓ where $(C_{in} \cdot R_f)$ is a constant, can be replaced by proportionality,


Hence $V_o \propto \frac{d(V_{in})}{dt}$

4) OP-AMP as Integrator

Defn: An amplifier in which o/p signal is directly proportional to the integral part of the input signal.

i.e $V_o \propto \int V_{in} dt$

Circuit Diagram:

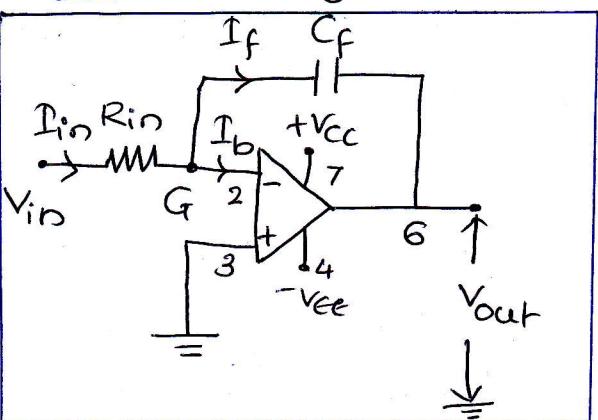

Derivation:

✓ Apply KCL to node "G"

$$I_{in} = I_b + I_f \rightarrow (1)$$

but $I_b = 0 \therefore Z_{in} = \infty$

$$\therefore (1) \Rightarrow I_{in} = I_f \rightarrow (2)$$

where $I_f = \frac{1}{C_f}$ i.e current flowing through capacitor "Cf" due to voltage drops across it

✓ Express currents as ratio of voltage drops to opposition

hence eqn (2) \Rightarrow

$$\frac{V_{in} - V_G}{R_{in}} = C_f \cdot \frac{d[V_G - V_o]}{dt} \rightarrow (3)$$

where $V_G = 0$ due to the concept of virtual ground,

$$(3) \Rightarrow \frac{V_{in}}{R_{in}} = C_f \frac{d[-V_o]}{dt} \quad \text{or} \quad -dV_o = \left[\frac{1}{C_f R_{in}} \right] V_{in} dt$$

$$\text{or} \quad dV_o = \left[-\frac{1}{C_f R_{in}} \right] V_{in} dt \rightarrow (4)$$

Integrate eqn (4) on both hand sides

$$\int dV_o = \left[-\frac{1}{C_f R_{in}} \right] \int V_{in} dt$$


$$\text{or} \quad V_o = \left[-\frac{1}{C_f R_{in}} \right] \int V_{in} dt \rightarrow (5) \Rightarrow V_o \propto \int V_{in} dt$$

eqn (5) is called o/p voltage expression for "Op-amp Integrator."

5> OP-AMP as NON-INVERTING AMPLIFIER:

Defn: An amplifier in which o/p signal is in phase with input signal.

Circuit Diagram:

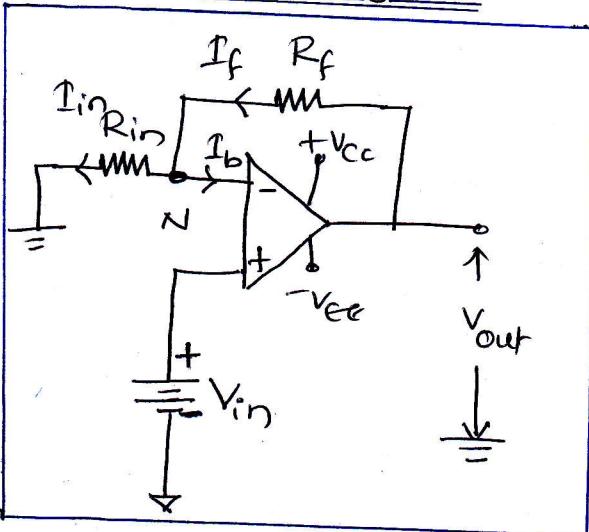

where $V_{in} \rightarrow$ is voltage drop across non-inverting terminal

$$\text{i.e. } V_2 = V_{in}$$

$$V_1 = V_N$$

$V_1 \rightarrow$ voltage drop across inverting terminal i.e. $V_1 = V_N$

According to ideal characteristics of an OP-AMP is,

$$V_1 \cap V_2 = 0 \quad \text{or} \quad V_1 - V_2 = 0$$

$$\text{but } V_2 = V_{in}$$

$$V_1 = V_2 = V_{in}$$

∴ Voltage drop across inverting terminal is also " V_{in} "

✓ Apply KCL to node "N"

$$I_{in} + I_b = I_f \quad \text{but } I_b = 0 \quad \therefore I_{in} = 0$$

$\Rightarrow I_{in} = I_f$ Express Currents as ratio of voltage drops to opposition,

Hence $\frac{0 - V_{in}}{R_{in}} = \frac{V_{in} - V_o}{R_f} \Rightarrow -\frac{V_{in}}{R_{in}} = \frac{V_{in}}{R_f} - \frac{V_o}{R_f}$

$$\therefore \frac{V_o}{R_f} = \frac{V_{in}}{R_f} + \frac{V_{in}}{R_{in}}$$

$$\frac{V_o}{R_f} = V_{in} \left[\frac{1}{R_f} + \frac{1}{R_{in}} \right]$$

or $V_o = V_{in} \left[\frac{R_f}{R_f} + \frac{R_f}{R_{in}} \right]$

$\therefore V_o = V_{in} \left[1 + \frac{R_f}{R_i} \right] \rightarrow (1)$


eq(1) is called o/p voltage expression for OP-AMP inverting amplifier.

or $A_v = \frac{V_o}{V_{in}} = \left[1 + \frac{R_f}{R_i} \right] \Rightarrow$ Voltage gain Expression.

6> OP-AMP as Buffer Amplifier:

Defn: An amplifier whose output is equals to applied input both in magnitude & phase.

Circuit Diagram:

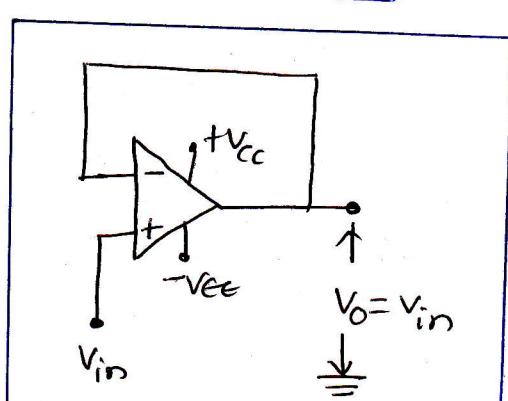

Circuit construction:

→ OP-AMP Buffer Amplifier is operated in non-inverting mode.

✓ Gain of non-inverting amplifier is given by,

$$A = \left[1 + \frac{R_f}{R_i} \right]$$

According circuit Diagram $R_f = 0$

$$\therefore A = \frac{V_o}{V_{in}} = 1 \quad \text{or} \quad V_o = V_{in}$$

Hence Buffer amplifier is called as "unity gain Amplifier."

F) OP-AMP SUBTRACTOR:


Defn: An amplifier in which output signal is difference of applied input signals.

i.e $V_{out} = V_2 - V_1$

where $V_2 \rightarrow$ Voltage applied to non-inverting terminal

$V_1 \rightarrow$ Voltage applied to inverting terminal

Circuit Diagram:

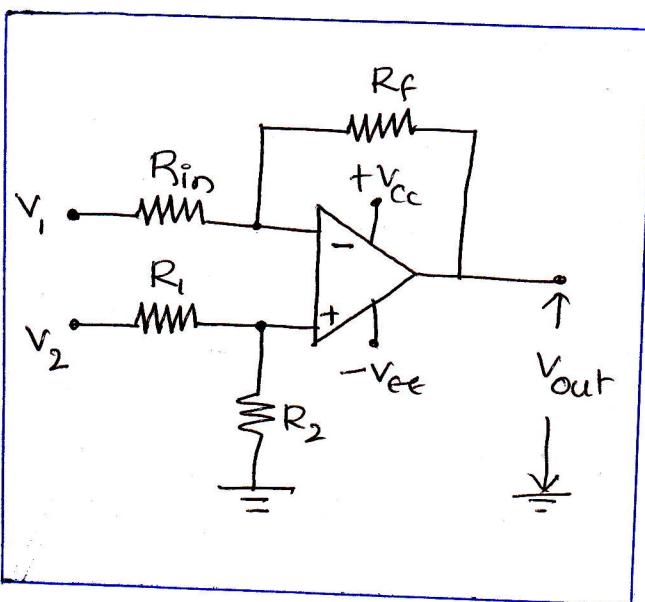

OP-AMP is operated in both inverting mode & non-inverting hence combined effectiveness of inverting mode output & non-inverting mode output generates difference b/w applied input signal.

i.e $\underline{V_{out} = V_{o1} + V_{o2}} \rightarrow (i)$

where $V_{out} \rightarrow$ Output of Subtractor i.e output because of combined effect of input signal V_1 & V_2


$V_{o1} \rightarrow$ Output due to only inverting mode of operation

$V_{o2} \rightarrow$ Output due to only non-inverting mode of operation

Hence study on subtractor circuit is conducted in two cases. One is inverting mode & case two is non-inverting mode. Therefore combined effectiveness of case(i) & case(ii) will be OP-AMP SUBTRACTOR.

Case i) OP-AMP is operated only in inverting mode

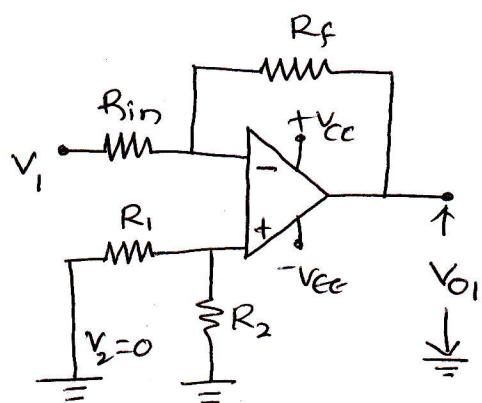i.e non-inverting terminal is grounded $\therefore V_2 = 0$




Output voltage expression for inverting mode of OP-AMP is,

$$V_{01} = \left[-\frac{R_f}{R_{in}} \right] V_1 \rightarrow (2)$$

Case ii) OP-AMP is operated only in non-inverting mode

i.e $V_1 = 0$

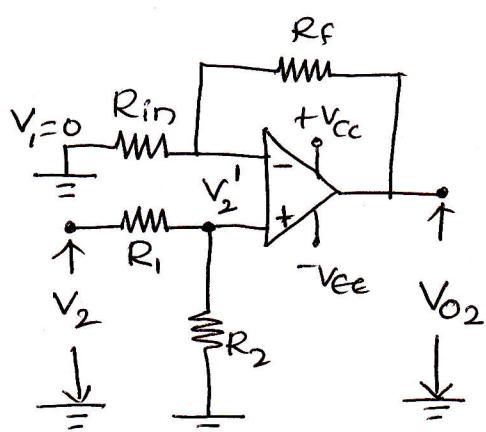

where V_2' is input voltage to non-inverting terminal, To determine V_2' apply voltage divider rule across resistor R_2 [R_1 & R_2 are connected in series]

$$\Rightarrow V_2' = \frac{V_2 R_2}{R_1 + R_2} \rightarrow (3) \quad \begin{bmatrix} \text{VDR is} \\ V_x = \frac{V_T R_x}{R_1 + R_2} \end{bmatrix}$$

Output Voltage expression for non-inv. OP-AMP is,

$$V_{02} = \left[1 + \frac{R_f}{R_i} \right] V_2' \rightarrow (4) \quad \text{Substitute eqn (3) in eqn (4)}$$

$$(4) \Rightarrow V_{02} = \left[1 + \frac{R_f}{R_i} \right] \frac{V_2 R_2}{R_1 + R_2} \rightarrow (5)$$

✓ Substitute eqns (2) & (5) in eqn (1)

eqn (1) \Rightarrow

$$V_o = \left[-\frac{R_f}{R_{in}} \right] V_1 + \left[1 + \frac{R_f}{R_{in}} \right] \frac{V_2 R_2}{R_1 + R_2} \rightarrow (6)$$

eqn (6) indicates output voltage expression for OP-AMP Subtractor

if $R_f = R_{in} = R_1 = R_2 = R$

Then

$$V_o = V_2 - V_1$$

OP-AMP

PROBLEMS

List of Formulae :

*> Output Voltage Expression for INVERTING AMPLIFIER is,

$$V_o = \left[-\frac{R_f}{R_i} \right] V_{in}$$

*> Output Voltage expression for NON-INVERTING AMPLIFIER is,

$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_{in}$$

*> Output voltage expression for 3 i/p's OP-AMP INVERTING

ADDER is, $V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$

if $R_f = R_1 = R_2 = R_3 = R$

Then $V_o = -[V_1 + V_2 + V_3]$

*> Output voltage expression for OP-AMP DIFFERENTIATOR

is, $V_o = \left[-R_f C_f \right] \frac{d(V_{in})}{dt}$

*> Output voltage expression for OP-AMP INTEGRATOR is,

$$V_o = - \left[\frac{1}{R_i C_f} \right] \int V_{in} dt$$

*> Output voltage expression for OP-AMP BUFFER AMP. is

$V_o = V_{in}$ or A_v is unity

*> Calculate the output voltage of a three input summing

amplifier: Given $R_1 = 200\text{ k}\Omega$, $R_2 = 250\text{ k}\Omega$, $R_3 = 500\text{ k}\Omega$ &
 $R_f = 1\text{ M}\Omega$, $V_1 = 2\text{ V}$, $V_2 = 2\text{ V}$, $V_3 = 1\text{ V}$ [6 marks]

Sol: V_{out} for 3 input summing amplifier is,

$$\begin{aligned}V_o &= - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \\&= - \left[\frac{(1 \times 10^6)}{(200 \times 10^3)} (2) + \frac{(1 \times 10^6)}{(250 \times 10^3)} (2) + \frac{(1 \times 10^6)}{(500 \times 10^3)} (1) \right] \\&= - \left[10 + 8 + 2 \right]\end{aligned}$$

$$V_o = -20\text{ V}$$

*> Design an adder circuit using OP-AMP to obtain an output expression $V_o = -(0.1V_1 + 0.5V_2 + 20V_3)$, where V_1, V_2 & V_3 are the inputs. Select $R_f = 10\text{ k}\Omega$ [5 marks]

Sol: V_{out} for 3 i/p adder is,

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \quad \text{Given } R_f = 10\text{ k}\Omega$$

$$\therefore V_o = - \left[\frac{10\text{ k}}{R_1} V_1 + \frac{10\text{ k}}{R_2} V_2 + \frac{10\text{ k}}{R_3} V_3 \right] \rightarrow (1)$$

$$\text{Given } V_o = -[0.1V_1 + 0.5V_2 + 20V_3] \rightarrow (2)$$

Compare eqns (1) & (2),

$$\frac{10\text{ k}}{R_1} V_1 = 0.1 V_1 ; \quad \frac{10\text{ k}}{R_2} V_2 = 0.5 V_2 ; \quad \frac{10\text{ k}}{R_3} V_3 = 20 V_3$$

$$\therefore R_1 = 100\text{ k}\Omega ; \quad R_2 = 20\text{ k}\Omega ; \quad R_3 = 500\text{ }\Omega$$

Draw the circuit

Diagram of 3 i/p

Adder Substitute

R_1, R_2 & R_3 values

*> Design an Inverting adder circuit using an OP-AMP to the given output expression. [8marks]

$V_o = -[3V_1 + 4V_2 + 5V_3]$, given $V_1, V_2 \text{ & } V_3$ are input voltages & $R_f = 100\text{ k}\Omega$

Sol: Output voltage expression for 3 i/p OP-AMP Adder is,

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Given $R_f = 100k$

$$\therefore V_o = - \left[\frac{100k}{R_1} V_1 + \frac{100k}{R_2} V_2 + \frac{100k}{R_3} V_3 \right] \rightarrow (1)$$

$$\text{Given } V_o = -[3V_1 + 4V_2 + 5V_3] \rightarrow (2)$$


Compare eqns (1) & (2)

$$\frac{100k}{R_1} V_1 = 3V_1 ; \frac{100k}{R_2} V_2 = 4V_2 ; \frac{100k}{R_3} V_3 = 5V_3$$

$$\therefore R_1 = 33.33\text{ k}\Omega ; R_2 = 25\text{ k}\Omega ; R_3 = 20\text{ k}\Omega$$

*> Find the output voltage for the circuit shown below.

[6Marks]

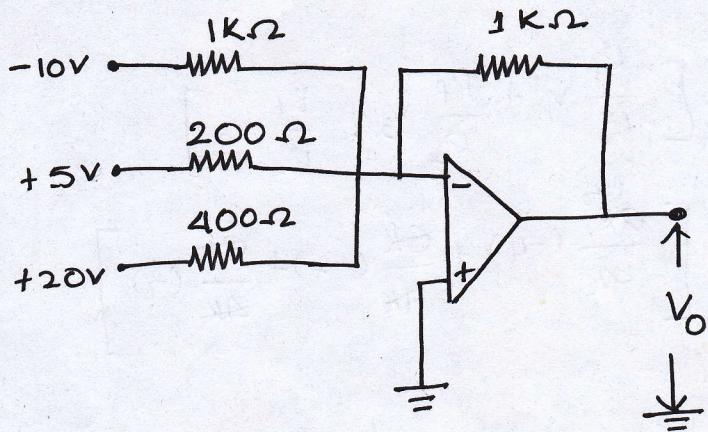

Sol: Vout for 3 i/p OP-AMP Adder is,


$$V_{out} = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$= - \left[\frac{1k}{1k} (-10) + \frac{5}{200} (5) + \frac{2.5}{400} (20) \right]$$

$$= -[-10 + 25 + 50]$$

$$\underline{\underline{V_o = -65V}}$$

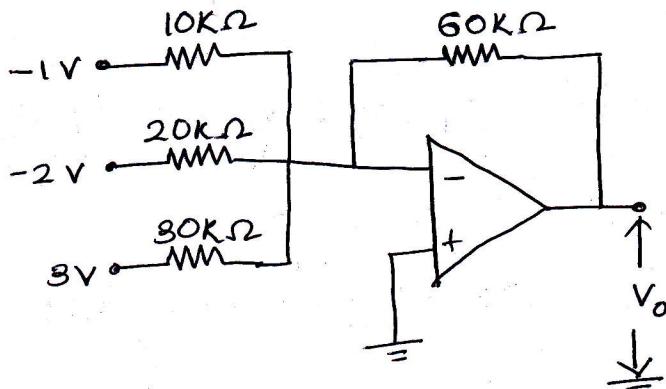*) Calculate the output voltage [V_o] for the Given circuit. [6 Marks]




Sol: V_{out} for 3 i/p Adder is,

$$\begin{aligned} V_o &= - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \\ &= - \left[\frac{60k}{10k} (-1) + \frac{60k}{20k} (-2) + \frac{30k}{30k} (3) \right] \\ &= - [-6 - 6 + 3] \\ \therefore V_o &= -3V \end{aligned}$$

**) Find the output voltage of the 3-input adder circuit shown below

[8 Marks]

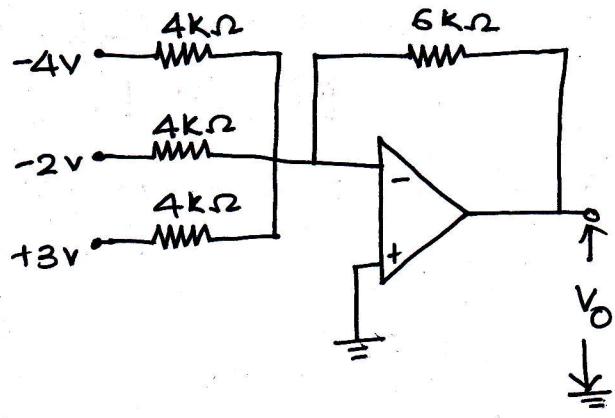

Sol:

V_{out} for 3 i/p Adder is,

$$\begin{aligned} V_o &= - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \\ &= - \left[\frac{1.5}{8k} (-4) + \frac{1.5}{4k} (-2) + \frac{1.5}{4k} (3) \right] \\ &= - [-6 - 3 + 4.5] \end{aligned}$$

$$V_o = -4.5V$$