




PES
UNIVERSITY

ELECTRONIC PRINCIPLES AND DEVICES

Department of Electronics and Communication.

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Voltage Regulator

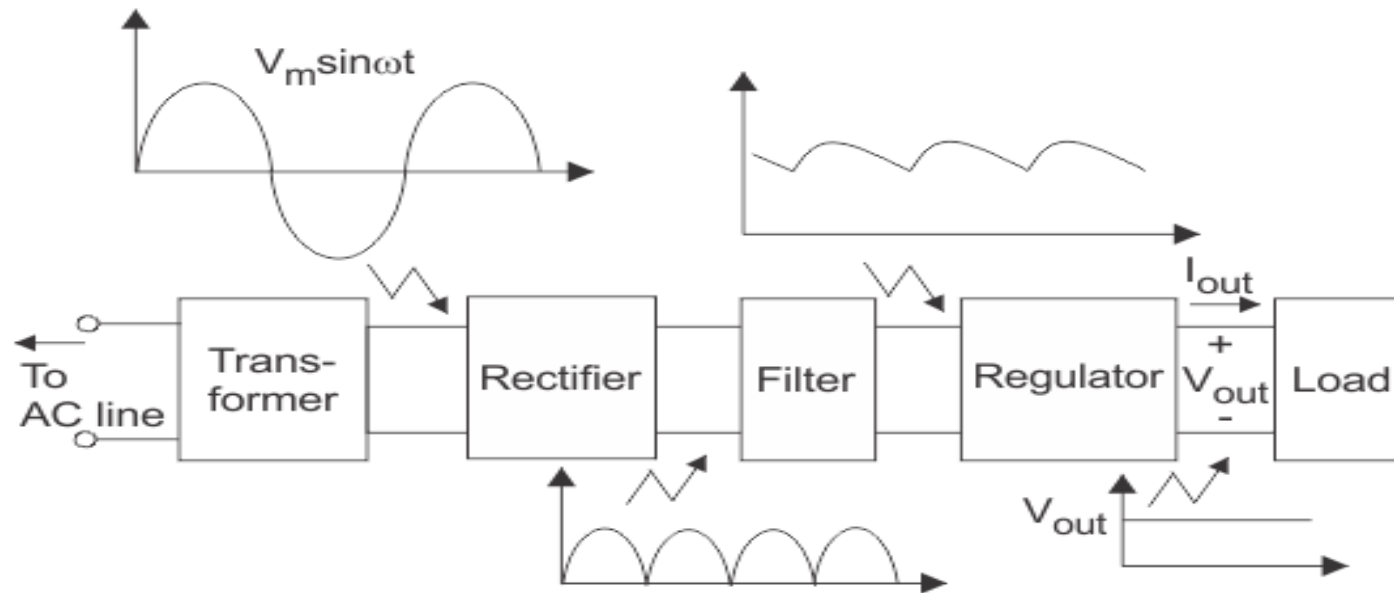


Components of typical linear power supply

A regulator is a combination of elements designed to ensure that the output voltage of a supply remains fairly constant.

- Heavily Doped PN-Junction Device Specially Designed to operate under breakdown region
- Zener Diode under forward Bias condition works like a normal semiconductor diode
- Zener Diode under reverse bias condition acts like Voltage regulator
- Zener diodes are usually heavily doped diodes hence the depletion layer is very narrow. When the reverse voltage across the junction is increased the electric field across the depletion layer becomes high so that electrons are pulled out of covalent bonds resulting in a sudden rise in current which is known as zener breakdown.

Structure of Zener Diode

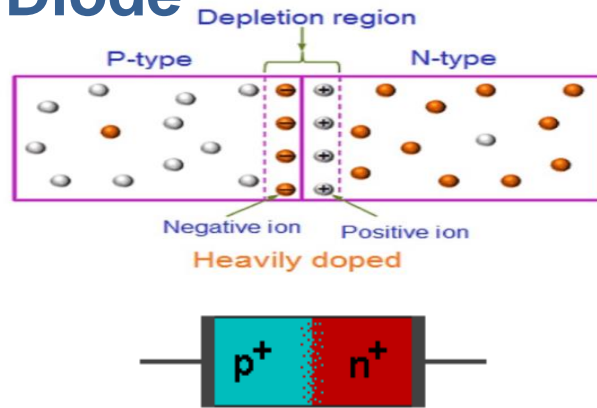

Symbol of Zener Diode

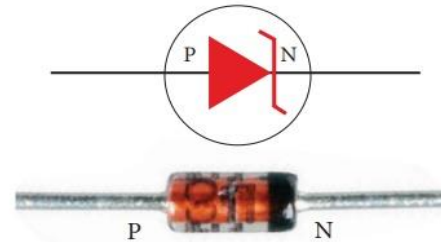


Figure (a) Zener diode and its symbol
(The black colour ring denotes the negative terminal of the Zener diode)

V-I Characteristics of Zener Diode


V-I Characteristics of Zener Diode in Forward Bias Condition

V-I Characteristics of Zener Diode in Reverse Bias Condition

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener Diode Characteristics

V-I Characteristics

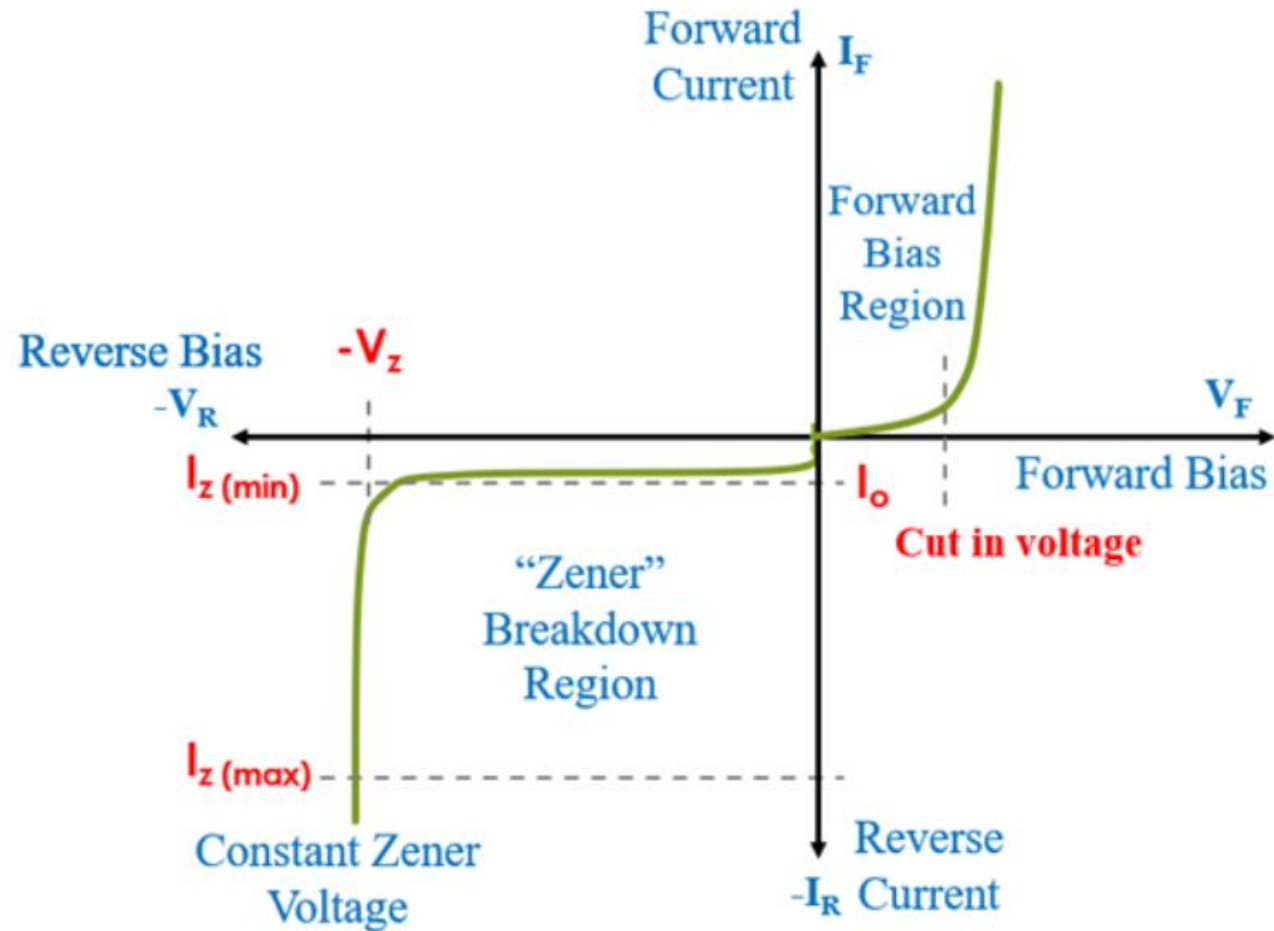



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener Diode as Voltage Regulator

Conditions required to operate Zener Diode as Voltage Regulator

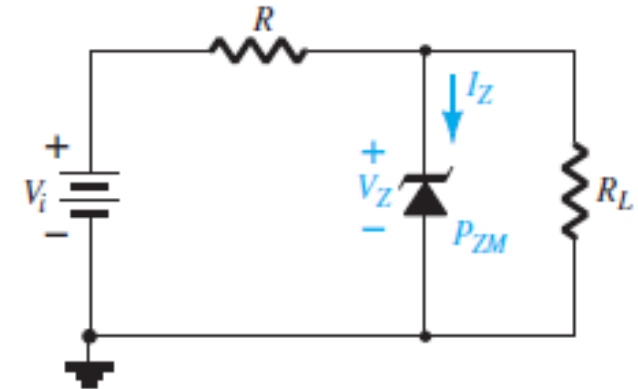- Zener Diode should be in Reverse Biased Condition
- V_{in} should be Greater than V_Z
- I_Z should be greater than I_{Zmin}
- I_Z should be less than or equal to I_{Zmax}



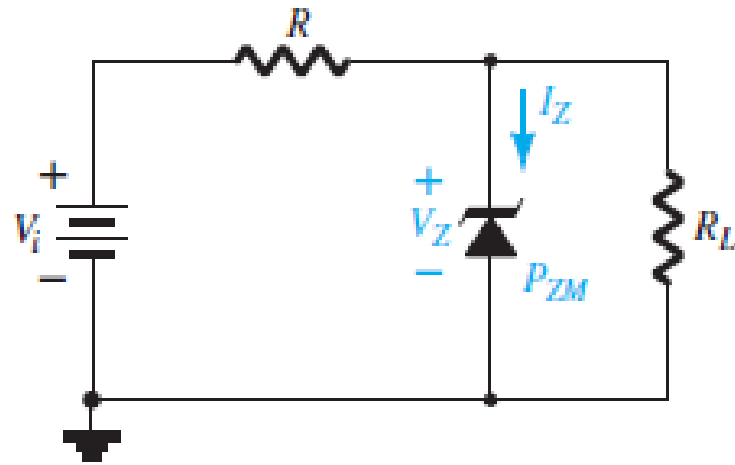


Different operating conditions of Zener Regulator .

- (i) Fixed quantities, (V_i and R are fixed)
- (ii) Fixed supply voltage and a variable load, (Fixed V_i and variable R_L)
- (iii) Fixed load and a variable supply. (Fixed R_L and Variable V_i)
- (iv) Variable Supply and Variable Load. (Variable V_i and Variable R_L)

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

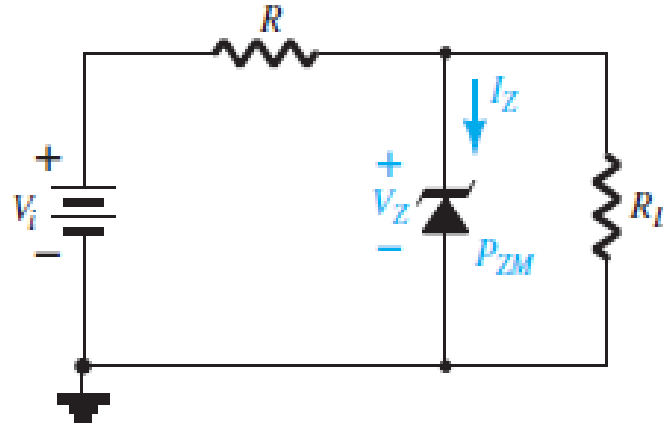CASE-1: Fixed V_i and fixed R_L Voltage Regulator




The analysis can fundamentally be broken down into two steps.

1. Determine the state of the Zener diode by removing it from the network and calculating the voltage across the resulting open circuit

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

If $V \geq V_Z$, the Zener diode is on, and the appropriate equivalent model can be substituted.

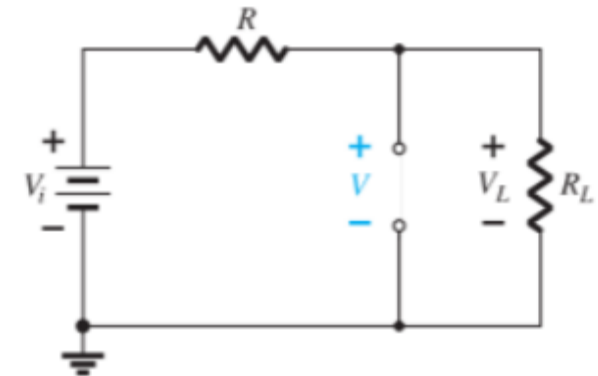If $V < V_Z$, the diode is off, and the open-circuit equivalence is substituted.



ELECTRONIC PRINCIPLES AND DEVICES


UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator

Conclusion:

If the Zener diode is in the “on” state, the voltage across the diode is not V volts.

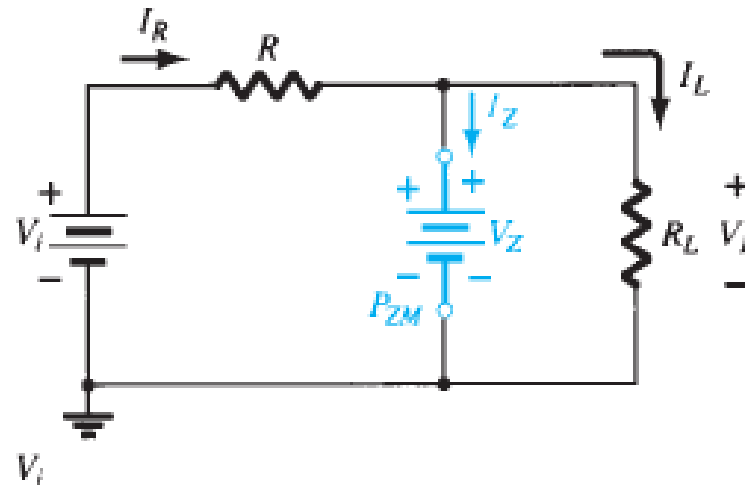The Zener diode will turn on as soon as the voltage across the Zener diode is V_Z volts. It will then “lock in” at this level and never reach the higher level of V volts.



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator




1. For the Zener diode network of Fig,

(i) Determine V_L , V_R , I_Z , and P_Z .

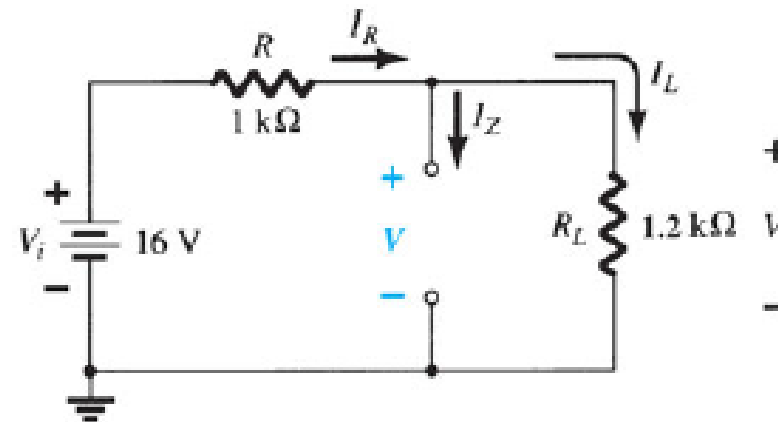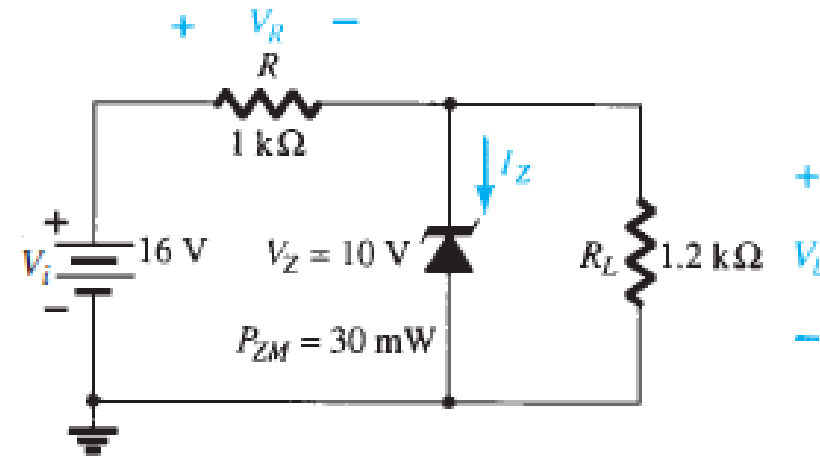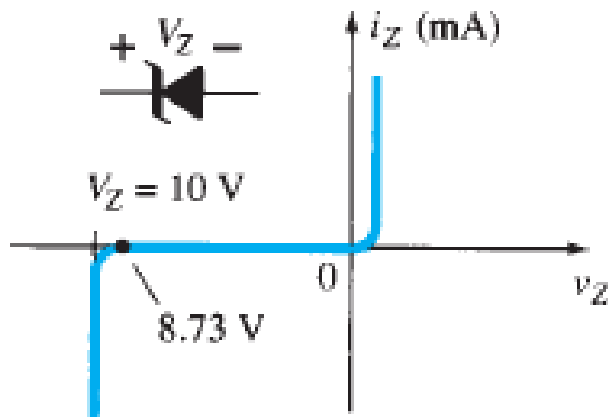(ii) Repeat part (a) with $R_L = 3\text{ k}\Omega$.

Solution (i):

$$V = \frac{R_L V_i}{R + R_L} = \frac{1.2 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 8.73 \text{ V}$$



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator


Solution (i):

$$V_L = V = 8.73 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 8.73 \text{ V} = 7.27 \text{ V}$$

$$I_Z = 0 \text{ A}$$
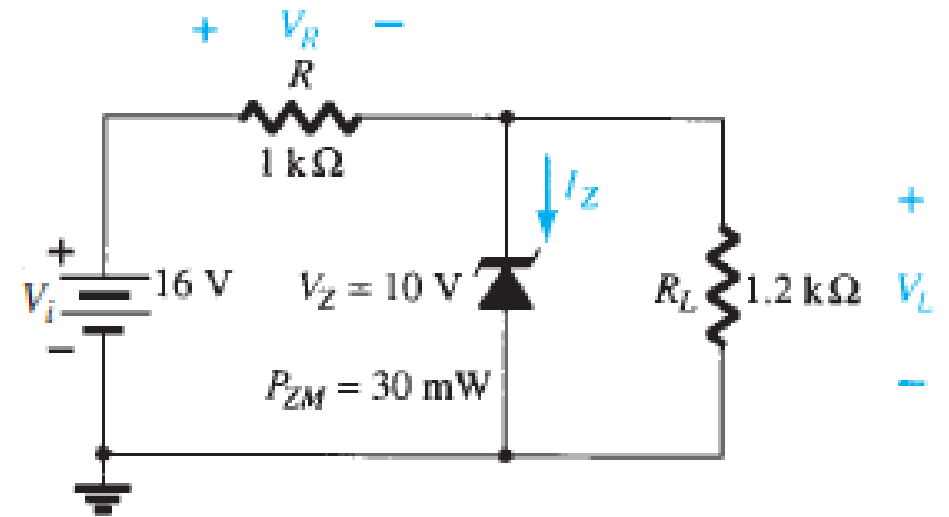
$$P_Z = V_Z I_Z = V_Z(0 \text{ A}) = 0 \text{ W}$$



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator

Solution: (ii)

$$V = \frac{R_L V_i}{R + R_L} = \frac{3 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 12 \text{ V}$$



$$V_L = V_Z = 10 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 10 \text{ V} = 6 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{10 \text{ V}}{3 \text{ k}\Omega} = 3.33 \text{ mA}$$

$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$
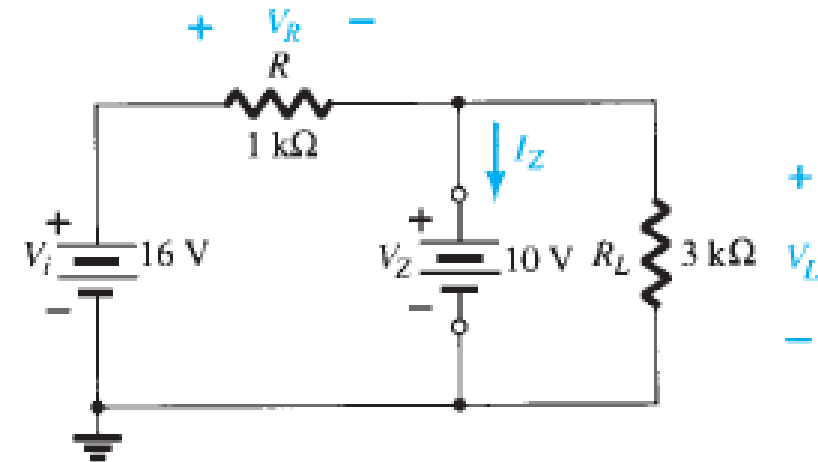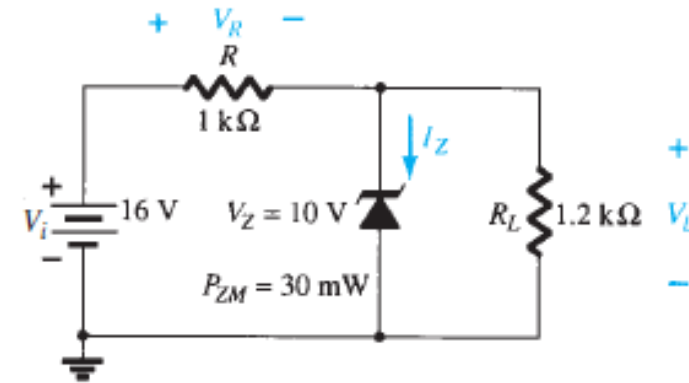
$$\begin{aligned} I_Z &= I_R - I_L \text{ [Eq. (2.18)]} \\ &= 6 \text{ mA} - 3.33 \text{ mA} \\ &= 2.67 \text{ mA} \end{aligned}$$



The power dissipated is

$$P_Z = V_Z I_Z = (10 \text{ V})(2.67 \text{ mA}) = 26.7 \text{ mW}$$


which is less than the specified $P_{ZM} = 30 \text{ mW}$.

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator

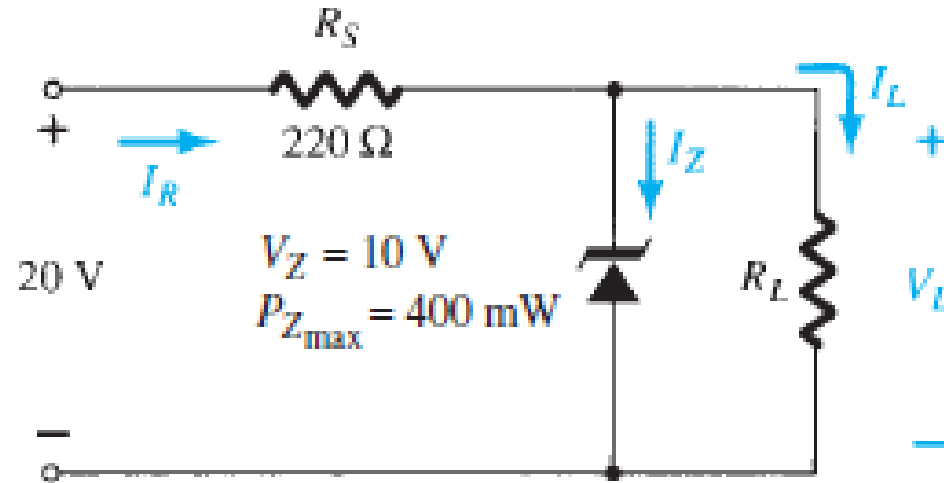2. (a) Determine V_L , I_L , I_Z , and I_R for the network of Fig. if $R_L = 180 \text{ ohm}$.
(b) Repeat part (a) if $R_L = 470 \text{ ohm}$.



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-1: Fixed V_i and fixed R_L Voltage Regulator

Solution a:

In the absence of the Zener diode


$$V_L = \frac{180 \Omega (20 \text{ V})}{180 \Omega + 220 \Omega} = 9 \text{ V}$$

$V_L = 9 \text{ V} < V_Z = 10 \text{ V}$ and diode non-conducting

$$\text{Therefore, } I_L = I_R = \frac{20 \text{ V}}{220 \Omega + 180 \Omega} = 50 \text{ mA}$$

with $I_Z = 0 \text{ mA}$

and $V_L = 9 \text{ V}$

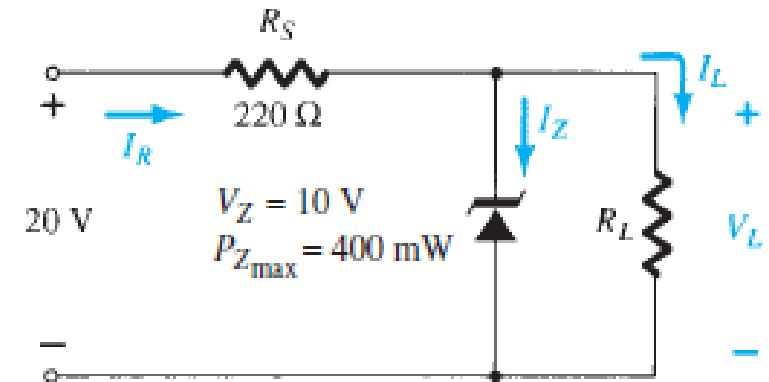

Solution b:

In the absence of the Zener diode

$$V_L = \frac{470 \Omega (20 \text{ V})}{470 \Omega + 220 \Omega} = 13.62 \text{ V}$$

$V_L = 13.62 \text{ V} > V_Z = 10 \text{ V}$ and Zener diode “on”

Therefore, $V_L = 10 \text{ V}$ and $V_{R_s} = 10 \text{ V}$

$$I_{R_s} = V_{R_s} / R_s = 10 \text{ V} / 220 \Omega = 45.45 \text{ mA}$$

$$I_L = V_L / R_L = 10 \text{ V} / 470 \Omega = 21.28 \text{ mA}$$

$$\text{and } I_Z = I_{R_s} - I_L = 45.45 \text{ mA} - 21.28 \text{ mA} = 24.17 \text{ mA}$$

CASE-2: Fixed supply voltage and a variable load

Conditions for R_L to Keep the Zener current I_Z in the operating limit

i.e $I_{Zmin} \leq I_Z < I_{Zmax}$

1: Condition for R_{Lmin} :

$$I_L = I_R - I_Z$$


$$R_L = \frac{V_Z}{I_L} \quad \text{Red italic: } R_L \text{ is Minimum when } I_L \text{ is Maximum}$$

$$I_{Lmax} = I_R - I_{Zmin} \quad \text{where } I_R = \frac{V_i - V_Z}{R}$$

$$R_{Lmin} = \frac{V_Z}{I_{Lmax}}$$

If $I_{Zmin} = 0$ then $I_{Lmax} = I_R$
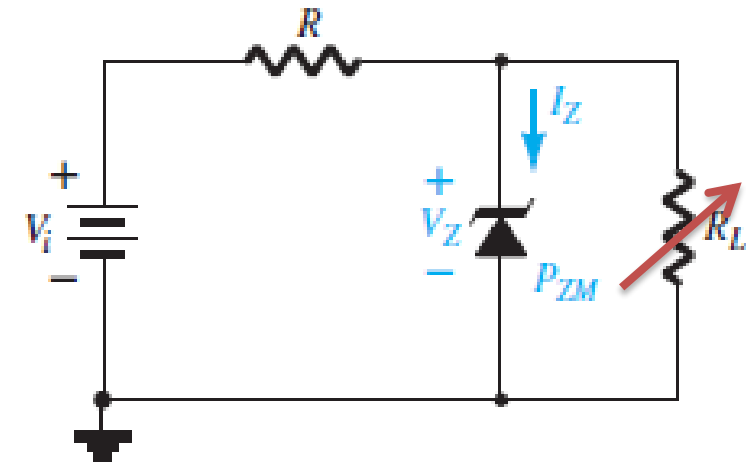
$$\text{hence, } R_{Lmin} = \frac{V_Z}{I_R} = \frac{V_Z R}{V_i - V_Z}$$



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-2: Fixed supply voltage and a variable load

Conditions for R_L to Keep the Zener current I_Z in the operating limit i.e

$$I_{Zmin} \leq I_Z < I_{Zmax}$$


2: Condition for R_{Lmax} :

$$I_L = I_R - I_Z$$

$$R_L = \frac{V_Z}{I_L} \quad R_L \text{ is Maximum when } I_L \text{ is Minimum}$$

$$I_{Lmin} = I_R - I_{Zmax} \quad \text{where} \quad I_R = \frac{V_i - V_Z}{R} \quad \text{and} \quad I_{Zmax} = \frac{P_{ZM}}{V_Z}$$

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

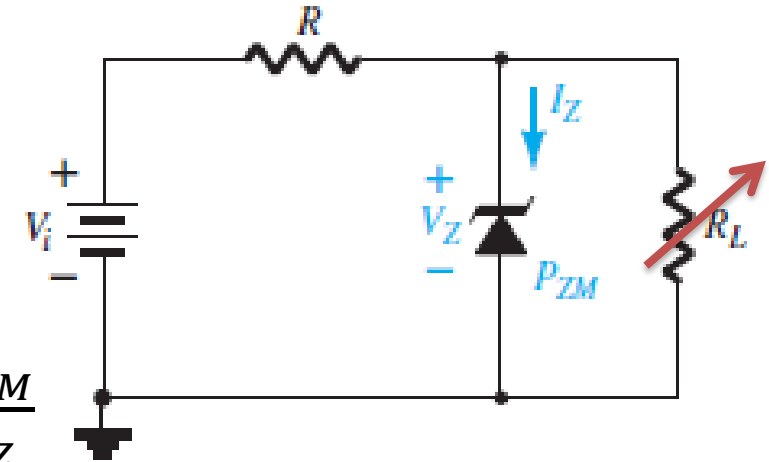


ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator


CASE-2: Fixed supply voltage and a variable load

3. For the network of Fig

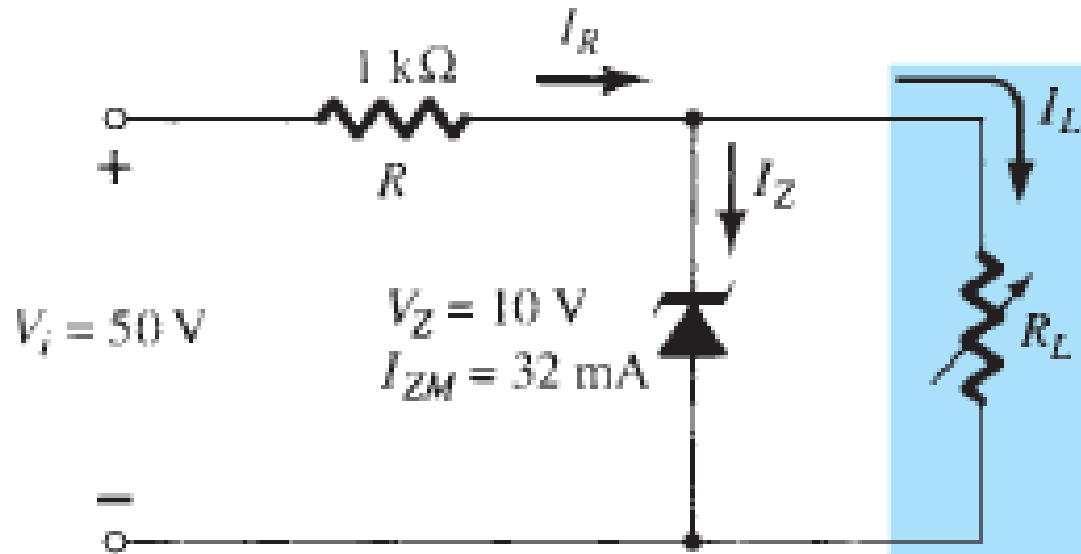- (i) Determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V. Given $I_{Zmin} = 1\text{mA}$.
- (ii) Determine the maximum wattage rating of the diode.



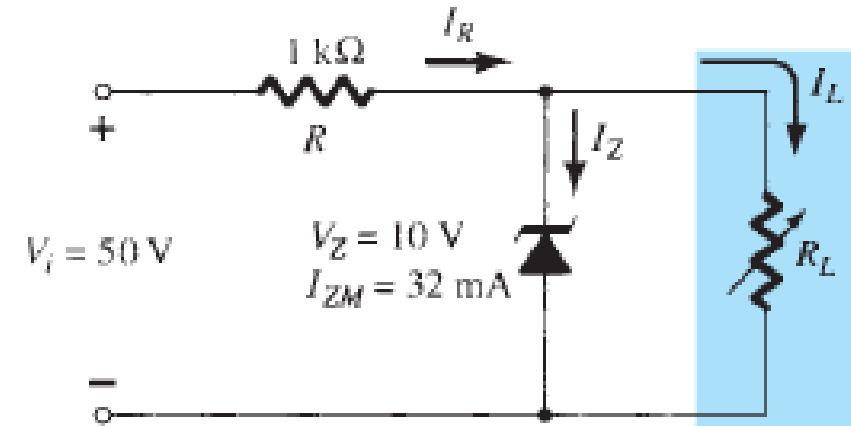CASE-2: Fixed supply voltage and a variable load



$$(i) \quad I_R = \frac{V_i - V_Z}{R} = \frac{50 - 10}{1\text{ k}\Omega} = 40\text{ mA}$$

$$I_{L\text{max}} = I_R - I_{Z\text{min}} = 40\text{ mA} - 1\text{ mA} = 39\text{ mA}$$

$$I_{L\text{min}} = I_R - I_{Z\text{max}} = 40\text{ mA} - 32\text{ mA} = 8\text{ mA}$$

$$R_{L\text{max}} = \frac{V_Z}{I_{L\text{min}}} = \frac{10}{8\text{ mA}} = 1.25\text{ K}\Omega$$

$$R_{L\text{min}} = \frac{V_Z}{I_{L\text{max}}} = \frac{10}{39\text{ mA}} = 256.41\ \Omega$$

ELECTRONIC PRINCIPLES AND DEVICES


UNIT - II: Zener diode as Voltage Regulator

CASE-2: Fixed supply voltage and a variable load

3. For the network of Fig

(ii) Determine the maximum wattage rating of the diode.

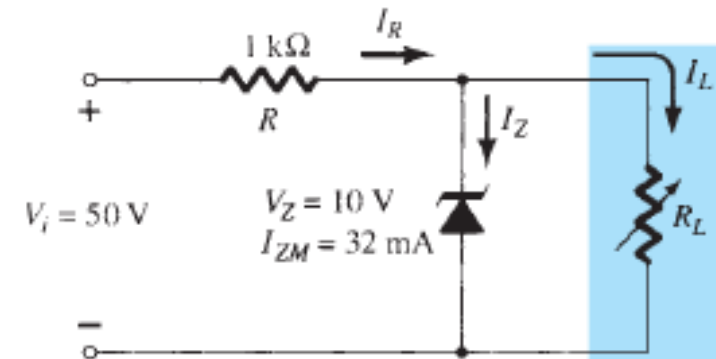(ii) Maximum Wattage $P_{Z_{max}} = V_Z * I_{Z_{max}} = 320\text{mW}$



CASE-2: Fixed supply voltage and a variable load

4. Determine the value of R_L that will establish maximum power conditions for the Zener diode.
Determine the minimum value of R_L to ensure that the Zener diode is in the “on” state.


$$P_{Z_{\max}} = 400 \text{ mW} = V_Z I_Z = (10 \text{ V})(I_Z)$$

$$I_Z = \frac{400 \text{ mW}}{10 \text{ V}} = 40 \text{ mA}$$

$$I_{L_{\min}} = I_{R_s} - I_{Z_{\max}} = 45.45 \text{ mA} - 40 \text{ mA} = 5.45 \text{ mA}$$

$$R_L = \frac{V_L}{I_{L_{\min}}} = \frac{10 \text{ V}}{5.45 \text{ mA}} = \mathbf{1,834.86 \, \Omega}$$

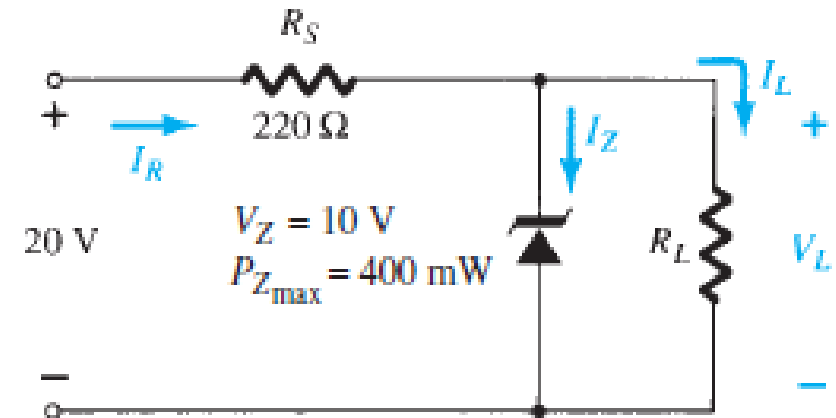Large R_L reduces I_L and forces more of I_{R_s} to pass through Zener diode.



In the absence of the Zener diode

$$V_L = 10 \text{ V} = \frac{R_L (20 \text{ V})}{R_L + 220 \, \Omega}$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200$$

$$R_L = \mathbf{220 \, \Omega}$$

CASE-3: Fixed R_L , Variable V_i

Conditions for V_i to Keep the Zener current I_Z in the operating limit i.e $I_{Zmin} \leq I_Z < I_{Zmax}$

1: Condition for $V_{i_{min}}$:


$$I_R = I_Z + I_L$$

$$I_{Rmin} = I_{Zmin} + I_L$$

$$I_{Rmin} = \frac{V_{imin} - V_Z}{R}$$

$$V_{imin} = V_Z + I_{Rmin}R$$
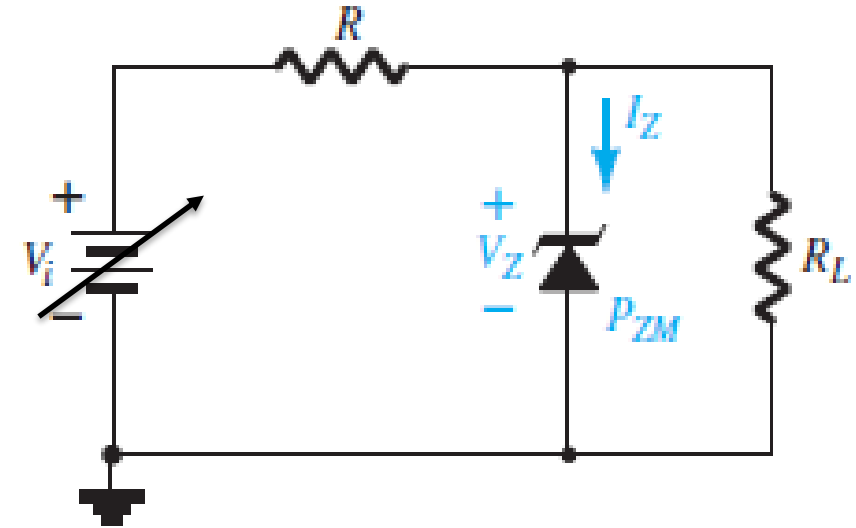
$$\text{If } I_{Zmin} = 0 ; \text{ then } I_{Rmin} = I_L; V_{imin} = V_Z + I_L R = \frac{V_Z(R_L + R)}{R_L}$$



CASE-3: Fixed R_L , Variable V_i

Conditions for V_i to Keep the Zener current I_Z in the operating limit i.e $I_{Zmin} \leq I_Z < I_{Zmax}$

2: Condition for $V_{i_{max}}$:

$$I_R = I_Z + I_L$$


$$I_{Rmax} = I_{Zmax} + I_L$$

$$I_{Rmax} = \frac{V_{imax} - V_Z}{R}$$

$$I_L = \frac{V_Z}{R_L}$$

$$I_{Zmax} = \frac{P_{ZM}}{V_Z}$$

$$V_{imax} = V_Z + I_{Rmax}R$$

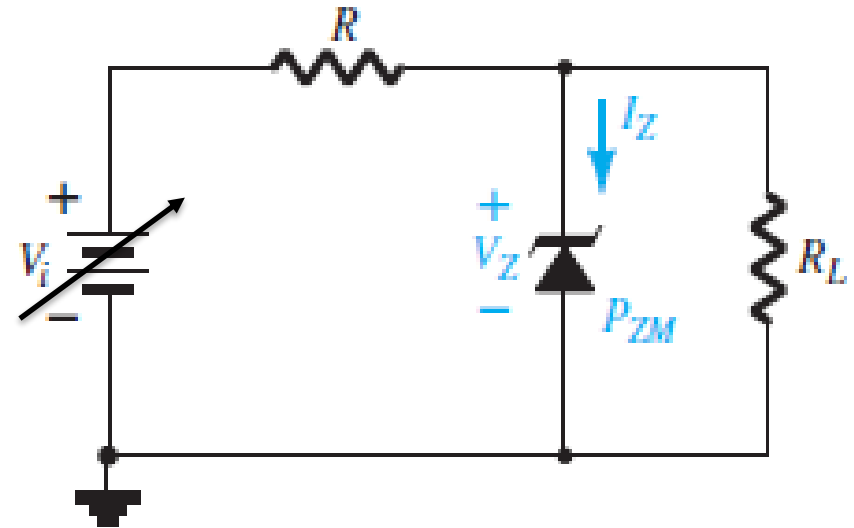


ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-3: Fixed R_L , Variable V_i

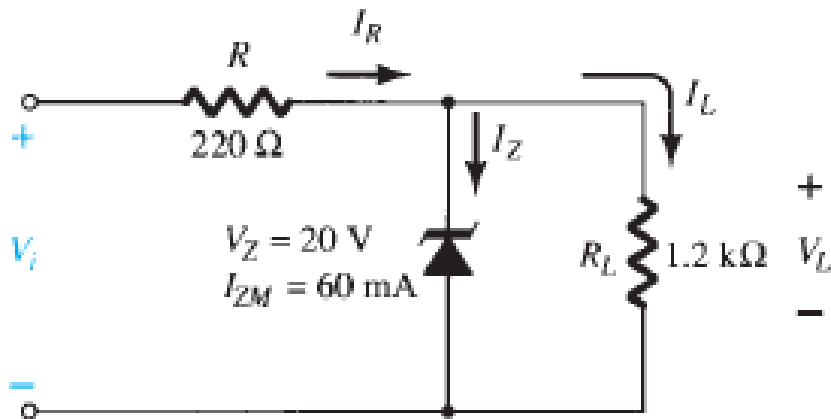5. Determine the range of values of V_i that will maintain the Zener diode of Fig. in the “on” state. Given $I_{Zmin} = 2mA$



$$V_{imin} = V_Z + I_{Rmin}R$$

$$I_{Rmin} = I_{Zmin} + I_L$$

$$I_L = \frac{V_Z}{R_L} = \frac{20}{1.2K\Omega} = 16.67mA$$

$$I_{Rmin} = 2mA + 16.67mA = 18.67mA$$

$$V_{imin} = 20 + 18.67mA * 220\Omega = 24.107V$$

$$V_{imax} = V_Z + I_{Rmax}R$$



$$I_{Rmax} = I_{Zmax} + I_L$$

$$I_{Rmax} = 60mA + 16.67mA = 76.67mA \quad V_{imax} = 20 + 76.67mA * 220\Omega = 36.86V$$

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-3: Fixed R_L , Variable V_i

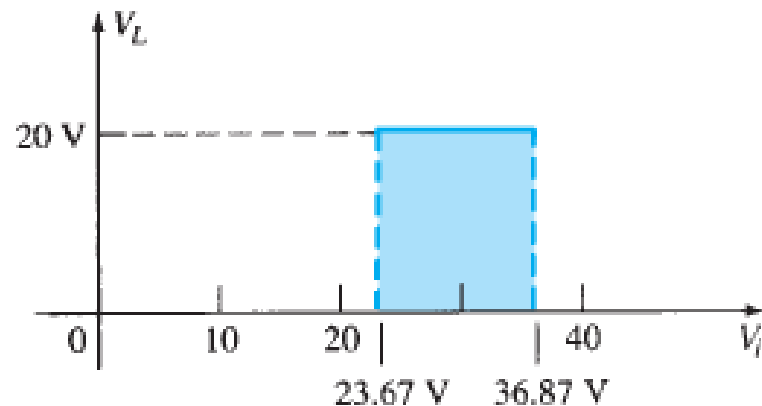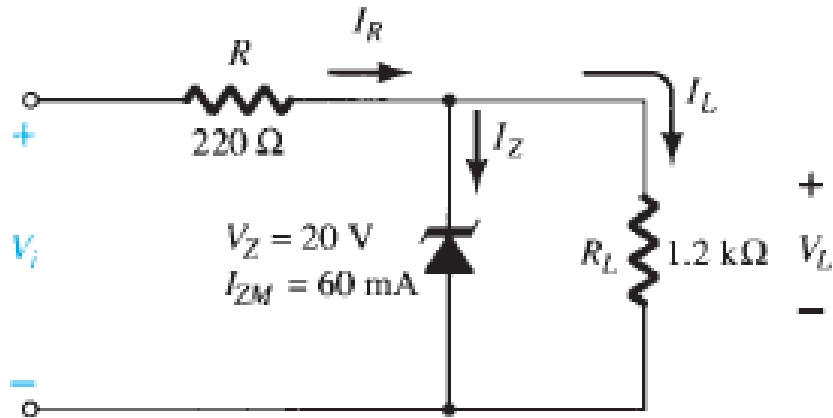

ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-4: Variable supply voltage and a variable load

Worst case conditions for Zener Diode:


1. For the diode to enter into the breakdown region, the necessary condition is $I_Z \geq I_{Zmin}$.

I_Z can become less than I_{Zmin} when

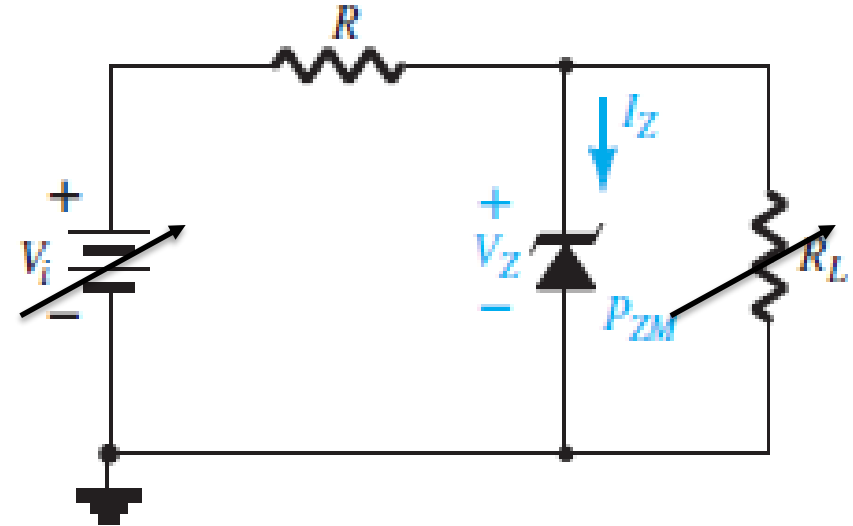- (i) I_L increases or R_L decreases.
- (ii) R increases or I_R decreases.
- (iii) V_{in} decreases.

Hence the value for R_{max} to ensure $I_Z \geq I_{Zmin}$ is

$$R_{max} = \frac{V_{imin} - V_Z}{I_{Zmin} + I_{Lmax}}$$



ELECTRONIC PRINCIPLES AND DEVICES

UNIT - II: Zener diode as Voltage Regulator

CASE-4: Variable supply voltage and a variable load

Worst case conditions for Zener Diode:


2. The upper limit for the Zener current is $I_Z < I_{Zmax}$.

I_Z can become greater than I_{Zmax} when

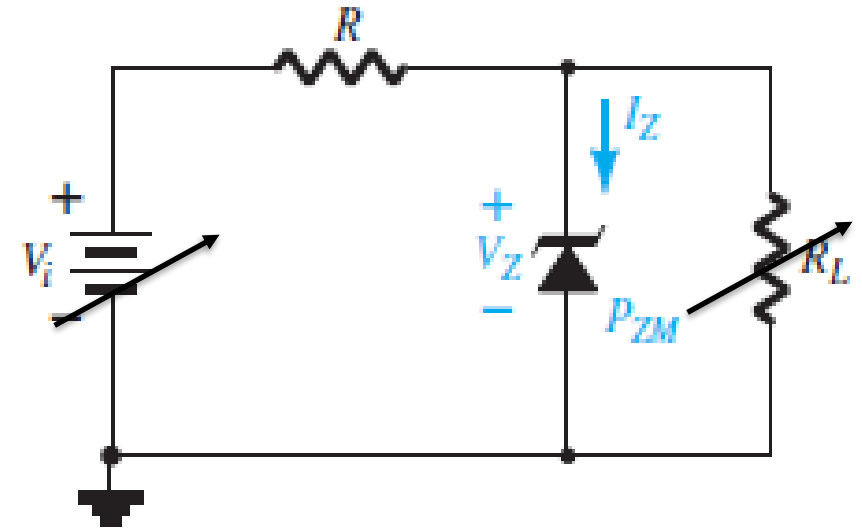- (i) I_L decreases or R_L increases.
- (ii) R decreases or I_R increases.
- (iii) V_{in} increases.

Hence the value for R_{min} is to ensure $I_Z < I_{Zmax}$ is

$$R_{min} = \frac{V_{imax} - V_Z}{I_{Zmax} + I_{Lmin}}$$



CASE-4: Variable supply voltage and a variable load

6. Design a Zener voltage regulator that maintains V_o at 10V for input voltage variation of $20V \pm 10\%$ and load current variation of $30mA \pm 20\%$. Given $I_{Zmin} = 2mA$ and $P_{Zmax} = 0.5W$

$$V_{imin} = 20V - 2V = 18V$$

$$I_{Lmin} = 30mA - 6mA = 24mA$$

$$V_{imax} = 2V + 2V = 22V$$

$$I_{Lmax} = 30mA + 6mA = 36mA$$

$$R_{max} = \frac{V_{imin} - V_Z}{I_{Zmin} + I_{Lmax}} = \frac{18 - 10}{2mA + 36mA} = 210.5 \Omega$$

$$R_{min} = \frac{V_{imax} - V_Z}{I_{Zmax} + I_{Lmin}} = \frac{22 - 10}{50mA + 24mA} = 162.16 \Omega$$

$$210.5 \Omega \leq R \leq 162.16 \Omega$$



THANK YOU

Department of Electronics and Communication