




ELECTRONIC PRINCIPLES AND DEVICES

Dr. Ananda M

Department of Electronics and Communication.

ELECTRONIC PRINCIPLES AND DEVICES

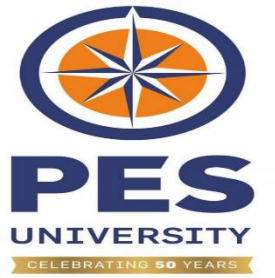

Unit-3 Digital Electronics

Other Logical Operation, Digital Logic gates (XOR and XNOR)

Dr. Ananda M


Department of Electronics and Communication.

Other Logical Operation, Digital Logic gates (XOR and XNOR)

- ❖ **XOR Gate** is a digital logic Gate which has two or more inputs and only one output that performs Exclusive OR operation. Hence it is also called as Ex-OR or XOR
- ❖ For two input XOR gate output is **logic-1** only when one of its input is logic-1 (unequal input i.e..A = 0 and B = 1 or A = 1 and B = 0).
- ❖ Output of XOR gate is **logic-0** if both inputs are same (i.e., A = 0 and B = 0 or A = 1 and B = 1)
- ❖ Truth Table of XOR Gate:

| Input A | Input B | Output Y |
|---------|---------|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

❖ Symbol

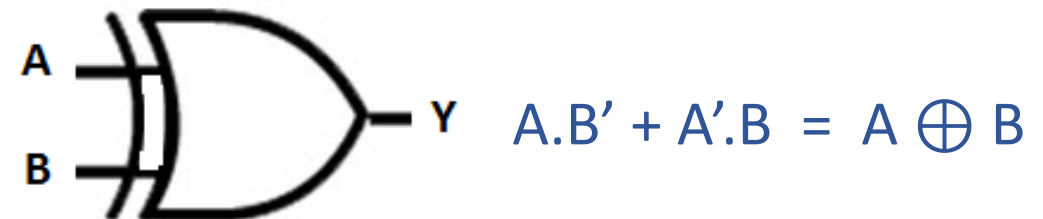

Other Logical Operation, Digital Logic gates (XOR and XNOR)

❖ XOR gate performs modulo sum operation without including carry.
i.e., $0+0 = 0$, $0+1 = 1$, $1+0 = 1$, $1+1 = 0$ (carry 1)

❖ Truth Table

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$$Y = A'.B + A.B'$$

$$Y = A \text{ XOR } B$$

$$Y = A \oplus B$$

$$A.B' + A'.B = A \oplus B$$

$$\text{LHS} = A.B' + A'.B$$

Case1: If $A = 0$ and $B = 0$
 $0.0' + 0'.0 = 0.1 + 1.0 = 0$

Case2: If $A = 0$ and $B = 1$
 $0.1' + 0'.1 = 0.0 + 1.1 = 1$

Case3: If $A = 1$ and $B = 0$
 $1.0' + 1'.0 = 1.1 + 0.0 = 1$

Case4: If $A = 1$ and $B = 1$
 $1.1' + 1'.1 = 1.0 + 0.1 = 0$


Hence $Y = A \oplus B = A.B' + A'.B$

Other Logical Operation, Digital Logic gates (XOR and XNOR)


❖ Implementation of XOR Gate using basic gates:

$$Y = A \oplus B = A.B' + A'.B$$

❖ Logic Diagram

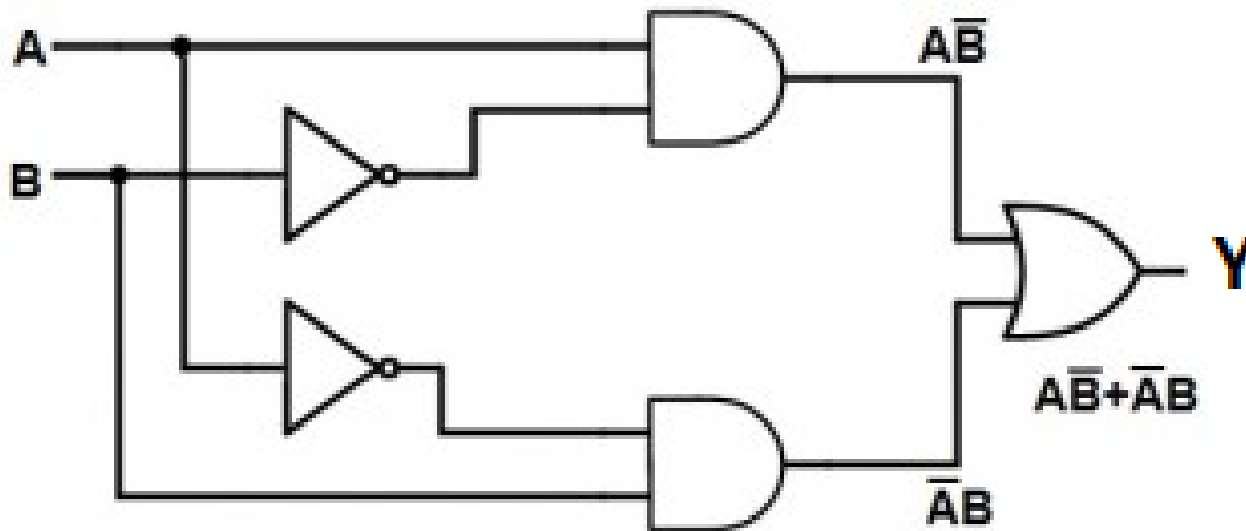

❖ Symbol

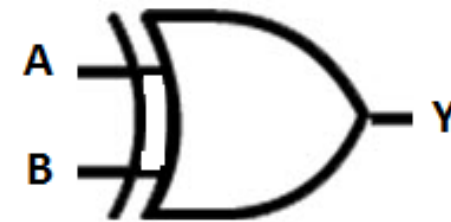


❖ 3 - Input XOR Gate: $Y = A \oplus B \oplus C$

Truth Table

| A | B | C | $A \oplus B$ | $A \oplus B \oplus C$ |
|---|---|---|--------------|-----------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

Symbol

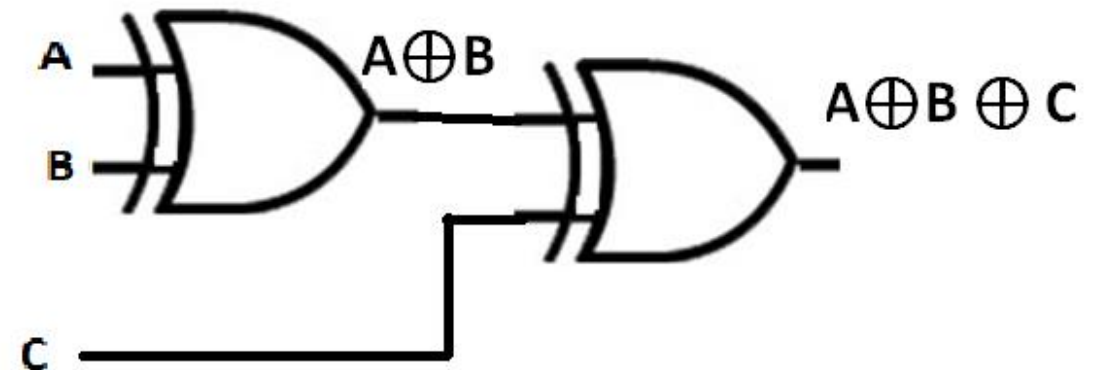

Associative Law:

$$(A \oplus B) \oplus C = A \oplus (B \oplus C)$$

❖ Even or odd Parity Bits

❖ **XNOR Gate:** Logical Complement of XOR Gate

❖ For two input XNOR Gate if both inputs are same i.e., $A = 0$ and $B = 0$ or $A = 1$ and $B = 1$. Then output of logic gate is logic-1 (High). Output of XNOR is logic-0 if inputs are unequal.

❖ Equality detector

Truth Table

| Input A | Input B | Output Y |
|---------|---------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

❖ **Boolean Expression**

$$Y = A.B + A'.B'$$

$$Y = A \odot B$$

❖ **Symbol**



❖ XNOR Gate:

$$Y = (A \oplus B)'$$

$$Y = (A.B' + A'.B)'$$

De Morgan's Theorem

$$Y = (A.B')' . (A'.B)'$$

$$Y = (A' + B) . (A + B')$$

$$Y = A'.A + A'.B' + A.B + B.B'$$


$$Y = 0 + A'.B' + A.B + 0$$

$$Y = A'.B' + A.B$$

$$Y = (A \oplus B)' = A \odot B$$

$$Y = (A \text{ XOR } B)' = (A \text{ XNOR } B)$$

❖ Logic Diagram:

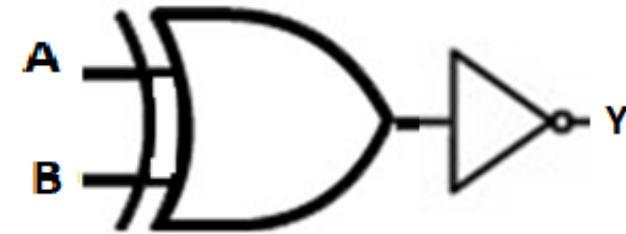


❖ Symbol:



❖ Implement the XNOR Gate using basic gates:

$$Y = A'.B' + A.B$$

❖ Logic Diagram:

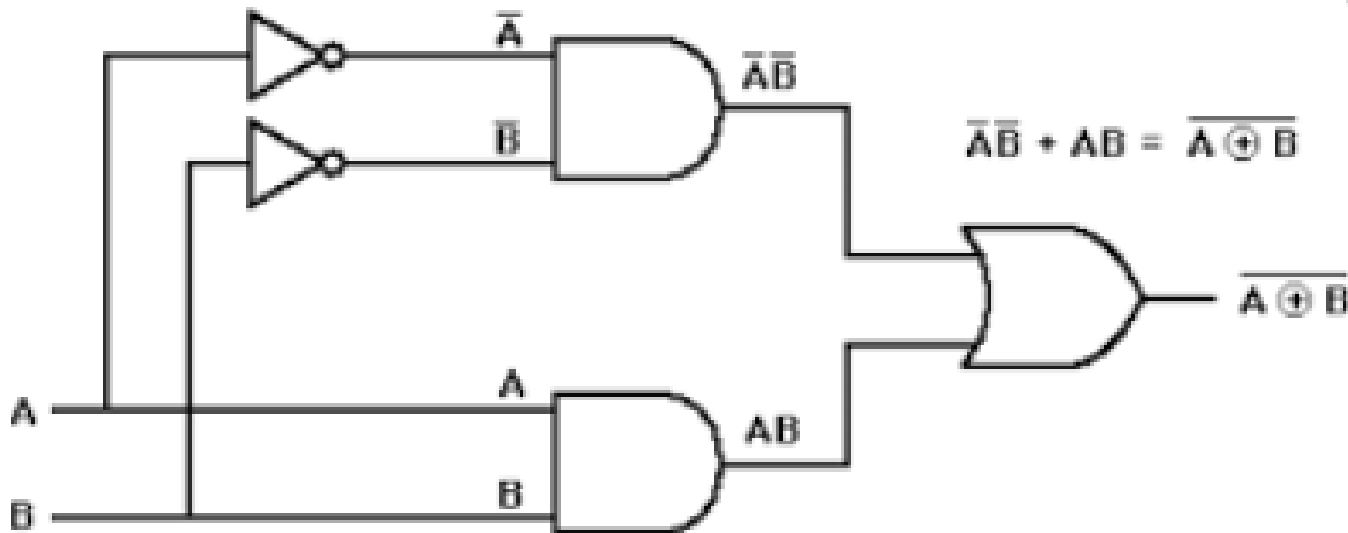

$$Y = (A \oplus B)' = A \odot B$$

❖ Properties of XOR Gate:

➤ Identity element: $A \oplus 0 = A$

➤ $A \oplus 1 = A'$

➤ $A \oplus A = 0$


➤ Commutative Law: $A \oplus B = B \oplus A$

➤ Associative Law : $A \oplus (B \oplus C) = (A \oplus B) \oplus C$



| Input A | Input B | Output Y |
|---------|---------|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

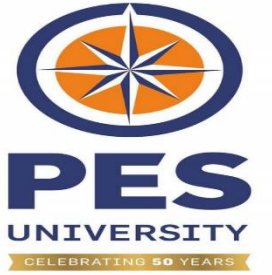Other Logical Operation, Digital Logic gates (XOR and XNOR)



❖ Applications of XOR and XNOR

- XOR gate is used in processor's Arithmetic Logic Unit (ALU) for binary addition.
- XOR logic gate is used to generate pseudorandom numbers in hardware.
- To generate parity bits and error detection
- Equality detector



THANK YOU

Dr. Ananda M
Department of Electronics and Communication
anandam@pes.edu