

Unit 2 - Single Phase AC Circuits

(1)

Numerical Problems & Selected Explanations

- 1) For a sinusoidal function of frequency 50 Hz, find i) Half time period ii) Angular frequency

Solution :- $T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s} = 20 \text{ msec}$

i) Half time period $T_{1/2} = \frac{T}{2} = \frac{20}{2} = 10 \text{ msec}$

ii) Angular frequency $\omega = 2\pi f = 2\pi(50)$

$$= 100\pi \text{ rad/sec}$$

- 2) The maximum value of a sinusoidal alternating current of frequency 50 Hz is 25 A. Write the equation for the instantaneous expression of current. Determine its value at 3 ms and 14 ms.

Solution :- $\omega = 2\pi f \text{ rad/sec} = 100\pi \text{ rad/sec}$


$$i(t) = 25 \sin(100\pi t) \text{ A}$$

$$i(3 \text{ ms}) = 25 \sin(100\pi \times 3 \text{ ms})$$

$$\boxed{i(3 \text{ ms}) = 20.22 \text{ A}}$$

$$i(14 \text{ ms}) = 25 \sin(100\pi \times 14 \text{ ms})$$
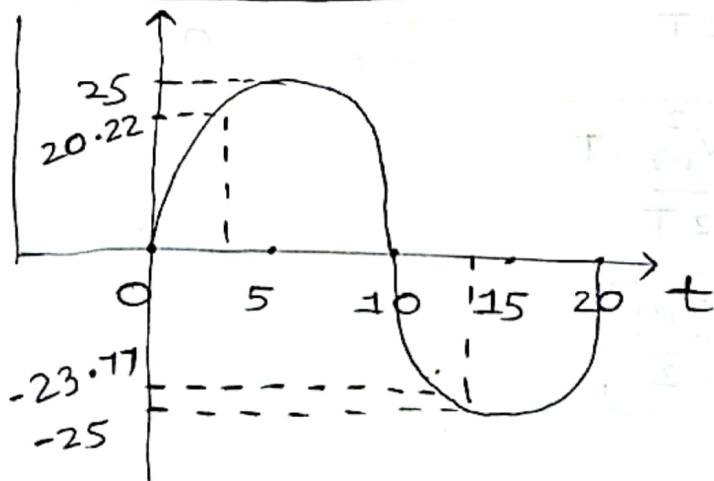
$$\boxed{i(14 \text{ ms}) = -23.77 \text{ A}}$$



② The average value of a sinusoidal function

$$f(t) = A \cdot \sin(\omega t) \text{ is } 0-$$

$$F_{\text{avg}} = \frac{1}{T} \int_0^T A \cdot \sin(\omega t) \cdot dt$$

$$F_{\text{avg}} = \frac{1}{T} \cdot A \cdot -\cos(\omega t) \Big|_0^T$$

$$= \frac{1}{T} \cdot A \cdot -[\cos\left(\frac{2\pi}{T} \cdot T\right) - \cos 0]$$

$$= -A [\cos(2\pi) - \cos 0]$$

$$\boxed{F_{\text{avg}} = 0}$$

RMS value of a Sine wave 0-

$$V = \sqrt{\frac{1}{T} \int_0^T [V_m \cdot \sin(\omega t)]^2 \cdot dt}$$

$$V = \sqrt{\frac{V_m^2}{T} \int_0^T \sin^2(\omega t) \cdot dt}$$

$$V = \sqrt{\frac{V_m^2}{T} \int_0^T \left[\frac{1 - \cos(2\omega t)}{2} \right] dt}$$

$$V = \sqrt{\frac{V_m^2}{2T} \left[T - \frac{\sin(2\omega t)}{2\omega} \right]_0^T}$$

$$V = \sqrt{\frac{V_m^2 \cdot T}{2T}}$$

$$\boxed{V = \frac{V_m}{\sqrt{2}}}$$

(3)

3) Write an equation to represent the following Sine waves of 50 Hz frequency?

- A sinusoidal current with RMS value 10A & starting at 5 msec
- A sinusoidal current with peak value 20A & starting at -2.5 msec. Also, comment on the phase relation between them?

Solution :- $\omega = 2\pi f = 100\pi \text{ rad/sec}$

case i) Angle = $\omega t = (100\pi * 5m) = \frac{\pi}{2} \text{ rad}$

$$i_1(t) = 10\sqrt{2} \sin(100\pi t - \frac{\pi}{2}) A$$

case ii) Angle = $\omega t = (100\pi * -2.5m) = -\frac{\pi}{4} \text{ rad}$

$$i_2(t) = 20\sqrt{2} \sin(100\pi t + \frac{\pi}{4}) A$$

4) Consider the following sinusoidal functions

i) $f_1(t) = 100 \sin(100\pi t)$


ii) $f_2(t) = 200 \sin(100\pi t + 60^\circ)$

iii) $f_3(t) = 100 \cos(100\pi t - 60^\circ)$

Note :- convert a cosine function to sine form before representing as a phasor

$$f_3(t) = 100 \sin(100\pi t - 60^\circ + 90^\circ)$$
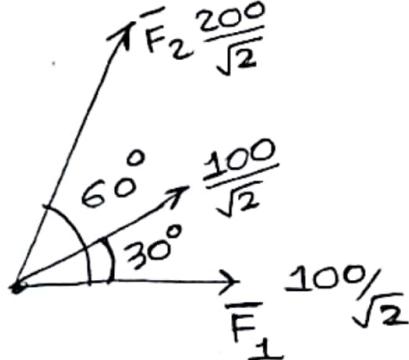
$$f_3(t) = 100 \sin(100\pi t + 30^\circ)$$



(4)

- 5) There are 3 conducting wires connected to form a junction. The currents flowing into the junction in two wires are $i_1 = 10 \cdot \sin(314t) A$ and $i_2 = 15 \cdot \cos(314t - 45^\circ) A$. What is the current leaving the junction in the third wire? What is its value at $t=0$?

Solution :- By KCL at the junction :-

$$i_3(t) = i_1(t) + i_2(t)$$

$$\bar{I}_3 = \bar{I}_1 + \bar{I}_2$$

$$i_1(t) = 10 \sin(314t) \Rightarrow \bar{I}_1 = \frac{10}{\sqrt{2}} 10^\circ A$$

$$i_2(t) = 15 \cdot \cos(314t - 45^\circ)$$

$$i_2(t) = 15 \cdot \sin(314t + 45^\circ) \Rightarrow \bar{I}_2 = \frac{15}{\sqrt{2}} 45^\circ$$

$$\bar{I}_3 = \bar{I}_1 + \bar{I}_2 = \frac{10}{\sqrt{2}} 10^\circ + \frac{15}{\sqrt{2}} 45^\circ = \frac{10\sqrt{2}}{\sqrt{2}} + 7.5 45^\circ \\ = 14.57 + 7.5 45^\circ$$

$$\bar{I}_3 = 16.39 \underline{27.24^\circ} A$$

$$i_3(t) = 23.18 \sin(314t + 27.24^\circ) A$$

Its value at $t=0$ is

$$i_3(0) = 23.18 \sin(27.24^\circ)$$

$$\boxed{i_3(0) = 10.61 A}$$

- ⑥ A capacitor of capacitance $100\mu F$ is connected across an AC voltage source $100 \sin(100\pi t) V$. Determine i) capacitive Reactance ii) Impedance iii) Instantaneous expression for the current. Also draw the phasor diagram?

Solution :- Given $V(t) = 100 \sin(100\pi t)$

$$\omega = 100\pi \text{ rad/sec}$$

i) capacitive Reactance, $X_c = \frac{1}{\omega C} = \frac{1}{100\pi \times 100\mu F}$

$X_c = 31.83 \Omega$


ii) Impedance, $Z = -j \cdot X_c = -j \cdot 31.83 \Omega$

iii) $i(t) = I_m \sin(\omega t + 90^\circ)$
 $= V_m \cdot \omega C \cdot \sin(\omega t + 90^\circ)$
 $= 100 \times 100\pi \times 100\mu F \times \sin(\omega t + 90^\circ)$

$i(t) = 3.14 \sin(\omega t + 90^\circ) A$

Phasor Diagram :-

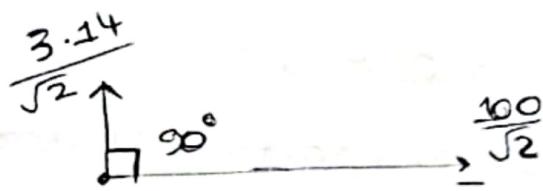$\bar{V} = \frac{100}{\sqrt{2}} / 0^\circ$



$\bar{I} = \frac{3.14}{\sqrt{2}} / 90^\circ$


$$\frac{100}{\sqrt{2}}$$

6

Numerical Examples on Analysis of Series RL & Series RC Circuits

1) When a resistor and an inductor in series are connected to a 240 V supply, a current of 3A flows lagging 37° behind the supply voltage, while voltage across the inductor is 171V. Find the resistance of the resistor, and the resistance and reactance of the inductor. Find the power factor of the circuit?

Solution :-

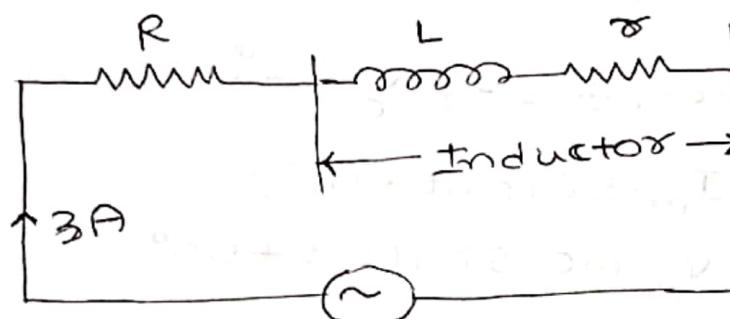

240V Current are

Solution :- In AC Systems, if voltage and given as numerical values, they represent RMS values

Let us consider current as reference

$$\bar{I} = 310^\circ A$$

Therefore, supply voltage phasor, $\bar{V} = 240/37^\circ V$

$$\bar{Z}_T = \frac{\bar{V}}{\bar{I}} = \frac{240/37^\circ}{310^\circ} = 80/37^\circ \Omega = [63.89 + j48.14] \Omega \quad -①$$

$$\bar{Z}_T = R + \sigma + jX_L \quad -②$$

Comparing ① & ② $X_L = 48.14 \Omega$

$$R + \sigma = 63.89 \Omega \quad -③$$

$$\text{Across Inductor } \frac{|V_{\text{inductor}}|}{|\bar{I}|} = \frac{171}{3} = \sqrt{\sigma^2 + X_L^2}$$

$$\text{Power factor} = \frac{(R + \sigma)}{|\bar{Z}_T|} = 0.798 \text{ lag}$$

$$\begin{aligned} \sigma^2 + X_L^2 &= 3249 \\ \sigma^2 &= 3249 - 2317.45 \\ \sigma &= 30.52 \Omega \end{aligned}$$

$$R = 33.37 \Omega$$

⑦ 2) A series RC circuit, with $R = 4\Omega$, $C = 120\mu F$ is connected across $230V, 50\text{ Hz}$ supply. calculate the current drawn by the circuit. Draw the phasor diagram?

Solution :- Given $V = 230V$; $R = 4\Omega$; $C = 120\mu F$; $f = 50\text{ Hz}$;
 $I = ?$

$$I = \frac{V}{Z}$$

$$Z = R - jX_C$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 120 \mu F}$$

$$X_C = 26.52\Omega$$


$$Z = R - jX_C$$

$$Z = 4 - j26.52\Omega$$

$$I = \frac{230}{4 - j26.52} = \frac{230}{26.82 \angle -81.42^\circ} = \frac{230}{26.82 \angle -81.42^\circ}$$


$$I = 8.57 \angle 81.42^\circ$$

Phasor diagram :-

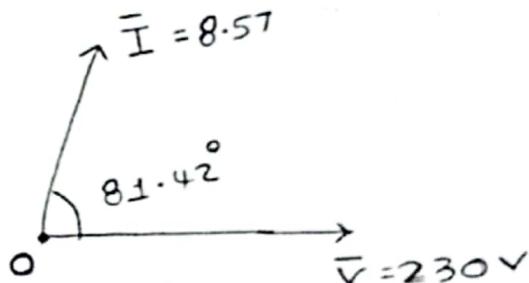

(8)

- 3) 3 coils A, B and C are connected in series. When a current of 3A is passed through the circuit, the voltage drops are respectively 12V, 6V and 9V on direct current and 15V, 9V and 12V on alternating current. Find for each coil i) Internal Parameters ii) Power dissipated when alternating current flows through the circuit iii) Applied voltage across it. Draw the phasor diagram. Find the overall power factor of the circuit?

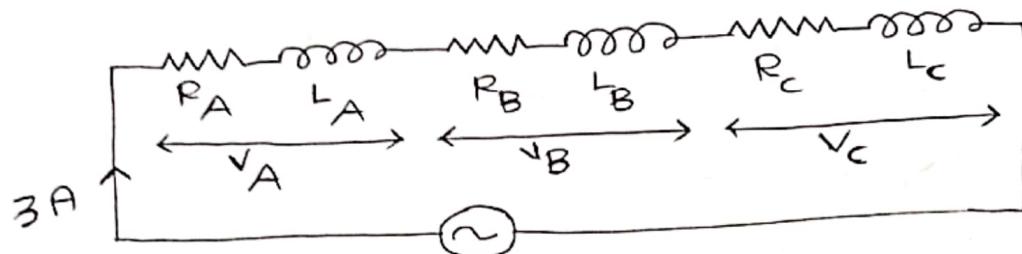Solution :-case(i) Direct current ($\omega = 0$)

under DC condition, inductance will not have any effect $Z_A = R_A ; Z_B = R_B ; Z_C = R_C$

$$R_A = \frac{12}{3} = 4\Omega ; R_B = \frac{6}{3} = 2\Omega ; R_C = \frac{9}{3} = 3\Omega$$

case(ii) under AC conditions

$$Z_A = \frac{15}{3} = 5\Omega ; \sqrt{R_A^2 + X_{L_A}^2} = 5$$

$$X_{L_A}^2 = 25 - 16 \Rightarrow X_{L_A} = 3\Omega$$

$$Z_B = \frac{9}{3} = 3\Omega ; R_B^2 + X_{L_B}^2 = 9$$

$$X_{L_B}^2 = 9 - 4 = 5 \Rightarrow X_{L_B} = 2.23\Omega$$

$$Z_C = \frac{12}{3} = 4\Omega ; R_C^2 + X_{L_C}^2 = 16$$

$$X_{L_C}^2 = 16 - 16 = 0 \Rightarrow X_{L_C} = 2.64\Omega$$

Power dissipated :-

$$P_A = I^2 \cdot R_A = 3^2 \times 4 = 36 \text{ W}$$

$$P_B = I^2 \cdot R_B = 3^2 \times 8 = 18 \text{ W}$$

$$P_C = I^2 \cdot R_C = 3^2 \times 3 = 27 \text{ W}$$

No power dissipated in inductor & capacitor.

$$Z_T = 4 + j3 + 2 + j2 \cdot 2 + 3 + j2 \cdot 64$$

$$\boxed{Z_T = 9 + j7.87 \Omega}$$

$$V = I \cdot Z_T$$

$$V = 3(9 + j7.87 \Omega)$$

$$\boxed{V = 27 + j23.61 \Omega}$$

$$\text{Power} = \frac{P}{|Z_T|} = \frac{9}{\sqrt{9^2 + 7.87^2}} = 0.75$$

4) Power dissipated in a series RC circuit is 25 W, while the current and voltage being 0.4 A & 230V respectively. Find the value of capacitance. (Assume supply frequency = 50 Hz) ?

Solution :- $P = VI \cdot \cos \phi$

$$\cos \phi = \frac{P}{VI} = \frac{25}{230 \times 0.4}$$

$$\cos \phi = 0.2717$$

$$\boxed{\phi = 74.23^\circ}$$

$$Z = \frac{V}{I} = \frac{230}{0.4 / 74.23^\circ} = 57.5 \angle -74.23^\circ$$

$$\boxed{Z = 156.27 - j553.35}$$

This is of the form :- $Z = R - jX_C$



$$X_C = 553.35; X_C = \frac{1}{\omega C}$$

$$C = \frac{1}{2\pi \times 50 \times 553.35} = 5.75 \mu F$$

(10)

- 5) The following phasor diagram find the following :-
- Power factor of the circuit
 - Reactive power in the circuit
 - Magnitude of Supply voltage

Also, Redraw the phasor diagram by taking Supply voltage as reference, mentioning all the voltages & currents. Current phasor is 10 A, V_C is 6 V and V_L is 10 V.

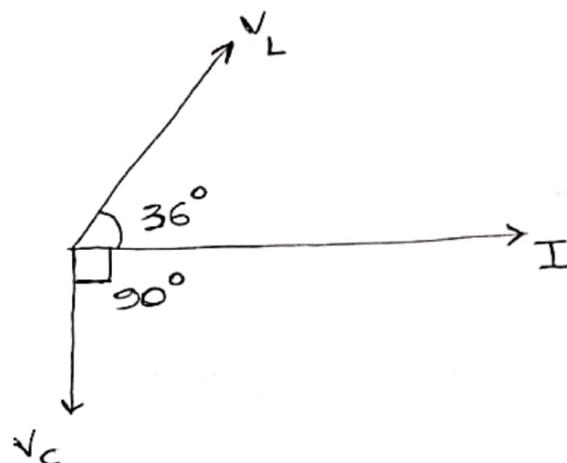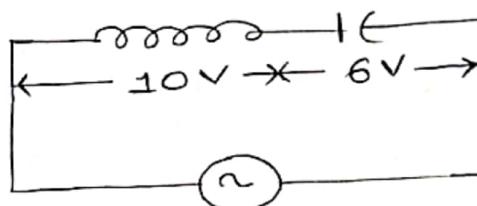Solution :-

$$\bar{V}_C = 6 \angle -90^\circ ; \bar{V}_L = 10 \angle 36^\circ$$

$$\bar{V} = \bar{V}_L + \bar{V}_C = 8.09 + 5.87i - 6i$$

$$\bar{V} = 8.09 - 0.122i$$

$$\boxed{\bar{V} = 8.09 \angle -0.865}$$


$\bar{I} = 10 \angle 0^\circ ; \phi = -0.86 ;$ Indicates voltage is lagging

$$PF = \cos \phi = 0.999 \text{ lead}$$

$$Q = VI \sin \phi$$

$$= 8.09 \times 10 \times \sin(0.865)$$

$$\boxed{Q = -1.214 \text{ VAR}}$$

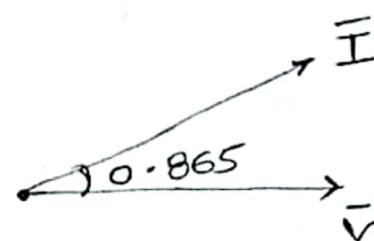

Numerical Problems on Series RLC Circuit :-

Q) A series RLC circuit draws a current of 20A when connected to 200V, 50 Hz supply. If the total active power drawn from the source is 500W and the circuit behaves effectively like an inductive circuit (series RL type), determine

- i) Power factor of the circuit
- ii) Inductance in the circuit if capacitance is 100μF?

Solution :- Given $V = 200V$; $I = 20A$ & $P = 500W$

$$\textcircled{i} \quad P = I^2 \cdot R$$

$$R = \frac{P}{I^2} = \frac{500}{(20)^2} = 1.25\Omega$$

$$\therefore \cos\phi = \frac{R}{|Z|}; |Z| = \frac{V}{I} = \frac{200}{20} = 10\Omega$$

$$\cos\phi = \frac{1.25}{10} = 0.125 \text{ lag}$$

$$\textcircled{ii} \quad \text{Net reactance} = X_L - X_C = \sqrt{Z^2 - R^2}$$

$$\sqrt{100 - 1.25^2} = X_L - X_C = 9.92\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$\boxed{X_C = 31.83\Omega}$$

$$X_L = 9.92 + X_C$$

$$X_L = 41.75\Omega$$

$$X_L = \omega L = 41.75\Omega$$


$$\therefore L = \frac{41.75}{2\pi \times 50}$$

$$\boxed{L = 132.89\text{ mH}}$$

(12)

2) A coil of power factor 0.6 is in series with a 100 μF capacitor. When connected to a 50 Hz supply, the potential difference across the coil is equal to the potential difference across the capacitor. Find the resistance and inductance of the coil?

Solution :-

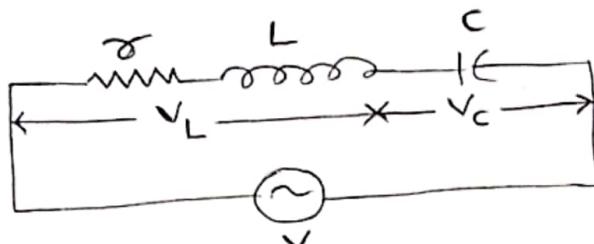

$$V_L = V_C$$

$$I|Z_L| = I|Z_C|$$

$$|R + jX_L| = | - jX_C \cdot \frac{1}{j} |$$

$$X_C = \frac{1}{\omega C} = 31.83 \Omega$$

$$\cos \phi = \frac{P}{S} = \frac{R}{|Z|}$$

$$R = |Z| \cdot \cos \phi$$

$$R = 31.83 \times 0.6$$

$$\boxed{R = 19.09 \Omega}$$

$$R^2 + X_L^2 = 31.83^2$$

$$X_L^2 = 31.83^2 - 19.09^2$$

$$\boxed{X_L = 25.46 \Omega}$$

$$\omega L = 25.46$$

$$L = \frac{25.46}{100\pi}$$

$$\boxed{L = 81 mH}$$

3) An EMF whose instantaneous value at time t is given by $283 \sin(100t + \pi/4) V$ is applied to an inductive circuit and the current in the circuit is $5.66 \sin(100\pi t - \pi/6) A$.

Determine

- the frequency of the EMF
- the resistance & the inductance of the circuit
- the active power absorbed

In series capacitance is added so as to bring the circuit into resonance at this frequency, and the above emf is applied to the resonant circuit, find the corresponding expression for the instantaneous value of the current and also find the value of the series capacitance. Draw the phasor diagram representing the circuit before and at resonance.

Solution :- $\bar{V} = \frac{283}{\sqrt{2}} 45^\circ ; \bar{I} = \frac{5.66}{\sqrt{2}} -30^\circ$

i) $\omega = 100\pi$

$2\pi f = 100\pi$

$f = 50 \text{ Hz}$

ii) $Z = \frac{\bar{V}}{\bar{I}} = \frac{283/\sqrt{2} 45^\circ}{5.66/\sqrt{2} -30^\circ} = 50 75^\circ = 12.94 + j48.29$

iii) $R = 12.94 \Omega ; X_L = 48.29 \Rightarrow L = 0.153 \text{ H}$

iv) $P = I^2 \cdot R = \left[\frac{5.66}{\sqrt{2}} \right]^2 \times 12.94 = 207.27 \text{ W}$

v) After resonance, $X_L = X_C = 48.29$

$\frac{1}{\omega C} = 48.29 ; C = 65.91 \mu\text{F}$


14

$$I = \frac{V}{R} = \frac{283/\sqrt{2} \angle 45^\circ}{12.94}$$


$$I = 15.46 \angle 45^\circ$$

$$i(t) = 21.863 \sin(100\pi t + 45^\circ)$$

Phasor Diagram before resonance :-

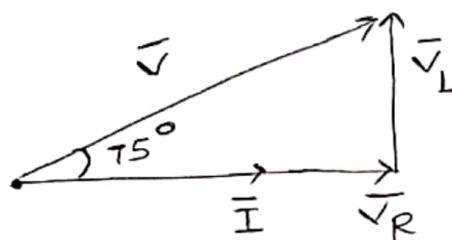

At resonance :-

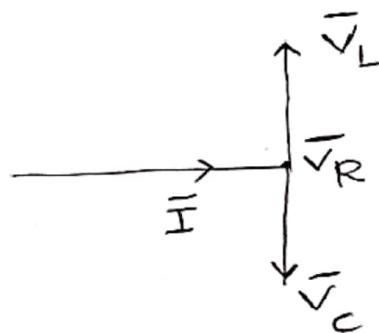

- 4) A series RLC circuit draws 400W from a 200V, 50Hz supply. If the overall resistance is 4Ω & the overall circuit behaves as inductive type, determine

- i) Power factor
- ii) Inductance in the network if capacitance is 1mF .
- iii) What must be the value of capacitance to bring the circuit into resonance?

Solution :- Given $P = 400\text{W}$; $V = 200\text{V}$; $f = 50\text{Hz}$;

$$R = 4\Omega; C = 1\text{mF}$$

$$\textcircled{i}) P = I^2 \cdot R$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{400}{4}} = 10 \text{ A}$$

$$P = V \cdot I \cdot \cos \phi$$

$$\cos \phi = \frac{P}{VI} = \frac{400}{200 \times 10} = 0.2 \text{ lag}$$

$$\textcircled{ii}) \quad \phi = \cos^{-1}[0.2]$$

$$\boxed{\phi = 78.46^\circ}$$

$$Z = R + j(x_L - x_C)$$

$$Z = \frac{V}{I} = \frac{200}{10 \angle -78.46^\circ} = 20 \angle 78.46^\circ$$

$$\boxed{Z = 4.00 + 19.59 j}$$

$$x_L - x_C = 19.59$$

$$x_L = 19.59 + \frac{1}{2\pi \times 50 \times 1 \times 10^{-3}}$$

$$x_L = 22.77$$

$$\omega L = 22.77$$

$$L = \frac{22.77}{100\pi}$$

$$\boxed{L = 72.47 \text{ mH}}$$

$\textcircled{iii})$ For Series resonance, $x_L = x_C$

$$x_C = 22.77 \Omega$$

$$\frac{1}{2\pi f C} = 22.77$$

$$C = \frac{1}{100\pi \times 22.77}$$

$$\boxed{C = 0.14 \text{ mF}}$$

(16)

- 5) A series RLC network draws a net reactive power of 3 KVAR from a 500V, 50 Hz supply and has an overall power factor of 0.8 lag. Determine
- Total resistance in the network
 - Inductance if the capacitance is $159 \cdot 15 \mu F$.
 - What is the new power factor if an extra resistance of 10Ω is added in series in the existing network?

Solution :- $Q = 3 \text{ KVAR}$; $V = 500 \text{ V}$; $f = 50 \text{ Hz}$; $\cos \phi = 0.8$

$$\phi = \cos^{-1}[0.8] = 36.86^\circ$$

$$Q = V \cdot I \cdot \sin \phi$$

$$I = \frac{3000}{500 \times \sin(36.86^\circ)}$$

$$\boxed{I = 10 \text{ A}}$$

$$Z = \frac{V}{I} = \frac{500}{10 \angle -36.86^\circ} = 50 \angle 36.86^\circ$$

$$Z = 40 + j30$$

$$\Rightarrow \boxed{R = 40 \Omega}$$

ii) $X_L - X_C = 30$

$$X_L = 30 + \frac{1}{2\pi \times 50 \times 159 \cdot 15 \times 10^{-6}}$$

$$X_L = 50 \Omega$$

$$L = \frac{50}{2\pi \times 50}$$

$$\boxed{L = 0.159 \text{ H}}$$

iii) If extra 10Ω is added to the network

$$Z = 50 + 30j$$

$$\cos \phi = \frac{50}{\sqrt{50^2 + 30^2}} = \frac{50}{58.30} = 0.857 \text{ lag}$$

6) A series RLC circuit consumes 2 kW of power when connected across 200 V, 50 Hz single phase AC supply. If the overall resistance of the circuit is 5 Ω and the circuit behaves effectively as capacitive type [series RC type], determine

i) Power factor of the network

ii) Total reactive power

iii) capacitance, if the inductance is 10 mH.

iv) what is the value of extra ^{inductance} connected in series

so that the circuit will be in resonance?

Given :- $P = 2 \text{ kW}$; $V = 200 \text{ V}$; $f = 50 \text{ Hz}$; $R = 5 \Omega$; $L = 10 \text{ mH}$

$$P = I^2 \cdot R$$

$$I^2 = \frac{P}{R} = \frac{2000}{5} = 400 \Rightarrow I = 20 \text{ A}$$

$$P = VI \cos \phi$$

$$\cos \phi = \frac{2000}{200 \times 20} = 0.5 \text{ lead}$$

$$\boxed{\phi = 60^\circ}$$

ii) total reactive power :- $Q = VI \sin \phi$

$$Q = 200 \times 20 \times \sin(60^\circ)$$

$$\boxed{Q = -3464 \text{ VAR}}$$

$$iii) Z = \frac{V}{I} = \frac{200 / 0^\circ}{20 / 60^\circ} = 10 / -60^\circ = 5 - j8.66$$

$$X_L - X_C = -8.66$$

$$\omega L - X_C = -8.66$$

$$X_C = \omega L + 8.66$$

$$X_C = \frac{2\pi \times 50}{10} + 8.66$$

$$X_C = \cancel{B22.81} \cancel{J} 11.8 \Omega$$

$$\frac{1}{\omega C} = \cancel{B22.81} \cancel{J} 11.8 \Omega$$

$$C = \frac{1}{100\pi \times \cancel{B22.81} \cancel{J} 11.8}$$

$$\boxed{C = 0.27 \text{ mF}}$$

(18)

iv) for series resonance :-

$$X_L = X_C$$

$$X_L = 11.8$$

$$\omega L = 11.8$$

$$L = 0.03756$$

already present 10 mH

$$37^{\text{mH}} - 10 \text{ mH} = 27.56 \text{ mH}$$

27.56 mH inductance should be connected in series so that the circuit will be in resonance.

Numerical Problems on Parallel RL & RC Circuit :-

1) The terminal voltage and current for a parallel circuit are $141.4 \sin(2000t)$ V and $7.07 \sin(2000t + 36^\circ)$ A. Obtain the simplest two element parallel circuit, which would have the above relationship?

Solution :- To find the elements in a network, use the impedance form if it is a series network and use the admittance form if it is parallel network.

$$V(t) = 141.4 \sin(2000t) \text{ V} \Rightarrow \bar{V} = \frac{141.4}{\sqrt{2}} / 0^\circ \text{ V}$$

$$I(t) = 7.07 \sin(2000t + 36^\circ) \text{ A} \Rightarrow \bar{I} = \frac{7.07}{\sqrt{2}} / 36^\circ \text{ A}$$

$$\text{Admittance } Y = \frac{\bar{I}}{\bar{V}} = \frac{\frac{7.07}{\sqrt{2}} / 36^\circ}{\frac{141.4 / 0^\circ}{\sqrt{2}}} = 0.05 / 36^\circ \text{ S}$$

$$Y = 0.04 + j 0.029 \text{ S}$$

Comparing this with the standard form :-

$$G + jB_C ; G = 0.04 \text{ S} ; B_C = 0.029 \text{ S}$$

Hence it is a parallel RC circuit

$$R = \frac{1}{G} = 25 \Omega ; B_C = \omega C \Rightarrow C = \frac{B_C}{\omega} = \frac{0.029}{2000}$$

$$C = 14.5 \mu\text{F}$$

2) A resistor of 30Ω and a capacitor of unknown value are connected in parallel across a $110V, 50Hz$ supply. The combination draws a current of $5A$ from the supply. Find the value of unknown capacitance?

$$\text{Solution :- } |Y_T| = \frac{|I|}{|V|} = \frac{5}{110} = 0.045 S \quad \text{--- (1)}$$

$$\text{For a Parallel RC network } |Y_T| = \sqrt{G^2 + B_C^2} \quad \text{--- (2)}$$

$$G = \frac{1}{R} = \frac{1}{30} = 0.033 S$$

Substituting G in (2) & equating (1) & (2)

$$0.045 = \sqrt{0.033^2 + B_C^2}$$

$$0.033^2 + B_C^2 = 2.025 \times 10^{-3}$$

$$B_C^2 = 9.36 \times 10^{-4}$$

$$\boxed{B_C = 0.0306 S}$$

$$B_C = \omega C \Rightarrow C = \frac{B_C}{\omega} = \frac{0.0306}{100\pi}$$

$$\boxed{B_C = 97.40 \mu F}$$

3) A parallel RL circuit has $R=4\Omega$, $X_L=3\Omega$. Obtain its series equivalent such that the series circuit draws the same current and power at a given voltage?

$$\text{Solution :- } R=4\Omega ; X_L=3\Omega$$

$$G = \frac{1}{4} S ; B_L = \frac{1}{3} S$$

$$G - jB_L = 0.25 - 0.33j$$


$$Y = G - jB_L = 0.25 - 0.33j$$

$$Z = \frac{1}{Y} = \frac{1}{0.25 - 0.33j} = 1.45 + 1.92j$$

Numerical Problems on Parallel RLC Circuit :-

- 1) Three circuit elements $R = 2.5\Omega$, $X_L = 4\Omega$ and $X_C = 10\Omega$ are connected in parallel, the reactances being at 50 Hz.
- Determine the admittance of each element and hence obtain the input admittance.
 - If this circuit is connected across a 10V, 50 Hz AC source, determine the current in each branch and the total input current?

Solution :-

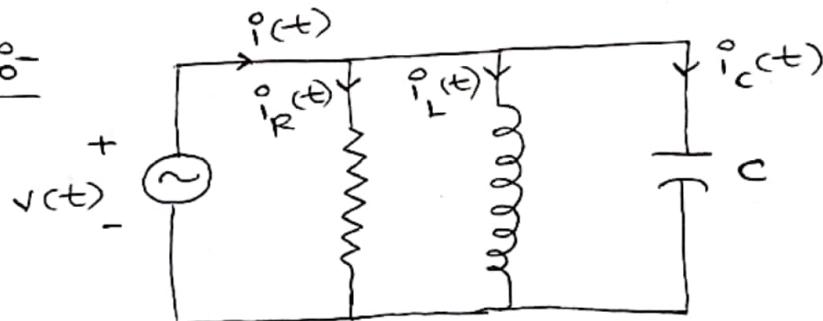

$$\text{Admittance of Branch 1} = Y_1 = \frac{1}{Z_1} = \frac{1}{2.5} = 0.4 \text{ S}$$

$$\text{Admittance of Branch 2} = Y_2 = \frac{1}{jX_L} = -jB_L = -j0.25 \text{ S}$$

$$\text{Admittance of Branch 3} = Y_3 = \frac{1}{-jX_C} = jB_C = j0.1 \text{ S}$$

$$\text{Input Admittance} = [0.4 - j0.15] \text{ S}$$

ii) Taking supply voltage as reference, $\bar{V} = 10 \angle 0^\circ$ (21)

$$\text{current in Branch 1} = \bar{I}_R = \bar{V} \cdot Y_1 = 10 \angle 0^\circ * 0.4$$

$$Y_1 = 0.4 \angle 0^\circ \quad I_1 = 4 \angle 0^\circ \text{ A}$$

$$\text{current in Branch 2} = \bar{I}_L = \bar{V} \cdot Y_2 = 10 \angle 0^\circ [-j0.25]$$

$$\bar{I}_L = 2.5 \angle -90^\circ \text{ A}$$

$$\text{current in Branch 3} = \bar{I}_C = \bar{V} \cdot Y_3 = 10 \angle 0^\circ * j0.1$$

$$\bar{I}_C = 1 \angle 90^\circ \text{ A}$$

Input current $\bar{I}_S = \bar{I}_R + \bar{I}_L + \bar{I}_C$

$$\begin{aligned} &= 4 - j2.5 + j \\ &= 4 - j1.5 \end{aligned}$$

$$\boxed{\bar{I}_S = 4.27 \angle -20.55^\circ \text{ A}}$$

2) The admittance of a circuit is $[0.05 - j0.08] S$. Find the values of the resistance and inductive reactance of the circuit if they are a) in parallel b) in series

Solution :- a) Parallel network

$$Y = 0.05 - j0.08$$

$$Y = G - jB_L$$

$$G = 0.05 ; R = \frac{1}{G} = 20 \Omega$$

$$B_L = 0.08 ; X_L = \frac{1}{B_L} = 12.5 \Omega$$

b) Series network :-

$$Y = 0.05 - j0.08$$

$$\frac{1}{Y} = \frac{1}{0.05 - j0.08} \times \frac{0.05 + j0.08}{0.05 + j0.08} = \frac{0.05 + j0.08}{0.05^2 + 0.08^2}$$

$$\boxed{Z = 5.617 + j8.988 \Omega}$$

$$R = 5.617 \Omega$$

$$X_L = 8.988 \Omega$$

(22)

3) Impedance of a two element parallel AC network is $[6 + j8]$ Ω . Determine the elements and their values if the supply frequency is 50 Hz?

Solution :- $Z = [6 + j8]$ Ω

$$Y = \frac{1}{Z} = \frac{1}{6 + j8} \times \frac{6 - j8}{6 - j8}$$

$$Y = \frac{6 - j8}{6^2 + 8^2} = \frac{6 - j8}{10}$$

$$\boxed{Y = [0.6 - j0.8] \text{ S}}$$

Comparing this with the standard form :-

$$Y = G - jB_L$$


$$G = 0.6; R = \frac{1}{G} = \frac{1}{0.6} = 1.66 \Omega$$

$$B_L = 0.8; X_L = \frac{1}{B_L} = \frac{1}{0.8} = 1.25 \Omega$$

$$X_L = \omega L = 1.25 \Omega$$

$$L = \frac{1.25}{100\pi}$$

$$\boxed{L = 3.97 \text{ mH}}$$

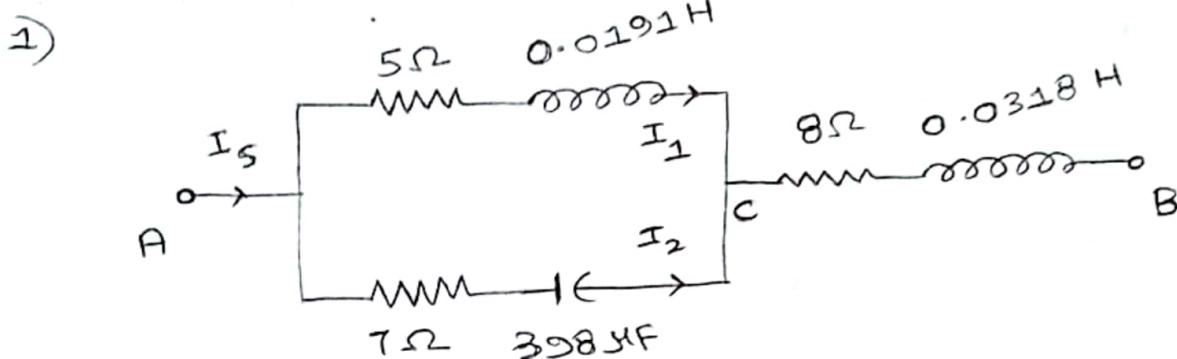

In the circuit shown, what voltage of 50 Hz frequency is to be applied across A & B that will cause a current of 10A to flow through the capacitor. Also draw the phasor diagram representing the circuit?

Solution :- $Z_1 = 5 + j 100\pi \times 0.0191$

$$Z_1 = 5 + j 6 \Omega$$

$$Z_3 = 8 + j 100\pi \times 0.0318$$

$$Z_3 = (8 + j 10) \Omega$$

∴ $Z_2 = 7 - j \frac{1}{100\pi \times 3984}$

$$Z_2 = 7 - j 8 \Omega$$

Since current through the capacitor is known, let us take it as reference phasor.

$$\bar{I}_2 = 10 / 0^\circ A$$

$$\bar{V}_{AC} = \bar{I}_2 \cdot Z_2 = 10 / 0^\circ [7 - j 8]$$

$$\bar{V}_{AC} = 10 * 10 \cdot 63 / -48.81^\circ$$

$$\bar{V}_{AC} = 106.3 / -48.81^\circ$$

(24)

$$\bar{I}_1 = \frac{\bar{V}_{AC}}{\bar{Z}_1} = \frac{106 \cdot 3 \angle -48.81^\circ}{5 + j6} = \frac{106 \cdot 3 \angle -48.81^\circ}{7.81 \angle 50.19^\circ}$$

$$\bar{I}_1 = 13.61 \angle -99^\circ A$$

$$\bar{I}_S = \bar{I}_1 + \bar{I}_2 = 13.61 \angle -99^\circ + 10 \angle 0^\circ A$$

$$\bar{I}_S = -2 \cdot 12 - 13 \cdot 44 j + 10$$

$$\bar{I}_S = 7.88 - 13.44 j$$

$$\bar{I}_S = 15.58 \angle -59.65^\circ A$$

$$\bar{V}_{CB} = \bar{I}_S * \bar{Z}_3$$

$$\bar{V}_{CB} = 15.58 \angle -59.65^\circ * [8 + j10]$$

$$\bar{V}_{CB} = 15.58 \angle -59.65^\circ * 12.80 \angle 51.34^\circ$$

$$\bar{V}_{CB} = 199.48 \angle -8.31^\circ V$$


$$\therefore \bar{V}_{AB} = \bar{V}_{AC} + \bar{V}_{CB} = 106 \cdot 3 \angle -48.81^\circ + 199.48 \angle -8.31^\circ$$

$$\bar{V}_{AB} = 70 - j79.99 + 197 \cdot 38 - j28 \cdot 83$$

$$\bar{V}_{AB} = 267 \cdot 38 - j108 \cdot 82$$


$$\boxed{\bar{V}_{AB} = 288.69 \angle -22.14^\circ V}$$

Phasor Diagram :-

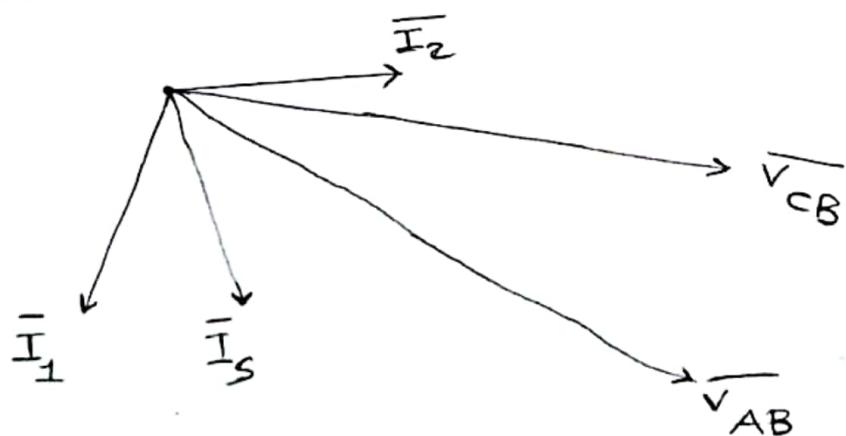

2) When a 220 V AC supply is applied across terminals A & B of the circuit shown, the total power input is 3.25 kW and the total current is 20 A lag. Find the complex expressions for currents through z_1 and z_2 , taking V_{AC} as reference phasor?

$$z_1 = [5 + j20] \Omega$$

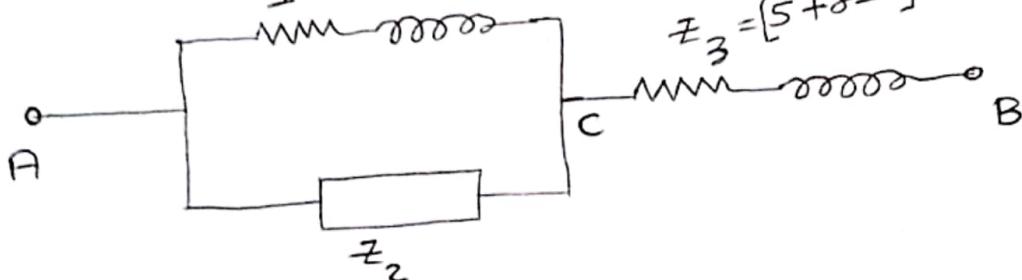

$$z_3 = [5 + j10] \Omega$$

Solution :- $\bar{V}_{AB} = 220 / 0^\circ \text{ V}$

Total power input = 3.25 kW

$$\bar{V}_{AB} \cdot I_s * \cos\phi = 3.25 \times 10^3$$

$$\cos\phi = \frac{3.25 \times 10^3}{220 \times 20}$$

$\boxed{\phi = 42.38^\circ}$

Since supply current is given as lag, $\bar{I}_s = 20 / -42.38^\circ \text{ A}$

$$\bar{V}_{CB} = \bar{I}_s * z_3 = 20 / -42.38^\circ * [5 + j10]$$

$$\bar{V}_{CB} = 223.61 / 21.05^\circ \text{ V}$$

$$\bar{V}_{AC} = \bar{V}_{AB} - \bar{V}_{CB} = 220 / 0^\circ - 223.61 / 21.05^\circ$$

$$\bar{V}_{AC} = 81.11 / -81.98^\circ \text{ V}$$

$$\bar{I}_1 = \frac{\bar{V}_{AC}}{z_1} = \frac{81.11 / -81.98^\circ}{5 + j20} = 3.93 / -157.95^\circ \text{ A}$$

(26)

$$\bar{I}_2 = \bar{I}_S - \bar{I}_1 = 20[-42.38^\circ] - 3.93[-157.95^\circ] A$$

$$\bar{I}_2 = 21.98 [33.1^\circ] A$$

We found that $\bar{V}_{AC} = 81.11 [-81.98^\circ] V$.


To make \bar{V}_{AC} as reference, add 81.98° to its phase angle.
Also, add the same angle to all the phasors.

$$\text{Thus, } \bar{I}_1 = 3.93 [-75.97^\circ] A$$

$$\bar{I}_2 = 21.98 [48.88^\circ] A$$

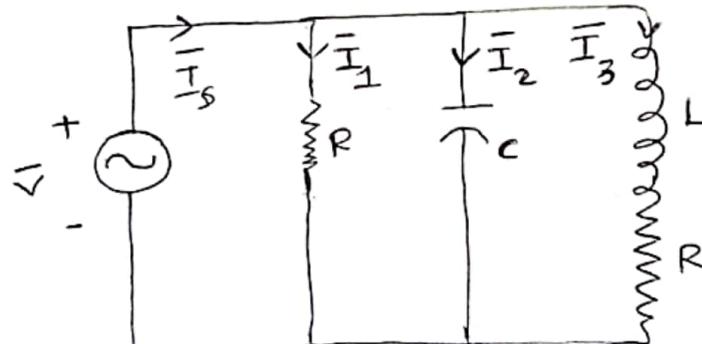3) A voltage of 200V is applied to a pure resistor (R), a pure capacitor (C), and a lossy inductor coil with resistance of 100Ω , all of them connected in parallel.

The total current is 2.45A, while the component currents are 1.5, 2.0 and 1.2 A respectively. Find the total power factor and also the power factor of the coil. Also, find the total active and reactive power?



Solution :- Let us consider supply as reference
 $\bar{V} = 200[0^\circ] V$

Therefore :- $\bar{I}_1 = 1.5[0^\circ] A ; \bar{I}_2 = 2[90^\circ] A$

In branch 3, $|Z_3| = \frac{200}{1.2} = 166.66 \Omega$

$$\text{Therefore, } \phi_3 = \cos^{-1} \frac{\gamma_3}{|Z_3|} = 53.13^\circ$$

(27)

$$\therefore \bar{I}_3 = 1.2 \angle -53.13^\circ \text{ A}$$

$$\begin{aligned}\therefore \bar{I}_S &= \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \\ &= 1.5 \angle 0^\circ + 2 \angle 90^\circ + 1.2 \angle -53.13^\circ \\ \boxed{\bar{I}_S &= 2.45 \angle 25.1^\circ \text{ A}}\end{aligned}$$

$$\text{Phase angle of the network} = \phi = \bar{V} - \bar{I}_S$$

$$\phi = -25.1^\circ$$

Overall Power factor = $\cos \phi = 0.905$ lead


Power factor of the coil = $\cos \phi_3 = 0.6$ lag

Total active power = $P_T = V * I_S * \cos \phi = 443.45 \text{ W}$

Total reactive power = $Q_T = V * I_S * \sin \phi = -207.85 \text{ VAR}$

4) The load connected across an AC supply consists of a heating load of 15 kW, a motor load of 40 kVA at 0.6 lag and a load of 20 kW at 0.8 lag. calculate the total power drawn from the supply in (kW & kVA) and its power factor. What would be the kVAR rating of a capacitor to bring the power factor to unity and how must the capacitor be connected?

Solution :-

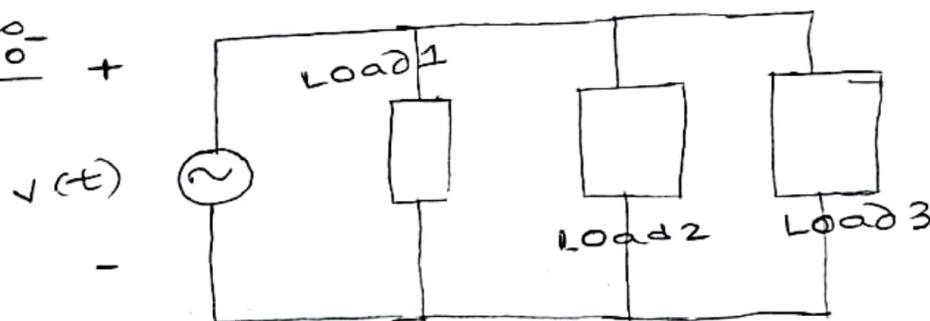

Load 1 :- Heating load \Rightarrow Resistive $\Rightarrow \cos \phi_1 = 1$

$$P_1 = 15 \text{ kW} ; Q_1 = 0 ; S_1 = \sqrt{P_1^2 + Q_1^2} = 15 \text{ kVA}$$

(28)

Load 2 % Motor load \Rightarrow Inductive

$$S_2 = 40 \text{ kVA} \text{ & } \cos \phi_2 = 0.6 \text{ lag (given)}$$

$$P_2 = S_2 \cdot \cos \phi_2 = 24 \text{ kW}$$

$$Q_2 = \sqrt{S_2^2 - P_2^2} = \sqrt{40^2 - 24^2}$$

$$\boxed{Q_2 = 32 \text{ kVAR}}$$

Load 3 % Inductive load

$$P_3 = 20 \text{ kW} \text{ & } \cos \phi_3 = 0.8 \text{ (given)}$$

$$P_3 = S_3 \cdot \cos \phi_3$$

$$S_3 = \frac{P_3}{\cos \phi_3} = \frac{20 \text{ K}}{0.8}$$

$$\boxed{S_3 = 25 \text{ kVA}}$$

$$S_3^2 = P_3^2 + Q_3^2$$

$$Q_3 = S_3^2 - P_3^2$$

$$Q_3 = \sqrt{(25 \text{ K})^2 - (20 \text{ K})^2}$$

$$\boxed{Q_3 = 15 \text{ kVAR}}$$

$$\text{Net active power} = P_T = P_1 + P_2 + P_3 = 59 \text{ kW}$$


$$\text{Net reactive power} = Q_T = Q_1 + Q_2 + Q_3 = 47 \text{ kVAR}$$

$$\text{Net apparent power} = S_T = \sqrt{P_T^2 + Q_T^2} = 75.43 \text{ kVA}$$

To make overall power factor unity, real net reactive power must be ~~zero~~. Hence, connect a capacitor of rating 47 kVAR in parallel to achieve this.

5) The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230V, 50 Hz. Find the value of capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging?

Solution :-

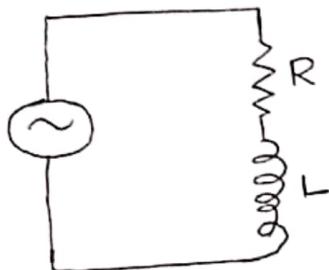

Given :- $P = 2.5 \text{ kW}$; $\text{PF} = 0.71 \text{ lag}$; $V = 230 \text{ V}, 50 \text{ Hz}$

$$P = V \cdot I \cdot \cos \phi$$

$$I = \frac{P}{V \cdot \cos \phi}$$

$$I = \frac{2.5 \times 10^3}{230 \times 0.71}$$


$$\boxed{I = 15.309 \text{ A}}$$

$$\cos \phi = 0.71$$

$$\phi = \cos^{-1}[0.71] = 44.76^\circ$$

$$\boxed{\text{I} = 15.309 \angle -44.76^\circ \text{ A}}$$

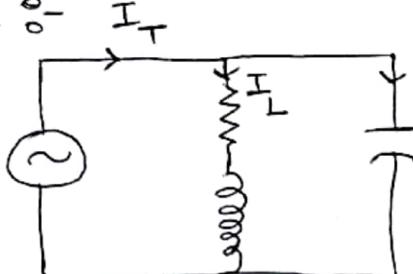For power factor improvement, we connect a capacitor in parallel :-



$$I_T \angle -30^\circ = 15.309 \angle -44.76^\circ + I_c \angle 90^\circ$$

(30)

By evaluating real parts $^{\circ}$

$$I_T \cdot \cos(30^\circ) = 15.309 \cos(44.76^\circ) + 0$$

$$\boxed{I_T = 12.55 \text{ A}}$$

$$I_C = I_T - I_L$$

$$I_C = 12.55 \angle -30^\circ - 15.309 \angle -44.76^\circ$$

$$I_C = 10.86 - 6.275 \angle -\{10.87 - 10.77 i\}$$

$$\boxed{I_C \approx 4.504 \angle 90^\circ}$$

$$X_C = \frac{V_C}{I_C} = \frac{230}{4.504}$$


$$\boxed{X_C = 51.065 \Omega}$$

$$\frac{1}{2\pi f C} = 51.065$$

$$C = \frac{1}{100\pi \times 51.065}$$

$$\boxed{C = 62.33 \mu F}$$

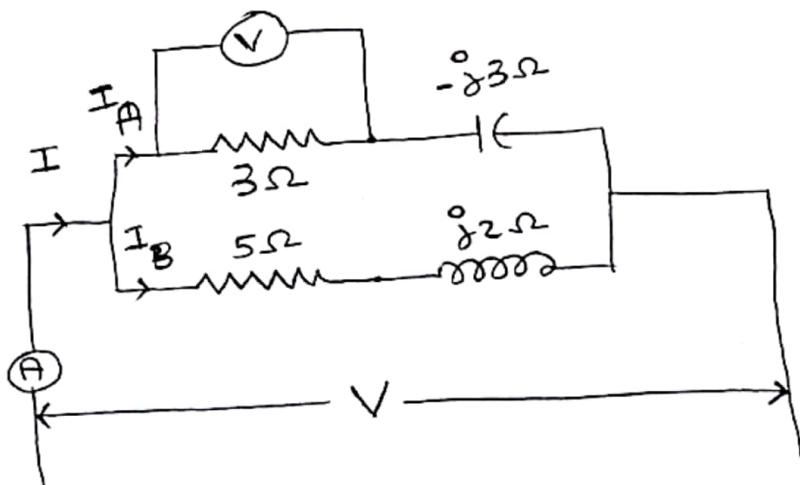- 6) Find the reading of the ammeter when the voltmeter across 3Ω resistor in the circuit shown reads 45 V?



$$\underline{Z}_A = 3 - j3 \Omega; \underline{Z}_B = 5 + j2 \Omega$$

$$I_A = \frac{\sqrt{3} \Omega}{3 \Omega} = \frac{45}{3} = 15 A$$

$$V_A = V_B = V$$

$$V_A = I_A \cdot Z_A = 15 \{3 - j3\} = 45 - j45$$

$$V_A = V_B = V = 63 \cdot 63 \angle -45^\circ V$$

$$V_B = I_B \cdot Z_B$$

$$I_B = \frac{V_B}{Z_B} = \frac{63 \cdot 63 \angle -45^\circ}{5 + j2}$$

$$I_B = 11.81 \angle -66.8^\circ A$$

$$I = I_A + I_B$$


$$I = 15 + 11.81 \angle -66.8^\circ A$$

$$I = 22.45 \angle -28.91^\circ A$$

7) Two impedances $\underline{Z}_1 = 6 + j8 \Omega$ and $\underline{Z}_2 = 4 + j3 \Omega$ are connected in parallel across 200V AC supply.

Determine

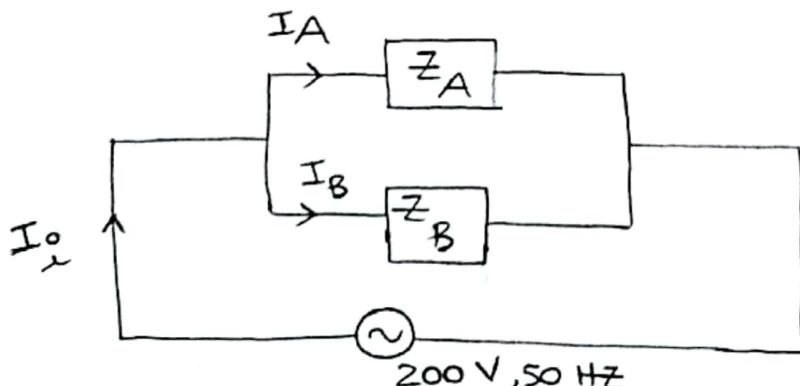- i) Active power in Branch 1
- ii) Reactive power in Branch 2
- iii) Source current
- iv) Power factor of the network



(32)

$$I_A = \frac{V}{Z_A} = \frac{200}{6 + j8} = 20 / 53.1^\circ A$$

$$I_B = \frac{V}{Z_B} = \frac{200}{4 + j3} = 40 / -36.8^\circ A$$

$$I_A + I_B = 20 / 53.1^\circ + 40 / -36.8^\circ$$

$$\boxed{I_o = 44.7 / -10.25^\circ A}$$

Only take magnitude of currents --

i) Active Power in Branch 1 = $P_1 = I_1^2 * R_1$
 $= 20^2 * 6 = 2.4 \text{ kW}$

ii) Reactive Power in Branch 2 = $Q_2 = I_2^2 * X_L$
 $= 40^2 * 3 = 4.8 \text{ kVAR}$


iii) Source current = $I_o = 44.7 / -10.25^\circ A$

iv) Power factor of the network = $\cos\phi$
 $= \cos(10.25^\circ)$

$$\boxed{\cos\phi = 0.98 \text{ lag}}$$

8) An AC circuit has two branches A & B connected in parallel across 230V, 50 Hz supply. Branch A consists of a coil with inductance 100 mH and the resistance of 10Ω. Branch B takes a leading current from the supply. If the total power drawn from the supply is 1 kW and overall PF is 0.6 lag, determine capacitance & resistance of B?

Solution :-

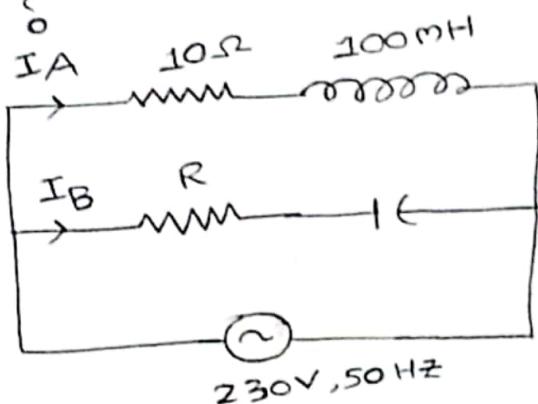

$$P_T = V \cdot I \cdot \cos \phi$$

$$I_T = \frac{P_T}{V \cdot \cos \phi} = \frac{1 \times 10^3}{230 \times 0.6}$$

$$I_T = 7.24 \text{ A}$$

$$I_T = 7.24 [53.13^\circ] \text{ A}$$

$$I_A = \frac{230}{10 + j\{100\pi * 100m\}} = \frac{230}{10 + 31.41j}$$

$$I_A = 2.1167 - 6.6486j = 6.97 [-72.34^\circ] \text{ A}$$

$$I_T = I_A + I_B \Rightarrow I_B = I_T - I_A = 7.24 [53.13^\circ] - 6.97 [-72.34^\circ]$$

$$I_B = 2.2295 + 0.8495j = 2.38 [21.03^\circ] \text{ A}$$

$$Z_B = \frac{V_B}{I_B} = \frac{230}{2.38 [21.03^\circ]} = 96.63 [-21.03^\circ] \Omega$$

$$Z_B = 90.19 - 34.67j; R = 90.19 \Omega$$

$$X_C = \frac{1}{2\pi f C} = 34.67$$

$$C = \frac{1}{100\pi \times 34.67} = 91.81 \mu F$$

(34)

8) The load connected across the AC supply consist of heating load of 20 kW, a motor load of 30 kVA at 0.8 lag and a load of 50 kW at 0.85 lag. calculate the power drawn by the load from supply in KW & KVA and its power factor. what would be the kVAR rating of a capacitor to bring the power factor to unity and how would the capacitor be connected?

Solution :- Load 1

$$P_1 = 20 \text{ KW} ; \cos \phi = 1 ; Q_1 = 0$$

$$\therefore S_1 = \sqrt{Q_1^2 + P_1^2} = 20 \text{ KVA} - (1M)$$

load 2

$$S_2 = 30 \text{ KVA} ; \cos \phi_2 = 0.8 ; \phi_2 = 36.86^\circ$$

$$P_2 = 24 \text{ KW}$$

$$Q_2 = 17.995 \text{ KVAR}$$

$$Q_2 \approx 18 \text{ KVAR} - (1M)$$

load 3 \cos

$$P_3 = 50 \text{ KW} ; \phi_3 = 0.85 ; \phi_3 = 31.788$$

$$S_3 = 58.82 \text{ KVA} ; Q_3 = 30.987 \text{ KVAR}$$

$$Q_3 \approx 31 \text{ KVAR} - (1M)$$

$$P_T = P_1 + P_2 + P_3 = 94 \text{ KW} - (1M)$$

$$Q_T = Q_1 + Q_2 + Q_3 = 49 \text{ KVAR} - (1M)$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = 106.004 \text{ KVA} - (1M)$$

$$\cos \phi_T = \frac{P_T}{S_T} = 0.866 \text{ lag} - (2M)$$


To bring the power factor to unity; Q_T must be
Hence we need to connect a capacitor of 49 KVAR in parallel - (1M)

Q) A branch with $z_1 = (15 + j10) \Omega$ is connected in parallel with another branch $z_2 = (10 - j5) \Omega$. If the total current supplied to the combination is 20 A, Find

- RMS Value of applied Voltage
- Branch currents in polar form
- Power factor of the total circuit
- Power consumed by each branch

Draw the phasor diagram representing the branch currents, supply voltage and supply current.

Solution :-

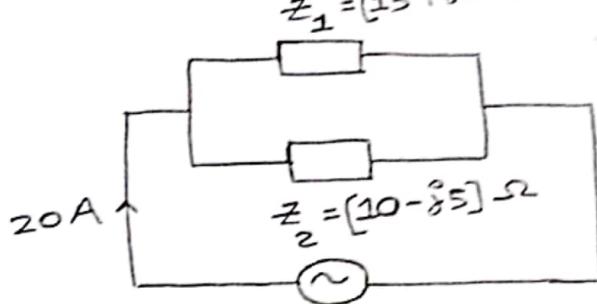

$$\bar{z}_T = \bar{z}_1 \parallel \bar{z}_2$$

$$\bar{z}_T = (15 + j10) \parallel (10 - j5) = [7.884 - j0.576] \Omega$$

$$\bar{z}_T = 7.9056 \angle -4.184^\circ \Omega \quad - (1M)$$

$$V = 157.692 \angle 11.53^\circ$$

or

$$V = 158.11 \angle -4.184^\circ V \quad - (1M)$$

$$I_1 = \frac{V}{z_1} = 8.77 \angle 33.69^\circ V \quad - (1M)$$


$$I_2 = \frac{V}{z_2} = 14.14 \angle 26.56^\circ V \quad - (1M)$$

$$\cos(\phi_T) = \cos(4.184) = 0.9973 \text{ lead} \quad - (2M)$$


$$P_1 = I_1^2 \cdot R_1 = 1153.69 W \quad - (1M)$$

$$P_2 = I_2^2 \cdot R_2 = 1999.39 W \quad - (1M)$$


Phasor diagram :-

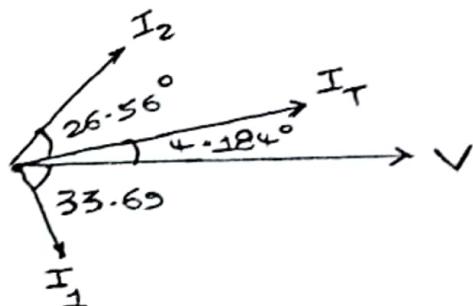

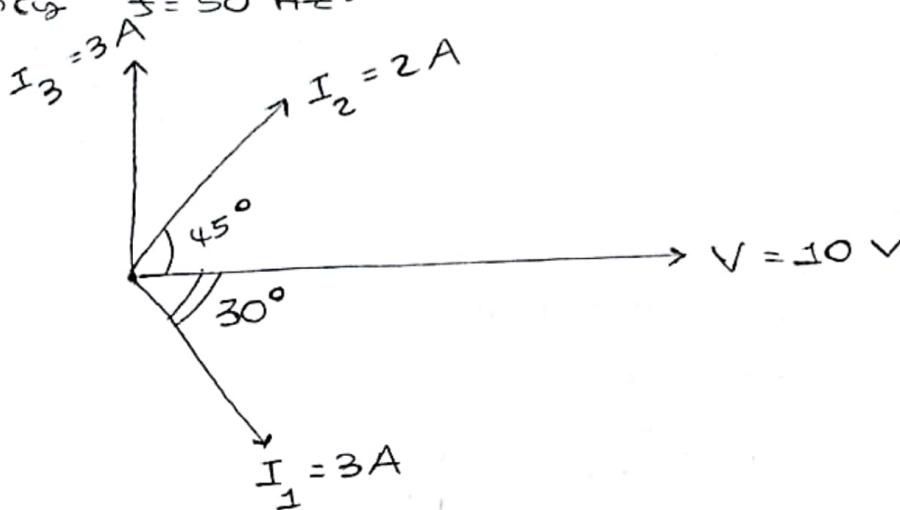2 a) From the given phasor diagram, draw the circuit and compute the different circuit elements by taking frequency $f = 50 \text{ Hz}$.



Solution :-

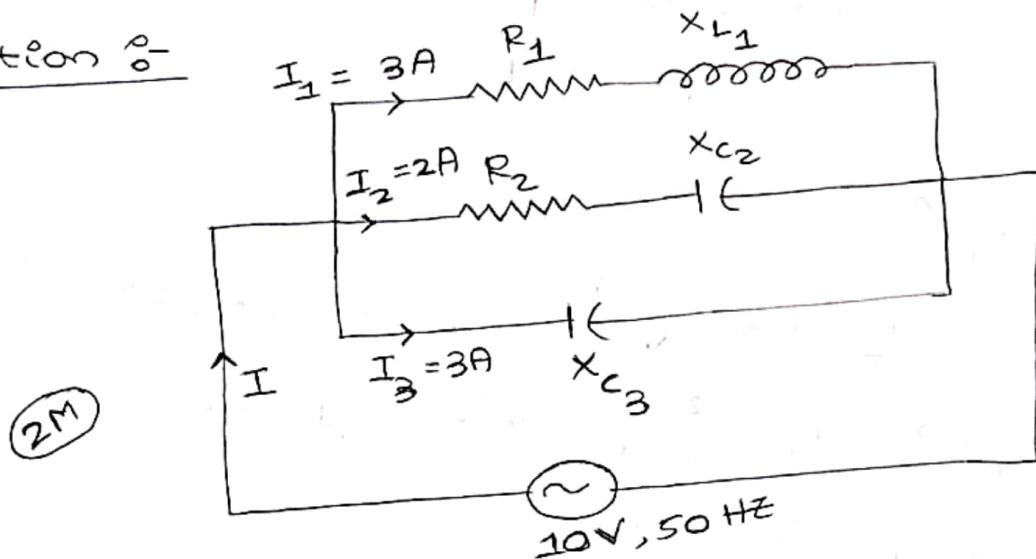

$$X_{C3} = \frac{V}{I_3} = \frac{10}{3} = 3.33 \Omega; \quad \frac{1}{2\pi f C_3} = X_{C3}$$

$$X_{C2} = \frac{1}{2\pi f C_2}$$

$$\Rightarrow C_3 = \frac{1}{2\pi \times 50 \times 3.33} = 955.8 \mu\text{F}$$

$$C_2 = \frac{1}{2\pi f \times X_{C2}}$$

$$Z_1 = \frac{V}{I_1} = \frac{10}{3(-30^\circ)} = 3.33 \angle -30^\circ = [2.88 + j 1.611] \Omega$$

$$C_2 = \frac{1}{2\pi \times 50 \times 3.541} = 900.4 \mu\text{F}$$

$$X_{L1} = 2\pi f L_1$$

$$L_1 = \frac{1.611}{2\pi \times 50} = 5.23 \text{ mH}; \quad R_1 = 2.88 \Omega$$


$$Z_2 = \frac{V}{I_2} = \frac{10}{2(45^\circ)} = 5 \angle -45^\circ = [3.53 - j 3.541] \Omega$$

$$R_2 \quad X_{C2}$$

(e)

(154) ②

2b) 2 impedances Z_1 and Z_2 are connected in parallel. The first branch takes a leading current of 16 A and the resistance of 5Ω . While the second branch takes a lagging current at a power factor of 0.8. The total power supplied is 5 kW and the applied voltage being $(100 + j200)$ V. Determine the complex expressions of branch currents & total current. Also, draw the complete phasor diagram representing the circuit taking voltages as the reference.

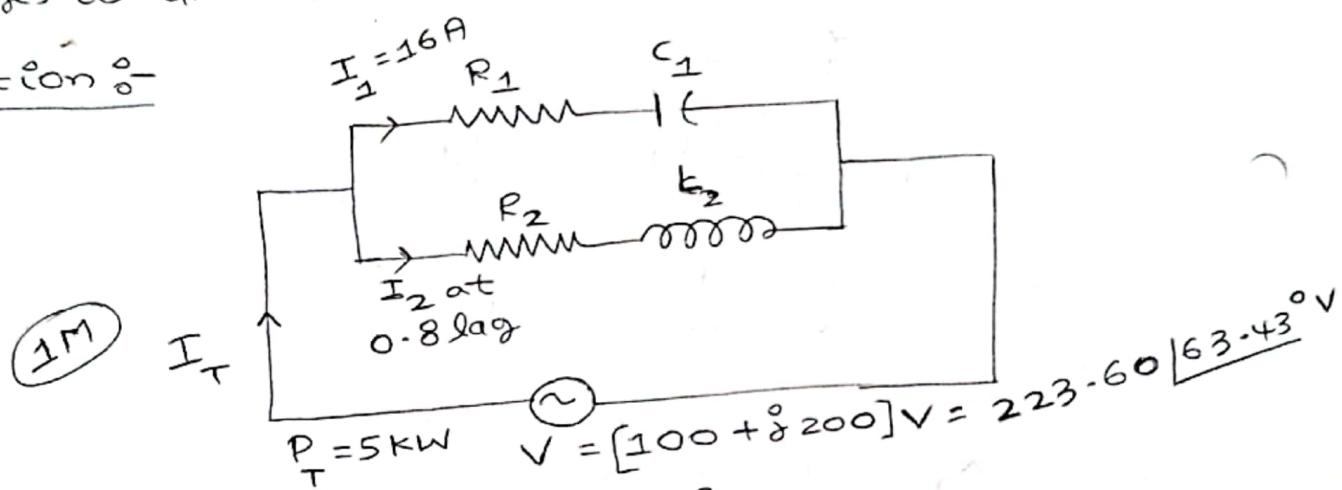Solution :-

$$P_T = P_1 + P_2; P_1 = I_1^2 \cdot R_1 = 16^2 \times 5 = 1.28 \text{ kW}$$

$$P_2 = P_T - P_1 = 3.72 \text{ kW}$$


$$P_2 = V \cdot I_2 \cdot \cos \phi_2$$

$$I_2 = \frac{3.72 \times 10^3}{223.60 / 0^\circ \times 0.8}$$

$$\boxed{I_2 = 20.79 / -36.86^\circ \text{ A}}$$

$$Z_1 = \frac{V}{I_1} = \frac{223}{16 / 63.43^\circ} = 13.975 \Omega$$
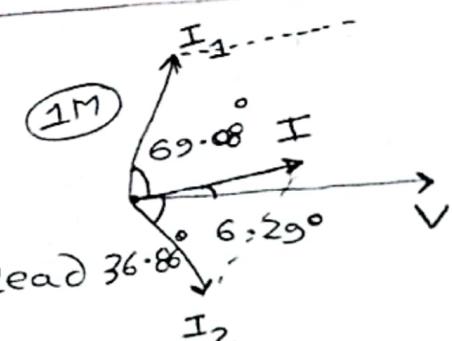
$$\cos \phi = \frac{R_1}{Z_1} = \frac{5}{13.975} = 0.357 \text{ lead } 36.86^\circ$$



$$\boxed{I_1 = 16 / 63.43^\circ \text{ A}} \quad (1M)$$

$$\bar{I}_T = \bar{I}_1 + \bar{I}_2 = 16 / 63.43^\circ + 20.79 / -36.86^\circ$$

$$\boxed{\bar{I}_T = 22.5 / 6.29^\circ \text{ A}} \quad (1M)$$

2c) When 100 V, 50 Hz 1φ AC supply is supplied to a coil A, the current drawn is 8 A and the power is 120 W. When the same voltage is applied to a coil B, the current drawn is 10 A and power is 500 W. What current will be taken when 100 V is applied to the two coils connected in Series? (3)

Solution :- $I_A = 8 \text{ A}$; $I_B = 10 \text{ A}$

coil A

$$P_A = V \cdot I \cdot \cos \phi_A$$

$$\cos \phi_A = \frac{120}{100 \times 8} = 0.15$$

$$\phi_A = 81.37^\circ$$

$$(1\text{M}) \quad \boxed{\bar{Z}_A = 12.5 [81.37^\circ] \Omega}$$

coil B

$$P_B = V \cdot I \cdot \cos \phi_B$$

$$\cos \phi_B = \frac{500}{100 \times 10} = 0.5$$

$$\cos \phi_B = 0.5$$

$$\phi_B = 60^\circ$$

$$(1\text{M}) \quad \boxed{\bar{Z}_B = 10 [60^\circ] \Omega}$$

$$\bar{Z}_T = \bar{Z}_A + \bar{Z}_B = 12.5 [81.37^\circ] \Omega + 10 [60^\circ]$$

$$(1\text{M}) \quad \boxed{\bar{Z}_T = 22.10 [71.88^\circ] \Omega}$$

$$I_T = \frac{V}{\bar{Z}_T} = \frac{100}{22.10 [71.88^\circ]}$$

$$= 4.52 [-71.88^\circ] \text{ A}$$

$$P_T = V \cdot I \cdot \cos \phi_T$$

$$P_T = 100 \times 4.52 [-71.88^\circ]$$

$$(1\text{M}) \quad \boxed{P_T = 140.72 \text{ W}}$$


2d) The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.

Solution :-

P_1

$= 2.5 \text{ kW}; V = 230V; f = 50 \text{ Hz}$

(4)

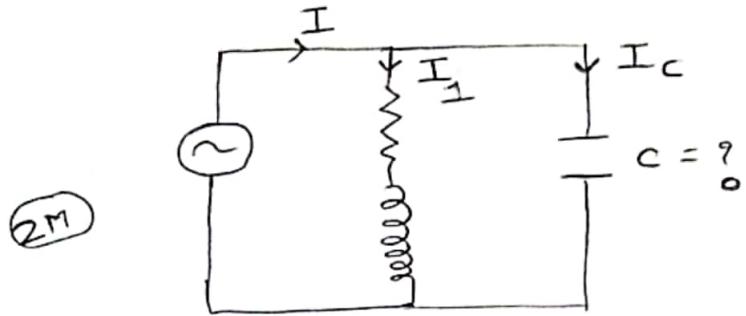

$$\cos \phi_1 = 0.71; P_1 = V \cdot I_1 \cdot \cos \phi_1$$

$$V \cdot I_1 = \frac{P_1}{\cos \phi_1} = \frac{2.5}{0.71} = 3.52 \text{ kVA} = S_1$$

(2M)

$$Q_1 = \sqrt{S_1^2 - P_1^2} = \sqrt{3.52^2 - 2.5^2} = 2.48 \text{ kVAR}$$

(2M)

$$P_1 = P_2 = 2.5 \text{ kW}; \cos \phi_2 = 0.866 \text{ lag}$$

$$P_2 = V \cdot I_2 \cdot \cos \phi_2 = 2.5 \text{ kW}$$

$$V \cdot I_2 = S_2 = 2.88 \text{ kVA}$$

$$Q_2 = \sqrt{S_2^2 - P_2^2} = \sqrt{2.88^2 - 2.5^2} = 1.44 \text{ kVAR}$$

(2M)

$$Q_C = Q_1 - Q_2$$

$$Q_C = 2.48 - 1.44$$

$Q_C = 1.04 \text{ kVAR}$

(2M)

$$Q_C = \frac{V^2}{X_C} \Rightarrow X_C = \frac{V^2}{Q_C}$$

$$X_C = 50.865 \Omega$$

$$\Rightarrow \frac{1}{2\pi f C} = 50.865$$

(2M)

$C = 62.57 \mu\text{F}$

