

UE21EE141B – JULY 2022 ESA ANSWER KEY

1a) $R_{AB} = 29.77\Omega$

1b) With only 12A source active, $I' = 8A$

With only 30V source active, $I'' = 1.67A$

With only 6A source active, $I''' = -4A$

By Superposition Theorem, current through 2Ω resistor = $I' + I'' + I''' = 5.67A$

1c) $V_{TH} = -5V$; $R_{TH} = 0.67\Omega$

Load current varies between 49.66mA and 0.468A

2a) i) It is a series RC network with $R = 10\Omega$ & $C = 183.78\mu F$

ii) $P = 500W$; $Q = -866VAR$; $S = 1000VA$

iii) Power factor = 0.5 Lead

2b) i) $P_T = 77KW$; $Q_T = 57.33KVAR$; $S_T = 96KVA$

ii) Overall Power factor = 0.802 Lag

iii) New value of Power factor = 0.899 Lag

2c) i) $Z_2 = (10 + j13.33)\Omega$

ii) Current in $Z_1 = 4A$; Current in $Z_2 = 6A$

iii) $Q_1 = 320VAR$; $Q_2 = 480VAR$

3b) New readings of Wattmeters: $W_1 = 1.42KW$; $W_2 = 3.58KW$

3c) i) $Z = 23.094\Omega$

ii) $R = 11.55\Omega$ & $L = 63.66mH$

iii) $P_T = 3.465KW$; $Q_T = 6KVAR$

4b) i) $f = 50\text{Hz}$

ii) $P = 4$

iii) Slip under Full Load = 0.04 pu (or) 4%

iv) f_r (Full load) = 2 Hz

v) No Load speed = 1485 rpm

4c) i) Constant Losses = 796W

ii) Efficiency (Motor) = 73.5%

iii) Efficiency (Generator) = 76.63%

5b) $C = 255.4\mu\text{F}$

5c) i) Total number of Units consumed = 224

ii) Monthly Bill = Rs. $2065.237/-$