

## Class 12 : Application of Differential Equations- LRC Circuits

1. Determine  $Q$  and  $I$  in an LRC circuit with  $L = 0.05$  H,  $R = 20$  Ohms,  $C = 100$  micro Farad given that  $Q = 0$ ,  $i = 0$  at  $t = 0$ .

Answer:  $Q = e^{-200t}(0.01\cos 400t - 0.005\sin 400t) + 0.01$ ,  $I = 5e^{-220t}\sin 400t$

2. Find  $Q$  and  $I$  in the LRC circuit with  $L=2$ ,  $R = 4$ ,  $C = 0.05$ ,  $E = 100$  and  $Q(0) = Q'(0) = 0$ .

Answer :  $Q(t) = 5 - \frac{5}{3}e^{-t}(3\cos 3t + \sin 3t)$  and  $I(t) = \frac{5}{3}e^{-t}(3\cos 3t + \sin 3t)$

3. At  $t=0$ , a current of 2 amperes flows in an RLC circuit with resistance  $R=40$  ohms, inductance  $L = 0.2$  henrys and capacitance  $C=10^{-5}$  Farads. Find the current flowing in the circuit at  $t > 0$  if the initial charge on the capacitor is 1 coulomb.

Answer :  $i = e^{-100t} (2 \cos 200 t - 251 \sin 200 t)$

4. A simple LR circuit is governed by the differential equation  $L \frac{di}{dt} + Ri = 0$  where  $i(t)$  is the current at any time  $t$ . If the resistance of the resistor is 2 ohms and the inductance of the inductor is 3 Henry find the current at  $t = 2$  seconds given that the current at time  $t = 0$  is 1 ampere.

Answer :  $i(t) = e^{\frac{-2t}{3}}$  in general .  $i(2) = e^{\frac{-4}{3}}$  amperes.

\*\*\*\*\*