



ELEMENTS OF ELECTRICAL ENGINEERING

Dr Kola Sampangi Sambaiah

Department of Electrical & Electronics Engineering

ELEMENTS OF ELECTRICAL ENGINEERING


Numerical Examples on Source Transformation

Dr Kola Sampangi Sambaiah


Department of Electrical & Electronics Engineering

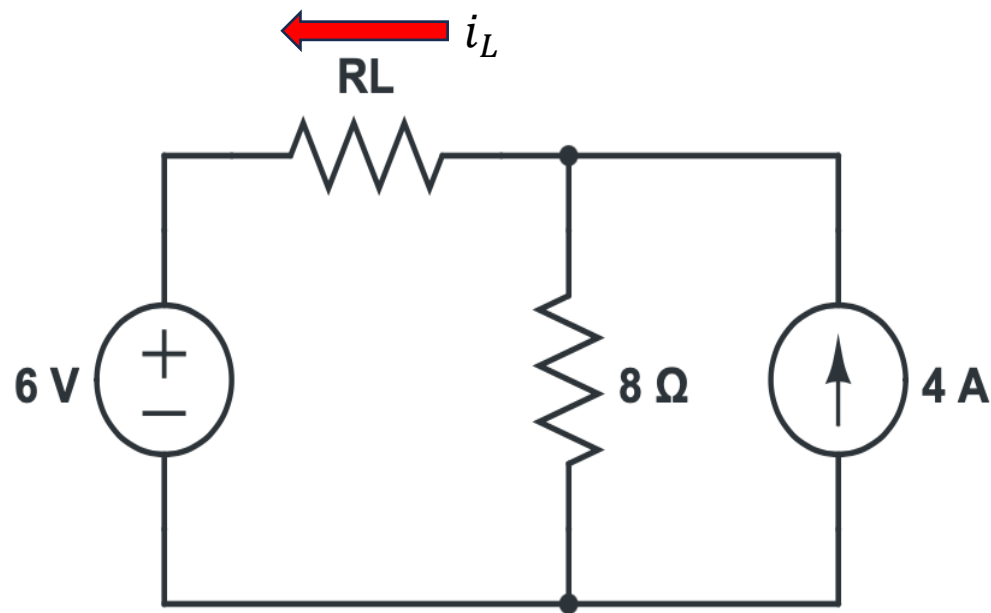Question:


Find the current i_L when $R_L = 2\Omega$ using source transformation.



Solution:

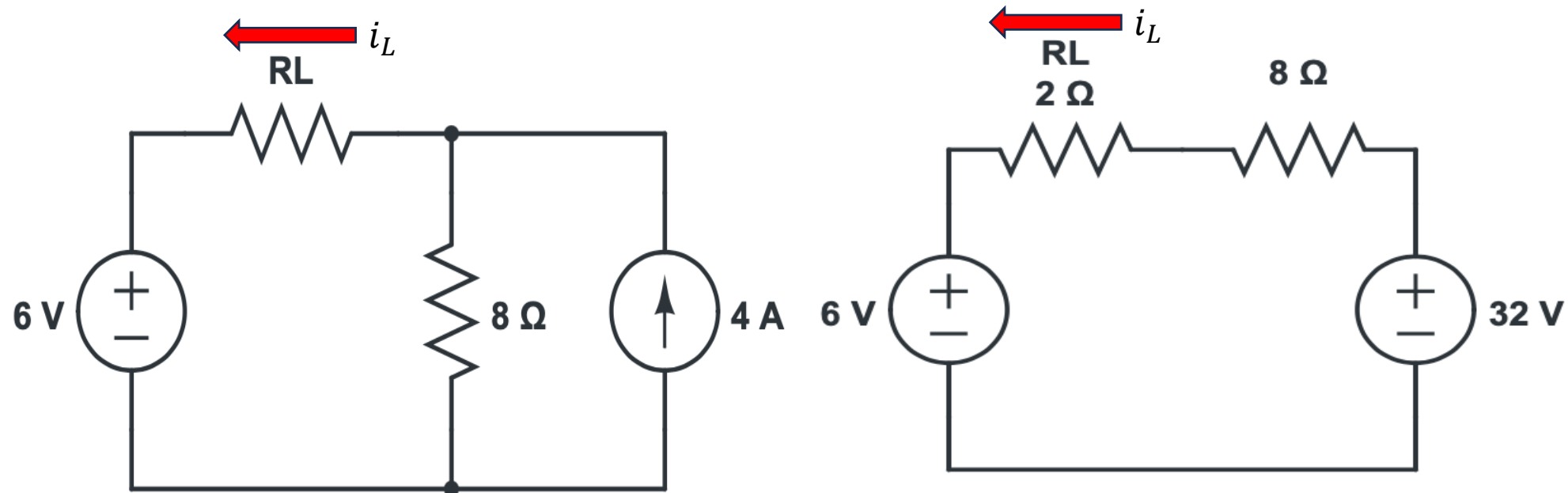

Solution:

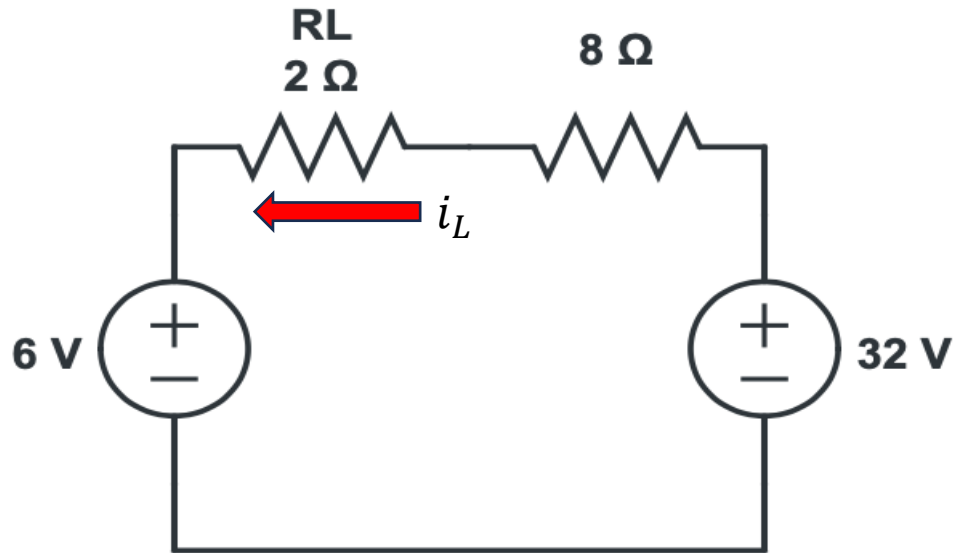

Apply KVL


$$32 - 8i_L - 2i_L - 6 = 0$$

$$10i_L = 26$$

$$i_L = 2.6 \text{ A}$$

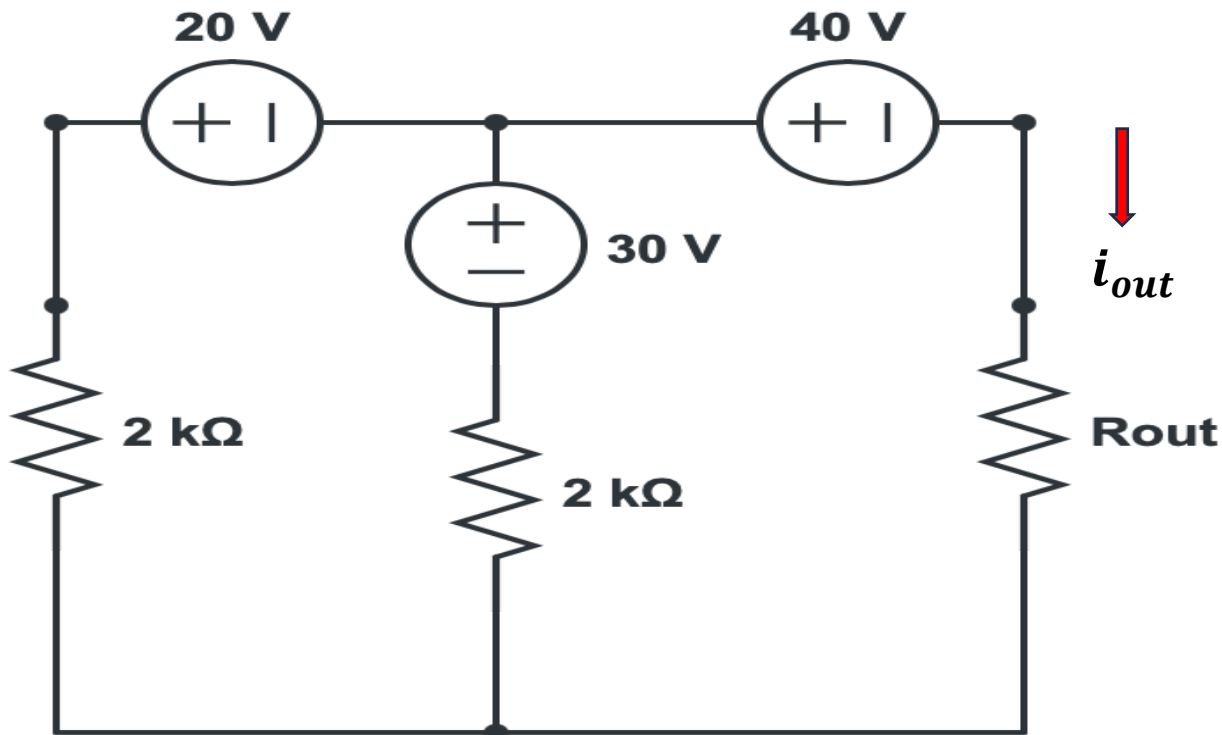Question:



Find the current i_{out} when $R_{out} = 3\text{ k}\Omega$ using source transformation.




ELEMENTS OF ELECTRICAL ENGINEERING

Source Transformations – Numerical Example 2

Solution:

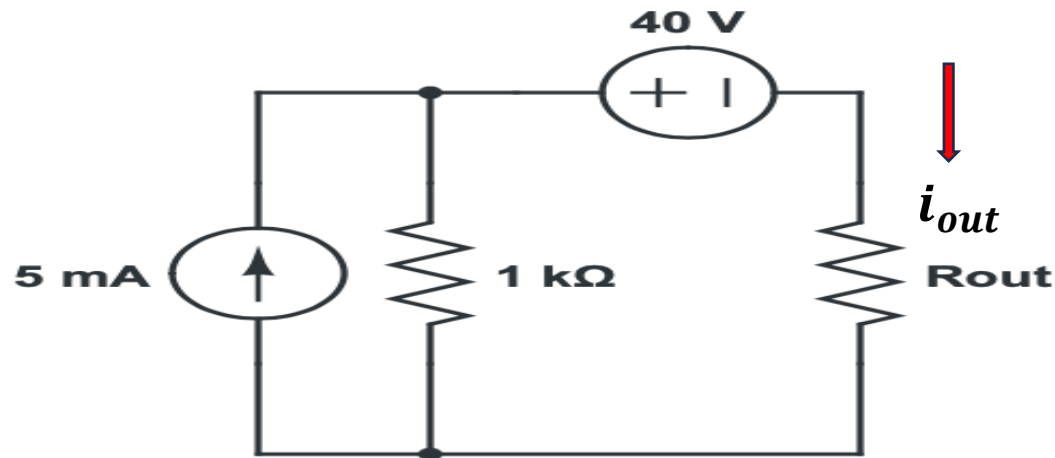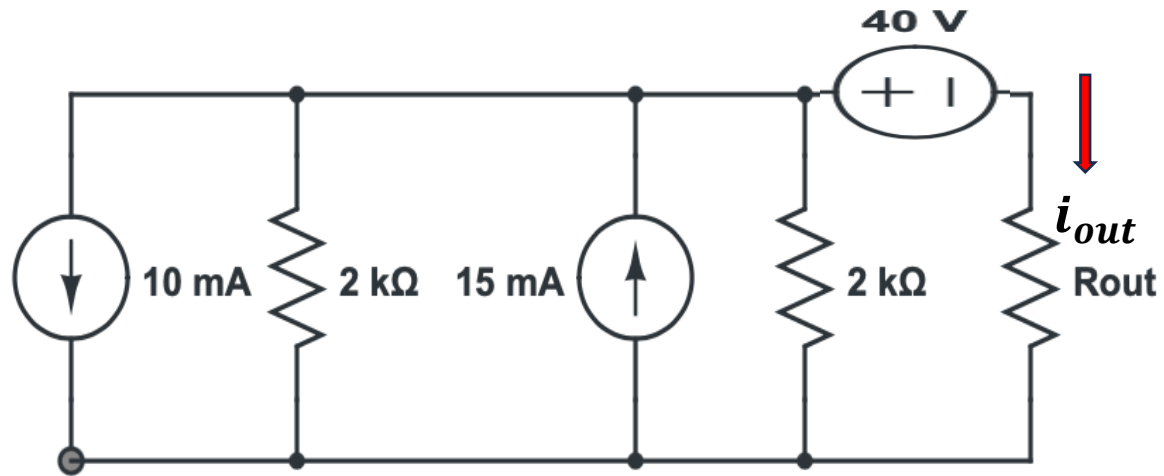

Solution:

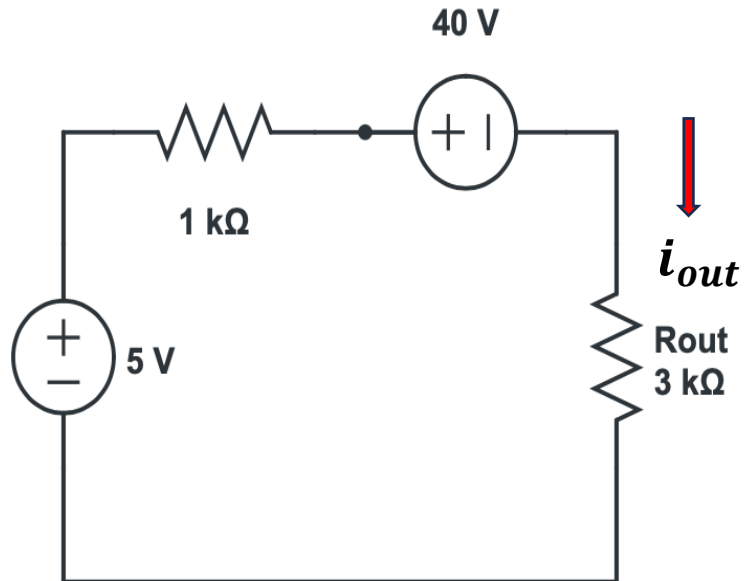

Apply KVL

$$5 - 1000 * i_{out} - 40 - 3000 * i_L = 0$$

$$4000i_{out} = -35$$

$$i_{out} = -0.00875 \text{ A or } -8.75 \text{ mA}$$

ELEMENTS OF ELECTRICAL ENGINEERING

Text Book & References



Text Book:

1. “Basic Electrical Engineering”, D. C. Kulshreshta, 2nd Edition, McGraw-Hill. 2019

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Dr Kola Sampangi Sambaiah

Department of Electrical & Electronics Engineering