

UE21EE141A – MARCH 2022 ESA ANSWER KEY

1a) $R_{AB} = 21.94\Omega$

1b) With only 5A source active, $I' = 3A$

With only 10V source active, $I'' = -2A$

With only 20V source active, $I''' = 4A$

By Superposition Theorem, current through 2Ω resistor = $I' + I'' + I''' = 5A$

1c) $V_{TH} = 12.5V$; $R_{TH} = 10\Omega$

2a) It is a parallel RL network with $R = 16.67\Omega$ & $L = 39.79mH$

2b) i) Power factor = 0.5 Lead

ii) Reactive Power = -3.464 KVAR

iii) $C = 269.71\mu F$

Extra inductance to be added in series for resonance condition is 27.56mH

2c) i) $Z_A = (80 + j60)\Omega$; $Z_B = (59.54 - j6.037)\Omega$

ii) $P_A = 320W$; $P_B = 665W$

3b) i) Line current = 28.87A

ii) $Z = 24\Omega$

iii) Power factor = 0.8 Lag

iv) $R = 19.2\Omega$; $L = 45.84mH$

3c) i) Line current = 69.28A

ii) $W_1 = 3.315KW$; $W_2 = 25.484KW$

When reconnected as star load & supply voltage reduced to 200V,

New Line current = 11.55A

New Wattmeter Readings are $W_1 = 276.31W$; $W_2 = 2.124KW$

4a) i) $N_s = 750$ rpm

ii) Slip under No Load = 0.0133 pu (or) 1.33%

iii) Full load speed = 712.5 rpm

iv) f_r (Full load) = 2.5 Hz

v) f_r at Standstill = $f = 50$ Hz

4b) i) Under Half-load condition, $I_1 = 5A$; $I_2 = 50A$

ii) $N_1 = 750$ turns

iii) Under Half-load condition, $I_1 = 2.5A$; $I_2 = 25A$

iv) $B_m = 1.2T$

v) EMF/turn = 2.67 Volts/turn

5b) i) $P_T = 12KW$; $Q_T = 7KVAR$

ii) $S_T = 13.89KVA$

iii) Overall Power factor = 0.863 Lag

A capacitor with KVAR rating = 7 KVAR must be connected in parallel.

5c) i) Total number of Units consumed = 202

ii) Monthly Bill = Rs. 1810.87/-